

Editorial



THERE isn't a great deal of apparent TV activity at the moment. Someone even suggested that the term "cold war" might be appropriate to indicate a lull between the first shots and the next manifestations of progress.

To a certain extent there is aptness in the phrase. Most TV interests are gathering their forces and facilities, training executives, hunting staff and negotiating for equipment.

Undoubtedly they are at last beginning to appreciate the task which lies before them. We do not hear so many optimistic statements about early starting dates, and confident predictions

about how and when things will be done.

The general feeling in both Sydney and Melbourne is that TV stations will not be ready to commence a regular service until about November of next year.

There is always the chance that someone will steal a march, but I am inclined to share the conservative view.

This does not mean that TV sets will not be available for purchase until then.

Already the receiver manufacturers are working out ideas to cash-in on the initial market, in which demand is almost certain to exceed supply.

It's rather too difficult at this stage to estimate how many receivers will be available initially but it is certain that some manufacturers already have receivers complete and ready for sale.

These are intended to tide them over the early period, giving time to start up a production line as soon as this becomes practicable.

There seems a strong likelihood that, by the time we get started, the TV screen may have jumped from 17 to 21 inches. Popularity of the larger size overseas may make standardisation here hard to sustain. In the USA particularly, smaller screens are going out.

On the other hand, manufacturers here seem to be getting more price conscious as time goes on. Maybe the possibility of lengthy import and credit restrictions may have something to do with this. Higher deposits and shorter terms will affect the price Mr. Public can afford for a TV set, just as it does everything else.

In this connection the Government has set something like a record. It has virtually classed TV as a necessity even before we have it!

John Boyle

INDEX

Ideas For New Fighter Planes ..	3	Constant Current Supplies ..	59
How Modern Physics Began ..	4	Five Valve Klokette ..	64
Novel Plane Soars And Flies ..	9	Parts For Audio Generator ..	75
Reactor For Medical Research ..	11	How Good Are Our Amplifiers? ..	80
Science Notes By Prof. A. M. Low ..	15	A Course In Television — Part 3 ..	91
Hydraulic Power In Industry ..	16	Let's Buy An Argument ..	96
Technical Review ..	21	Trade Reviews And Releases ..	101
News And Views ..	29	Off The Record ..	104
Playmaster Crystal Control Unit ..	32	Short-Wave Notes ..	112
Seven ..	32	Ham Bands ..	113
From The Serviceman Who Tells ..	39	Answers To Correspondents ..	125
Here's Your Answer Tom ..	46		
Designing A Mixer Unit ..	48		

RADIO

TELEVISION & HOBBIES

A NATIONAL MAGAZINE OF RADIO, TELEVISION, HOBBIES AND POPULAR SCIENCE

EDITOR

JOHN BOYLE,
S.M.I.R.E. (Aust.)

TECHNICAL EDITOR

NEVILLE WILLIAMS
M.I.R.E. (Aust.)

TECHNICAL STAFF

REG RAWLINGS
PHILIP WATSON
L. VARADY
MERYNN HUDDLESTON

Vol. 17, No. 3

SUBSCRIPTION RATES

Cwealth, NZ, N. Guinea, Fiji—18/- pa.
United Kingdom—£1 0/6 pa.
B. Empire—£1 3/- pa.
Foreign—£1 5/- pa.

Published on the first Friday of each month by Associated Newspapers Ltd., 60-70 Elizabeth St., Sydney.

Phone BQ 333

OUR COVER PICTURE

Not so long ago television cameras had, of necessity, to be big and bulky to accommodate all the necessary components. By a process of simplification they can now be reduced to the modest dimensions shown.

The **Palec** VACUUM TUBE **VOLT-OHMMETER**

MODEL TV-M

FOR SERVICE & LABORATORY

This new "Palec" instrument is destined to become a BASIC NECESSITY in every branch of electronics—NOW and in the television days ahead. A product appropriate to the times, its performance makes it the most essential and valuable piece of equipment in its field.


SPECIFICATIONS:

	RANGES
D.C. VOLTS—11 Megohm Input Res.	0-1.5, 5, 15, 50, 150, 500, 1500
D.C. VOLTS—1000 Megohm Input Res. (with H.T. probe)	0-150, 500, 1500, 5000, 15,000, 30,000 Max.
A.C. VOLTS—R.M.S. Sine Wave.	0-1.5, 5, 15, 50, 150, 500, 1500
A.C. VOLTS—Peak to Peak.	0-4.2, 14, 42, 140, 420, 1400, 4200
RESISTANCE—(1/4 of an Ohm to 1000 Megohms).	0-1000, 10,000, 100,000, Ohms—1, 10, 100, 1000 Megohms
DECIBELS odb = 1mW in 600 Ohms.	-30/-3, -10/+17, +10/+37, +30/+57
DECIBELS odb = 6mW in 600 Ohms.	-20/+4, 0/+24, +20/+44, +40/+64
	Total ranges

FREQUENCY RESPONSE 25 cycles to 5 megacycles. The Crystal Diode Probe extends the range to 400 megacycles.

SPECIAL ACCESSORIES:

Prices on Application.

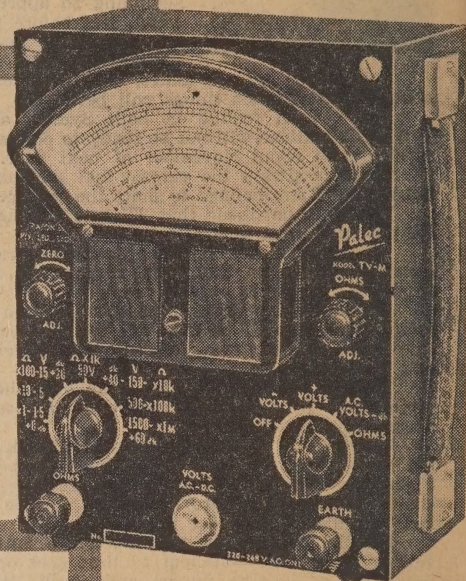

MODEL TV-M, Vacuum Tube Volt-ohmmeter for A.C.-D.C. and Ohms measurements, complete with comprehensive instruction book.


Price on application

SIZE: 8x9½x6 inches. WEIGHT: 8-lbs.

OTHER FEATURES:

Plus and Minus D.C. Readings: Centre zero scale for F.M. Alignment: All ranges as listed above read direct on scale: Linear balanced push-pull circuit: 6inch sector type meter giving accurate readings with overload protection from circuit.

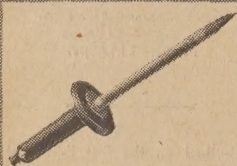- Service: Our Australian built products have the advantage of being backed by local Factory Service.
- Technical Problems: Our Technical experience is at your disposal.



HIGH TENSION D.C. MULTIPLIER PROBE and shielded lead to extend operation of the TV-M to 30,000 volts. D.C.




CRYSTAL DIODE PROBE and coaxial lead for ultra H.F. measurements up to 400 M.C.

PATON ELECTRICAL


PTY.  LTD.

Manufacturers of all Types of Radio & Electrical Test Equipment & Meters
90-94 VICTORIA ST., ASHFIELD, SYDNEY. UA 5266. TELEGRAMS: "PALEC"


IDEAS FOR NEW FIGHTER PLANES

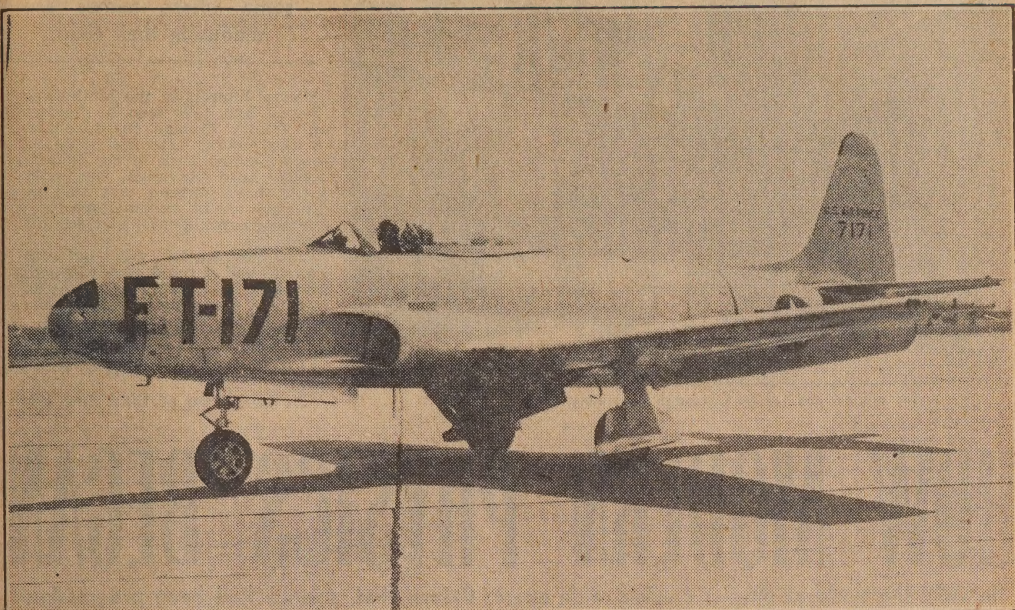

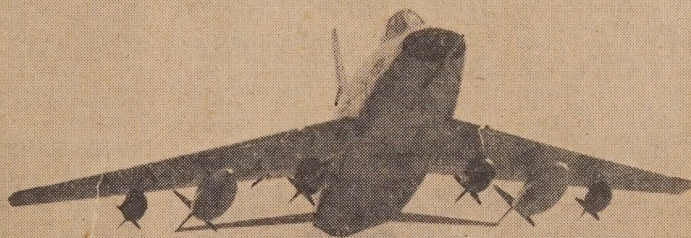This looks just like any other Shooting Star single jet fighter but it isn't. This one is made of magnesium instead of aluminium. Magnesium is more rigid than aluminium although it is lighter, and fewer parts are needed in consequence. This F-80C is probably the world's first magnesium aircraft, and is faster than the regular model.



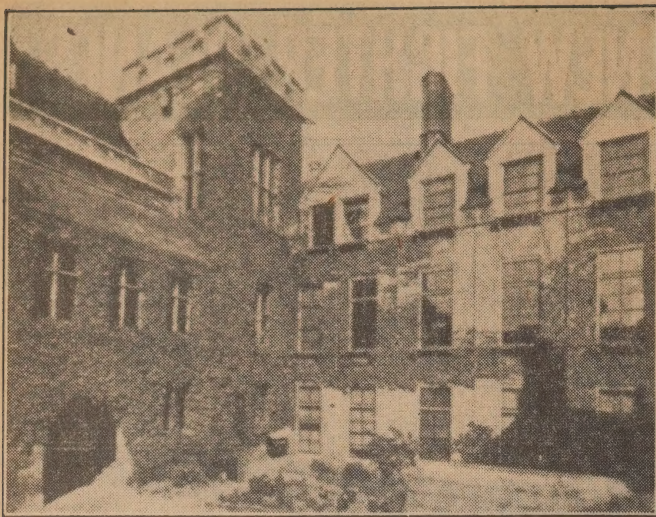This queer looking speedster has a potent array of power plants designed to give it long range as well as a big punch when required. It is a version of the Super Sabre F-100C and can carry atom-bombs at super-sonic speeds. It is in use by the US Air Force.



The original and famous Cavendish Laboratory building, 1874.

● This is the first of a series of articles on the birth and use of Atomic Physics, written by well-known scientists including some whose names are famous in their field.

guished himself in the Mathematics Tripos and had won a Fellowship at Trinity College for his mathematical work. He had done some experimental work in the laboratory under Lord Rayleigh, but nobody could have foreseen that this theoretician would become one of the greatest experimental geniuses of all time.

J.J.—for so he was universally called—had a mind that worked incessantly with boundless enthusiasm and with a deep and accurate knowledge of the scientific literature. As an experimenter, his peculiar limitation gave him perhaps his greatest strength. He was awkward with his hands.

He had none of those fine quali-

HOW MODERN PHYSICS BEGAN

In 1895 the world of physics cracked wide apart. Before that, science had been progressing steadily and it was apparent that Man's understanding of the Universe was approaching perfection. A few trifling discrepancies could be found, but most physicists felt that all that remained was to make measurements to a couple of extra places of decimals.

THEN, in the space of barely two years, came the discovery of x-rays and of the radioactivity of uranium; two striking phenomena which fitted absolutely nowhere in the scheme of things. Perhaps for the first time, such scientific news captured the imagination of the general public as well as the scientists.

Public reaction was comparable to that more recently aroused by the explosion of the first atomic bomb. As excitement was at its peak, Professor J. J. Thomson in his Cavendish laboratory at Cambridge demonstrated the existence of electrons—little particles far smaller than the smallest elemental atoms, which had been the basic building blocks of fin-de-siècle physics.

BASIC DISCOVERIES

Modern physics began with these three discoveries: x-rays, uranium and the electron. They opened a new era in the art of scientific research and brought forth a new type of laboratory scientist. The quickened pulse of the new science attracted more and more men to the laboratories; their research papers began to flood the learned journals as more and more men came advancing through the breach in our knowledge into the open and inviting territory that lay beyond.

Nowhere was the change more obvious and intense than in the Cavendish Laboratory at Cambridge University. Only some twenty years

before, it had been erected as the first building in the world designed for physical research. Its first director James Clerk Maxwell, had lavished on it all the care he had previously brought to bear on his beautiful experimental work and on his working out of the mathematical theories of heat and of electromagnetic waves.

His successor, Lord Rayleigh, owner of the finest private laboratory in the country, had given five years to developing the Cavendish as a national resource.

In 1884, Joseph John Thomson,

**By Dr. D. J. PRICE,
Ph.D., Curator, Whipple
Museum of the
History of Science
Cambridge.**

barely 28 years old, was appointed Cavendish Professor of Experimental Physics. At the time there were many who thought it a dubious appointment. The University had tried to get Lord Kelvin, great pioneer of the Atlantic telegraph, but he had been unwilling to leave Glasgow.

After long deliberation the choice fell on the brilliant young man from Manchester, who had distin-

ties of manipulation that one usually associated with the delicate work of the laboratory.

The fact remains that he did most of his work through his experimental assistants and the band of research workers at the laboratory. Throughout his working life he threw out an endless stream of suggestions for building apparatus and sending it often unwillingly to work, correcting its errors and perversities. Under his direction apparatus was built up and torn down again and new results came in at a terrific rate.

MANY HANDS

He was a brain with dozens of pairs of hands to do his bidding, elaborate on his ideas, and then go out and work on their own with the inspiration of the master. Such is the background of the "sealing-wax and string" which was the striking feature of those early days of atomic physics.

J.J. was one of the first modern scientists to specialise narrowly. When he was appointed professor he took up the study of electrical discharges in gases—then an obscurity, but now familiar by its products; neon tubes, radio valves, cathode ray tubes for television, x-ray bulbs. He remained in this field all his life.

Fortunately it was just the place where physics boiled over in 1895. Thomson was in "on the ground



Sir John Cockroft



Sir J. J. Thomson



Lord Rutherford

floor". Fortunately for him, too, just at that time Cambridge accepted the Research Student movement, and graduates from other universities all over the world came to work and learn at the Cavendish and other laboratories.

J.J. had an unlimited supply of fresh and vigorous pairs of hands for his work, and his laboratory became the greatest centre for the new physics.

Soon after Roentgen's discovery of x-rays, the laboratory settled down, and interrupted only by the clamor of all local medical men for the taking of x-ray photographs of their patients' broken bones, each research worker began to inquire whether the new rays could help their own specialised investigations.

EFFECT ON GASES

J.J. tried the effect of the rays upon electrical discharges in gases and found that it was just what was needed to simplify his attack on the problem. Gases usually needed unwieldy violence (e.g. a spark) to make them conduct electricity, but under the influence of x-rays they conduct easily and normally. The little particles of gas become charged or ionised by the bombardment.

Using this phenomenon, J.J. extended a method used by his student, John Townsend (later Sir John), and was able to find the size of the charge produced. Combining this with results obtained from measuring cathode rays he was able to confirm his guess that the cathode rays were not rays at all, but streams of tiny charged particles, far smaller than atoms. He confirmed the existence of the electron.

Another of the students, C.T.R. Wilson, was concerned with the effect of x-rays on quite a different speciality. In 1894 he had spent a few weeks at an observatory on the top of Ben Nevis. The wonderful effects of light on the mists and clouds at the summit fascinated him, and he returned to the laboratory to reproduce such cloud effects artificially and find how they worked.

Wilson was able to do it by suddenly expanding moist air so that it condensed in tiny drops. If the expansion was just right the drops

would form round the particles of dust present in the air—particles so small that they were little bigger than individual molecules. He was excited at the prospect of being able to count and "see" such tiny particles. Like everyone else he tried x-rays.

To his delight he found that even in quite dust-free air, the x-ray bombardment produced centres of condensation which made clouds form. This was the beginning of the work which later led Wilson to construct a special cloud chamber in which the drops of condensed cloud could be seen and photographed to record visually the paths of these rays and minute particles, invisible themselves.

For the first time atoms and rays could be seen "at work" and their effects studied in great detail. Today, the Wilson Cloud Chamber is probably the most important single piece of apparatus used generally by the atomic physicist.

ORIGINAL MODEL

It is remarkable that the first model, built by Wilson in 1911 and still preserved in the Cavendish Laboratory museum, was erected by him and used without significant alteration or replacement throughout his long and important series of investigations.

Having tackled rays of negative

electrons with such great success, J.J. turned over, later, to the study of positive rays. Such rays had been known for a couple of decades, but with the great improvements in technique which had been made by about 1905, Thomson was able to produce them and make measurements impossible before.

For one thing, the old vacuum pumps were tedious to work and could not remove condensable gases from the apparatus. Now it was possible to use charcoal cooled by liquid air to remove such vapors and gases and obtain a really efficient vacuum.


SPECTRUM ANALYSIS

One success led to another. J.J. showed that the positive ray particles were individual atoms and molecules from substances in the tube, and he devised a technique for spreading out the rays into a sort of spectrum of particles of different weight and charge.

It was the dream of the analytical chemist come true. You just put the substance into the bulb, worked the apparatus and out came a record from which you could tell what sort of atoms and molecules there were present. In fact, the new positive ray apparatus did more than chemistry ever could; it showed that for some elements there existed



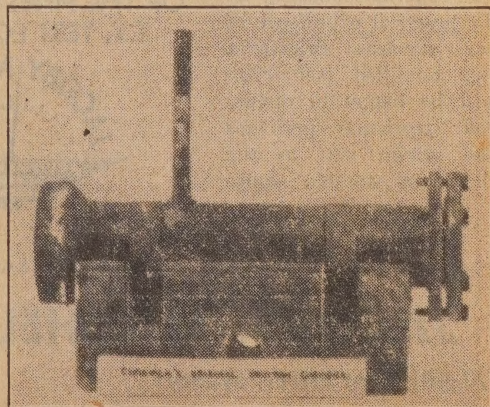
The original chamber with which Chadwick confirmed the existence of the neutron.



T.V. SERVICEMEN!

ARE YOU READY WITH YOUR ESSENTIAL TEST EQUIPMENT?

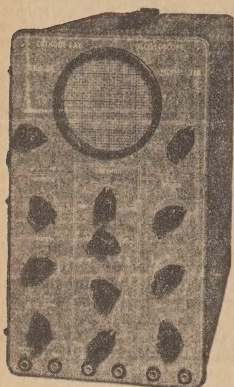Don't make the expensive mistake of waiting till transmission commences before selecting your test gear. Technicians who have their test equipment in time will enjoy increased profits while others regret their losses. Make sure you have the best when you need it — order NOW from the finest range of T.V. test equipment, **designed for Australian conditions.**



TAYLOR OSCILLOSCOPE MODEL 31A

This versatile and robust instrument is designed primarily for T.V. applications.

FEATURES INCLUDE:

- Wide bandwidth: 10 c/s-6 Mc/s.
- Hard valve linear time-base.
- 4in. diam. Cossor 88J (blue) C.R. tube.
- Y amp. cathode follower input, push pull output.

Finish — Hammertone grey, perspex engraved control panel.

PRICE: £112/18/6 (plus tax)

DISTRIBUTORS
OF THE FINEST MAKES OF
T.V. TEST EQUIPMENT




SOLE AUSTRALIAN AGENTS:—

JACOBY, MITCHELL & CO. PTY. LTD.

477-481 Kent Street, Sydney

Phone: MA8411

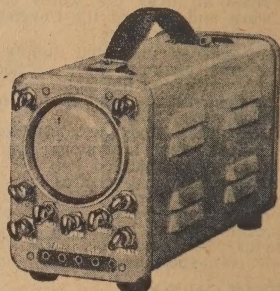

COSSOR 1039M PORTABLE OSCILLOGRAPH

Height, 5½in. Width, 4½in.
Length, 11½in.

Features include:

- Wide Bandwidth: 25 c/s to 1/5 M/cs.
- LF range: increased gain 25 c/s to 120 Kc/s.
- Continuously variable time base from 10 c/s to 50 Kc/s in 5 ranges.
- Input connections by five recessed sockets giving access to X and Y plates, amplifier, synchronisation and earth.
- Tube: 2½in. diameter.
- Weight: 9½lb.

PRICE: £54/11/- (plus tax)

two or more forms, identical chemically but of different weight.

For example, neon, whose chemical "weight" is 20.183, was found to be a mixture containing two varieties weighing 20 and 22 respectively. The recognition and disentangling of these different varieties of isotopes did much to help the formulation of new ideas on the structure of the atoms of elements.

It introduced regularity and whole numbers where discrepancy and apparently capricious values had been before. The work on isotopes was later developed to great heights by F. W. Ashton, who built his first Mass Spectroscope in the laboratory in 1919 and designed improved models in 1925 and again in 1937; it has now become a standard apparatus for industrial purposes.

ERNEST RUTHERFORD

The greatest of all J.J.'s band of research students was a young man who came from New Zealand to the Cavendish Laboratory in the crucial year, 1895. He was the first of the graduate students from other universities to be admitted to the laboratory.

So as not to waste time, young Ernest Rutherford brought his research with him and set about it immediately on arrival. He had made a new type of detector for radio waves, a magnetic apparatus that could receive signals over what was then a record distance of 1½ miles. Lord Kelvin advised him it was not worth taking out a patent, since there was no great financial future in radio—Kelvin's telegraph was very efficient!

Perhaps it was this discouragement, more probably it was the universal excitement over x-rays and the stimulus provided by the laboratory; by 1896 Rutherford was working with the new rays. He had entered the field of atomic physics which was to be his life work.


Soon he was off on his own track, trying to find out if the rays from uranium recently reported by Becquerel would give effects similar to those produced by x-rays. He quickly noticed that there were two types of ray from uranium and he called them by the first letters of the Greek alphabet, alpha and beta rays.

This was an exciting time for Rutherford. His private life was also exciting just then for he was successful in applying for the Professorship of Physics at McGill University, Montreal, and at last, in spite of the financial disappointment of the radio detector, he could afford to bring his fiancée over from New Zealand and marry her in Canada.

EXCITING TIME

Taking up the strings of his research again, Rutherford rode the crest of a wave. The isolation of radium by Pierre and Madame Curie had excited everybody, and Rutherford had triumphed after triumph in his ingenious and powerful experiments. He hunted down all the successive members in the many families of substances which undergo radioactive decay; changing from one element to another at each stage and emitting rays of various sorts in the process.

WHERE SO MUCH OF IT BEGAN

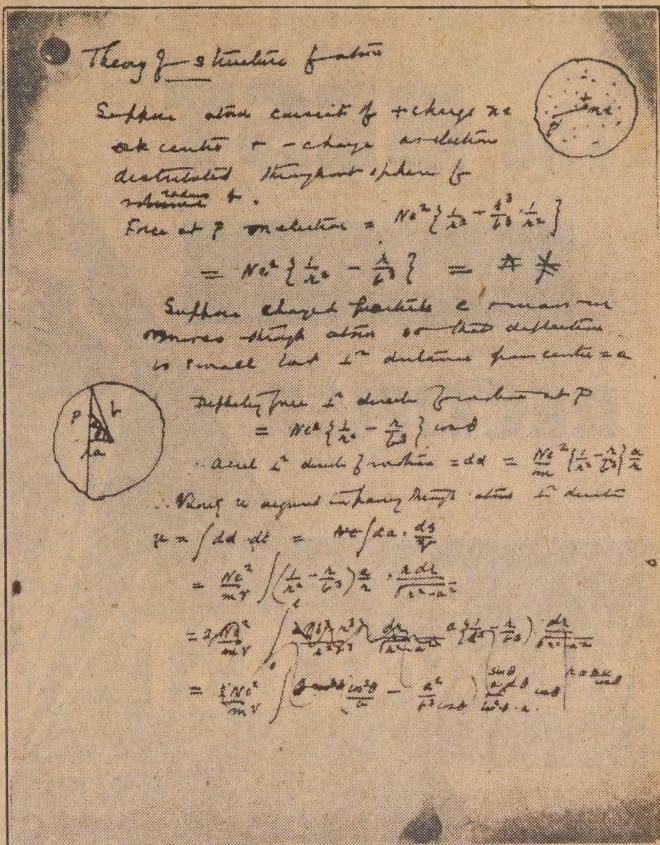

Lord Rutherford's first rough notes on the nuclear atom.

He investigated the rays themselves and found that the alpha rays consisted of charged atoms of helium. He was already the acknowledged leader in this field of research.

In 1907 Rutherford returned to Europe to hold the Chair of Physics at Manchester University. His work continued, and gradually the facts of radioactivity began to fit into a scheme.

His colleague at Manchester, Geiger, had been studying the way in which such particles could pass through solid matter. The atom must consist of a small solid core, surrounded by a lot of empty space, and the nature of the scattering gave Rutherford the clue as to how the solid core was constituted.

In 1911 he announced his theory of the nuclear atom consisting of a positively charged core surrounded by a sphere of electrification; the theoretical consequences agreed completely with the measurements of scattering. This model was quickly elaborated and adapted into the picture that is still in use today.

The Dane, Niels Bohr, was the first to see that the inherent contradictions of Rutherford's static

model could be saved by applying the new quantum theory, which had just been developed to account for the distribution of light given off by hot bodies. The whole new theoretical approach to atomic physics was off to a flying start.

The first world war broke up Rutherford's team of research workers and more pressing needs deflected his attention from the purely academic atomic research. In 1919 he was able to publish another epoch-making investigation. He had continued his work with alpha particles and, while bombarding nitrogen gas, he noticed a curious effect.

ANOTHER DISCOVERY

Careful checking revealed that the alpha particles must have broken up the normally stable nitrogen and made it split just like a radioactive substance. With a pocket-sized, simple piece of apparatus he had been the first man to "split the atom" artificially.

In the same year he returned to the Cavendish Laboratory as its

(Continued on Page 15)

The BEST

MINIATURE

RECTIFIER

at
NO extra COST

350 volts
at
90 milliamperes D.C.

"Miniwatt"

6 V 4

PHILIPS ELECTRICAL INDUSTRIES PTY. LIMITED



PHILIPS



INNOVAL Type 6V4

An indirectly heated miniature rectifier designed to meet the requirements of modern multi valve equipment, offering as it does the highest output current of any miniature rectifier. For equipment requiring less current, the added safety factor is of real value.

For full data and characteristics apply
to your nearest Philips branch.

PV12A.55

Sydney, Melbourne, Adelaide, Brisbane, Perth

NOVEL PLANE SOARS AND FLIES



Shown in flight, the convertiplane combines the features of a helicopter and a normal airplane.

The McDonnell XV-1 convertiplane recently performed for the first time in history full conversion in flight from helicopter to conventional forward flight and then back again to helicopter flight to make its landing. The plane has a rotor overhead, a pusher propeller, and stubby wings. It is being developed for the US Army

THE aircraft uses the overhead rotor, like that of a conventional helicopter, to take off vertically. Upon gaining a safe height above the ground, the pilot shifts the power from the rotor to the pusher-type propeller behind the cabin, or pilot's compartment.

Thereupon, the machine moves forward as an airplane. Its overhead rotor is kept spinning at a speed to provide a little lift and the least drag.

To land, the pilot reverses the process, transferring power from the pusher propeller to the rotor and then, when forward speed has diminished, settles to earth like a helicopter.

The XV-1 is designed to carry three passengers, or two litter patients, and a medical attendant, in addition to the pilot. It is 30 feet (nine meters) long, 10 feet (three meters) high, and 26 feet (7.8 meters) wide. Since it is mounted on skid-type landing gear, it is unable to land as a conventional plane.

Military experts view this type of plane as having potentials for many important military tasks, although there is a long way to go before it is perfected. They point out the plane embodies all the versatility of the helicopter—the ability to perform reconnaissance, liaison, search and rescue and troop carrying and cargo-carrying operations—but it

will be able to carry out missions at much greater speeds and in longer range than the helicopter.

The exact performance capabilities of the XV-1 are secret, but its speed is much greater than that of the helicopters of comparable size. Helicopters are limited in speed because of their dependence solely on the overhead rotor.

Convertible enthusiasts see a great commercial future for the craft in

the medium-range field. Unlike vertical take-off planes, it rises with the cabin in level position. It has the safety advantage of being able to pull up short if it runs into trouble and to come down vertically in the nearest clearing. However, its commercial future is viewed as being some years away.

Several countries are developing convertiplanes, but this is the first to prove in actual flight that the convertiplane works.

SUPERSONIC SPEED RESEARCH

THE worlds fastest, highest-flying airplane, the rocket-powered Bell X-1A, is currently being used for research on the heat barrier. The Bell X-1A has been flown by a pilot to a world's record speed of 1650 statute miles (2654 kilometres) an hour and to a world's record altitude of more than 90,000 feet.

A sister plane, the Bell X-1E, is under modification for an extremely thin wing and for large tanks for its rocket fuel. It too will be used for the study of aerodynamic heating at supersonic speeds.

A third Bell experimental plane, the X-1B, is at Langley Field, Virginia, having structural temperature gauges installed throughout to check heating in great detail at every point or air friction.

Meanwhile, a Douglas rocket-powered Skyrocket plane is being used to explore means of carrying bombs or fuel tanks beneath the wings at supersonic speeds. The Douglas Skyrocket has been flown 1,327 statute miles (2135 kilometres) an hour and has reached an altitude of 83,235 feet (25,370 metres).

Still another experimental aircraft, the stiletto-like Douglas X-3, is testing the puzzling behavior of air in the transonic range — the extreme buffeting that occurs in the speeds ranging from 600 to 800 statute miles (960 to 1,280 kilometres) an hour. This plane, whose performance is secret, is longer and heavier than the Douglas DC-3 transport plane, yet it flies on wings smaller than a DC-3's tail.



"THE LANDING OF CAPTAIN COOK" by Philip Fox. By Courtesy of the NATIONAL GALLERY OF VICTORIA.

"Captain Cook Discovers New Continent"



RADIO AUSTRALIA flashes daily news around the world. Jocelyn Terry is shown here broadcasting messages from home to Australians in lonely outposts in Antarctica.

This was stirring news to the world of 1770, but it was three months before King George III of England heard about it.

Today, news like this would be flashed round the world by radio.

In Australia from Cape York to Hobart, from Brisbane to Perth, radio listeners hear immediately about any important national event.

Research Helps Radio Progress

The SHELL Company employs 5,000 research scientists. Some of the work they have done for radio has improved various parts of electrical equipment such as enamelled wires, insulating materials and resins which effectively seal radio condensers.

If it were not for these important things which are used in your radio, the set would not stay in such good order that you can be sure of being able to hear every item of news in which you are interested.

Shell shares in the advancement of radio technical equipment for the benefit of listeners.



REACTOR FOR MEDICAL RESEARCH

The first atomic energy reactor specifically designed for medical treatment and research will be built for the University of California at Los Angeles Medical Centre by North American Aviation's Nuclear Engineering and Manufacturing Division, it was announced recently in the USA.

THE new reactor will produce gamma rays and neutrons for cancer therapy, and also has been designed to serve a variety of additional medical and non-medical uses. These include the production of radioisotopes, and radiation for experimental sterilisation and preservation of food and drugs by nuclear energy.

The reactor, which is expected to be completed within one year, also will be available for use by the Atomic Energy Commission in conjunction with the Atomic Energy Project at UCLA, where both classified and unclassified research in biology and medicine is carried on.

WORKING MODEL

A working model of the reactor was demonstrated at a conference on the UCLA campus near the site where the actual machine will be installed in a new underground wing of the University's Medical Centre.


Designed to operate at a power level of 5 kilowatts, with a maximum power of 50 kilowatts, the medical reactor will produce a high intensity of neutrons, subatomic particles available only from a nuclear reactor in the large amounts required for medical therapy and other atomic research. Gamma rays produced by the reactor will be of greater intensity than those produced by 50 pounds of radium.

The reactor's atomic fuel is to be obtained on loan from the AEC, and will consist of about four gallons of uranyl sulphate solution, highly enriched in Uranium 235, contained in a one foot stainless steel sphere, or core.

CORE SHIELDING

It is the "splitting up" or fissioning of the Uranium 235 atoms in the solution which provides the gamma rays and neutrons for medical treatment, and other nuclear research. The core will be located inside a 5 x 5 x 8 foot stack of graphite bars, shielded by five feet of high density concrete. Radiation ports will lead from the core to a patient treatment room, laboratory, and another room where research on animals can be performed. An access port will permit materials to be irradiated in a channel leading inside the core itself where radiation will be the strongest.

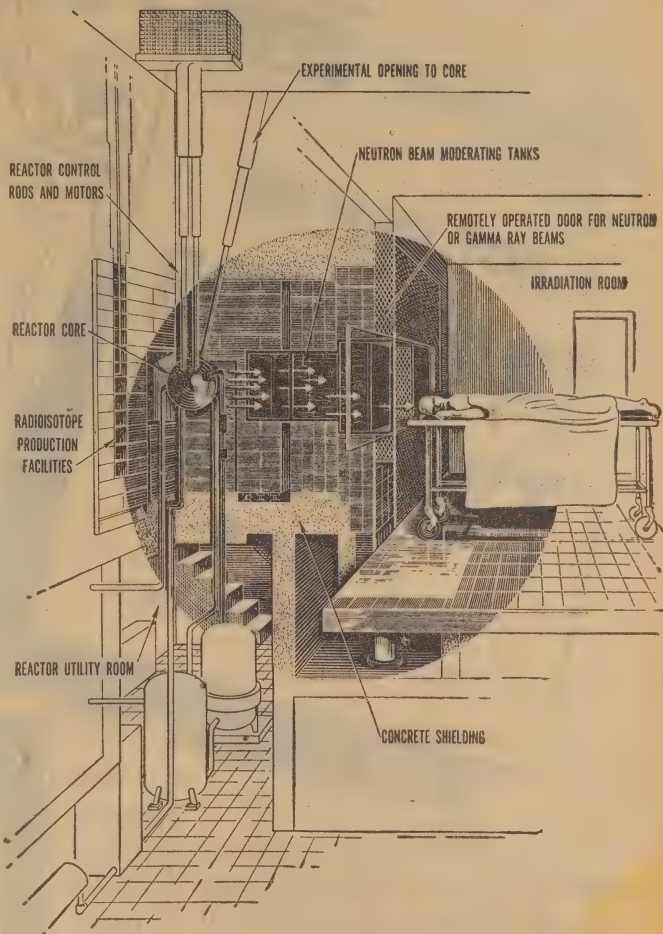The underground reactor wing housing the complete installation



Artist's sketch of the reactor. It will also be used to produce radioisotopes and radiations for studies in the preservation and sterilisation of food. This picture shows the reactor proper.

will be about 45 feet wide, 60 feet long, and 27 feet high.

Rate of fission will be adjusted by control rods made of boron, which can be moved in and out of the core areas. Boron absorbs neutrons, thus when the rods are near the core neutrons are "soaked up". As the Uranium 235 atoms are split when hit by neutrons, fission will stop when the neutrons are caught by the boron rods.

The solution type reactor will be self-contained, with no radioactive particles, fumes or smoke being exhausted into the atmosphere or public disposal systems.

Either gamma rays or neutrons can be obtained from the reactor for cancer treatment. While both are

radiated from the reactor during the fission process, gamma rays or neutrons can be selected by use of special shielding equipment between the patient's room and the reactor core. The size of the radiation port can also be varied to provide radiation in the required amounts of intensities.

DEEPER PENETRATION

Gamma rays destroy cancer cells much in the same way as is done by x-rays, but the gamma rays penetrate deeper through tissue, and are much stronger than x-rays.

Irradiation of cancer cells with neutrons is often accomplished by the "boron capture" technique. This requires the injection into a tumor



- * HERMETICALLY SEALED
- * METAL CLAD
- * ROBUST, RELIABLE
- * OPERATES EFFICIENTLY UP TO 300 KC.

A virtually unlimited range of applications awaits this new transistor in the field of INDUSTRIAL ELECTRONICS AND RADIO.




MINIWATT DIVISION
PHILIPS ELECTRICAL INDUSTRIES
PTY. LTD.

69 CLARENCE STREET, SYDNEY

PV14-55

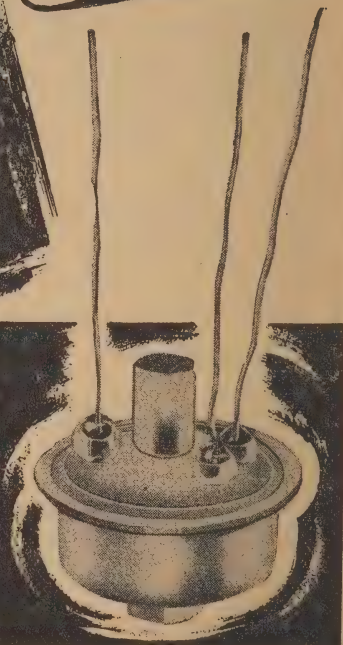Send this coupon for technical information and data sheets.



PHILIPS ELECTRICAL INDUSTRIES PTY. LTD.

Please send me technical data sheets for Transistor Type OC15.

NAME _____

ADDRESS _____

DATE _____ Signature _____

f a solution containing the element oron. Due to the particular nature f the cancer cell, the cancerous tissue absorbs the boron much more ickly and in greater amounts than es healthy tissue. When the caner area is bombarded by a stream f neutrons, the boron atoms in the cancer cells release "alpha particles". These particles, which are tiny masses carrying an electrical charge, nd weigh about four times as much s a neutron, are effective cancer ell killers. Alpha particles have a hort penetration range, primarily onfining their destruction to caner cells and doing relatively little arm to healthy tissue.

RADIOISOTOPES


As a local source of radioisotopes he new reactor could make a aterial contribution to the expanding echnology in this rapidly growing field. Radioisotopes, particles made radioactive by neutron exposure from the reactor, can be "salted" into almost any material concerned with the fields of medicine, agriculture, or industry. By radioactive detection devices, these radioisotopes can be followed or traced to reveal what goes on inside human systems, plants, processes, and machinery.

Although radioisotopes are available from reactors located in various parts of the country, the strength of the radioactivity of these materials is often dissipated by the time they have travelled long distances to the point where they are needed. The UCLA reactor could provide these materials at near full strength for requirements in this area.


The experimental use of radiation from nuclear reactors to preserve and sterilise foods and drugs is a promising field which is expected to lead to revolutionary processing methods. Research in this field has already demonstrated the possibility of increasing the "fresh" life of meat, vegetables, and dairy products by atomic radiation.

Use of radiation. sterilisation in the pharmaceutical field also offers a number of benefits. For example, sterilisation processing requiring high temperatures which often reduce the strength and effectiveness of drugs might be replaced by radiation processing at room temperature. Nuclear researchers at UCLA have scheduled times with the reactor for this type of developmental work in addition to their other studies.

MODEL OF THE MEDICAL REACTOR

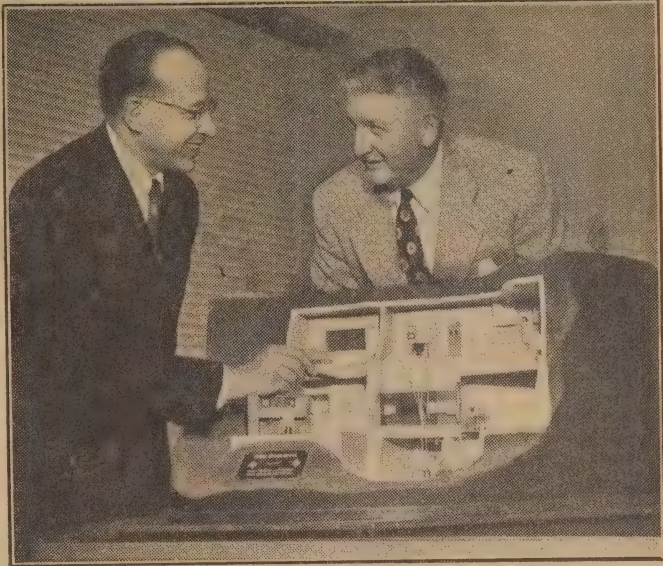

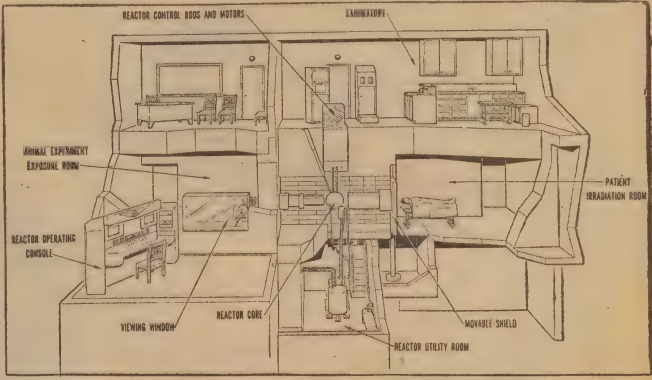Dr. Chauncey Starr, left, and Dr. Stafford L. Warren, Dean of the UCLA Medical School, discuss model of the 50 kilowatt reactor. Scheduled for completion in about one year the reactor will be used for other nuclear studies in addition to medical research.



This sketch shows the general layout of the reactor. Compare with picture on page 11.

ARMY WANTS "FLYING MATTRESS"

BRITAIN'S M.L. Aviation Company state that they are constructing several development prototypes of the light utility aircraft which, when first announced in August, achieved international recognition as the "flying mattress". The subject of a Ministry of Supply contract, this aircraft was designed as a simple, cheap, light aeroplane for use with the Services, particularly the army. In order to provide adequate wing area and structural strength and, at the same time, keep down the total weight, an air-inflated wing of delta shape was specified. Aerodynamic contour is maintained by internal, spanwise diaphragms which join the upper and lower surfaces so that the ex-

ternal shape, when inflated, is similar to that of a conventional aerofoil. This wing, which is made of high quality, dinghy-type fabric, is cheap to produce and light—it weighs about 100lb. When not in use, it can be rolled up into a relatively small container. It is inflated by means of a mechanical pump or bellows and, in the air, a windmill pump maintains the required pressure of under 1lb per sq. in. Inflated elevons—controls that can be used together as elevators or differentially as ailerons—are fitted to the trailing edge of the wing. The wing is attached to the fuselage—which, on the first proto-

type, was a wooden carriage providing positions for pilot, passenger, engine and fuel—by vertical struts. Control is exercised by means of a hanging control column connected by cord or cable to the pneumatic control surfaces. The first prototype was fitted with a constant-speed American 65 hp engine intended for pilotless aircraft. Obviously, more suitable power plants will have to be fitted to later models, and the M.L. Company plan to adopt a British engine for production versions. The aircraft weighs 550lb and can carry a load of some 400lb. Take-off and maximum speeds are 18 m.p.h. and 45 m.p.h. respectively.

A new Range
of

ROLA

MIDGET MODELS


for...

A.C. and Battery Models


Personal Portables

Drive-In Theatre Systems

Inter-Com. Applications

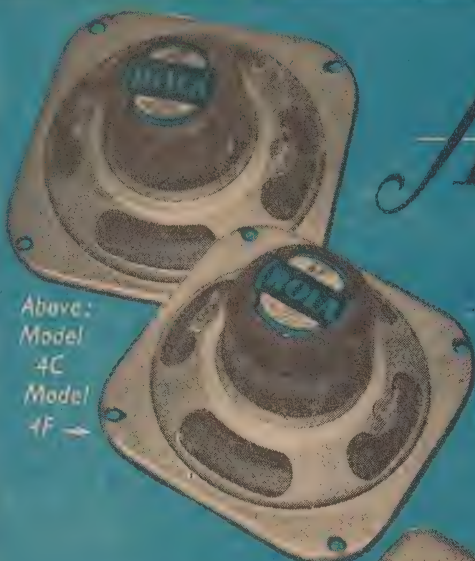

Above:
Model
4C
Model
4F →

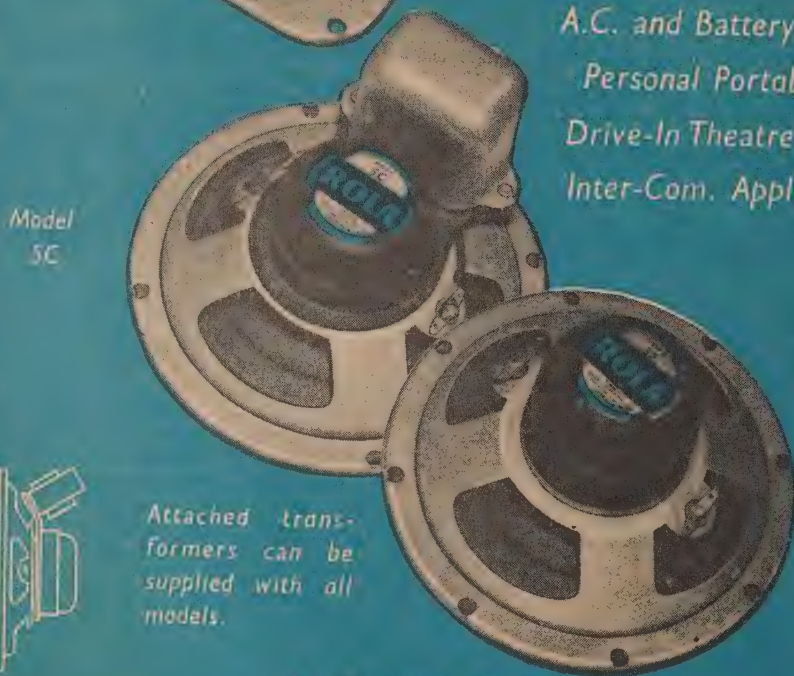

Model
5C

Model
5F

Attached trans-
formers can be
supplied with all
models.



Full Technical Details From:

ROLA COMPANY (AUST.) PTY. LTD.

THE BOULEVARD, RICHMOND, VIC. 3121. 116 CLARENCE STREET, SYDNEY, N.S.W. BX 3996.

SCIENCE NOTES BY PROF. A. M. LOW

By now we are quite used to the idea of flight into the stratosphere by man but not, I think, by insects. Our impressions are due for an overhaul, I'm afraid.

A FEW years ago a small "Scientific Army" explored the upper air in order to find out how certain insects, fatal to the well-being of man, spread out all over the world.

The aircraft used were equipped with special insect-catching traps.

Spiders were found three miles above the earth and mosquitoes as high as 5000ft!

That menace to the world's cotton crops, the pink bell-worm moth, was caught more than a mile above our earth and numbers of ants, sandflies, lady-bird beetles and various small insects were found in the traps at a height of 15000ft.

WIND CURRENT

It was obvious to experts that these "travellers" took advantage of favorable wind currents. They do not like rough and variable winds and will not set out on a sky trip when there is a calm. But with the winds as they want them, insects use these aerial routes to distribute themselves around the world.

On investigation it was also discovered that there are actually insect "tramps" which crawl on to the backs of other insects and squat there, travelling in perfect comfort.

It is strange that, while man is so proud of his flights into the "stratosphere", he forgets that insects have been using this route for centuries! But enough of that.

It is strange that we still specify the testing machinery by distance, "Drive slowly for the first 500 miles," we say.

Then again, after a general overhaul we are often told not to exceed, say, 35 miles per hour.

Although it is not a good thing to produce a high cylinder temperature by a wide open throttle, the main reason is not one of explosion pushing the piston too hard but of the terrific forces, amounting to many tons, exercised in the engine by the reversal of reciprocating parts.

TIME AND DISTANCE

Time and distance, if not the same thing, are closely connected and, in the aircraft world, we mix distance and time almost indiscriminately. The fact is the faster we travel, the more time matters instead of distance.

I was at an exhibition of flying models recently and saw an improved type of skimmer, part aeroplane and part high-speed seacraft.

Think for a moment of the problems of science in connection with boats, waves and ocean-going liners. Our present ideas of ship design are very conservative.

This is my point. On a small outboard boat, when air is passing gaily under the hull, slight ripples in the water do not matter terribly. But, if the boat were a model I fly long the least ripple would swing it.

Supposing it were a quarter-mile long, would it not by the same argument skim over quite large waves simply because it covered sufficient of them to produce what we call smoothness?

If so, it suggests the possibility of fast skimming ships for carrying freight across the Atlantic, leaving it to aircraft to take expensive passengers, at least before the days, when space ships ultimately take the air.

Or rather, not the air, for these 5000 mph vessels which we shall undoubtedly have in the far future could not possibly travel where our atmosphere exists.

Rockets work far better in a vacuum.

SELF DECEPTION

One has to be very careful to avoid self deception. When a car is running forward on the level with throttle closed preparatory to braking, it often seems to leap forward when it is put into neutral.

This forward leap on level ground is simply an illusion. The reason is that deceleration is decreased because, unless power is given to the car, it cannot jump forward.

The retarding effect of an engine acting as a brake is very considerable, for mechanical efficiency is never high. Disconnect the engine

and the rate of deceleration is greatly reduced.

Doubtless, you will have witnessed the trick of lifting the heavy man. He is sat in a chair and four people put their hands under him in various places, then find that they cannot move him an inch.

The person who is carrying out the trick instructs two of the audience to put their crossed first fingers under his armpits and two others their crossed fingers under the bend of the knee.

He seriously checks that fingers are crossed; he warms his hands, rubs them on his coat and puts them close together not quite touching as if he were trying to feel some tension between them.

He explains to his audience how friction generates electricity, talks of clouds rubbing together and producing lightning, or the simple experiment of drawing sparks from dry brown paper.

HIS "LINE"

He tells the audience that he can electrify the man and thus reduce his weight by interfering with gravity. They will believe anything if it is said convincingly enough.

Having "electrified" the man by placing the rubbed hands behind his head, he very solemnly and slowly tells his lifters all to lift together on "three". Count one, two, three and up will go the man like a rocket.

The reason, needless to say, is that never before have they with confidence lifted together. You try it!

How Modern Physics Began

(Continued from Page 7)

chief. J.J. had been called to the Mastership of Trinity College, though he continued to hold a professorship and work at the laboratory until his death in 1939.

Rutherford was much stimulated by returning to the Cavendish Laboratory, and he found a keen assistant there in Aston, who was then just publishing his results on the discovery of isotopes. He continued his work on artificial disintegration, and was led by the results to throw more light on the structure of the nucleus of the atom.

Already in 1920 he was forecasting—though from erroneous data—the existence of neutrons, "heavy" hydrogen and other atomic entities.

From 1920 onward the pace of atomic physics had increased so greatly that any history of the period tends to become a list of names and discoveries. In 1932 alone, Chadwick was able to confirm the existence of the neutron and measure some of its properties, and Cockcroft and Walton were able to make the great two-million volt machine which could shoot protons at such high speeds as to split atoms completely artificially.


This machine with its strange and futuristic appearance, marked the beginning of a new attitude in the

laboratory. Large and complicated pieces of machinery were needed for atomic research; teams of workers had to be mobilised around each device to satisfy its needs and to take from the monster all the results it could supply.

Rapidly following the apparatus of Cockcroft and Walton came the development in America of the cyclotron, which provided an even more efficient gun for shooting at the atomic nucleus.

The discovery of the neutron soon led to the study by Fermi of the effect of neutron bombardment on uranium and the production by Hahn of the artificial elements beyond uranium. By the beginning of World War II nuclear physics was already very near, in theory, to the possibilities of the atomic pile and the bomb.

It required tremendous expenditure of manpower, money and scientific inquiry to bring them to success, but the basic facts of atomic structure were known. They had been elucidated by men like Thomson and Rutherford, and their colleagues all over the world. These men had penetrated the simple, hard and solid Victorian atoms, and founded a new science to explain the intricate mechanism of subatomic building blocks.

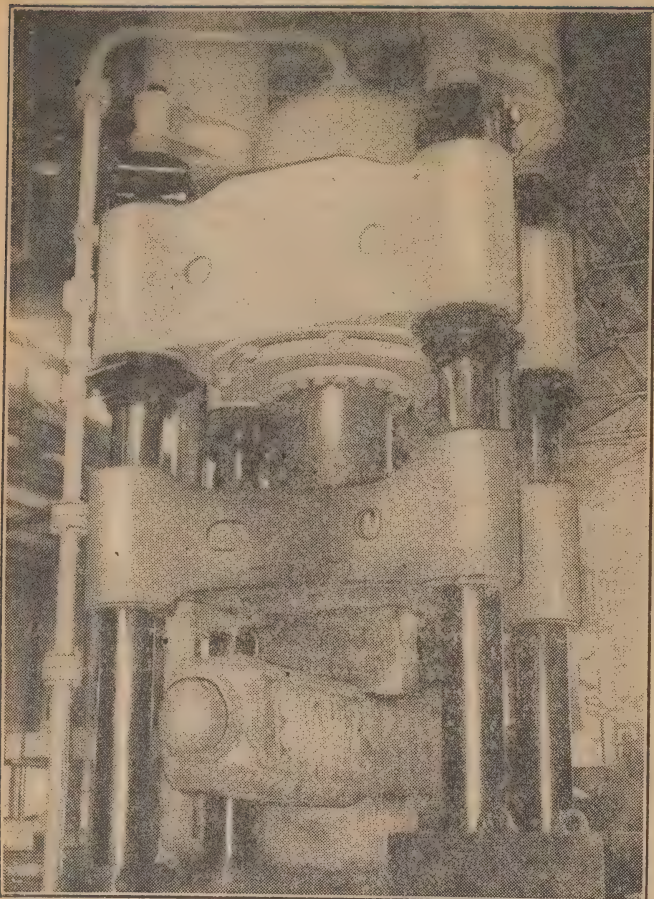

This picture of a 2000-ton hydraulic press shows clearly the large piston and cylinder, the 15-ton ingot resting on the anvil and the hammer guided by the four pillars at each corner of the press.

shapes from thick metal, compress cotton and wool bales, express oils, bend iron plates and bars, raise bridges into position, lift automobiles and heavy trucks into the air, stop the same vehicles with powerful brakes, prop up the roofs of mines and scores of other things.

The term hydraulics does not necessarily mean that water is used as the motive power. This was so in the early days but nowadays all kinds of fluids are used including oil, water and glycerine, water and glycol and synthetic fluids.

Now Pascal did not live long enough to see his law put to much use for it was not until about 150 years later that an English chappie named Brahmah, working as an apprentice to a cabinet maker, had a bright idea. He invented a hydraulic press.

All he did was to enclose some water in a cylinder and pump it into another cylinder of different dimensions, whereupon the piston contained in the latter was caused to rise and lift a flat plate which was attached to it. The plate came into contact with a similar fixed plate and anything placed between was, of course, subjected to considerable pressure.

HOW PRESSURE MULTIPLIES

Now this sounds a bit haywire at first, because how can the mere pumping of fluid from one cylinder to another cause an increase of pressure? Easy. Just look at the annexed figure.

Here we have two cylinders A & B fitted with pistons, or rams as they are commonly called, which are ewsed (sorry) used to apply and receive the forces.

The cylinders are watertight, and the rams slide freely in the cylinders,

HYDRAULIC POWER IN INDUSTRY

The great progress made in the use of hydraulic power has been one of the outstanding features of engineering in the present century. There are many engineering processes which just cannot be satisfactorily carried out by any other method.

WHEN, in the 17th century, the French philosopher and mathematician Blaise Pascal, enunciated his Law of Hydrostatics he little thought that it would have such widespread effects.

This law states: "The pressure exerted anywhere upon a mass of liquid contained in a closed vessel is instantaneously transmitted undiminished in all directions and acts with the same force on all equal areas of the surface of the vessel in a direction perpendicular to the inner surface of the vessel at any point."

There you have it, and because it says what it says we are able by means of a fluid enclosed in a vessel to raise lifts full of people, steer ocean liners, stamp out various

ders, which are connected at the lower end by a pipe.

The cylinders are filled with fluid. It must be remembered that fluids are incompressible. This is a very important thing to remember.

Now let us imagine that ram (a) has a piston area of 50 square inches cross section and ram (b) has a piston of 100 square inches.

In the picture (a) is at the top of its stroke thus causing cylinder A to be full of liquid while (b) is at the bottom of its stroke and the cylinder B contains a minimum of liquid. It is important to digest all

by Calvin
Walters

this, so I will give you two minutes to read it all again while I go and listen to Jack Davey on the radio.

OK! Here I am back again. It wasn't worth listening to. Sooner have Bob Dyer.

Now you have got all this straight we will assume that a force of 50,000 pounds is applied to the top of ram (a). As the area of this ram is 50 square inches the pressure applied to the liquid is 50,000 divided by 50 which equals 1000 pounds to the square inch.

This pressure is transmitted throughout the whole liquid into cylinder B and acts upon the under surface of ram (b) in cylinder (b).

Ram (b) has to go somewhere, so it goes up, and the force acting on the bottom of this ram is 1000lb per square inch. But this ram has an area of 100 square inches, so that the total force transmitted to this ram is 1000 times 100, or 100,000lb per square inch.

As can be seen this is an enormous multiplication of force in the simplest possible manner.

Another point worthy of note is the balanced system of load and effort. This can be seen from the following:

A SIMPLE SUM

When ram (a) has fallen say a distance of 10 inches, a volume of fluid equal to 10 inches times 50 square inches (the area of this ram) passes into cylinder (b). That is, 500 cubic inches of fluid have passed into cylinder (b). Ram (b) will therefore rise a distance of 300 cubic inches divided by 100 square inches, the area of ram (b). This equals five inches rise.

Thus the work applied to ram (a) equals 10in movement x 50,000lb load equals 500,000 inch pounds. The result of the effort on ram (b) equals 5in movement x 100,000lb load equals 500,000 inch pounds.

This is a bit mathematical, but I put it in for those inclined that way. Really it is very simple.

These mathematics are the basis from which all hydraulic power transmission calculations are developed. Now I hear someone say "So what?" Well, if you are interested enough to read this far you might as well go the distance, which embodies no more mathematics.


If you look again at the diagram you can see that cylinder (A) could be a pump while cylinder (B) could be a hydraulic machine such as a press, lifting jack and so on.

All sorts of combinations can be obtained. There can be combinations of low power and long stroke, high power and short stroke and so on.

SIZE AND STRENGTH

There are devices which, are attached to hydraulic systems which feed extra fluid into the system when required—valves and electrical contacts and many other extra devices. There are intensifiers which increase or intensify the pressures exerted. All these reinforce the

CANNON BARREL UNDER PRESSURE

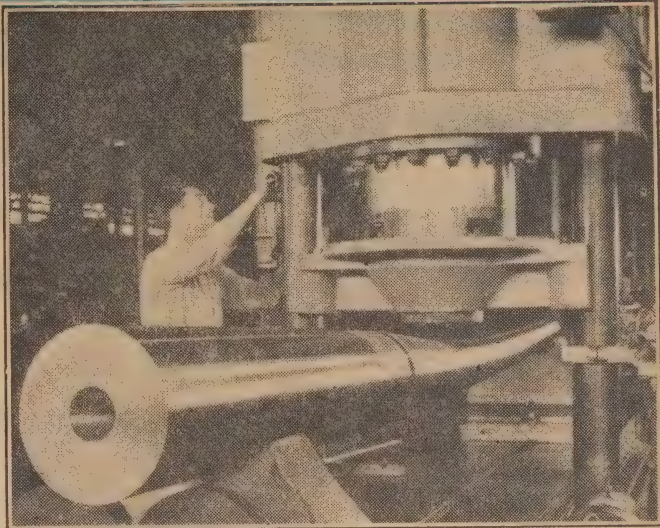

Some idea of the great pressure exerted by even a small press is illustrated by this picture of a big gun barrel being straightened. One can imagine the great force needed to bend the barrel.

effectiveness of the hydraulic power system to enormous figures.

The design of hydraulic machines is all a matter of size and strength. Needless to say if a cylinder has to withstand pressures of say 12,000 tons per square inch it must be pretty strong. Many presses do indeed apply pressure of this nature and they are enormous structures.

It is easy to see that the only limit to the pressures that can be generated lie in the ability of engineers to make cylinders strong enough to withstand them.

Imagine instead of the simple apparatus described above, a machine consisting of a ram with one cylinder as before applying a pressure of say 100 tons per square inch to the larger plunger. This latter could be used to apply pressure to a second system and so on. The pressures could be applied indefin-


itely so that fantastic pressures could eventually result.

Hydraulic presses have superseded the old steam hammer, which was a noisy affair. It consisted of a heavy weight which was dropped onto the red hot metal to be forged. Present day technique uses a hydraulic press, which not only applies far greater pressure but which is almost noiseless.

Some presses used in powder metallurgy can press powdered metal into a mass so solid as to be almost indistinguishable from a piece of cast metal.

By means of dies the powder is shaped by filling the die and applying pressure with a hydraulic press. The result is mostly better than forging or casting because of the lack of flaws and distortion by heat and so on.

Today it is possible to obtain

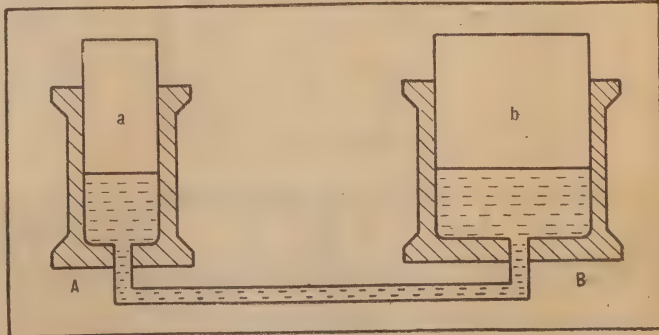

This diagram illustrates the principle of the hydrostatic force multiplier.

• **EVERYTHING** for the Radio Hobbyist


IT PAYS TO USE **MAGNAVOX**

PERMAGNETIC CENTRE POLE SPEAKERS

The **ONLY** Speakers with all these outstanding features:

- Fully detachable and interchangeable cone head assemblies. (See illustration.)
- Damaged cones easily replaced in 3 minutes.
- All transformers tropic proofed and interchangeable throughout the range.
- Full range of transformers with impedance clearly branded.
- Transformers held with P.K. screws—no drilling or punching—no nuts to lose.
- 5in, 6in, 8in, 10in, 12in speakers available with heavy or medium duty magnets.

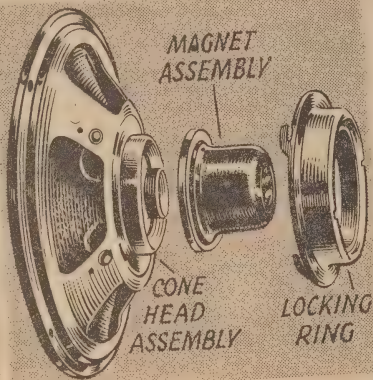Spare Cone Heads also Available from Stock



NOTE THESE COMPETITIVE PRICES

MODEL	PRICE	MODEL	PRICE
525	43/-	8P1	63/-
6P2	54/7	10P2	67/3
6P1	58/11	10P1	72/9
8P2	57/5	12P2	72/4
		12P1	81/-

The **WARBURTON** **FRANKI PAGE**

Check it each month

PHILIPS' TRANSISTORS

TYPE OC70	£1 17 10 ea.
TYPE OC71	£1 17 10 ea.
TYPE OC72	£2 10 5 ea.

ALUMINIUM CHASSIS

6 x 4 x 2	7/9ea.	13 x 10 x 2½	18/9ea.
8 x 5 x 2½	10/6ea.	17 x 8 x 3	22/7ea.
10 x 6 x 2½	11/6ea.	17 x 10 x 3	25/8ea.
11 x 8 x 2½	15/1ea.	17 x 12 x 3	27/3ea.
13 x 7 x 2½	15/1ea.		

HYDROMETERS

ORMISTON 11/- ea. Vesta 7/6 ea.

MAGNETOPHON TYPE L.G.S. RECORDING TAPE

1200' 65/- 600' 39/-

SPINTITES

1/8" WHIT 8/8 ea.; 5/32" WHIT 8/- ea.;
3/16" WHIT. 8/4 ea.

Select records in an instant

... FILE IN

"RECORDEX"



- Holds 10in or 12in records.
- Engraved easy to read index strip.
- Complete with index card and gummed identification numbers for the records.

25 RECORDS CAPACITY --- 17/9
50 RECORD CAPACITY --- 35/-

WARBURTON FRANKI (MELB.) LTD.

380 BOURKE ST., MELBOURNE, C.1... PHONE: MU6355

**OPEN
SATURDAY
MORNINGS**

**TRADE
SUPPLIED**

... **POSTAGE OR FREIGHT MUST BE INCLUDED WITH ALL ORDERS** ...

metal sections of an infinite variety of shapes. These are usually made by forcing solid metal through dies by means of hydraulic machines.

In the forming of large panels for cars and aircraft a stretching press is usually employed. The sheet of metal is first roughly shaped into the required profile in the flat. This is then held by grips along the four sides and laid in the flat over a die. A hydraulic ram then applies the necessary pressure and so stretches the metal into the required shape.


In the rubber industry where moulding and vulcanising play an important part hydraulic presses are used almost exclusively, and the very long life of a present day motor tyre is due to a large extent to the very effective bonding of the various layers made possible by the great pressure available from the presses.

The plywood industry is dependent upon hydraulic presses for the high quality of modern bonded woods.

Some interesting applications of hydraulic power exists in the mining industry, two notable examples being the hydraulic burster and the hydraulic pit prop.

In order to obviate the dangers

DIAGRAM OF
HYDRAULIC
PIT PROP

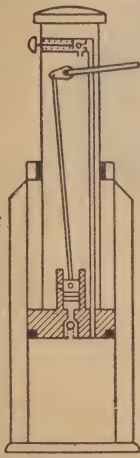

attendant by explosive charges for blowing down a face of coal in a mine, the hydraulic burster was developed.


Explosives can ignite dangerous gases and cause disasters. It can shake the foundations of the roof and cause these to collapse.

The hydraulic burster consists of a round stainless steel bar with chambers at intervals containing a series of telescopic pistons which act at right angles to the axis. These are prevented from coming right out by means of stops at the inner ends.

In use, the burster, which is about 2½ in diameter, is placed in a hole about 3 in diameter, previously bored in the coal or rock.

The burster is connected with a hose to a pump at a safe distance and pressure applied. Pressures of up to six tons per square inch are applied and the effect is to literally burst the seam of coal asunder. Up to 20 bursts per hour can be achieved with one burster which is,

12,000 TON PUSH FOR AIRCRAFT

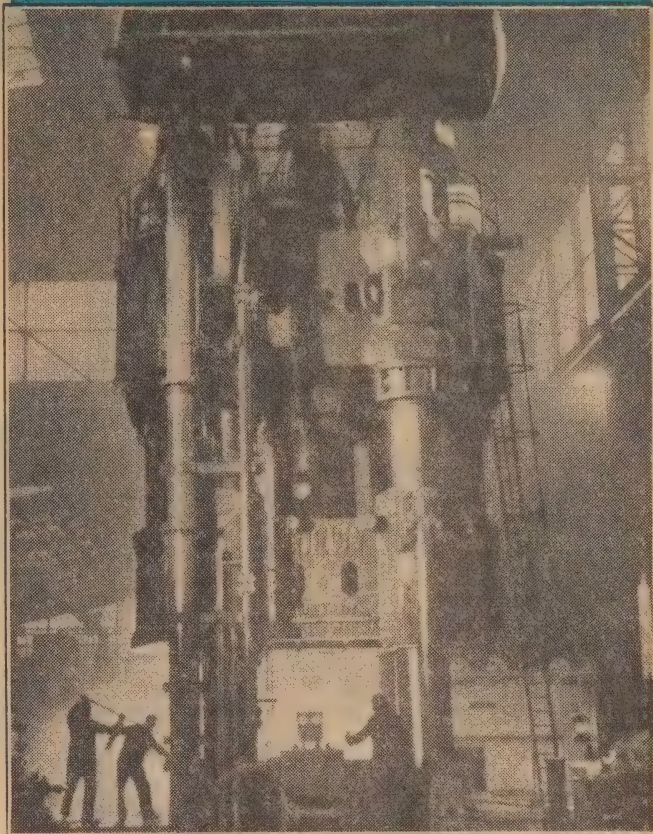


One of the largest presses in Europe, this monster creates a push equal to 12,000 tons and is used for fabricating light alloy parts for the aircraft industry. It is 42ft 9in high, with a 13ft 7in section underground. It cost £500,000 to build and instal.

of course, recovered from the coal afterwards.

The hydraulic pit prop is rapidly finding favor because it does away with expensive timber propping of the roofs of mine tunnels. It is


really a single acting hydraulic jack with a built-in manually operated pump.

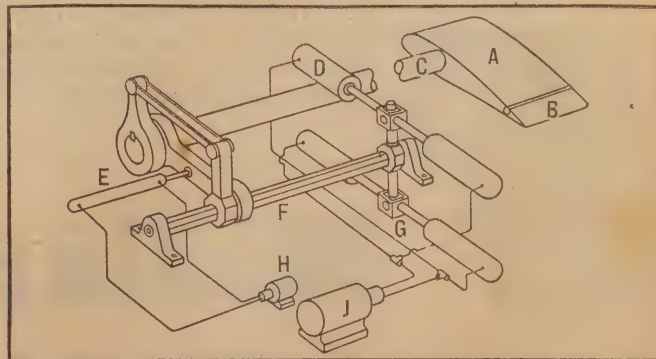It can be extended from 23 to 92 inches and has at the top a friction (Continued on Page 79)



This diagram illustrates the principle of the Denny-Brown ship stabiliser.

New Neat...

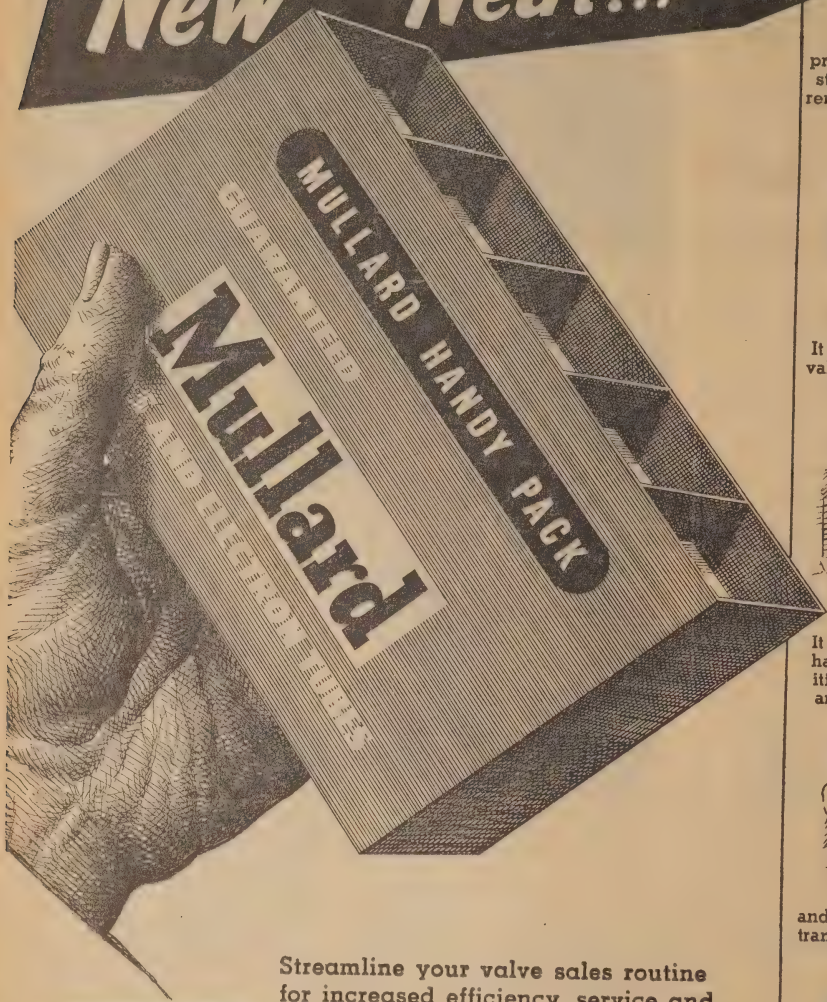

Streamline your valve sales routine for increased efficiency, service and turnover. Stock and sell Mullard valves and **SAVE TIME** with the all-purpose **HANDY PACK**.



The **HANDY PACK** provides a precise shelf stowage unit and visual reminder of stock quantity.



It facilitates systematic valve ordering, packing and despatching.



It allows rapid and easy handling of large quantities of cartoned valves and eliminates this . . .



and it is an ideal valve transit package for the Serviceman.



Mullard

HANDY PACK

★ **HANDY PACK**

—a container open at top and firmly holding 5 individually cartoned valves



Technical Review

NEW EYE MAGNET REMOVES NON-FERROUS PARTICLES

The idea of using magnetism to remove particles of copper, brass, aluminium &c., from the eye may, at first glance, appear to be among those things normally rated as "impossible". Emphasis on the idea that nothing is really impossible any more is given by a report from the United States of a device which does just this.

EYES penetrated by particles containing sufficient magnetic material are usually saved by the ordinary electro-magnet; eyes penetrated by fragments of non-ferrous metals are commonly lost.

Development of a magnet for non-ferrous metals, first operated on 60 cps and used to pick up relatively large objects such as silver coins and copper rings, resulted in a study of possible application to eye surgery. Tests were made on particles of brass, lead, aluminium and copper suspended by threads, using an oscillator and 30-watt amplifier.

HIGHER POWER NEEDED

Results were promising, but indicated need for relatively high power over a considerable frequency range. Facilities for testing at 2 kilowatts were provided. Using that equipment, a 2mm copper wire clipping was moved about 3mm through cow-eye vitreous (jelly-like substance filling the posterior chamber of the eye between the lens and the retina) in a tray.

The office of the Surgeon-General of the US Army became interested when it developed that about 25 pc of the numerous eye injuries in the Korean conflict due to metal fragments involved non-magnetic metals.

The new electromagnet has been developed to a point at which particles of copper, aluminium and magnesium have been extracted from the eyes of animals, using a water-cooled electromagnet supplied from a 25 Kw amplifier at 5 to 10 Kc.

When a simple coil carrying alternating current surrounds a closed conductor or a short-circuited coil, and a conducting object (the particle to be attracted) is adjacent to the inner member (see figure 1) currents of substantially like phase are induced in the object and the inner fixed member, setting up attraction forces between them.

ATTRACTION ZONE

With proper configuration and geometry there is an attraction zone approximating a cone with its base in the surface of the structure. A conducting object situated so that the principle induced current paths lie within this region will be at-

tracted by predominance of the attractive force over repulsion. Outside this zone there is repulsion.

This simple form is shown in figure 1, in which the attraction zone for

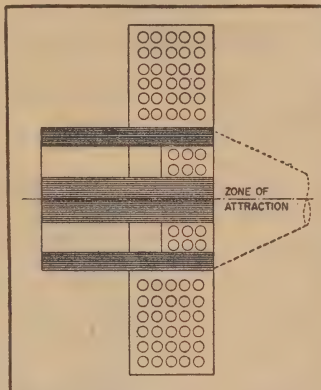


Fig. 1. Details of the non-ferrous magnet showing the cone shaped space in which effective pull occurs. The device is still in the experimental stage.

large objects is shown in dotted lines. The model shown in the figure has a central magnetic core filling, an opening in the attractor, and also an intermediate core between the attractor and field coil, which intensifies the field of the main coil.

The power plant is rated at 25 Kw from 3 Kc to 12 Kc and the useful range can be extended to 50 Kc by changing the driver power transformer. (Figure 2.)

POWER CONTROL

The power level of the large amplifier output is set by the output control of a variable frequency oscillator which fixes the voltage impressed on the input to a 20 watt preamplifier.

A tapered coil, 4in outside diameter, 1 1/2in inside diameter, wound with .06 by .04in copper tubing, using 8000 ampere turns, without the intermediate core and with attractor open circuited, creates a field of 2000 gauss at 1cm out on the axis.

The pull on a 2mm particle of copper in this arrangement, but with intermediate core and 7-8in attractor, is measured at 20 times gravity at 7mm from the attractor aperture and off centre where the pull is great.

No trials have been made with human eyes, but the near term outlook seems to be favorable for objects 1mm or greater in the smallest dimension, especially those of copper or aluminium, if early operation can be provided. (Electronics, Sept., 1955.)



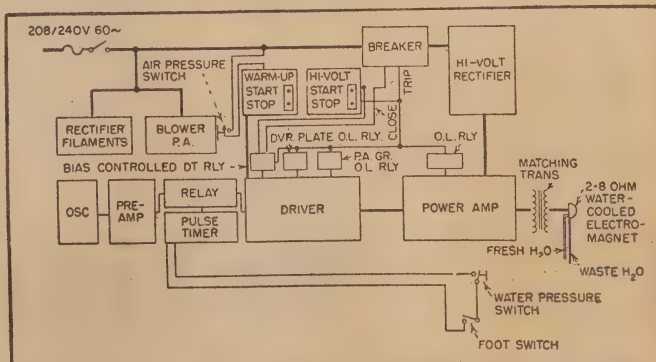


Fig. 2. Simplified diagram of the oscillator and amplifier used to power the non-ferrous magnet. Note the provision for water cooling in the magnet proper and which is dictated by the high power involved.

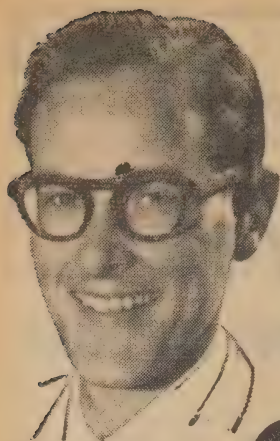

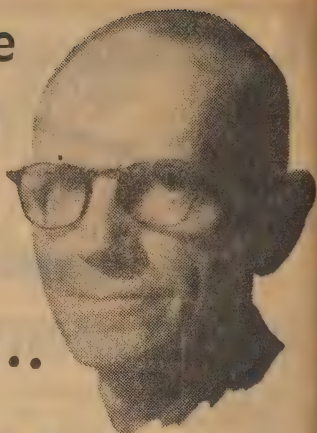Engineers in the World's leading Radio Networks and Recording Studios *specify..*



"Festival Records Pty. Ltd. use 'SCOTCH' Brand Sound Recording Tape Exclusively" says Mr. R. R. Iredale, Recording Engineer.

TRADE MARK
SCOTCH
BRAND

"'SCOTCH' Brand Sound Recording Tape is used by 2GB Macquarie" says Mr. H. K. R. Thomas, Chief Sound Recording Engineer.

SOUND RECORDING TAPE

Rigid manufacturing standards, continuous research and testing ... analysing ... testing ... analysing ... over and over again, always add up to the same answer. "SCOTCH" Brand Sound Recording Tape is the No. 1 sound recording tape on the market. Ask for it ... look for it in the distinctive plaid dec-

orated box. It costs no more and the brand name "SCOTCH" is your assurance of sound quality. Insist on "SCOTCH" Brand Sound Recording Tape.

Enjoy These "Scotch" Features

1. "SCOTCH" Tape is wound on precision spools of international standard. Slit to wind and track evenly.
2. Low-stretch factor and adequate strength.
3. Gives more output for a given input.
4. "Dry" lubricated, preventing sticking to the recording and assuring long wear.
5. Widest frequency response and maximum saturation level.
6. Minimum distortion—maximum signal to noise ratio.
7. Unequalled uniformity reel to reel.

ANOTHER



PRODUCT

MINNESOTA MINING AND MANUFACTURING (AUSTRALIA) PTY. LIMITED, ST. MARYS, N.S.W.



NEW ALUMINIUM-IRON ALLOY IMPROVES TAPE HEADS

One of the biggest problems in producing satisfactory tape recording and playback heads is to find a core material which combines physical hardness, to reduce wear to a minimum, with the most desirable magnetic qualities. These two normally opposing qualities are combined in a new alloy announced in the United States.

ALFENOL, a binary alloy of between 10 and 16 per cent aluminium with the balance iron, is one of the first high-aluminium content aluminium-iron alloys to be produced in a thin, ductile cold-rolled sheet form.

That such alloys possess good soft magnetic properties has been known for many years. However, owing to their extremely hard and brittle character, they could not be produced in sheet form suitable for fabrication into laminations for magnetic structures.

UNUSUAL QUALITIES

A material that is magnetically soft and physically hard is unusual. This is evidenced by the fact that a physically soft material is used in practically all applications of magnetic recording and reproducing.

Ferrites employed in an effort to circumvent the head wear problem have not, despite their physical hardness, had entirely suitable magnetic properties. In addition, other problems of physical and magnetic non-uniformities lead to fabrication or

accurately the physical-vs-electrical gap spacing, high-precision, hard-tempered beryllium-copper foil was utilised as a spacer material. Foil thicknesses varying from 1000 to 230 micro-inches were used.

Although several core configurations were made, most of the data here reported was taken on units having a core 0.7 inch inside diameter and 1 inch outside diameter.

The electrical resolution of the units was measured at a tape speed

case, where the core material permeability remains high and abruptly drops to a value of 1 (that of air) at the gap insert.

Curve B shows the effect of a slight permeability surface, while curve C illustrates a more severe or deep boundary that would result from excessive cold working. From a comparison of the electrical and physical gaps it may be concluded that Alfenol shows this effect only slightly and would be represented by a curve like that of B.

Figure 2 shows the frequency response curves for an Alfenol unit with a 230-microinch physical gap. That the electrical resolution of this unit approaches very closely the physical gap is apparent from these curves.

PRACTICAL CURVES

High electrical resistivity should result in a considerable decrease in core losses for record and reproduce units employing this material.

To check this, a single frequency of 5000 cycles was recorded at a tape speed of 5 in a second, using a standard head. The tape was then played back, using an Alfenol reproduce head, at speed increments to obtain playback frequencies of 5, 10, 20, 30, 40, 50 and 60 Kc. For comparison, a duplicate set of measurements was

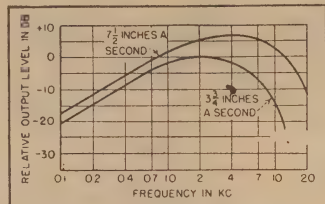


Fig. 2. Frequency response of the new tape head with 230 micro-inch reproducing gap.

of 3.75 in a second by determining the frequency at which the first null appeared. This null in head output occurs when the recorded wavelength on the tape is equal to the electrical gap dimension of the reproducing head.

In all new alloy units measured, it was observed that the electrical resolution and physical gaps were practically the same.

The physical measurements were made by directly measuring the gap under an optical microscope using a Filar-type eyepiece that had been calibrated by a precision ruled stage. Comparison of the two shows a close correlation for the Alfenol units.

The excellence of Alfenol in holding an electrical resolution nearly the same as the physical resolution is accounted for, in part, by the fact that during the lapping of the gap faces little loss in magnetic properties is incurred.

LAPPING PROBLEMS

It is known that a lapped surface is severely cold-worked. This cold-working results in virtually complete loss of high permeability in the material. However, due to the new material's extreme hardness, the depth of the cold-worked permeability loss is apparently small.

A softer material has a tendency to flow or smear, resulting in a much deeper penetration of the cold-worked surface. Thus a limitation is established on electrical resolution that is caused by the loss of magnetic properties of the inner surface of the gap. This permeability boundary creates an apparent air gap with poorly defined limits.

This effect is illustrated in Fig. 1. Here curve A represents the ideal

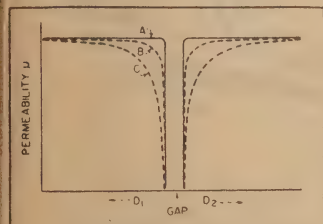


Fig. 1. Showing the difference between the physical and effective magnetic gap with typical materials. The solid line represents the ideal case.

other difficulties that may result in inferior units.

On the basis of both electrical resistivity and hardness, the new material possesses exceptional properties, particularly for an application such as record and reproduce heads. The extremely high electrical resistivity gives a low eddy-current loss value.

Hardness approaches that of tool steel. Because of the material's extreme physical hardness it resists degradation of its magnetic properties through strain induced in processing and handling.

In the as-rolled sheet form, Alfenol has a very thin, tightly adherent film of aluminium-oxide on its surface. This film in turn forms an excellent surface insulation when laminations punched from the sheet stock are stacked.

Several experimental units were used in this investigation. The heads were fabricated from 0.006 in cold-rolled sheet stock using conventional fabrication techniques. To measure

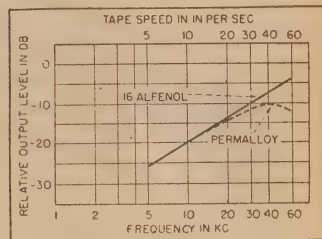


Fig. 3. Graph showing comparative losses of permalloy and Alphenol heads. In the latter case there is no appreciable loss at 60 Kc.

made, using a conventional playback head.

Results of these tests are shown in Fig. 3. Up to a playback frequency of 60 Kc (the limit of the measuring equipment used), the new unit showed no deviation from the normal 6 db per octave rise, as compared to a drop of approximately 7 db in the other unit at 60 Kc.

The three advantages of wear resistance, increase in resolution, and decrease in core losses of the new material all combine to make its use extremely promising for video recording on tape. Here high tape speeds, the need for high-frequency reproduction at low losses and especially the requirement for high resolution in the reproduce head all fall in line with available properties.

("Electronics" — June, 1955)

Magraths recommend



SOLDER

ENTRIVEN

Superspeed



rosin cored
SOLDER

SUPERSPEED ACTIVATED ROSIN-CORED SOLDER

Dry or H.R. joints are impossible with SUPERSPEED SOLDER, for the flux is always released in exactly the correct proportion. This faultless fluxing action is achieved by the unique STELLATE CORE, which gives six points of rapid solder collapse. At soldering temperature the ACTIVATED ROSIN flux is released immediately for effective spreading and wetting. SUPERSPEED Six Channel Core Solder is being used more and more in the production of radio, television, and radar equipment where faultless soldered joints are essential. That's why we recommend it to amateurs and servicemen alike!

SUPERSPEED is SELF-FLUXING!
SUPERSPEED is NON-CORROSIVE!
SUPERSPEED overcomes DRY JOINTS!

Recommended for general electrical, electronic, and telecommunication work and all standard uses. A.I.D. and G.P.O. approved. Complies with M.O.S. Specifications DTD 599. In all standard, tin-lead alloys, 10-22 s.w.g. Used by leading Australian manufacturers and Government Departments.

Superspeed



Available in quantity and 1lb packs. Samples of SUPERSPEED and the comprehensive SUPERSPEED booklet gladly sent on request to the Australian Managing Agents:

J.H. MAGRATH & CO. PTY. LTD. 208 LT. LONSDALE ST., MELB. VIC.

BETWEEN SWANSTON AND ELIZABETH STREETS. TELEPHONE FB 3731 (3 Lines)

NEWS AND VIEWS OF THE MONTH

Ice projectiles

THE use of ice bullets to remove one's enemies has been the subject of comic strip writers for a long time, but now a possible practical use of a similar idea has been suggested by a USA scientist.

He is Dr. Lincoln La Paz, Director of the University of New Mexico's Institute of Meteoritics.

"In range-testing inter-continental ballistic missiles in peacetime, a shrewd opponent for obvious reasons would seek to employ test objects leaving no tangible trace of their existence or use," he said.

Dr. La Paz said that since 1948 representatives of the Institute of Meteoritics had been investigating luminous phenomena seen in the sky.

They had asked observers if pieces of ice or drops of water were seen falling from the sky at the time of the observed incident.

Dr. La Paz said an ice projectile could be shot from a plane at high altitude many miles away from the US.

The ice projectile, melting rapidly as it shot, through the atmosphere, then would be photographed or traced by radar.

The opponent then would have a fair idea of where the real thing would hit.

TV "cuts crime"

RELIEF from the many reports of the evils of television to modern youth was provided by a recent report from England. It states that many welfare officials believe that TV, at home and in youth clubs, has helped cut juvenile crime by keeping young people off the streets.

Remand home officers at Brentwood (Essex) say the postwar peak in child crime is over.

The Brentwood home's capacity for 40 boys has often been over-taxed in the past few years. Now there are only 20 boys in the home.

Several other remand homes throughout the country have been closed in the past year.

Warming the Arctic

VAST man-made geological changes were predicted by a Russian engineer recently. One project being considered was to lock the gateway between the Arctic and Pacific Oceans with a mammoth dam across Behring Strait.

A battery of hundreds of giant pumps would pour a tremendous amount of water from the Pacific into the Arctic Ocean.

This would produce an artificial warm current about equal to that of the Gulf Stream, greatly moderating the climate in the Arctic zone and north-eastern Asia, he said.

The permanent Siberian, anticyclone could be broken.

Asia, North America and part of Europe would escape the frigid breath of the Arctic.

Transistors at UHF

IMPROVEMENTS in techniques by the Bell Telephone Laboratories have resulted in the manufacture of experimental "npn" type transistors for use at frequencies exceeding 1000 megacycles. This has been made possible by the reduction of the thickness of the central "p" layer to less than .0002 of an inch in width. This transistor is of the tetrode type.

In addition to these details of the Bell Telephone units other transistors of the tetrode type are available from other USA companies for operation in the video and vhf frequencies.

More image othicons

TWO other companies have now joined RCA as manufacturers of the image othicon tube. These are General Electric and Westinghouse. The major difficulty in the manufacture of these tubes is in the target and mesh assembly.

It consists of a copper mesh of 500 wires to the inch, spaced two thousandths of an inch from a glass membrane which is the target. This target itself is between one and two-tenths of a thousandth of an inch in thickness.

Solar energy

THE use of solar energy for hot-water systems, refrigeration, and the distillation of brackish water in the outback of Australia was predicted by Professor A. H. Willis on his departure for America recently. Professor Willis, who is the Professor of Mechanical Engineering at the Sydney University of Technology, was on his way to the USA to attend the first international conference on the uses of solar energy.

He predicted that a heater suitable for use in outback areas would initially cost £70 but that the heater would cost nothing to run.

The major drawback to the system is its unreliability for, unless the sun shone, there would be no output. For this reason the professor felt that this form of energy would not replace the use of electricity where this was readily available.

Off-shore radar

THE first of the American off-shore radar warning stations is steadily going ahead at a location one hundred miles east of Cape Cod. A number of these radar towers are to be built at points approximately one hundred miles off the east coast of the USA.

These stations will operate in conjunction with the Continental Air Defence Commands shore based stations, and will be fitted with both search and height finding radar systems.

The first of these stations has a main platform supported 87 feet above the water level to be out of the reach of large waves. The main steel platform itself weighs 6000 tons.

In addition to all the radar equipment that has to be housed, accommodation has to be provided for 70 personnel who will be stationed at the site for periods of up to 30 days at a time.

POPULAR SCIENCE QUIZ

Q. What is reverse TVI?

A. This is the interference caused by television receivers to other TV receivers or radio receivers. It is caused in the main by harmonics of the line frequency oscillator and by local oscillator re-radiation.

Q. Can television be wired to homes in the same way as radio programs are in some overseas communities?

A. Yes, it can be done but the problems are much greater than for radio programs due to the higher frequencies involved. Such systems can be used in a large hotel where there is one main receiver and the other units are merely slave units.

Q. Is it economical and practical to use a common tower for two television stations?

A. It is practical and considerable savings can be achieved. This is because for maximum coverage, the aerial needs to be as high as possible. It is reaching this height that the major cost is involved. Once this has been accomplished it does not require much additional expense to add an additional radiator to the tower. Such an installation is at the present moment being carried out in Cuba where two RCA 10 Kilowatt television transmitters are being coupled to a common mast. This mast is supported on the roof of a new 23-storey hotel and the stations will transmit on

Channels 4 and 6.

In New York, several television stations radiate from the summit of the Empire State Building. It has the additional advantage that all receiving aerials can be directed toward the one point, thereby eliminating the need for rotating aerial arrays.

Q. What is a camera light filter and what is its purpose?

A. It is a piece of tinted glass or tinted gelatin sandwiched between two layers of glass. Its effect is to modify the tones of black and white in a photograph. It can be used to highlight certain effects in the scene being taken such as to improve the cloud detail in an outdoor shot.

New Release



SOUND REINFORCEMENT SPEAKERS FOR CONTROLLED SOUND DIFFUSION



PA 344
Speech range
low-level speaker.


PA 343
General purpose
music and speech
medium-level speaker.

PA 342
Wide range medium
level speaker.


The line source principle, combined with the especially developed A.W.A. speaker units and cellular acoustically damped inverted pyramidal housing, make possible a polar pattern of projection which puts the sound where it is required, and a response character which makes sound live.



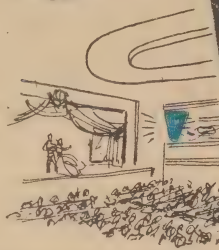PA 353
Weather-resistant
for outdoor and
industrial applications.
General purpose music
and speech medium-level
speaker



Models PA 342, 343 and 344 for indoor applications, and Model PA 353 for outdoors, are the product of extensive acoustic research by A.W.A. development engineers. Wide angle coverage horizontally, with narrow beam vertical plane projection, plus smooth frequency response, ensures far more effective reproduction without reverberation. No resonances to cause feedback and boom, no valleys to make voices unreal.

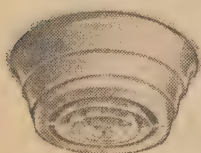


PA 188—
For surface mounting,



PA 187—For flush mounting with small surround. The face panel and louvre project slightly below the ceiling line.



PA 218—
Is for suspension by chain or rod.

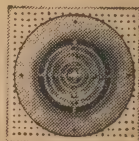

PA 186—For flush mounting has a recessed surround which mounts the complete assembly above the ceiling line.

A.W.A. offers the most comprehensive range of speaker assemblies for every requirement in audio reproduction.

All models are planned for optimum faithfulness of sound reproduction in keeping with physical and cost requirements. Special designs are included for high power projection in open space, and also for wide angle, wide audio range fidelity.

A complete range of audio system basic units is available . . .

AMALGAMATED WIRELESS (AUSTRALASIA) LIMITED
47 YORK STREET, SYDNEY 167 QUEEN STREET, MELBOURNE

Available in other States from
Newton McLaren Ltd., Adelaide. Noyes Bros. (Melbourne) Ltd., Hobart. Chandlers Pty. Ltd., Brisbane.
Nicholson's Ltd., Perth. Also from leading wholesalers.

Glass-plastic bond

CHEMICAL bonding can join plastic and glass more solidly than the usual glues and cements. The bonded materials can be made into laminated panels that hold together through repeated test foldings, showing that the finished material combines plastic's flexibility with the strength of the glass fibres.

Part of each of the new compounds will unite chemically with one of the plastic materials while another part will join the structure of glass.

Aeroplane bodies, boats and cars in the near future may be made of glass and plastic chemically bonded together. Five new bonding compounds, all belonging to a class known as chlorosilanes, have been developed to combine with the different types of plastics.

TV imports

THE Federal Government will allow the import of television receivers on a restricted basis.

Announcing this, the Minister for Trade and Customs (Senator O'Sullivan) said the Government was not establishing new import licensing quotas for television receivers.

The Government would issue import licences for receivers from other than the dollar area to "B" category quota holders—against their existing quotas. However, it would restrict the maximum number of sets to be licensed to any "B" category quota holder to 200 a quarter.

Senator O'Sullivan said importers would have to declare that the sets conformed to the standard specifications at the Broadcasting Control Board.

The Government would also have to issue licences for the importation of picture tubes in the early stages of TV set manufacture in Australia.

The Commonwealth would not establish quotas to import these tubes, but would consider applications from individual manufacturers.

The number of tubes imported would depend largely on manufacturers' estimates of probable sales.

The Commonwealth had made an allocation from July 1, 1955, of overseas currency to import components for TV sets.

TV for schools

THE use of television to offset the shortage of teachers in schools was commented upon by Miss Kinnane, Script Editor and Producer for the ABC's Youth Education Department on her recent return from three months in Canada and USA.

She said Americans were becoming increasingly aware of the fascination TV held for children.

The New York Board of Education, as well as many universities, school and community television stations, ran special programs for schools.

Most popular courses included arts, languages, history, geography, literature, and music.

Shop at home!

TELEVISION in the USA continues to find applications to mediums other than entertainment. The latest is an aid to "shopping at home". Articles which are televised on the screen can be ordered from the shop in the same way as the week-end groceries.



MI

1 The AEE "Microcap" incorporates the modern technique of metallised paper in place of conventional alternative layers of paper and metal foil thus producing light weight ultra-miniature, space saving capacitors.

2 The Self-Healing feature is a very valuable characteristic which enables the "Microcap" capacitor to sustain accidental over voltage and provides an additional safety factor.

3 In the "Microcap" capacitor the wire pigtail leads are soldered directly to the capacitor unit in a manner that renders them free from intermittent contact, and the strength of the joint exceeds the tensile strength of the lead.

4 An insulation resistance exceeding 20,000 megohms for all values at working voltage of 20° C, is obtained on "Microcap" Type W99.

5 They have a power factor better than 1% at 1000 C/S at 20° C.

6 The "Microcap" W99 with all the BIG Features mentioned above offers stable long life in MINIATURE form and is available in a wide range of Capacitance and voltages.

Microcap

METALLISED PAPER CAPACITORS

Write or call for leaflets giving further technical details of "Microcap"


W99 Metallised paper capacitors.

Manufactured in Australia under licence from A. H. Hunt (Capacitors) Ltd., England

AUSTRALASIAN ENGINEERING EQUIPMENT

CO. PTY. LTD.

476 LATROBE STREET, MELBOURNE. FJ4161

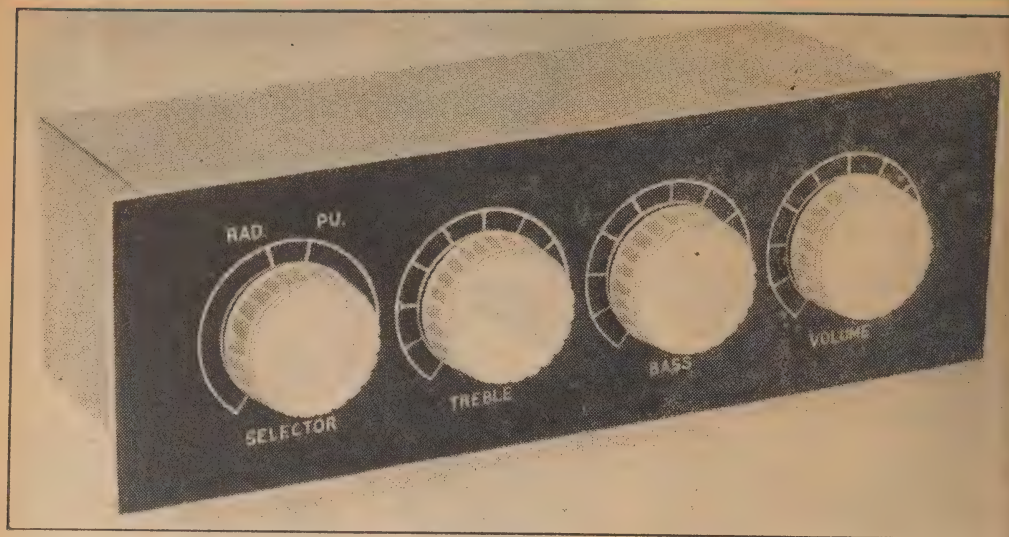

The front panel showing order of controls. There is a panel light at bottom centre.

CONTROL UNIT FOR CRYSTALS

Here is a simple but effective control unit for use with crystal pickups and the Playmaster series of amplifiers. It has no preset compensation, but a wide range of bass and treble adjustment which will accommodate most standard pickups.

FOR various reasons our readers frequently strike trouble when attempting to use crystal pick-ups with Playmaster amplifiers.

Invariably they have merely connected their pick-up to the control unit input terminals and immediately struck trouble.

The control units concerned were designed primarily for pick-ups of the magnetic type with an average output of not more than about 100 millivolts.

The input resistor for such pick-ups is generally about 25,000 ohms, and a resistor of around about this value was used with most of the units.

However, the intention was that the initial resistor should be of the correct value specified by the manufacturers for the pick-up used. Particularly if an input transformer were used to couple the pick-up, its value might be considerably higher.

Connecting the average crystal pickup into a low load of 25,000 ohms or less causes it to behave very much like a magnetic type in that the bass end is greatly reduced in output.

This isn't an entirely satisfactory solution, however, unless a value is found which provides the right turn-over point for the bass response, at the same time reducing the over-all output sufficiently to avoid overload-

ing the grid of the pre-amplifier valve.

It is clear that this overloading has taken place in many cases reported to us. Reference to the graph on this page will illustrate the point. Reducing the pickup load has quite clearly altered the bass characteristics, but has affected the response very little over about 2 Kc

OVERLOAD DANGER


As most crystals show a peak of some kind following this point, the danger of overloading in this part of the frequency response is obviously most probable, even on LP records.

It is inevitable in the case of those readers who have blithely connected a .5 meg resistor at the input of the amplifier and hoped for the best.

Quite a good idea, which we have often suggested, is to replace the initial grid resistor with a .05 potentiometer connected across the pick-up terminals, the control unit grid connection being made to the moving arm.


The .05 meg is enough to flatten down the bass response more or less to reference, and the moving arm is set to that position which gives adequate output voltage from the pick-up.

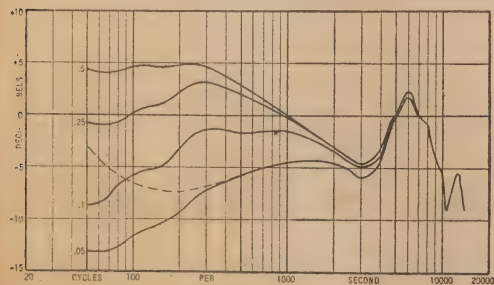The control unit is then used in the normal manner, remembering



This graph shows how the GP-20 head changes characteristics with change in load.

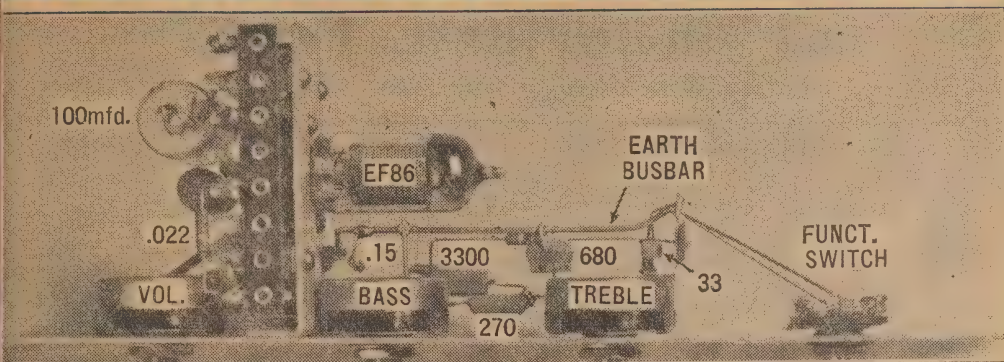A SIDE VIEW SHOWING POSITION OF COMPONENTS



A side view showing the position of many components in our unit.

hat, because few crystal pick-ups have a flat response, the various compensation settings will not be particularly accurate.

It has long been obvious, therefore, that a special control unit for crystal pick-ups which would operate with the Playmasters in the normal manner would be a very good thing, and would be a great help to readers who have pick-ups of this type.

The publication of some amplifier and radiogram circuits using a tone control borrowed from the Mullard amplifier led us to believe that the entire front end could be successfully adapted as the basis of a suitable unit.

SIMPLE CIRCUIT

In general terms, this arrangement connects a simple resistance-capacitor network immediately between the pick-up and the first valve, which allows both bass and treble boost and cut to be obtained in addition to a volume control.

There is considerable loss in the compensation circuit, so that the voltage available for the valve is quite small—estimated at about 50 millivolts from an input of about 600 millivolts.

This would represent the probable peak limit of voltage output from the pick-up, and the drop of about 12-1 in the compensation circuit virtually guarantees that the following valve is quite safe from overload under any circumstances.

Now the average input sensitivity of a Playmaster is from 250 to 350 millivolts—some might need a little more than this. We estimate that this is about the right degree of sensitivity to allow it to be fully loaded from the average crystal with an adequate safety margin.

So that if we arrange for the overall gain of the control unit to be unity, that should work out quite nicely.

Obviously this means that, with a loss of about 12 in the compensation, the pre-amplifier valve in the unit should have a gain of 12 to make up for it.

This is accomplished quite easily by using a triode-connected EF86 as a pre-amplifier.

Any triode having a similar gain can be substituted, but the EF86 has proved itself an excellent low noise performer with very little if any tendency to microphonics.

A 6AU6, for instance, would be a satisfactory substitute, and its gain should be about the same with the same plate load. The low input voltage which the grid is required to handle renders the circuit non-critical as to exact operating conditions, and even with the grid bias removed a little from optimum, the distortion should be negligible.

As mentioned in previous articles dealing with this type of input circuit, exact compensation for crystal pick-ups, apart from perhaps one or two special types, is rather a futile business, because the output curve is not only far from flat but is rather unpredictable from one cartridge to another, and even between different samples of the same type.


The curve already referred to, although representing quite a good make of pick-up, illustrates the formidable job involved in flattening out the response.

UNIFORMITY

Experience has shown that, although reasonable success has been obtained by specific compensation circuits for certain pick-ups, the results are actually worsened unless the cartridge used is reasonably close to optimum. This is often a doubtful assumption.

It is far less trouble, and in general more satisfactory in the long run, to operate the pick-up into a load which reasonably restricts the bass, and then to adjust the balance by continuously variable controls which allow boost or cut of both bass and treble.

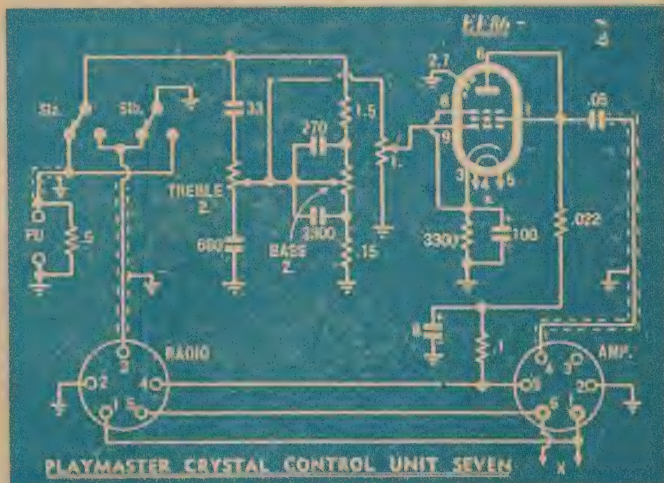This is exactly what this unit has been designed to do.



The circuit is exceedingly simple. The overall gain of the unit is approximately unity. The .5 meg pickup load resistor will suit most pickups, but can be varied if desired.

"ACOS" CRYSTAL MICROPHONES and MICROPHONE INSERTS

A Complete Range For Every Purpose

DESK or HAND MICROPHONE

MIC 36



£6/18/6

Housed in attractive plastic case, this Microphone is ideal for home recording and public address, etc. Response unexcelled for its size and price. The performance is not affected by vibration, shock or low frequency wind noise. Omni-directional frequency response substantially flat from 30 to 7000 c.p.s. Recommended load resistance not less than 1 megohm dependent on low frequency response. Can be supplied complete with switch and floor stand adaptor as required at a small extra cost.

HIGH QUALITY MICROPHONE

Designed to meet even the most exacting requirements, this Microphone incorporates the world famous floating crystal sound cell construction. Its special characteristics are that its fine performance is not affected by vibration or shock. The fidelity is not impaired by low frequency noise.

SPECIFICATION

Recommended load resistance—not less than 1 megohm.
Output level—-65 db ref. 1 volt/dyne/cm².
Frequency response—substantially flat from 30 c.p.s. to 10,000 c.p.s.
Directivity—non-directional.
Size—2-1/8in spherical diameter.
Connector—Standard international 3-pin.


MIC 16



£24/19/6

GENERAL PURPOSE

MIC 35

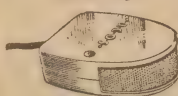

£2/15/-

The MIC 35, undoubtedly the best value ever offered, is ideal for amateur transmitters, public address, etc. Housed in an attractive die-cast case, it features a high sensitivity and substantially flat characteristics. Provided with a built-in shunt resistance of 2 megohms, it will, when connected to the grid of the input valve, give a substantially flat response from 50 to 5000 c.p.s.

SPECIFICATION

Output level: -55 db ref. 1 volt/dyne/cm².
Cable—approx. 4ft. of co-axial supplied.
Weight—6ozs. unpacked, 7 ozs. packed.
Dimensions—microphone only 2 1/4in x 2 3/4in x 1 1/2in.

MICROPHONE INSERTS



(MIC 32 illustrated)

CRYSTAL MICROPHONE INSERTS

These inserts are available in varying sizes ranging from as small as 15/16in square to 1-13/16in round, with various thicknesses from 7/32in to 9/16in. Suitable for every purpose such as hearing aids, public address, tape recording, amateur broadcasting, etc., they have responses from 2250 c.p.s. to 3500 c.p.s. at 5 db to 30 db. Insert can be supplied with or without 10 meg. resistor as required.

MIC 19/4 and MIC 32, £2/15/6; all other, £1/19/6.

SOLE AUSTRALIAN AGENTS:

AMPLION (A'sia) PTY. LTD.

88 Parramatta Rd., Camperdown, Sydney, N.S.W.

Victorian Distributors: **DISTRIBUTORS CORPORATION** 403 BOURKE ST., MELBOURNE.

TABLE or STAND MICROPHONE

This omni-directional Microphone is robust in construction, with a pleasing appearance. Vibration, shock or low frequency wind noise will not affect the performance. The low frequency cut-off is dependent on the load resistance. The cut-off is given by the quotation, $F = 80$ divided by R , where $F =$ c.p.s., $R =$ megohms. An adaptor (floor mounting) is available at low extra cost.

SPECIFICATION

Output level = -50 db ref. 1 volt/dyne/cm².
Output impedance—equivalent to approximately 0.002 uF (0.8 megohm at 100 cycles).
Frequency response—substantially flat from 40 to 6000 c.p.s.
Recommended load resistance—not less than 1 megohm, dependent on low frequency response.

MIC 22



£9/18/6

LAPEL MICROPHONE

Designed to give freedom of movement, this Microphone is small and non-directional. Housed in a soft moulded rubber case, which gives protection against shock, it is provided with a pin at the rear of the case for pinning to the lapel.

MIC 28



£5/19/6

Output level—approx. -55 db ref. 1 volt/dyne/cm².
Recommended load resistance—5 megohms.
Frequency response—level throughout the whole of the audible spectrum.
Capacity—0.0015 uF. at 1000 c.p.s.
Impedance—100,000 ohms at 1000 c.p.s.
Cord—6ft. shielded cable.
Size—1-9/16in wide x 2 1/4in long x 5/8in thick.

HAND or DESK MICROPHONE

This Microphone has been designed for the high quality public address and home recording field. High sensitivity and flat characteristics are obtained by a specially designed acoustic filter. Housed in an attractive plastic case with an unexcelled response for its size and price. Unaffected by vibration, shock or low frequency wind noise. Omni-directional frequency response substantially flat from 30 to 7000 c.p.s.

MIC 33




£6/18/6

MICROPHONE INSERTS



(MIC 23 illustrated)

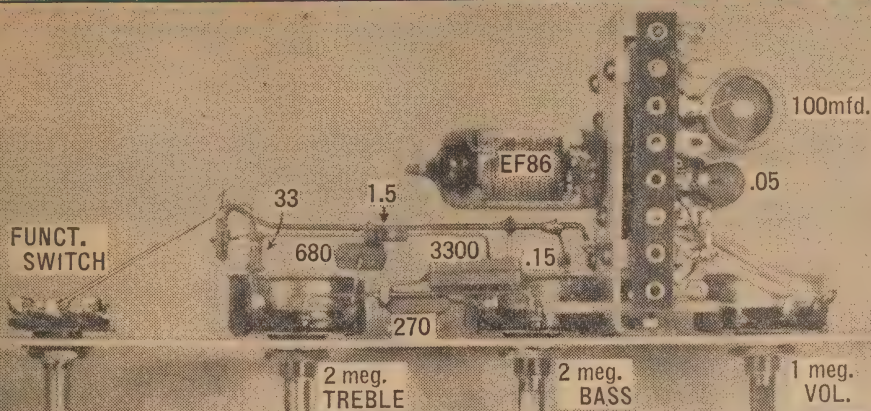FURTHER CONSTRUCTIONAL DETAILS IN PICTURES



Another view from the side. The panel light was not fitted when the picture was taken.

There is no reason why you should experiment with various kinds of compensation circuits for the pick-up should you so desire, remembering, however, that such circuits always involve further attenuation of the actual pick-up output voltage, and may leave you without sufficient drive to satisfactorily load up the amplifier.

BEST LOAD

The best load value will be that which gives the right amount of bass with the bass control in its mid position—that is with no appreciable bass or cut. This will enable you to add or subtract from this setting by a useful amount in each case.

The actual resistor value will probably lie between .5 and .2 meg, and you will be well advised to experiment for the best effect.

The range of control with the circuit constants given is from 11 db of boost at 20 cycles to 5 db of cut, and from 10 db of boost at 10 Kc to 10 db of cut. At approximately mid-position the controls are inoperative. As with practically all continuously variable controls there is some inter-action between them at the 1 Kc point, but it is not enough to be serious.

PARTS LIST

- 1 Panel and shield box as for Control Unit No. 6.
- 1 EF86 valve.
- 1 2-position switch.
- 2 2-meg. potentiometers.
- 1 1-meg potentiometer.

RESISTORS

- 1 1.5 megs, 1 .5 megs, 1 .1 megs,
- 1 .022 megs, 1 3300 ohms, all $\frac{1}{2}$ watt.

CONDENSERS

- 1 3300 pf, 1 680 pf, 1 270 pf, 1 33 pf
- all mica or ceramic. 1 .05 mfd 400V,
- 1 8 mfd, 350V, 1 100 mfd, 40V.

SOCKETS

- 1 Noval, 1 6-pin, 1 5-pin.

SUNDRIES

- 4 Knobs, panel light bracket and bezel,
- 2 8-terminal tag strips, 1 3 terminal tag strip, hookup wire, 1 ft 16 or 18 gauge tinned copper wire, 6 round head $\frac{1}{16}$ in nuts and bolts, 6 countersunk $\frac{1}{16}$ in nuts and bolts.

Constructionally the unit is quite simple and follows closely the technique used for the units already described. The same panel and box shield are used as for the Control Unit No. 6. Only one of the valve mounting brackets will be required because there is only one valve. The bracket is mounted between the volume control and the bass control.


Starting with the function switch, the other controls in order are treble control, bass control and volume control.

Most of the components associated with the valve are mounted on the tag strips bolted to the mounting bracket, and a little diagram with this article shows how we connected them.

The layout isn't critical and it's not essential that it be exactly adhered to.

The filament circuit is not connected to the unit at any point, being earthed in the amplifier itself. As there is little danger of earth loops, earthed points may be made to any part of the mount or panel.

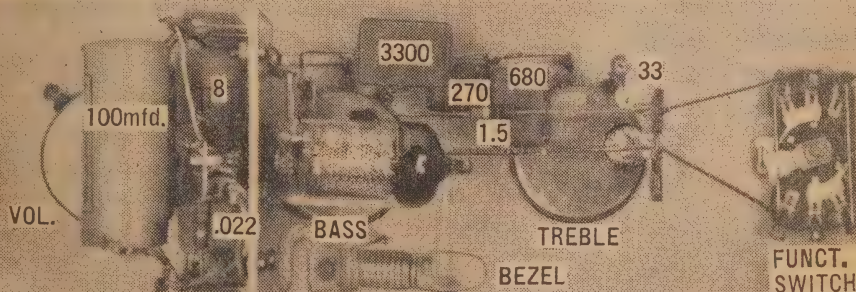Note however that an earthing wire runs from the function switch



This top view completes the picture story. Note the panel light fitted for this picture.

COLLINS RADIO

Mail Order Service Fastest and Cheapest in the Commonwealth
409 LONSDALE STREET, MELBOURNE, C.I., MU1033

Goods sent by ordinary parcel post, except when over 11lb. which are sent by rail, freight payable your end. Postage rates shown against goods advertised. For registered post send 1/- extra. Goods required air-freight sent F.O.N. unless air-freight charges remitted with order. To save delay send exact amount (M.O., Postal Notes, Stamps, Cash, Cheque [add exchange]). If in doubt about prices and postage on goods not advertised, send ample and brief description of goods. Refer to page and date of advertisement in Radio and Hobbies if possible.

THE NEW "Q-PLUS" CRYSTAL SET


- PERMEABILITY TUNED.
- LITZ WIRE COIL.
- GERMANIUM DIODE DETECTOR.
- COMPACT.
- PLASTIC CABINET 5in x 3in x 3in.
- THE MIGHTY ATOM. 49/6



EXTRAS:
100ft Aerial 7/6
BROWN'S Sensitive Phones 49/6
for

PLUS 2/-
POSTAGE.

STOP! FIND THOSE LITTLE THINGS FAST!

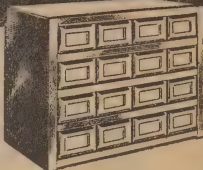

16 DRAWERS
1 1/2 in x 2 3/8 in x 5 1/2 in
or 4 Long Drawers
1 1/2 in x 10 1/2 in x 5 1/2 in
IN THIS ALL-STEEL
COLRAD
HANDY CABINET

A craftsman-built unit, attractively painted in baked grey hammertone enamel with provision for fitting identification card on each drawer.

For any other type or sizes, use our FAST QUOTE SERVICE. A strong and most useful cabinet for holding small parts or tools. Ideal for mechanic, engineer, garage, or home workshop. Provision is made for stacking into units. OVERALL SIZE 11 1/2 in wide, 9 in high, 5 1/2 in deep. 48/-
Postage: Vic., 3/8; NSW, ACT, SA, Tas., 6/-; Qld., WA, NT, 8/4.

ALUMINIUM CHASSIS

Spot Welded Ends



ALL POST FREE

6 x 4 x 2	4A13	7/6
8 x 6 x 2	4A14	10/-
10 x 6 x 2	4A15	12/-
11 x 8 x 2	4A16	14/-
13 x 7 x 2	4A17	14/-
13 x 10 x 2	4A18	17/6
17 x 8 x 3	4A19	22/6
17 x 10 x 3	4A19	25/6
17 x 12 x 3	4A21	26/6

First grade aluminium, carefully turned corners, easy to drill or punch. Special sizes, 50 pc more.

TELEVISION EXPERIMENTERS

BRAND NEW CATHODE RAY TUBES

5BP-1
SYLVANIA &
RCA

U.S. Price

22.50

DOLLARS

WHILE THEY
LAST.

OUR PRICE

£2/10/-

PLUS 5/-
PACK & POST.



(Metal CRO Cables to suit—Price on application)

SPECIAL!!!

Brown's English High Impedance Phones. Stalloy Diaphragms. Powerful Alnico Magnets. Extra long cords. Double headband. Super-sensitive. (To R.A.F. Specifications). 49/6

Pair Postage 1/6 extra.

BAKELITE BOXES

FOR SPEAKERS, CLOCKS, ETC.

No. 1 Round. 8in x 2 3/8in with 5in dia. opening. Takes 6in speaker.

Use two to make self-enclosed movable remote speaker.

Black or walnut.

6/- EACH POST FREE

No. 2. 4 1/2 in x 4 in x 1 1/2 in deep. Takes 3in Rola speaker. Possible uses: Small remote speaker case, sub-miniature receiver cabinet, crystal set case and clock case.

White, Cream, Walnut, Blue, Black.

5/- EACH POST FREE

25 pc discount either type in lots of 50.



NEW IMPORTANT BERNARD RADIO PUBLICATIONS

57	3/9	AN ULTRA SHORTWAVE HANDBOOK
61	3/9	AMATEUR TRANSMITTER'S CONSTRUCTION MANUAL
63	5/3	RADIO CALCULATIONS MANUAL
65	3/9	RADIO DESIGNS MANUAL
66	3/9	COMMUNICATIONS RECEIVERS' MANUAL
68	3/9	FREQUENCY MODULATION RECEIVERS' MANUAL
69	3/9	RADIO INDUCTANCE MANUAL
71	3/9	MODERN BATTERY RECEIVERS' MANUAL
73	3/9	RADIO TEST EQUIPMENT MANUAL
78	3/9	RADIO AND TELEVISION LABORATORY MANUAL
81	3/9	USING EX-SERVICE APPARATUS
82	3/9	AC/DC RECEIVER CONSTRUCTION MANUAL
85	5/3	MINIATURE RADIO EQUIPMENT CONSTRUCTION MANUAL
86	5/3	MIDGET RADIO CONSTRUCTION
93	6/9	POWER PACK MANUAL
94	5/3	PRACTICAL CIRCUITS MANUAL
96	1/6	CRYSTAL SET CONSTRUCTION
97	4/6	PRACTICAL RADIO FOR BEGINNERS, BOOK 1
99	2/3	ONE VALVE RECEIVERS
100	7/6	A COMPREHENSIVE RADIO VALVE GUIDE, BOOK 1
101	2/3	TWO VALVE RECEIVERS
102	4/6	40 CIRCUITS USING GERMANIUM DIODES
103	2/3	"RADIOFOLDER" A, THE MASTER COLOUR CODE INDEX FOR RADIO AND TELEVISION "THREE VALVE RECEIVERS"
104	2/3	RADIO CIRCUITS HANDBOOK, No. 4
106	3/9	HIGH FIDELITY RADIO; DESIGN AND CONSTRUCTION BY N. BONAVIA HUNT
109	5/3	

RADIO & HOBBIES CIRCUITS

USE OUR FAST QUOTE SERVICE FOR PRICES OF PARTS YOU NEED FOR

SEPTEMBER ISSUE	A Simple Set for Beginners	(p. 32)	(p. 64)
High Powered Playmaster			
Audio Signal Generator		(p. 48)	NOVEMBER ISSUE
1955 Radiogram		(p. 64)	Playmaster Crystal Control
OCTOBER ISSUE			Unit No. 7 (p. 32)
High Selectivity Set		(p. 32)	5-Valve Kloxette (p. 64)

We supply the parts, but cannot enter into any technical correspondence.


FAST QUOTE SERVICE,

For quickest possible service, write on the left-hand side of a sheet of paper the radio parts that interest you—one beneath the other. If a kit, itemize. Add your name and address and send it to us with a stamped, self-addressed envelope. We will add the latest prices and return to you. Use this sheet as your order form and return to us with remittance for cost and postage as quoted. Goods will be sent same day. Any surplus refunded. Sorry, no C.O.D.

EVERYTHING FOR THE RADIO AND ELECTRICAL EXPERIMENTER

p to a three-tag strip soldered to the outside case of the treble control (for convenience) and thence to the same mounting bolt to which the volume control is earthed. This provides a direct earthing path between these points just in case.

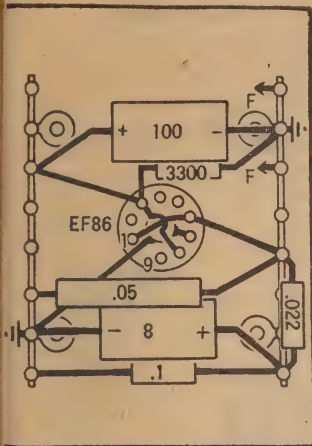Various components in the compensation network are earthed



This diagram shows how we arranged various components on the valve mounting bracket.

Directly to this wire at convenient points. The position of some components is indicated on the photographs.

The filament, high tension and earth leads to the unit are made to appropriate points on the tag strips, and connected to the sockets mounted at the rear of the shield box. The leads are first made to the sockets, of such length that they can be soldered to the tag strip as the unit is inserted in the box. There is no point in making these leads any longer than is necessary.

The shield box is quite essential to avoid hum pick-up on the unit wiring. This is a high impedance circuit and very susceptible to interaction with stray fields. With the shield in position, however, it is quite free from this trouble.


COUPLING LEAD

The input lead to the amplifier grid circuit should be made with low capacitance shielded cable or co-ax, as the impedance at this point is high enough for a long lead of high capacitance braid to bypass high frequencies. Two or three feet should be long enough, and all the wires connecting the amplifier to the unit may be run together through a protecting length of plastic tubing.

Any of the Playmaster tuners can be used with this unit. Note that when switching to pick-up or to tuner, the unwanted circuit is earthed to avoid any play-through effects, more particularly of course on radio.

As usual, a design for a front panel has been prepared to suit this unit and will be supplied to those of our advertisers who are interested in producing them.

MODEL TV STUDIO FOR BBC SHOW

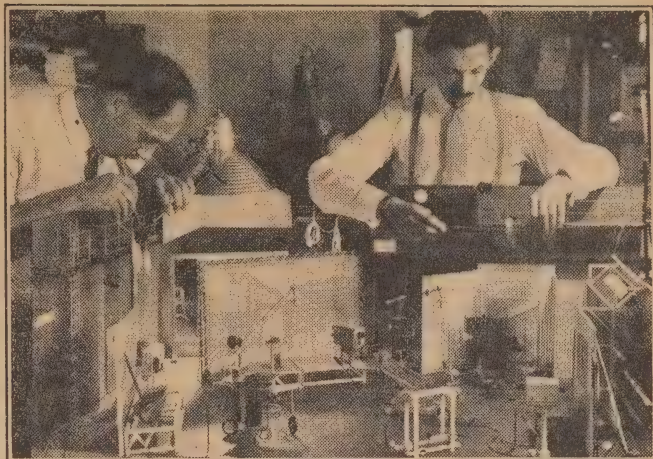

This beautifully made model of a BBC TV studio was used in the 1955 National Radio and TV Exhibition in England.

RADIO & TELEVISION ENGINEERS' REFERENCE BOOK

Here is **BIG** news for Radio men: a brand-new work for those engaged in the installation and servicing of Radio and T.V. equipment, and in design and manufacture.

PROVE ITS VALUE -

FREE FOR 7 DAYS

The most up-to-date work of its kind in existence

WRITTEN BY **36 SPECIALISTS**

Be one of the first to examine it without cost or obligation.

POST THE COUPON TODAY!

Includes: Formulae, calculations, electron optics, studio equipment, transmitter power plant, aerials, amateur radio equipment wave guides, V.H.F. transmitter-receiver equipment, commercial H-F links, navigation and radar, industrial T.V. valves, tubes, transistors, diodes, interference, magnetic and disc recording, radio and TV installation, and servicing, projection T.V. units and symbols, &c. &c.

★ ★ ★


It is impossible to list above more than a very small fraction of the contents of this important new work—so we provide you with the opportunity to examine it freely in your own home and without obligation. Seize this opportunity by posting the coupon now.

OVER 1600 pages crammed with information to meet your everyday needs.

45 main sections, written and compiled by leading authorities.

1860 diagrams, tables, data, standard formulae, calculations, measurements, &c.

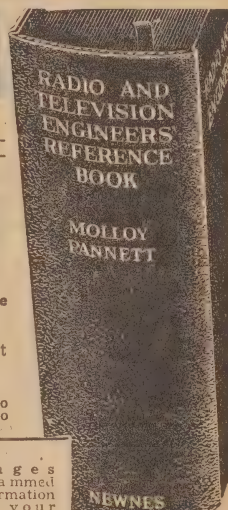2500 cross-referenced index entries enabling wanted information to be found in an instant.



To: George Newnes (Aust.) Pty. Ltd., 119 York St., Sydney, N.S.W.

Please send me Newnes' **RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK**. It is understood that I may return the work within eight days. If I keep it I will send a first payment of 9/- eight days after delivery and 16/- monthly thereafter, until £5/6/- has been paid. Cash price, £5/1/-.

Name

Address

Occupation

Your Signature

(Or your Parent's if under 21)

Place X where it applies.

Houseowner
Tenant
Living with Parents
Lodging Address

WINDING WIRE ENAMEL

18-20-22-24-26 S.W.G.

4oz. Reels 4/6

Postage 9d

EXPANDED ALUMINIUM

for Speaker Grills, etc.
Silver or Gold.

10/- sq. ft.

Postage 11d

BUILD YOUR OWN CLOCK RADIO

Smith Clock movements, complete
with WIRING DIAGRAM.

£5/19/6

Postage 1/3

INSTRUMENT RECTIFIERS

Suitable for meters of from 1 ma
to 5 ma.

18/9 each

Postage 5d

SPEAKER CROSS- OVER NETWORKS

To suit 15 ohm
speakers, $\frac{1}{4}$ section
type.

3000 Cycles,

£6/5/-

800 Cycles,

£8/5/-

To suit 3 speakers.

800 and 5000

Cycles. £14/5/-

Postage, Vic. 2/-;

Inter. 5/-.

Coils only. Suit
above, 3000 Cycles.

35/- pair

800 Cycles,

50/- pair

Postage, Vic., 1/7; Inter. 3/5.

JABEL PLANETARY VERNIER DRIVES

Ratio 5:1. 3/8in to $\frac{1}{4}$ in.

11/6

Postage 5d

FAMOUS ACOS

Crystal Microphones.

MIC35—£2 15 0.....Hand Mic.

MIC22—£9 18 0.....Table Mic.

MIC28—£5 19 6.....Lapel Mic.

MIC33—£6 18 6.....Desk Mic.

Postage 1/3

MIC32 Insert 55/6

MIC19/4 Insert 59/6

Postage 9d

UNIVERSITY

O-1 m.a. meters.

Plain Scale or Multimeter Scale.

Type R4—Black case $\frac{1}{4}$ in square.

Type U4—Clear plastic case $\frac{1}{4}$ in sq.

£5/7/6 each

Postage, Vic., 1/7; Inter. 3/5.

SHUNTS

to Suit above Meters.

10 m.a. — 50 m.a. —

100 m.a. — 250 m.a. . . . 9/- each

1 amp 13/6 each

3 watt, 14.8 and 166.6 ohm 1 pc

Resistors 3/11 each

1 watt multiplier Resistors

1 pc 2/6 each

Postage 3d

LEATHERETTE MULTIMETER CASES

SIZE INSIDE 8in x $\frac{7}{8}$ in x $\frac{1}{2}$ in.

55/- each

HINGED LID IS REMOVABLE.

Postage, Vic., 2/-; Inter. $\frac{1}{4}$ /4.

MANTLE CHASSIS

Little General.

17/11 each

Vic., 1/7; Inter. 3/5.

PRE-AMP CHASSIS

1 valve 6in x $\frac{1}{2}$ in x $\frac{1}{4}$ in.

3/11 each

Postage 11d

JENSEN 2 SPEAKER SYSTEMS

Comprising Heavy Duty 12in Bass
Unit and a 6in Tweeter. Complete
with 1 mfd. Coupling Condenser.

£7/12/6

Freight forward.

BAKELITE BOXES

SUITABLE 6in SPEAKERS

Round 4/11

SUITABLE 3in SPEAKERS

Square 3/11

Postage 1/1

LEATHERETTE SPEAKER BOXES

6-inch 41/-

Postage: Vic. 2/6; Inter. 5/2.

8-inch 45/1

Vic., 1/7; Inter. 3/5

12-inch 57/11

Vic., 1/7; Inter. 3/5

ELECTROLYTIC CONDENSERS

24/525 Upright

Mounting,

5/- each

8/525 Upright

Mounting,

3/11 each

300/12 Upright or

Pigtail,

5/- dozen

8/350 Upright or

Pigtail,

1/11 each

TUBULAR

.5/400 Tub.

Condensers,

10/- dozen

.25/400 Tub.

Condensers,

8/- dozen.

Postage, each 3d, doz. 1/1

TOOLS

Long Nose Pliers 6/-

Side Cutters 9/-

Wire Strippers 6/3

Postage 9d

TRANSFORMERS

STOCKTAKING BARGAINS

Type OP11 6600 P.P./500, 250, 125,
and 25 watts.

59/6

Postage, Vic., 3/3; Inter., 7/2.

Type OP17 10,000, 6600, 5000 P.P./
500, 250, 125 and 32 watts.

79/6

Vic. 4/-; Inter. 9/10

Type IP2 Class A Driver S.E./Class
A, AB2, Grids

45/-

Vic. 2/-; Inter. 4/4.

VIBRATOR TRANSFORMERS

Type VT112 12 volts/200. volts
and 50 m.a.

25/-

Vic. 2/-; Interstate 4/4.

Type VT109 24 volts/90 volts and
15 m.a.

19/11

Vic. 2/7; Inter. 6/5.

Type VT103 *6 volts/200 volts and
50 m.a.

25/-

Vic. 2/-; Inter. 4/4.

Type CF108 12 henry/150 m.a.

CHOKES

49/6

Vic. 3/3; Inter. 7/2

Homecrafts
RADIO PARTS SPECIALISTS
FOR 40 YEARS

290 LONSDALE ST., MELBOURNE

FB3711

SPEAKER TRANSFORMERS

Type D 8000/3.7 ohms . . . 4/11

Type D 10,000/3.7 ohms . . . 4/11

Type C 7000/2 ohms 6/11

Postage 1/1.

HEAVY DUTY TURNTABLES

Suit B.S.R. Motors.

£6/7/6 each

Bearing to suit.

15/-

Postage 8/6

1200ft. REELS PAPER

RECORDING TAPE

39/6 each

Postage, Vic., 1/3; Inter., 2/9.

MICRO SWITCHES

Plunger type or ball type.

8/11 each

Postage 5d

METER SCALES

Suit 3in meters.

Multimeter Calibration

1/3 each

Postage 3d

FROM THE SERVICEMAN WHO TELLS

In marked contrast to last month's article, wherein we amused ourselves with stories of RF in audio amplifiers and butchered speakers, this month's stories bring us right back to the service bench with a bump. They are, in fact, the description of two very routine jobs.

WHILE neither presented problems which would unduly tax the imagination of the average serviceman, I have particularly selected them for two reasons.

For one thing they really are typical, and in this sense I am directing them to my younger readers who may have ideas of becoming a serviceman some day. They give quite a good idea of the average kind of job that has to be done in a service shop; the type of set which has to be handled every day and contains much more routine work than glamor.

I quote them just in case my stories of unusual faults and the exciting chase which goes on to track them down may have created the wrong impression; the impression that a serviceman spends his entire working life in a high-pressure battle of wits. Well, these two stories should serve to bring things into their proper perspective.

BATTLE OF WITS

The truth is that the exciting battle of wits is comparatively rare, the average job being, basically, routine checking and replacement. Of course, there is plenty of variety in the faults and in the types of sets and this in itself is a welcome safeguard against any suggestion of monotony.

But the fact remains that one must put in a lot of routine and often not very interesting work for every spectacular discovery of an unusual fault. Sometimes, as well as being uninteresting, they are downright frustrating. Provided this is appreciated, no one is likely to be disillusioned.

My second reason for recounting the stories is that both sets contained faults which I think reflect to the discredit of the manufacturer and are in line, to some extent, with readers' remarks recently published in these pages.

My first was a five-valve radiogram, not particularly old but definitely of the pre-microgroove, pre-miniature valve era. It was a little more elaborate than the usual five-valve chassis in that it boasted a 6L6 output valve and a 5V4 rectifier to power it. It carried the brand of a well-known maker.

MULTIPLE COMPLAINTS

The owner's complaints were (1) it picked up noise from an automatic electric iron, (2) it "mumbled" (the owners description, not mine), and (3) it had a broken dial cord. I gathered that this last trouble was the main reason for my assistance being sought. Presumably the first

two faults had been tolerated for some time whereas the last one rendered the set inoperative.

Being a radiogram, I had to visit the owner's home and collect it. This also enabled me to observe the interference—and the "mumbling"—in its natural setting. This happened to be a dwelling behind a suburban shop.

By reaching into the back of the cabinet I was able to manipulate the dial drum and tune in a few stations. It was immediately obvious that the set was in a hopeless state of oscillation, even when a couple of the weaker local stations were tuned in. In fact the only way the weaker stations could be received was by tuning to zero beat and this provided the clue to the "mumbling".

Apparently this was the owner's term for the low frequency growls which occurred when the frequency of the set's oscillations drifted slightly and set up a beat note.

The condition was aggravated by the very small and inefficient aerial attached to the set. This was simply a length of wire strung under an iron roof at the rear of the dwelling and in close proximity to sundry machines, neon signs, &c., as found in a typical shopping area.

LOW PICKUP

With such low signal pickup it was also not surprising that interference from the automatic iron and similar domestic appliances was objectionably strong.

These facts having been established I set about getting the chassis out of the cabinet. It was mounted

vertically and the only way it could be removed was to first remove the dial panel in the top of the cabinet. But the screws holding this were hard against the sides and back, so that I had to unscrew the lid stays before I could get the lid back far enough to allow a screwdriver to work on the rear screws.


Then I had to disconnect various leads and cables relating to power, speaker, pickup, &c., finally reaching the stage where I could lift the chassis free.

SPEAKER PROBLEM

Normally I like to take a set's own speaker with me, but a glance at this installation discouraged me. For one thing the speaker transformer was mounted on the baffle board alongside the speaker.

Removing the baffle with speaker and transformer would have been awkward and removing the transformer and speaker separately would have involved setting up a soldering iron and undoing the leads. The connection would have had to be noted, of course, and restored when the set was finished. I didn't fancy either course and decided that this was one case where the universal bench speaker would earn its keep.

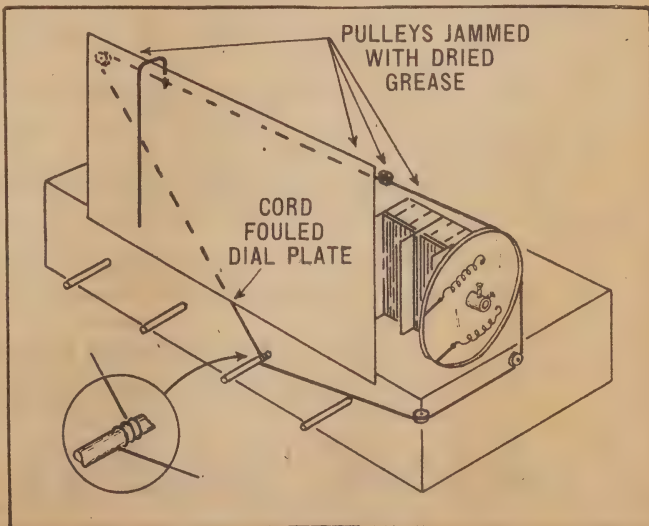What I didn't realise at the time was that the speaker system was part of the feedback network, the voltage being picked up from the speaker voice coil. While not a fatal error it meant that I had quite a job tracing the various connections to the speaker socket and mocking up a suitable replica of the speaker before I could test the chassis.



Right—illustrating some points about dial movements as discussed here.

MANUFACTURERS
OF COMMERCIAL
RADIO RECEIVERS
FOR 14 YEARS

CLASSIC RADIO



FOR QUALITY
FOR ECONOMY

BEFORE PURCHASING YOUR RADIO, SEE AND HEAR THE NEW
RANGE OF HIGH-FIDELITY CHASSIS BY CLASSIC.

Compare these new features of our Hi-Fi nine valve D.W. radio-gram chassis with dual triconed speakers and separate bass and treble boost.

Priced at **£35/15/-** F.O.R.

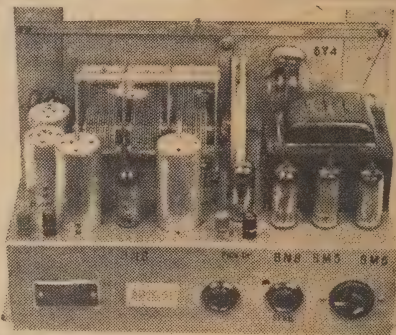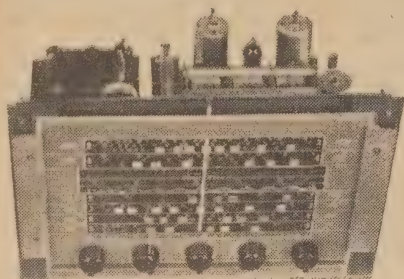Frequency Response 40 to 13,000 Cycles — Max. Output 10 Watts.



- NEW** • Ultra modern circuit using nine high gain valves including "magic eye" tuning indicator, Permatuned iron cored coils and intermediates giving excellent interstate reception and a short wave range of 12,000 miles. All valves used are the new Philips nine pin innova series.
- NEW** • Separate tone control stage using a twin triode (12AU7) with bass and treble controls in a Baxandall negative feed back tone control stage giving + or - 15db boost or cut at 50 cycles L.F. and 10,000 cycles H.F. combined with push-pull output with inverse feed-back gives you really high fidelity reproduction from your radio or favourite recordings.
- NEW** • Dual speaker combination using a heavy duty woofer (12in M.S.P. Jensen AU54 special) with twin coned 5in tweeter and cross-over network giving a frequency response of 46 to 13,000 cycles. Speakers are mounted coaxially making only one 1 1/2in mounting hole necessary.
- NEW** • Large calibrated edge-lit dial in perspex (11in x 7in) with main stations of each State in prominent type. Dial fitted with counterweight drive giving smooth tuning. Indicator lights are fitted showing which band is in operation. Dial can be supplied in cream or brown with matching knobs and escutcheon to suit blond or walnut finished cabinets.
- NEW** • Sensitive "magic eye" tuning indicator (EM80) making tuning simple and positive even on interstate and country stations.

All chassis are wired for the fitting of an F.M. tuner or tape recorder, special plug being provided on back of chassis also pick-up terminals and three-pin outlet for grammo. motor. Power switch is fitted to volume control, radiogram switch combined with wave change switch. Audio end of set can be used with T.V. receiver if required.

ALL CHASSIS GUARANTEED FOR A PERIOD OF 6 MONTHS

A New 10 Valve Dual-Wave Radiogram Chassis

WITH BASS AND TREBLE BOOST

The ideal chassis for those difficult locations where reception is doubtful. Specifications as nine valve unit but with the addition of high gain tuned R.F. stage giving greater sensitivity and selectivity on both broadcast and short wave bands.

£39/15/-

F.O.R.

NEW—7-VALVE WORLD-RANGE CHASSIS

WITH BASS AND TREBLE BOOST

SPECIFICATIONS AS NINE VALVE UNIT, BUT WITH SINGLE OUTPUT VALVE AND SINGLE 12in SPEAKER.

£28/15/-

F.O.R.

WRITE FOR ILLUSTRATED BROCHURE GIVING FULL SPECIFICATIONS.

Large range of Radiogram and Console Cabinets from £12

RECORD PLAYERS AND CHANGERS

We have a complete range of 3-speed record playing equipment, including B.S.R. or Garrard Players, with turn-over crystal pick-ups or your choice of Garrard, Stromberg-Carlson, Collaro or the new B.S.R. 3-speed changer that will play 7, 10 or 12in records intermixed. All changers have turn-over Crystal pick-ups.

CLASSIC RADIO

245 Parramatta Rd.,
Haberfield, N.S.W.
Phone UA2145

While it doesn't sound much on paper it can give rise to some dark mutterings, as it did on this occasion.

First I tackled the oscillation. This was still very bad even on a better aerial and obviously due to a major defect. It didn't take me long to track it down. The valve shields used were of the form fitting variety and they were earthed by means of flexible braids soldered to the shell and running through the chassis to the main earthing system underneath.

BROKEN BRAID

In the case of the 6B8 the braid was broken and the valve had no effective shielding. Apparently some heavy-handed character who had previously serviced the set had heaved the valve from its socket without dissembling the shield so that the braid had been snapped. No one had considered it worth while to replace it, hence the violent oscillation.

Although the violent oscillation ceased when I fitted a new braid, the set was still right on the verge of instability. While this would not prevent proper reception of the local stations it could be objectionable on very weak signals and is the kind of thing which one tries to avoid on principle. I could well imagine the set "spilling over", for example, with high line voltage.

But though I checked every likely component in the set and tried every trick I know—and I've learnt a few over the years—nothing that I tried was of any use. I just couldn't make it once and for all stable.

While I hate passing the buck I was finally forced to the conclusion that it was simply the nature of the set and that the designer had cut things a little too fine in the compromise between sensitivity and stability. This being so, I considered I was justified in increasing the 6U7 cathode resistor from 300 to 500 ohms. This was quite enough to make it a completely stable set.

Next I tackled the dial, and not without some trepidation. It was one of those gloriously complex arrangements at which every serviceman shudders on sight. The gang was mounted parallel to the front of the chassis, with the drum at right angles to the dial. Conveying the drive from the tuning knob to the dial and drum involved more than the average length of cord.

NO STICKER

To make matters worse, the usual stringing sticker on the back of the chassis had long since vanished and, as I had never tackled this particular type before, I was really on my own.

Before actually starting the re-stringing I tackled the various mechanical movements associated with the dial, and which I suspected had probably contributed to the failure of the cord. These were mainly the pointer slide and the various pulleys, all of which were hopelessly gummed up with congealed grease and the inevitable layer of fluff which collects on every chassis.

As I have remarked in these columns before, I can never agree with the general practice of applying liberal quantities of oil and grease to these parts. The result is always the same. The grease invariably hardens, jamming the

pulleys and impeding the pointer movement, thus throwing extra strain on the dial cord and hastening its failure.

It seems a far better proposition if the various parts are allowed to run without lubrication of any kind. After all, they are not running at high speed and the amount of wear over the lifetime of the set would be negligible.


Most mechanisms will run quite smoothly without copious lubrication and those which won't are probably examples of poor design, anyway. The person who designed and built them should retire to a corner of his laboratory and start all over again.

But to return to this particular dial. Having cleaned and freed the various movements I set about analysing the system and working out the correct path for the cord. In general terms this wasn't particularly difficult and I soon worked out

ened up. There was only one snag; I had miscalculated the number of turns required to provide sufficient grip. No amount of wangling with the pulleys, slider, &c., would give me completely reliable operation right over the band.

There was only one thing for it, pull it down and add another turn. This I did, running into much the same strife as before. However, I was gratified to find that the extra turn was sufficient; the thing worked quite positively.

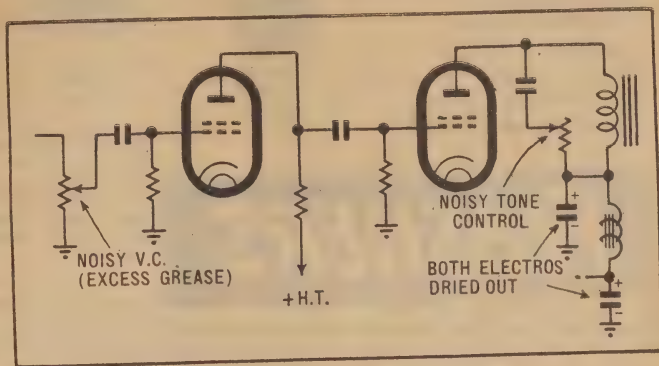I tuned up and down the band and checked for any other snags. And I found one. One section of the cord running to the tuning shaft approached it from a top corner of the dial plate, meaning that it lay across the plate at an angle of approximately 45 degrees. I had wound the cord around the dial in such a fashion that this part was at the front of the three loops.



Multiple faults made this set unsatisfactory.

a scheme which seemed to avoid such elementary pitfalls as having the knob rotate in an obviously reverse direction or bringing in 2SM on 2FC's calibration and vice versa.

One point that worried me though, was how many turns to take around the main drive shaft. On the one hand there were so many pulleys and turns involved that it was obvious that the cord would need to have a good grip on the shaft. On the other there was no groove in the shaft to keep the loops in place and it was obvious they would "walk" from front to back as the shaft turned.

Since there wasn't a great deal of room I obviously had to select enough turns to get a good grip, yet not so many as to cause the whole assembly to bind at extreme ends of the dial.

RESTRINGING

After due consideration I decided to take a chance on two turns around the shaft, and set to work. I can recall many dials that were easier than this one. The normal problems of trying to keep the cord in all the pulley grooves at the same time, while fastening the ends to the drum and tension spring, were aggravated by the fact that system required over 4ft of cord.

(Where have I heard a similar comment recently?)

Finally, with many unkind remarks about the designer, I managed to get everything in place and tight-

As I tuned toward one end of the dial the loops "walked" toward the tuning knob and eventually brought the dial cord against the lower edge of the metal dial plate, where it rubbed merrily as I turned the knob back and forth. It was obvious that no cord would stand much of that.

It was also obvious—now—that I should have arranged the loops the other way around, so that the offending cord would have formed the rear loops instead of the front one. This would allow enough—though only just enough—clearance to avoid the complication.

YET AGAIN

So, consoling myself as best I could, I undid the whole assembly once more, reversed the order of the loops, and strung it up again. I found I was getting quite good at it by this time.

I checked it over carefully and could find nothing wrong, so I set about a routine alignment check. This passed off without any complications and I considered the job as good as finished. Purely as an afterthought (and to provide a little music while I worked) I left the set playing on the bench.

Imagine my surprise when I looked at the dial a little later and noticed that the pointer, which I was sure I had left exactly on calibration, was now something like half an inch to the left of it.

More careful checking soon revealed the cause. The tension re-

FLASHERS



Adaptor No. 1.
15-100W
200-240V

FLASHERS



"Safety Flasher"
6V or 12V
3 amp.

FLASHERS

FLASHERS

FLASHERS

Truck Flares
Garage Ramps
Auto Stop Lights
Auto Turn Signal
Auto Theft Alarms
Truck Safety Switches
Bells . . . Horns . . . Sirens
Electric Fence Controls
Filling Station Signals



Heavy Duty "B"
25-100W
200-240V



Heavy Duty type "C"
60-500W
200-240V

FLASHERS

Q'LAND: S. L. Farr,
Perry House,
Elizabeth St., Brisbane. B4897.
VIC.: Ronald J. T. Payne & Co.,
434 Collins St., Melbourne.
MU1416.

N.S.W.: Industrial Controls Pty.
Ltd.,
243 Castlereagh St., Sydney.
MA3448.
W.A.: Sales Pty. Ltd.,
1142 Hay St., Perth. BA9781.

WHOLESALE INQUIRIES INVITED.

ACOS

HGP38 Hi-g Turnover Crystal Pick-up

Another superb "Acos" Hi-g pickup, designed to give the utmost in satisfaction. Will track with ease all present-day recordings and those of the foreseeable future, too. Incorporates the HGP37 cartridge with cantilever sapphire styli which features vertical compliance that nullifies "needle talk" as well as increasing lateral compliance. Cartridge utilises a new method of crystal drive, a bisectional control element that achieves independent characteristics for standard and microgroove.

SALIENT FEATURES

High compliance, hermetically sealed crystal unit,
High output and low stylus pressure.

SPECIFICATION

Output—1 volt on standard records
1/3rd volt on microgroove records
Tracking weight—10 grammes



Price complete with
HGP37 Cartridge
£5/15/-

Sole Australian Agents:—

AMPLION (A'sia) PTY. LTD.

88 Parramatta Rd., Camperdown,
Sydney, N.S.W.

Victorian Distributors:—

DISTRIBUTORS CORPORATION 403 BOURKE ST., MELBOURNE.

quired to pull the gang around, via all the pulleys, was quite considerable and was apparently stretching the cord. When left alone this stretch took up, moving the pointer and, presumably, the tuning knob. Admittedly the type of cord I used was supposed to be suitable for radio dials but I imagine the manufacturers did not envisage it being used in 4ft 6in lengths.

As far as I could see I had only one hope left. I had on hand some nylon dial cord which was also described as free from stretch. I hadn't occasion to check this characteristic before, so I couldn't be sure that it would be any better than that I had used.

I could only try it and see.

AND AGAIN!

Which meant, of course, that I had to pull the whole thing down and restring it—for the fourth time. My only consolation was that I had done it enough times in a short period to have learnt all the tricks.

Fortunately, the nylon cord did the trick and the drift now appeared to be negligible. Which was just as well, because I don't think I could have faced another bout with the thing.

I don't know whether his Satanic Majesty has a special section of his domain set apart for the damnation of incompetent dial designers but, if he has, I can imagine no more appropriate punishment than to condemn the fiend to string one of his own dials with a special cord—designed to snap as soon as the job is completed. This process to be repeated until the end of time.

Returning the set to the owner I was able to demonstrate that the general performance was very much better and that there should be no further trouble due to "mumbling". But I pointed out that it was asking a lot of any set to expect it to work well on the aerial provided. In particular, I explained, it made the interference from the iron and other appliances just that much harder to cure.

For a start, therefore, I suggested that a better aerial and a good earth be tried and the owner intimated that he could probably rig up something himself. If this failed I suggested a line filter, but I felt that this would probably not be necessary.

And so I left the owner to rig his aerial, check the interference, and let me know the result. I've a feeling it will be favorable.


PLENTY OF TROUBLE

The next case, which did in fact follow hard on the heels of the previous one, was also a five-valve set, rather more pretentious than average and which was also minus its speaker. This time because the owner delivered the chassis to the shop and simply omitted to bring the speaker.

The owner listed four complaints: it hummed, it made strange noises, the volume control was rough, and it had a faulty tone control. Which, I imagine, is quite enough for one set at a time.

Having no speaker I was forced to set up the bench speaker again, and again I encountered a voice coil feedback system. It seemed to be my unlucky day.

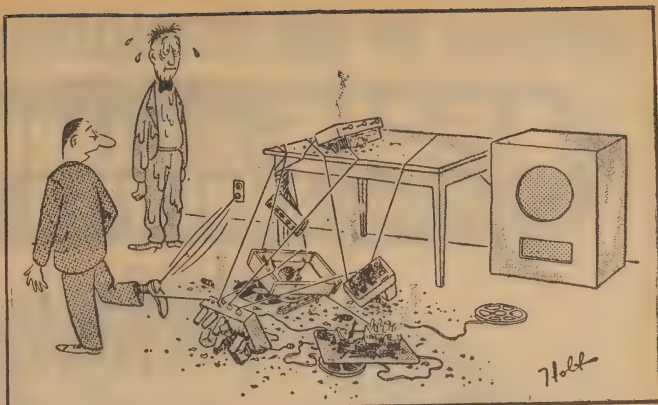Having traced the connections and mocked up a speaker, I switched



"Oops! Sorry! (Radio Bulletin).

it on. There was no doubt about the hum, it was quite bad. It presented no problem, being quite obviously due to electrolytics that had seen better days. A couple of new ones quickly silenced it and I turned my attention to the other faults.

The strange noises were not immediately obvious so I checked the volume control. There was no doubt about this either, it was absolutely atrocious. I pulled it out and was about to discard it and fit a new one when I decided that a control as noisy as all that was worth investigating. So I pulled the cover off and had a look inside.

And what a sight met my gaze. The inside was liberally plastered with a brown looking grease and, while it is quite normal for the makers to lubricate these devices, I imagine the operator must have ladled the grease into this one with a teaspoon!

GREASE EVERYWHERE

Not only was it gumming up the sliding contact to the moving arm but there were also smears of it on the element. No wonder it was noisy! I decided that it could well be that there was nothing more wrong with it than this and that it might be worth trying to salvage it. In my case it would be an interesting experiment.

Accordingly I set to with some petrol and an old toothbrush and cleaned out the mess of brown goo. I probably removed some that should have been left there but there was little I could do to avoid this. With the worst removed I rinsed it in fresh petrol to remove the last traces, particularly from the element where small patches might be hard to detect.

Then I wired it back into the set and tried it. It was as silent as the grave, the element apparently being in perfect condition. This being so I decided that there was little point in charging the customer for a new one. Admittedly I had spent a few minutes cleaning it, but this was small compared with the price of a new control.

Next the tone control. This appeared to have been the victim of some heavy handed user who wanted more treble cut than the system was designed to give; so he had just kept on turning. The result was a broken stop inside the control and mutilation of the "innards". There was no suggestion of salvage here, I dropped it in the waste bin and reached for a new one.

This fitted, I began to wonder what might be the story behind the strange noise the owner had mentioned. Was there really something else wrong with the set or were these noises merely the combined effort of the volume and tone controls? I decided that this latter could well be the explanation and that, if it did not show up in a reasonable time, I could only return it to the owner with the explanation that I had been unable to observe the complaint.

DIAL LAMPS

In the meantime I set to work on the dial lights. The owner hadn't mentioned them but they were all inoperative. There were five in all, some illuminating the dial proper and the others mainly serving fancy little "whatsits" on the dial to indicate broadcast or short wave, bass-treble, bandspreads, &c.

While this was all very well, I felt that the designer might have more profitably devoted his energies to devising a more satisfactory method of mounting the dial lamps. In a chassis which had obviously been designed for an expensive set the method employed was woefully shoddy.

The lamp and socket assembly was held in the usual rubber holder and forced under a three sided metal channel fitted to the top and two sides of the dial assembly. The channel was bolted to the metal back plate of the dial and extended across the space between it and the dial glass, eventually finishing up in front of the glass.

In this respect there was nothing very unusual about the arrangement. Where it failed was in the fact that the channels did not extend to the ends of their respective sides, thus locating the lamp assembly where it could very easily short to the metal back plate. Also, by the

(Continued on Page 127)


Introducing the NEW AUSTRALIAN-built

AEGIS-MULLARD

"five-ten" AMPLIFIER

Here at last is a fine-quality high fidelity Amplifier — made in Australia to suit Australian conditions. Approved in all aspects by Mullard-Australia Pty. Ltd.

**HIGH-QUALITY
AT LOW PRICE**

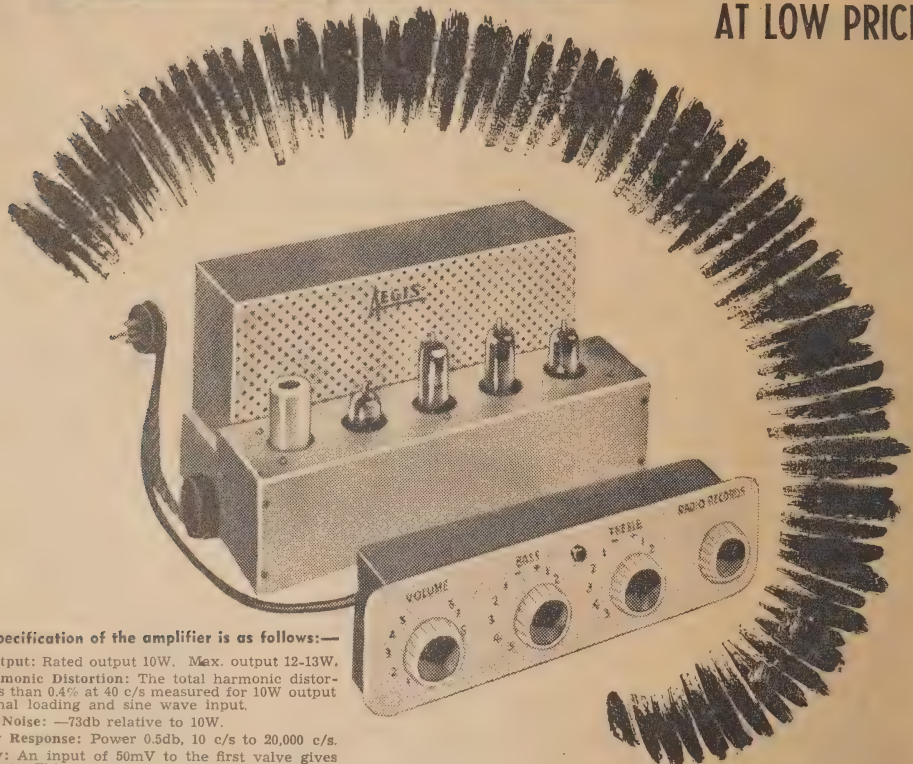

A brief specification of the amplifier is as follows:—

Power Output: Rated output 10W. Max. output 12-13W.
Total Harmonic Distortion: The total harmonic distortion is less than 0.4% at 40 c/s measured for 10W output with normal loading and sine wave input.

Hum and Noise: —73db relative to 10W.

Frequency Response: Power 0.5db, 10 c/s to 20,000 c/s.

Sensitivity: An input of 50mV to the first valve gives 10W. output. This output is produced by an input of 600mV to the tone control circuit.

Pick-up: As supplied with normal control panel, the voltage output of the pick-up should be at least 0.5 volts to obtain specified output. A special Pre-Amplifier is available for low-level magnetic and moving coil pick-up units.

Treble Control: Continuously variable control of treble from +10db to —10db at 10,000 c/s.

Bass Control: Continuously variable control of bass from +11db to —5db at 20 c/s.

Valves: 1 EF86 Low noise pentode input stage.

112AX7/ECC83 Double triode phase splitter.

20BQ5/EL84 Pentode push-pull output stage.

1 6V4/EZ80 Full wave rectifier.

Output Impedance: Standard 375 ohms and 15 ohms.

Alternative impedances available.

Dimensions: 11½in x 6½in x 8in (amplifier).

Tone control panel, 12in x 3in x 1½in.

**PRICED
AT ONLY**

48 GNS.

COMPLETE

AEGIS

208 Lt. Lonsdale St., MELBOURNE, C.1, Vic. PHONE FB3731

Our QUEENSLAND AGENTS are CHANDLERS PTY. LTD., Cnr. ALBERT & CHARLOTTE Sts., Brisbane

If you experience difficulty in obtaining the Aegis-Mullard contact us or the Agent in your State:—

N.S.W.
Watkin Wynne P/L, 173
Pacific Highway, Nth. Syd.

STH. AUST.
George Procter, 40 Pirie St.,
Adelaide.

WEST AUST.
A. J. Wyle, 1064 Hay St.,
Perth.

TASMANIA
W. & G. Genders Pty. Ltd.,
Hobart.

MANUFACTURING CO PTY LTD

AEGIS

EXTENSION SPEAKER

S.P.5 JUNIOR. An attractive 7in. circular moulded plastic cabinet 2in. deep with contrasting coloured feet and louvred front grille. Complete with 5in. unit (3 ohms input. imped.).
LESS TRANSFORMER Terminal block for easy connection. In Walnut and Natural only.

£3/8/9



FOR SUPER QUALITY

Extension Speaker Control Box

MAINS FILTERS



S.B.—1 3-WAY CONTROL BOX for above speakers. Allows use of RECEIVER only — EXTENSION only — BOTH together. Finished in attractive Hammerstone grey lacquer. Flanges facilitate attachment to wall or receiver cabinet.

£4/7/-



Model M.F.—1.
 £2/8/-
 Model M.F.—2
 With R. F. Chokes
 £2/18/9

EXTENSION SPEAKER

S.P.7 SENIOR. Plastic Cabinet 11 1/2 in. wide, 10 1/2 in. high, 4 1/2 in. deep with spinner type front. 7in. unit (3.7 ohms input imped.)
LESS TRANSFORMER Volume Control in centre of grill. In Walnut and Natural only.

£7/10/9




Full range of Extension Speakers always in stock.

All wave Noise Reducing

AERIAL SYSTEM

The most comprehensive and efficient noise reducing aerial available. The A.F.1 is a complete system and includes two matching transformers, 40ft copper aerial, 50ft lead-in, 40ft earth, three porcelain insulators. Complete with instructions. Packed and ready to use.

£9

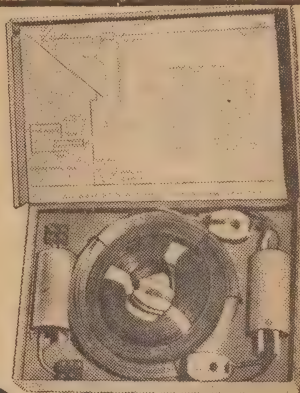

CHANDLERS

PTY. LTD.

FREE —

CATALOGUE

Head Office & Wholesale Depts.

Albert & Charlotte Streets, Brisbane
 Phone FA0341

to readers in Queensland, New Guinea and Northern N.S.W.

range of Aegis Products. Send the Coupon below for your copy.



TO CHANDLERS PTY. LTD.

Albert & Charlotte Sts., Brisbane

Please send me a copy of the Aegis Catalogue.
 FREE and Post Paid.

NAME

ADDRESS



Here's your answer, Tom!

Although the science of electronics is expanding from day to day, bringing with it new developments, new words and new expressions, it is wise not to forget about older things. At least Tom seems to think so, judging by the questions he has put forward this month.

VOLUME expanders, dial lamps and transmitters appear on this month's "menu".

What is a volume expander? Is it just another kind of amplifier? How does it work and what is it used for?

Uninitiated people, like yourself, Tom, are often misled into thinking that a volume expander simply provides higher volume from records than would otherwise be possible. In point of fact, it does nothing of the kind.

This varying DC voltage is used to control the grid bias of one or more variable- μ valves in the amplifier proper.

Initially, these valves have a very high negative bias, keeping their amplification down. The DC from the volume expander, on the other hand, is of opposite polarity, and, if applied to the grid, tends to reduce the bias, making the stage more sensitive.

The higher the original signal level the higher the sensitivity of the amplifier becomes. The net effect of this is that strong signals are amplified much more than weak signals, and the difference in level made larger.

This means that the dynamic range of the amplifier is extended.

This action takes place, no matter what the setting of the volume control. The average level of the sound is quite immaterial.

Present day EP and microgroove recordings have a far greater dynamic range than earlier standard records so that volume expanders are now largely outmoded, except perhaps for listening to vintage recordings.

WIFE TROUBLE

In any case, Tom, volume expanders have never been very popular with we married fellows; we run into plenty of strife as it is trying to convince our wives that an orchestral record needs to be played at something like the original volume for best results. Add a volume expander and we'd never hear the last of it!

And so for the next one.

Why is it necessary to make transmitter coils of copper tubing or rod? Would ordinary wire not be good enough?

The conductor size used in the construction of transmitter coils depends entirely on the current carrying capacity of the conductor and the maximum current expected to occur in the circuit.

Usually, the highest currents occur in the tank circuit of the final power amplifier and it is particularly here that heavy copper conductors are used for the coils.

The solution to the problem lies in a little equation:

$$P = I^2 R$$

Where P is the power in watts, I the current in amps and R the resistance in ohms.

Now, whenever current flows through a conductor, there will be

some power lost in it due to the ohmic resistance of the conductor. This is very handy if one wants to generate heat, but hardly useful when one wants to feed all the available power to the aerial, to be radiated into space, as is the case with a transmitter.

A closer look at the formula reveals that the power dissipated in a resistance increases with the square of the current.

It may seem, according to the formula, that a resistance of fractions of ohms would make very little difference when there is usually much less than an amp of DC plate current flowing in the coil. What is more the plate current only flows for a comparatively small part of a cycle, as most RF power amplifiers operate under class C conditions.

The trouble is that besides DC current there is a much larger RF current flowing in the tank circuit, usually called the circulating current.

This circulating current will be quite a few amperes, even in a



"... plenty of strife as it is ..."

The device does not produce any acoustic output of its own, but controls the output from an amplifier. Usually it is an integral part of the amplifier.

Its purpose is to make pianissimos sound softer and fortissimos sound louder in music played from gramophone records. Putting it into other words, it expands the dynamic range of recorded music.

Particularly on older records the dynamic range was deliberately restricted, in order to keep soft passages above the noise level and allow loud passages to be recorded at a reasonable amplitude. Needless to say such recordings lacked the contrast and volume range the composer intended them to have.

So a "volume expander" was sometimes used to restore the dynamic range as much as possible.

The basic principle of volume expansion is quite simple. Part of the input voltage of an amplifier is sidetracked and used to control the output from the amplifier.

In practical circuits the sidetracked signal is amplified separately, fed to a detector and rectified to provide a DC voltage which varies with the signal level.



"End-on view of a conductor!"

modest 100 watt transmitter. It is quite sufficient to heat appreciably a tank coil wound with 18 g. wire.

When the power output of a transmitter is calculated in kilowatts, this circulating current skyrockets and with it the resistance losses in the coil, unless steps are taken to reduce the resistance.

Add to this the fact that the RF resistance of a conductor may be many times the DC resistance of a conductor, owing to skin effect (RF current flows only on the surface of the conductor) and you will soon realise, that a conductor of ex-

tremely low resistance is required for such applications.

And just what causes this "skin effect?" Well, Tom, it is a by-product (if we may use the term) of the self inductance of the wire. As you probably know, even a straight wire has inductance, even though the effect is much less than when it is wound into a coil.

The inductance itself is probably not hard to visualise, being simply a product of the magnetic lines of force which surround the wire, expanding and collapsing as the current rises and falls. As with any inductive effect, the result is to generate a counter EMF which opposes the applied EMF.

So far all is plain sailing, but we have yet to explain the skin effect. This is due to the fact that those magnetic lines which are generated at the centre of the wire must cut all the conductor as they expand and collapse. Those generated closer to the outside cut only a portion of the conductor and those generated right at the surface would not cut it at all.

STRONGER FIELD

Thus there are much stronger magnetic forces at work in the centre of the wire than at the outside, making it a lot easier for the current to travel closer to the surface. This effect becomes more pronounced as the frequency increases and, at very high frequencies, there is so little of the centre of the conductor used that tubing is just as efficient as solid wire of the same diameter.

In an effort to illustrate the effect, Tom, we asked our artist to draw an end-on view of a conductor. Unfortunately he seemed to get the wrong idea!

Even at broadcast frequencies the effect is quite marked and has led to the use of stranded (Litz) wire in place of solid wire for virtually all coils used today. By using several strands of very fine wire in place of one heavier one the effective surface area is increased, reducing the resistance at radio frequencies.

As "skin effect" resistance increases with rising frequency, copper is adequate for broadcast and the lower short wave frequencies, but silver plated copper is preferred for VHF and UHF, to reduce further the resistance of the surface.

There are too many variables involved in the calculations for inclusion in this article, but foregoing will illustrate adequately the need for large conductors in transmitter coils.

While we are on the subject of transmitters, here is another question, which concerns not big, but small transmitters.

Some years ago I saw a little set advertised, for playing records through a radio set without having wire connections between the receiver and the pickup. Could I build such a unit?

A unit for such a purpose could indeed be built, Tom. They have even been produced commercially at one time, but we would definitely advise against it.

You see, Tom, such a unit, if not connected to the set by wires, would necessarily have to be a "wireless",

and that is the nigger in the woodpile.

It would have to be a transmitter, to which the pickup is connected. The music from the record would then be broadcast, and picked up by any normal receiver, if tuned to the frequency of the transmitter.

The trouble is that it may not only be picked up by your own receiver, but by others in the immediate vicinity. And before you knew where you were, you might have the wireless inspector on to you.

As you probably know, to cause a radio interference is an offence against the law, involving possibly a fine and confiscation of equipment.

That would make the playing of records rather expensive, Tom.

Commercial units of yesteryear operated at the extreme end of the broadcast band, and the receiver to be used with it had to be able to cover this frequency.

So, take our tip, Tom, and "stay off the air".

In any case, the reproduction is likely to be better with the pickup fed directly into the audio system. It avoids the complications and distortions of impressing the signal on an RF carrier, then passing it through the receiver's tuning system and detector—all needlessly!

I have a circuit, in which the dial lamps are shown to be connected to the 5V winding of the transformer. No matter how hard I have tried, though, I could not get any 5V dial lamps. Could I use ordinary 6V dial lamps?

Within certain limitations the answer is Yes, Tom. Normally a 6.3 V dial lamp will work quite effectively from a 5V supply. After all, they are only required to illuminate the dial scale, and not double as a reading lamp as well.

At the same time there is less strain placed on the lamp filament on the lower voltage, thus extending the life of the lamp and preventing blackening of the glass bulb.

So there you are. It is actually of an advantage to run dial lights at lower than rated voltage.

BE CAREFUL

It is not all plain sailing, though. Normally, the 5 V winding on transformers is provided for directly heated rectifiers or rectifiers in which the cathode is tied to the filament. The rectifier filament or cathode being anything up to 400 volts above chassis potential, connecting dial lights to the transformer winding would place these also on the same potential, making them extremely inconvenient, if not dangerous.

Dial lamp sockets are not provided with insulation sufficient for such voltages and may easily break down. Also, being in an exposed position on the chassis, they are easily touched, when the set is removed from its cabinet. And 400 volts are nothing to play around with.

So, for safety's sake, Tom, don't connect anything to the 5V transformer winding, unless you are sure it is unused.

If it is used, leave it strictly alone.

The RADIOMASTER

RADIOGRAM CHASSIS . .

A great performer on Radio and Records

MODEL E15 FEATURES: Eight Valves, world range — Push pull output — Inverse feed-back — R.F. stage — three position switch for radio and gramophone — Switchpot for volume and power supply—Latest type Radiotron valves—Straight line dial in four colours — Moulded escutcheon plate, size 12in x 7in — 12in Lensen speaker—Six months' £32/10/- guarantee. Price . . .

MODEL E21: Same as model E15 but has separate controls for treble and bass boost (five controls in all). Price £34/10/-

MODEL F47: A custom built 5-valve radiogram chassis with superb tonal quality and high undistorted output.—Complete with Radiotron valves and Magnavox 12in speaker. £21/10/- Price


Extra for matched "tweeter" speaker and crossover network 35/-.
Freight Extra.

MONEY BACK GUARANTEE

If you are not satisfied with Radiomaster Radiogram chassis money will be refunded promptly and in full providing you despatch within seven days of receiving goods and pay freight both ways.

Cocktail and Standard

RADIOGRAM CABINETS

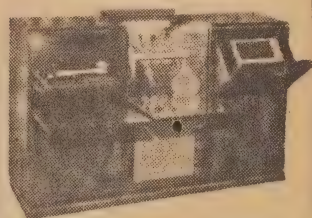


Many popular designs available including Swedish and models incorporating vented speaker enclosures. Latest American design vented speaker enclosures can also be supplied. First-class finish.

ALL TYPES OF THREE-SPEED RADIOGRAM UNITS

WRITE FOR CATALOGUE

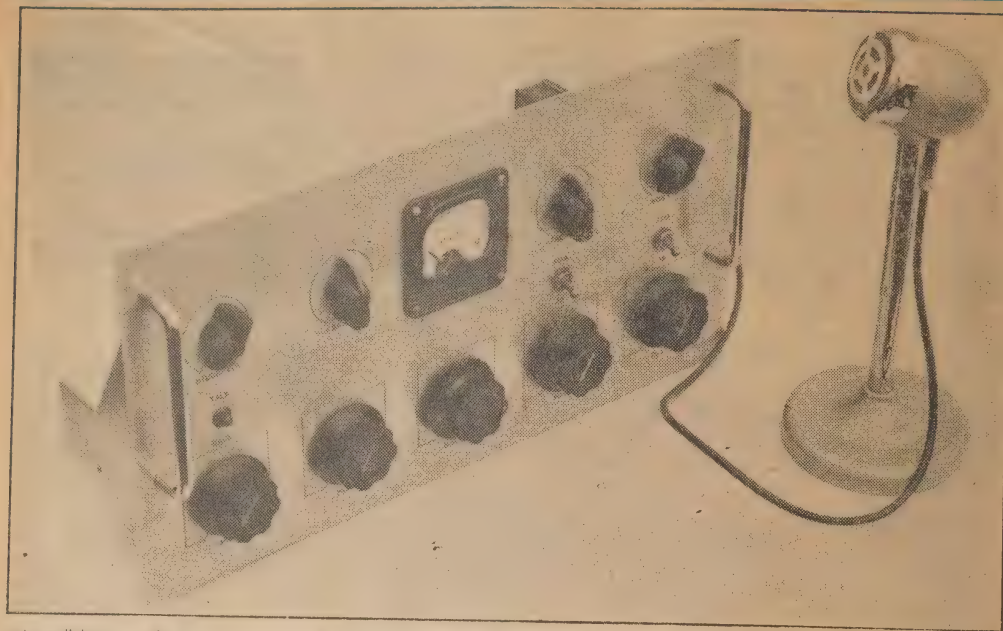H. B. Radio Products

5 Carrington Street,
Lewisham, SYDNEY.
Telephone: LM5580
Established 24 Years



A small but versatile mixer panel which we currently have under development. It will accept the input from two microphones two pickups or two external channels. Full compensation facilities are built in, plus booth monitor, program monitor, level indicator, low impedance output, etc. The microphone in the picture is a crystal insert type which might, for example, be used for talk-back.

DESIGNING A MIXER UNIT

We have had many requests in recent months for information on preamplifiers and mixing systems. In this first article, we plan to discuss the whole subject, having in mind the techniques and components which apply for home-built equipment. Next month we anticipate being able to describe the mixing panel pictured above.

IN the professional broadcasting and recording field, the design of preamplifying and mixing systems has, of necessity, become a very exact science. Over the years, it has been the subject of numerous papers, articles and textbooks.

The microphones normally employed have very low orders of output signal, in the interests of fidelity, but this signal has to be amplified to usable levels without the listener being aware of any background noise or hum.

MIXING FACILITIES

At the same time, mixing facilities have to be provided, whereby the signals from several microphones can be combined and varied at will and finally fed into a single program channel.

For dramatic work, bridge music and sound effects may also have to be fed into the channel from disc and tape, requiring very elaborate "mixing" facilities. The relevant controls must be centralised, com-

pletely smooth in operation and completely silent.

Normal practice in broadcast and recording studios is to use microphones with an output impedance of between about 50 and 500 ohms. These are fed, through twin balanced and shielded lines, to centralised preamplifiers.

Pickups also are normally of the low impedance type, equalised as necessary and then likewise fed to preamplifier stages.

It is common practice to use telephone-type patching panels which allow alternate amplifier sections to be substituted in the case of a

fault and which also allow various microphone, pickup and line circuits to be directed to different control consoles.

The control and mixing facilities often involve the use of low impedance stepped attenuators which, while rugged and reliable, are very expensive.

The associated valves are low-noise types, hand-picked for good characteristics and fed from remote power supplies and/or batteries.

TOO SPECIALISED

As can readily be imagined, this whole approach is completely beyond the means and the requirements of the average audio enthusiast.

He cannot afford the expensive array of lines and transformers which go with the low impedance techniques, nor can he think in terms of stepped attenuators.

He must be prepared to work, wherever possible, directly into grid circuits and use ordinary good qual-

by *Neville Williams*

ity potentiometers to provide volume control and mixing.

He must be prepared to use ordinary—and even disposals—type valves, running them from conventional AC supplies and taking what precautions he can against hum and noise.

And last but not least, his equipment must be of the type which he can carry away when its job is done.

It is for this type of reader that we present this article.

Nowadays, many applications are suggesting themselves for simple amplifier-cum-mixing facilities. You may recall that, in the October issue for 1954, we featured an amplifier intended for use by film and film-strip enthusiasts. There is a very definite tendency, these days, to “dress up” the presentation of home movies and film strips with a background of music and a spoken commentary through a microphone.

FOR RECORDING

Many have gone to the extent of pre-recording commentaries and music on tape, with the addition of sound effects and even limited dramatics. For such purposes a fairly versatile mixing system is essential.

The same would be true for synchronised sound or “striped” films.

Then again, for stage presentation and dramatic work, it is often desirable to use a number of microphones and pickups to feed the main PA system—calling once again for limited mixing facilities.

Additionally, many readers have come to light with special requirements. One such reader, having an apparent connection with a local dance band, wanted to make tape recordings with certain sections of the band, or the vocal accompaniment, accentuated to varying degrees. He wanted to use multiple microphones, with a separate fader on each one.

Another wanted equipment to train an amateur group so that they would be able to present short religious programs over the local country radio station. If the equipment was good enough to produce acceptable tapes directly, so much the better.

Such then are the requirements. How can they best be met?

Before we can answer this question properly, it is really necessary to examine the kind of microphones and pickups which non-professional folk have to use, the limitations of ordinary carbon volume controls, the tricks necessary to minimise noise and hum in ordinary preamplifier stages and so on.

VOLUME CONTROL

Strangely enough, the most appropriate point of entry into the whole subject is with the volume control and its most appropriate position in an amplifier circuit. Actually, the position of the volume control is so conventional that we sometimes lose sight of the fact that it is, in fact, fairly critical.

If the volume control is located too near the input of a high-gain amplifier, valve hiss and residual hum may be apparent to an annoying degree, even with the volume control turned right off.

There is also the danger that small

TYPICAL MIC. RESPONSE CURVES

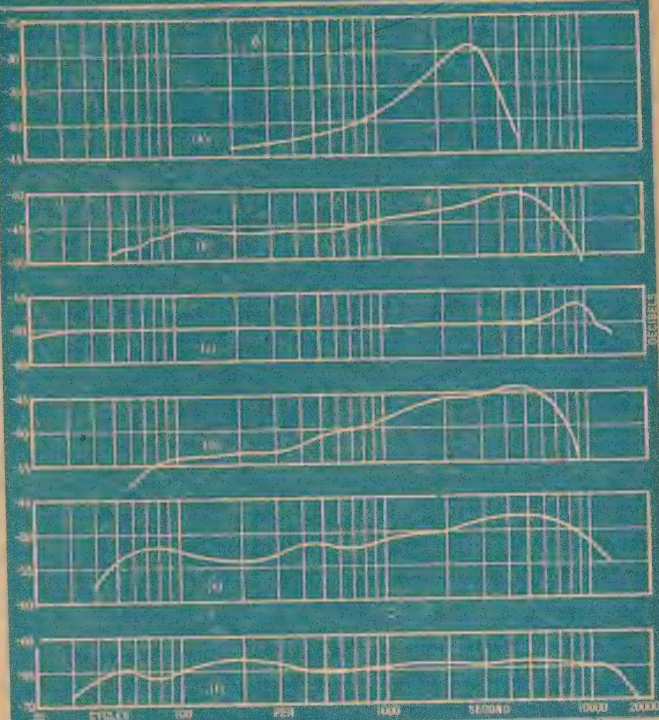


Figure 1: A group of fairly typical response curves for microphones ranging from cheap crystal inserts to medium-priced ribbons and dynamics. In general, the better the microphone in terms of response, the lower is the output voltage.

discontinuities, which are inevitable in the resistance element, will produce an objectionable scraping noise when the control is operated.

Conversely, a control which is located too far from the input may not protect early valves from overload with strong input signals. Severe initial distortion can result from this effect, even though the rest of the amplifier is operating at quite low level.

SIGNAL LEVEL

It is conventional practice, nowadays, to locate ordinary carbon volume controls at a point in the circuit where the input for full output is about 0.25 volt RMS.

The audio system in an ordinary receiver is commonly designed with about this order of sensitivity. The input grid is connected via the gain control to the radio tuner or crystal pickup as required and, since the output from both is normally well over 0.25 volt, there is usually gain to spare.

In more specialised equipment involving such things as magnetic pickups, photocells or microphones, the available signal may not be sufficient to drive an amplifier having the above mentioned order of sensitivity. At least one extra stage of amplification is necessary.

If the extra stage were wired into circuit AFTER the volume control,

difficulties would be encountered as aforementioned with valve hiss, residual hum and control noise.

To avoid such troubles, it is normal practice to provide the extra stage BEFORE the volume control, with the reservation that the extra stage will never be called upon to handle an input signal large enough to produce overload and distortion in its plate circuit.

On the basis of this explanation, we can follow the conventional practice of referring to the stages after the volume control system as the “basic” amplifier. Stages ahead of the volume control system can be referred to as “preamplifiers”.

PREAMPLIFIER

We can further state, by way of definition, that the purpose of a preamplifier is to raise small signal voltages to a level where they can be applied successfully to a volume control or, in fact, to a complete volume control cum mixing system.


The amount of gain required from a preamplifier stage depends naturally on the input signal from which it has to operate. If the input signal is very small, then the gain of the preamplifier stage (or stages) must be quite high to raise the level over the required quarter-volt or so.

Conversely, a higher input signal does not require as much preampli-

PERFECTION in PICKUPS

The manufacturers of the famous GP 20 proudly bring to you a new
HI-compliance pickup:—

THE ACOS

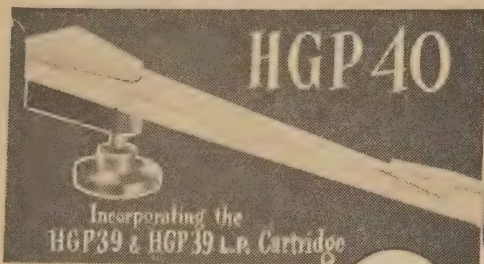

Incorporates the GP20 arm and features the HGP 39 STD and HGP 39 LP interchangeable cartridges with replaceable stylus.

REPLACEMENT STYLUS

SB-1 Standard
SB-2 Microgroove

Price

12/- ea.

£9/15/-

complete with standard
and microgroove heads



SPECIFICATION

Response.....	From 40 C.P.S. to 13 Kcs
Overall response.....	20 C.P.S. to 17 Kcs
Output.....	1 volt on std records, 1/3 volt on l.p. record.
Tracking weight.....	8 grammes

Sole Australian Agents:—

Victorian Distributors:—

AMPLION (A'sia) PTY. LTD. 88 Parramatta Rd., Camperdown,
Sydney, N.S.W.
DISTRIBUTORS CORPORATION 403 BOURKE ST., MELBOURNE.

Accent on **RELIABILITY**

From the **LARGEST** to the **smallest**



U.C.C. can supply high quality capacitors
for every application, including:

- Power Factor Correction • Carrier
- Coupling • Fluorescent Lighting • Motor
- Start • Radio Receivers • Telephone Equip-
- ment • Interference Suppression • Auto-
- motive Ignition • High Power R.F.
- Applications • Super Tropical Types
- U.H.F. and T.V. Types.

Capacitors *for every application*

UNITED CAPACITOR CO. PTY. LIMITED
433 Punchbowl Road, Enfield, N.S.W.

UW3511



MELBOURNE: U.C.C. Pty. Limited, 486 Bourke Street.
ADELAIDE: Stephen and Co., 83 Grenfell Street.

BRISBANE: Tecnico Ltd., 103 Albert Street.

PERTH: O. F. Gamble, 384 Murray Street.
N.Z.: H. W. Clarke (N.Z.) Ltd., 42 Cable Street, Wellington. TAS.: G. A. W. Wood, 46 Brisbane Street, Launceston.

fication and the circuit problems are fewer.

The microphones, which are likely to be pressed into service by private individuals, would naturally constitute a varied array of current and obsolete types ranging from cheap crystal inserts to near-professional models ranging up to about £30.

To assess the merits and demerits of each and every likely type would be an impossible task, but certain general remarks can be made about frequency response and output. They should at least help to put readers on the right track.

Carbon type microphones can be ruled out immediately as quite useless by modern standards.

By far the most numerous—and the cheapest—microphones currently available are the crystal inserts which retail for something under £2 each. These are used very commonly and successfully in paging systems, communication equipment, "Ham" shacks and so on—all of them "voice" applications where clarity is of utmost importance.

RESONANCE

However, their "clarity" invariably springs from a prominent diaphragm resonance in the middle of the range. It distorts the character of voice so much that the inserts are useless for more ambitious work, where it is normally desired to retain as much as possible of the natural timbre of the person's voice.

For music, of course, a peak in the range spoils the reproduction completely.

Curve (a) in figure 1 is fairly typical for this type of cartridge. It shows a 10db peak at about 3 Kc, falling away sharply above about 5 Kc. The bass response is also poor, so that it is not hard to understand why such inserts are often described as having a "crisp, metallic quality".

It is also not difficult to understand why they are very prone to acoustic feedback, when used anywhere near the loudspeaker or a public address system; or why the feedback is evident as a high-pitched howl. But for the presence of the peak, the amplifier gain could be advanced several db before feedback showed up.

The main advantage of such microphones is their relatively high output, as evidenced by their rating of about -40db below the usual reference of 1 watt-dyne per sq. cm. In actual fact, the output of the unit shown peaks to higher than -30db.

MODERATE GAIN

With an output of this order, only a very modest preamplifier is necessary to ensure ample overall gain. However, as we mentioned earlier, such units are intended for voice communication only, and are quite unsuitable for the more ambitious applications we have in mind.

The "wide-range" or "high fidelity" inserts—neither term being really appropriate—are a better proposition. Curve (b) is typical for such an insert, although some manufacturers claim a response somewhat flatter than this.

In broad terms, one can expect

from such cartridges a useful response from about 40 to 7500 Kc, with a 2 to 4db rise somewhere in the middle of the range.

At the present time, these cartridges retail separately for something under £3 and are used, in one brand or another, in many of the complete microphones retailing around the £7 to £9 mark. Curve (b)—and the foregoing remarks—may therefore be regarded as broadly typical of all such microphones.

In practice, the majority of such units still sound somewhat "peaky" but are sufficiently natural for modest stage work, recording voice commentary and so on. They can only be recommended for musical recording on a limited scale.

In most cases, the wider range

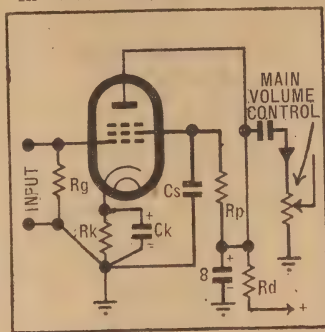


Fig. 2: A basic preamplifier circuit which is discussed in the following pages.

cartridges are basically similar to the high-output voice types, except that an acoustic filter in front of the diaphragm is used to damp the resonance peak. It also reduces the output by about 2:1, as is evident from the fact that curve (b) shows an average level of about -45db.

Rather more preamplifier gain is required, but still not more than can be provided by a fairly high-gain triode preamplifier.

HIGHER PRICE

From the diaphragm type crystal inserts (or complete mics.) the next step appears to be to the semi-professional sound-cell type crystals. These are capable of a much better order of performance, but retail for upward of £15, depending on their specifications.

From such microphones one can expect a response something like curve (c) and, while they are not widely used for serious professional work, they would be good enough to keep a private enthusiast happy for quite a long time. As with all crystal devices, however, they must be protected from extremes of temperature and humidity.

Curve (c) shows an output level of -59db, which is a good deal down on the diaphragm types previously mentioned. One would expect to follow such a microphone with a high-gain pentode preamplifier.

Coming to a different class of microphone, quite a number of inexpensive dynamic (moving coil) microphones have been sold on the

local market. For the most part, these have been intended primarily for public address work, with high output and extreme ruggedness as their main virtues.

Curve (d) is fairly typical. It shows an 8db rise between 500 and 4500Kc, falling away below about 50cps and above about 6Kc. The output is shown as about -50db, so that a fairly high-gain preamplifier is desirable, usually a pentode.

In general, the same remarks would apply as for the cheaper crystal inserts: They give a crisp, metallic quality on speech but are too unnatural and too peaky for more serious work.

One can obtain better quality dynamic units, of course, but once again the price is likely to run to between £15 and £20. Curve (e) is typical enough for one of the better quality dynamics.

TO LINE OR GRID?

It is worth noting that dynamic microphones can usually be supplied with in-built output transformers intended to operate into lines of one impedance or another, or directly into grid circuits. The output voltage from the "line" types is quite low, unless it is stepped up, as intended, by a separate line-to-grid transformer.

Ribbon or "velocity" microphones make up the remaining group which needs to be mentioned. These range from inexpensive little units selling for a few pounds to high-quality professional types selling for anything between £30 and £100.

The latter can be dismissed as beyond the means of most private enthusiasts. We can also dismiss certain very small types, having the ribbon enclosed at the rear and intended for speech work only.

In between these extremes, a variety of ribbon types have been sold. The cheaper ones, though free from peaks, have usually lacked somewhat in treble response and output, due to limitations of the magnet structure and coupling transformer. The dearer ones—those approaching £20 in price—are generally better and equal any likely demands of a private enthusiast.

Curve (f) is typical of what one can expect.

Because they should not be used "close-up" and because their output is low, anyway, ribbon microphones usually have to be followed by a high-gain preamplifier. At the very least, a high-gain pentode stage would be required, with preference for a two-stage preamplifier, if a margin of gain is to be available at all times.

TRANSFORMERS

Like the dynamic types, velocity microphones are produced with either "line" or "grid" type coupling transformers built in. The "grid" type is necessary if its output is to be fed directly to the input terminals of the preamplifier.

At this stage, one might logically include a discussion of pickups and their preamplifier requirements, if any. However, this whole subject has been examined most exhaustively in connection with control units, domestic amplifiers and such like, so that repetition here is unnecessary.

Perhaps it should be sufficient to

HOMECRAFTS

RADIO IS OUR BUSINESS

100 CLARENCE ST., SYDNEY. BX 4451



SCOPE

SOLDERING IRONS 6sec.

Standard	£2/10/-
Instrument	£2/10/-
Vibroscope	£1/15/-
Transformers	£2/7/11

FOR THE SERVICEMAN

5in CRO. KITS
1in CRO. KITS
Senior Sig. Tracer Kit
Mod. Oscillator Kit

UNIVERSITY

MVA2 Multimeter,
TST Valve and Circuit Tester
VOA Oscillator

PALEC

M32 Multimeter
M42 Multimeter
ET4 Valve Tester

SERVICE MANUALS

Vol. 13 24/-

VALVE DATA BOOKS

Philips 10/6
Radiotron 6/6

Transistor Books 2/-

SERVISOL ½pt. tins, 8/-
ENGLISH Multicore Solder
40/60 & 60/40 Spintites 3/-

EXPANDED ALUMINIUM

27in x 13½in
24/- Sheet

MULLARD 5/10 HI FIDELITY AMPLIFIER KIT

PLAYMASTER AMPLIFIER

17 WATT Ultra Linear
No. 9 Ultra Linear
No. 10 Ultra Linear
No. 11 Amplifier
No. 12 Ultra Linear

RADIO & HOBBIES

Kit Sets available
Quotes on request

COLLARO

3-Speed Single Player
£11/10/-

"MONARCH"

3-Speed Automatic Mixer Changer
with HGP37 Cartridge
£19/10/-

BSR GU4.A

3-Speed Single Player
£12/-/-

Output Transformers

By A & R Electronics
and Fergusons

Power Transformer and Chokes

Ferguson and National
Prices available on request
Aegis Loop Sticks 20/9
Aegis Magnet Aerial 40/-
"Q Plus" Crystal Sets 49/6

**ALL ITEMS IN THIS AD-
VERTISEMENT EXCEPT
SPECIALS ARE AVAIL-
ABLE FROM YOUR RE-
TAILER.**

NEW RELEASES

OC72 Output Transistors Single

£2/10/6

Matched Pair

£5/0/6

Jabel Planetary Drive
with Insulated Bush
15/6

DIAMOND stylis

by Goldring

£6/10/-

DUCON Miniature Potentiometers

.5 Meg
.5 Meg Tapped
.5 Meg with D.P. Switch
.5 Meg Tapped with Switch

SPECIALS

Spintites 3/-
1 Meg Sw/Pots 5/-
4 Pole 3 Pos. waffer 5/-
12V-240V — 74 Watt Inverters.

£10/10/-

Double Pole Single
Throw Switches Long Neck, 5/-
Output Trans. 32 Watt
5000 Push Pull
500-250-125 Sec., £6/12/6

Power Trans. 325/45MA

5V 2 amp.

6.3 2 amp.

34/6

Chokes 50 MA

13/6

Hook Up Wire 10/010
Rubber Insulated Cotton
Braided Push Back
in red and green
100 yards

£2/10/-

COUNTRY CLIENTS ARE REQUESTED TO ADD FREIGHT

HOMECRAFT'S FAST DESPATCH SERVICE



YOUR ORDER



IS



ASSEMBLED BY EXPERTS



AND



RUSHED TO YOU

say that crystal pickups need no pre-amplification and no special compensation, being normally fed via a 0.5 meg. potentiometer to the input of the basic amplifier.

Magnetic pickups, on the other hand, do require a preamplifier stage, designed to give both gain and bass compensation. A high-gain triode is often sufficient, though the lower output magnetics require a pentode stage.

We shall have more to say about this particular subject when discussing the design of our complete mixer unit.

GAIN PROBLEMS

Because the inclusion of a preamplifier stage (or stages) automatically involves a much higher overall gain, difficulties are likely to be encountered, which do not occur to any great degree in lower gain audio systems. These difficulties include microphony, hum pickup, valve and circuit noise, and instability.

Microphony is the tendency for early valves in the amplifier to generate noise when they are subjected to mechanical shock. Vibration of the electrodes produces a sympathetic variation in plate current, which is amplified by succeeding stages just as if it were a signal.

Microphony is least serious in equipment which can be rigidly mounted, and is not disturbed during operation. It can be quite a problem, however, where strong impulses from the loudspeaker can reach the preamplifier or where it is mounted in a mixing console subject to jarring by the operator's movements.

Ordinary valves are often used in preamplifier stages, but there can be no guarantee that they will be non-microphonic in operation. It is always helpful if the best of several such valves can be selected for the position, or if a flexibly mounted socket can be employed.

The best precaution against microphony is undoubtedly to use, in the preamplifier stage, one or other of the currently available "low-noise" valves, especially intended for the purpose. These include the Z79, EF86, 6BR7, &c.

All these valves are pentodes and give the highest gain when so connected. However, by strapping screen to plate, they can be used as low-noise triodes, giving medium stage gain in cases where this is adequate.

The use of a low-noise valve usually guarantees freedom from microphony troubles except in the most difficult applications. Flexible socket mountings are not normally required.

SHIELDING

Hum injection is another likely problem which needs specially to be considered.

As an initial precaution, the input circuit and leads to a preamplifier must be completely shielded to avoid pickup of hum voltages by capacitive coupling to AC wiring. The same shielding will be effective also against instability due to input-output coupling.

For the same reason, a shielded plug and socket is much to be preferred for a microphone connection to open terminals or an unshielded earphone-type jack.

Hum, which is due to eddy cur-

SOME TYPICAL MIXING CIRCUITS

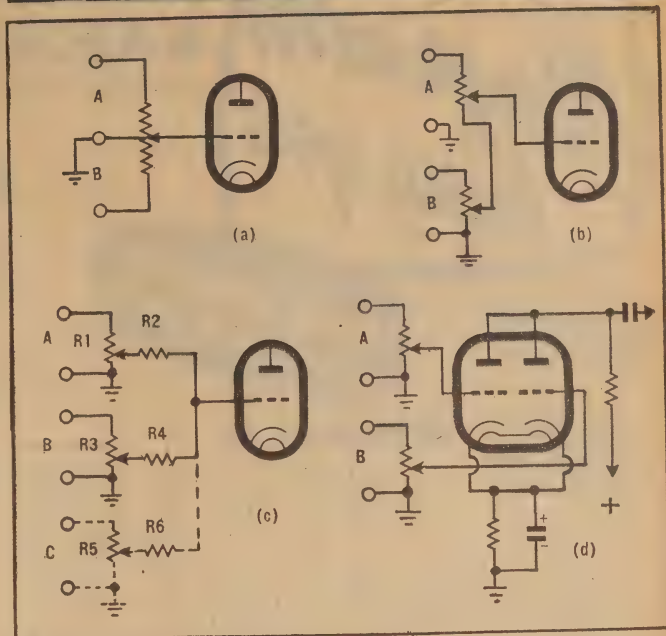


Fig. 3: Diagrams (b), (c) and (d) illustrate the basic mixer circuits which are commonly used in conventional audio equipment. A combination of methods (c) and (d) is often used where four or more channels have to be provided for.

rents in the chassis, cannot be eliminated by mere shielding, because the eddy currents create minute hum voltages along the chassis and earth wiring itself.

At the very least, the "earthy" side of the signal input circuit, the cathode circuit return and the screen bypass (if any) should be made to one point only on the metal chassis. This will minimise the injection of hum voltages into the first stage (See figure 2).

SEPARATE CHASSIS

In actual fact, where low hum level is required and a lot of low-level audio circuitry is involved, it is most unwise to mount the preamplifier stage (or stages) on the same chassis as the power supply. Separating the low-level circuitry from the source of hum fields avoids the necessity for awkward single-point earthing techniques.

Now for a few words about preamplifier circuitry.

In the typical preamplifier circuit of figure 2, the resistor R_g would normally be selected to present a suitable load to the microphone (or other device) feeding into it. For crystal microphones it would most likely be 5 megohms, but could well be reduced to as low as 0.1 meg. for magnetic types.

If a variety of input devices is anticipated, requiring different loads, the wisest course is to make R_g equal to 5 megohms, which will suit most crystal microphones. Other microphones or devices which might, according to manufacturers' ratings, require a lower load, can then have

a suitable additional load wired into the device or its input plug.

This additional resistor should be chosen such that, when connected in parallel with 5 megohms, it presents a net load of the required value. Since the 5 meg resistor is permanently in circuit, it ensures that the grid will not be left floating, even if no input device is connected to it.

The cathode resistor R_k will depend on the type of valve and its published operating conditions. However, the bypass C_k should be as high in value as practical and one of the new small 100 mfd. electrolytics is a good compromise between capacitance and size. A large cathode bypass is a good general precaution against hum injection from the heater-cathode circuit.

The heater circuit itself is important, but rather unpredictable. When using special low-noise preamplifier valves, it is usually sufficient to earth the heater circuit, either by an actual centre-tap in the heater winding or by way of a centre-tapped resistor across the winding.

POSITIVE RETURN



It occasionally happens, however, particularly with ordinary amplifier valves, that lowest hum is obtained when the heater return is made to a positive potential of up to about 20 volts. The idea of the positive heater return is to discourage emission effects and consequent current flow between heater and cathode.

JUST RELEASED!

THE NEW AUSTRALIAN-BUILT

● AEGIS-MULLARD

5-10 AMPLIFIER!

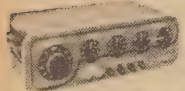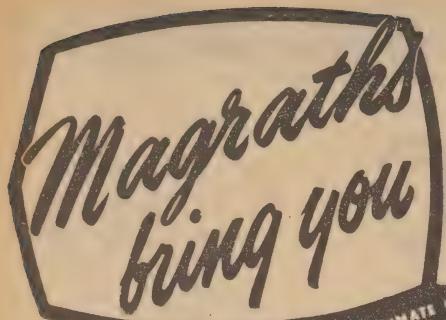


THE ULTIMATE IN
**HIGH FIDELITY
EQUIPMENT**

QUAD II

AMPLIFIER
AND CONTROL UNIT
103 gns.

The most distinguished audio achievement in recent years! Unique stability with less than 0.1 pc total distortion. Higher order distortion. 0.3 pc. Full range fidelity 10 to 60,000 cps plus or minus 1 db. Push-button recording equalisation and program channel selection. Complete input flexibility. Built-in pre-amp. 15 mV sensitivity upwards. Automatic circuit correction. Bass and treble independent of harmonic filtering.

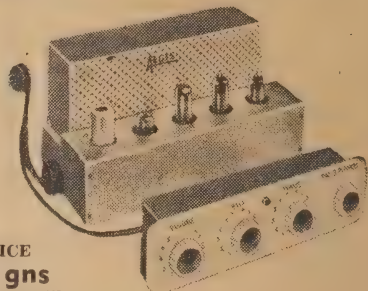

PRICE
48 gns
COMPLETE

Power Output: Rated output 10W. Max. output 12-13W.

Total Harmonic Distortion: The total harmonic distortion is less than 0.4 pc at 40 c/s measured for 10W, output with normal loading and sine wave input.

Hum and Noise: -73db relative to 10W.

Frequency Response: plus minus 0.5db, 10 c/s to 20,000 c/s.

Sensitivity: An input of 50mV to the first valve gives 10W output. This output power is produced by an input of 600mV to the tone control circuit.

Treble Control: Continuously variable control of treble from plus 10db to -10db at 10,000 c/s.

Bass Control: Continuously variable control of bass from plus 11db to minus 5db at 20 c/s.

Connoisseur



VARIABLE
3-SPEED
GRAMOPHONE
MOTOR

PRICE
£35


3-speed Unit (33 1/3, 45 & 78 rpm), 12m turntable, lathe-turned, non-ferrous material. Precision-ground main spindle, lapped to mirror finish, phosphor bronze bearings. Dynamically balanced, resiliently mounted, virtually vibrationless, synchronous motor. Low noise level, low hum induction. Mechanical speed change with a 2 pc variation on all speeds. Input voltages 220/250V AC 50 cycles, or as specified to order for 200/250V AC 60 cycles, or 110V AC 50 or 60 cycles. Mounted on 4in die-cast board, 15 1/2in x 13 1/2in with 32 clearance below motorboard.

COLLARO



**TURNTABLE, 3-speed MOTOR
and TRANSCRIPTION UNIT**
Price £29/10/-.

Model 2010 (note inset sketch of turntable): the perfect record reproduction for the critic! Complete unit mounted on rectangular plate. Equipped with a STUDIO "P" Hi-fi pick-up head with special low resonance arm and bearing. Balanced (flywheel effect) non-magnetic turntable (approx. 8 1/2lb) with rubber turntable mat. "Wow-free" motor per sec. Entirely new type 3-speed mechanism free from rumble and frequency modulation. Features also Voltage Control Panel. Unit is finished in cream scratch-proof enamel.

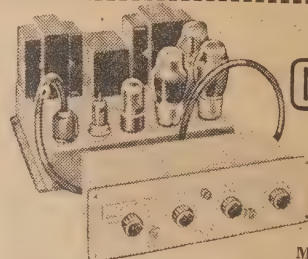

LEAK

AMPLIFIER
AND
PRE-AMPLIFIER
(TL10)
67 gns

Model TL12 110gns.

TL10 Power Amplifier and "Point One" Pre-Amplifier. Triple loop feedback circuit. Max. Power Output: 10 watts. Frequency Response: plus/minus 1 db 20 c/s to 20,000 c/s. Harmonic Distortion: 1 pc. 1000 c/s 7.5 watts output. Feedback Magnitude: 26 db main loop. Damping factor: 25. Hum. 80 db ref. to 10 watts. Speaker Impedances: 16, 8, and 4 ohms. Pre-Amplifier operates from any branded pickup. Instantaneous use of crystal, moving-iron, and moving-coil pickups. Radio input sockets permit connection of any tuner-unit. Distortion: order of 0.1 pc. Hum: negligible. Input Selector, radio, tape, records accurately equalised. Continuously variable Treble and Bass. Features Vol. control and power switch and Tape Recording Jacks.



380 ST. KILDA RD., MELB
208 LT. LONSDALE ST, MELB
Phone: MX 3653 FB 3731
Open Saturday Morning

The usual idea, where such a course is indicated, is to return the heater circuit to the cathode of an output valve—again quite a common practice in "Playmaster" type amplifiers.

In special cases, it may be found that lowest hum level is achieved by providing an earth or "earthy" return to a particular side of the heater circuit rather than the centre-tap. Even if it amounts to cancelling one hum component with another, it may be a worthwhile step.

Screen and plate circuits will normally be completed in accordance with recommended operating conditions for the particular valve. For pentode connection, the screen will be separately fed, and bypassed back to the common earth point for the stage, if trouble with eddy currents is anticipated.

TRIODE OPERATION

For triode connection, the screen will simply be tied to plate and not bypassed. If not connected internally to cathode, the suppressor grid may usually be tied to plate or to cathode, whichever is the more convenient.

Decoupling of the plate (and screen) circuit is almost invariably required and should be provided as a matter of course. Such decoupling will minimise filter hum problems, as well as feedback or "motor-boating" troubles via the power supply.

Instability of this nature is seldom a problem, with a single preamplifier stage, but quite extensive decoupling is called for if the number of stages has to be multiplied to obtain higher gain or extra facilities. More will be said about this when we present the design for a complete mixer panel.

In conclusion, it may be appropriate to add a few general remarks about mixing circuits. Quite a few such circuits have been devised, but many of them are mainly applicable to low impedance techniques, involving lines, balanced transformers and stepped attenuators.

The circuits which are most likely to interest private enthusiasts are illustrated in figure 3.

Figure 3a shows an elementary arrangement which strictly isn't a mixing system, because it does not allow the content of both channels to be heard simultaneously. The centre of the potentiometer is earthed so that the central setting of the knob is "off". Rotating the knob toward one extreme or the other allows the content of channel "A" or channel "B" to be heard, as desired.

SPECIAL CONTROL

Success of the scheme depends on obtaining a potentiometer with a tapping at half rotation, which is also the electrical centre of the element. For smooth control from zero to maximum volume, the input to channels "A" and "B" should not be too high, since the action of the potentiometer will be restricted both by lack of taper and by the reduced rotation on either channel.

Figure 3b illustrates a series mixer which is useful in special cases only. The input to channel "A" should preferably be from a high impedance source as, for example, from the plate of a pentode preamplifier stage. The associated control might

typically be a 0.5 meg. potentiometer.

Conversely, channel "B" and its associated potentiometer should be of fairly low impedance, otherwise channel "A" cannot be reduced to anything approaching zero volume unless channel "B" is also turned off.

Figure 3c is a much more useful circuit arrangement. It can accommodate several channels and there is no special restriction on the value of the individual gain controls. However, the isolating series resistors R2, R4, R6, &c., must all be of the same value and should preferably be no smaller in value than the largest of the controls R1, R3, R5.

Under these conditions, the maximum effect one control can have on the other is about 3db, but, in practice, it is always a lot less than this. For most purposes, the interaction of the controls can be regarded as imperceptible.

The series resistors introduce a loss into each channel, being about 6db for a two-channel circuit. The loss rises to 10db for a three-channel circuit and by about 2db for each additional channel.

This loss has to be made good by extra valve gain and may lead to ultimate difficulties if carried too far. Too much extra gain AFTER the volume control-mixing system may lead to high background noise.

The proper course is to see that the input to all channels is fairly high so that, even after the mixing circuit loss, only moderate gain is required. This may necessitate the use of separate preamplifiers in at least some of the channels.

TREBLE LOSSES

One point that must be watched is the possible deterioration in treble response due to Miller effect in the associated valve. Where R2, R4, and R6 are, say, 0.5 megohm, it is wise to use a pentode following the mixer. A high mu triode would be the least desirable type.

Figure 3d illustrates the well-known scheme of feeding inputs independently to the grids of two amplifier valves, the plates being connected in parallel.

Twin triodes are often used in this application, being quite satisfactory provided that the design does not call for a high output signal from the composite plate circuit.


Pentodes are better electrically than triodes in this application, because the mutual loading between the two valve sections is less and each can give higher gain and output than is possible with triodes. However, two valves would be called for.

The arrangements of figure 3c and 3d are often combined where four or more channels have to be accommodated. Two or three channels are mixed into each grid circuit and the output all four (or six) taken from the composite plate circuit. The valve gain may be controlled so that it just offsets the mixer loss.

Alternatively, the valve circuit may be allowed to provide whatever gain it will, but a "Master" control added to permit the overall mixer gain to be set to some convenient level.

Next month, we plan to show how these principles are all brought together to produce a single, comprehensive mixing console.

METAL UTILITY CABINETS

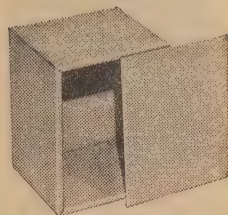

This line of cabinet is for housing electronic equipment of all types. It has fixed back and removable front. Basic colour is grey.

Catalogue No.	D.	W.	H	Price plus Sales Tax
MC6	6in	6in	6in	8 3
MC5	5in	6in	9in	9 4
MC7	7in	8in	10in	13 9
MC67	6in	7in	12in	13 9
MC81	8in	10in	10in	17 0
MC811	8in	11in	12in	£1 1 0
MC79	7in	9in	15in	£1 1 0

SLOPING FRONT CABINETS

SF7	7in	6in	6in	11 6
SF79	7in	9in	6in	13 9
SF71	7in	11in	6in	16 0
SF8	8in	13in	8in	19 3
SF10	10in	18in	10in	£1 11 3

SPEAKER BOXES

5in hole	7in	7in	4in	12 3
6in hole	8in	8in	4in	14 3
8in hole	10in	10in	6in	19 3

ANY CABINET, TO
ANY SIZE.

48 HOURS SERVICE

R. H. OXFORD & SON,
PTY. LTD.


97 MARRIOTT ST.,
REDFERN MX3764

Please send cash with order.

SERVICE

Our 24-hour per day, 7-day week phone service is at your disposal with first-class practical technical know-how to assist you with your Radio and Amplifier problems and needs.

DAY LA3845 — NIGHT XW5956

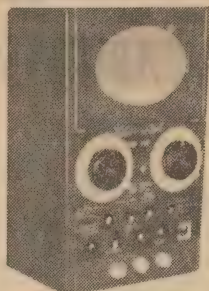

AR8 COMMUNICATIONS RECEIVER

12 Valve. Converted to 240V A.C.
Thoroughly Tested. Re aligned.
Latest Ovaltone Permug Speaker.
Noise Limiter added.

£34/17/6

NEW — RT34 APS13

TAIL END CHARLIE

12 Valve, 420 Meg Transmitter
Receiver Gene Powered
5-UJ6, 9-UAG5, 1VR150 2-2D2
Complete with Circuit and
Conversion Circuit.

£10

LESS VALVES, £6/17/6

NEW VALVES

1C6	12/6	723A/B	
1D4	12/6	KLYSTRON	£3
1G4	12/6	6K7	7/6
1J6	12/6	1K5	2/6
1K4	12/6	12SJ7	12/6
1K6	12/6	12SK	12/6
1LH4	12/6	12SL7	12/6
1LN5	12/6	38	12/6
1P5	12/6	39/44	10/-
1R4	12/6	46	12/6
1V	12/6	47	12/6
2A6	12/6	78	12/6
3A4	15/-	304H	£5
3B7	10/-	717A	6/6
3D6	10/-	809	£2
6AC7	9/6	828	£2/10/-
6AG5	9/6	843	£1/10/-
6AM5	15/-	957	6/6
6AM6	17/6	1619	£1
6H6	17/6	1625	£1
6J6	15/-	1629	10/-
6J7G	9/6	2050	£1
6N7	10/-	4307A	10/-
6SK7	12/6	9001	8/6
6SL7	12/6	9003	12/6
6SN7	9/6	9004	8/6
6X5	10/-	RK75	10/-
6Y6	17/6	RK48A	£3
10	15/-	VR75/30	15/-
12A6	12/6	VR105/30	15/-
12H6	12/6	VR150/30	15/-
KTW62/6U7	7/6	NR74	7/6
VR65A/SP41	2/6	ATP35	12/6
KT66	27/6	EB34/6H6	2/6
833A	£15	EF50	3/6



DULWICH HILL, UNDERCLIFFE, EARLWOOD
EVENINGS and WEEKENDS: "KALUA",

AR8-ATS — COMPLETE STATION

AIR TESTED

Transmitter-Receiver, Aerial Coupler,
Cables, Plugs, Phones, Mike.

1 Crystal to desired Frequency.
24V Power Supply & Circuits of 3 units
GUARANTEED IN PERFECT ORDER.

£62/10/-

Other voltages available.

CRYSTAL CALIBRATORS

TESTED. PERFECT ORDER

£9/10/-

New ROLA
3-inch SPEAKERS
£12/6

AR7 RECEIVERS

COMPLETELY RECONDITIONED
With 5-coil boxes. Perfect order.

£47/10/-

BENDIX

BC221 FREQUENCY METERS,
AIR TESTED

Original Crystal and Calibration Book

£45

NEW C.R.O. TUBES

VCR.138 **£2/2/6**

VCR.97 **£2/2/6**

Connections & Basic Circuit included

5-B.P.I. **£1/7/6**

New Telephone Wire

American 7 Strand Rubber Insulated
1/2 MILE DRUMS 15/-

CASE OF 6 DRUMS, 3 MILE **£4/-**

DON 8 WIRE, 3 MILE **£10/-**

Throat Mikes, new **3/6**

12v 420 watt Prefocus Globes **7/6**

ROTARY CONVERTERS

150 WATT

24 to 32V DC Input

230V AC 50 Cycles Output

£20

"COLLINS"

TSC6 TRANSMITTER & RECEIVER

1.5 TO 12.5 MEGS.

4 Position Crystal on both units.
4-Band Variable Tuning on Receiver
100 Watt Input to Transmitter
Plate Modulated.

Receiver. Sensitivity 2MV
12V Operation. Circuits included.

£57/15/-

Power Supplies available for various
voltages. Prices on application.

TRI-MAX O.P. TRANSFORMERS

NEW HI-FI

20 Watt 6600 P to P to 600

£2/5/-

TYPE S POWER SUPPLIES

FOR AR8-ATS STATION

240V AC operation. Air tested

£45

RELAYS

1700 SPDT **7/6**

1300 SPDT **7/6**

500 x 500 SPDT **7/6**

500 x 500 ohm **12/6**

12 volt DPDT 5 amp **£1/-**

24 volt DPDT **12/6**

8-16 volt DPDT **12/6**

110 volt AC **£1/-**

Hi-speed Polarised relay **£2/10/-**

400 ohm **12/6**

1300 ohm DPDT **15/-**

1/2 in Square Section DURAL TUB-

ING UP TO 12ft lengths 1/- per ft.

Hi-Lo Phone Transformers **4/6**

Spirit Level bubbles, mounted **4/6**

Canadian Signal Lamps **12/6**

24v 1500 watt Generators

£12/10/-

H. Voltage Lead-Thru Insulators, ..

1/6 each, 15/- doz.

Hydrometers, Battery testers **5/9**

Torches 3-cell Focusing **9/9**

Torches 2-cell Focusing **6/9**

Multi-strand 5-core Cable.

Yard, 1/-; 100 yards **£2/17/6**

Tx. Var. Condensers. 300 pf **£1/5/-**

100 pf **£1/1/-**

60 pf with Vernier **£1/1/-**

30 pf **10/-**

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

RADIO

PHONE

LA 3845

136 VICTORIA RD. MARRICKVILLE, SYDNEY, N-S-W

TRAM AT DOOR. STOP No. 42

COLLAROY ST., COLLAROY—XW5956

AT5 -TRASMITTERS

6 Position Crystal Control
Complete with valves and Circuit

£5/10/-

NEW REBECCA

Transmitter Receivers

170 meg to 220 meg.
15 Valve. Turret Tuned. 6 Position.

£9/10/-

SHOCK MOUNTS

NEW — BENDIX

Mount your Mobile Gear Amplifiers, etc.,
on these 11 x 8 rubber and steel shockers.

2/6

ALDIS LAMPS

12 Volt

For Signalling, Shooting,
Yachtsmen, etc.,

£3/17/6

NEW TRANSFORMERS

FERGUSON

225 x 225 50MA. 6.3 17/6

VIBRATOR

150 x 150 40MA. 6V £1/4/6

300 x 300 100 6V £1/17/6

325 x 325 125 12V £2/17/6

INVERTOR TRANSFORMERS

6V 240V 40 watt £2/17/6

12V 240V 60 watt £2/17/6

C.R.O. TRANSFORMERS

SMALL FULLY-SHIELDED 2500V

£1/17/6

SELENIUM RECTIFIERS.

2500V 10MA £2/7/6

TUBULAR CONDENSERS

.25, .1, .02, .008 .. 600v 9/- doz.

.5, .25, .1 400v 7/6 doz.

.5, .25, .1 200v 6/- doz.

New Coils & Intermediates

Standard or miniature to suit

all valves.

Coils B/C 455 KC 7/6

Coils S/W 455 KC 7/6

Inters 9/6

Loop aerial coils 7/6

Slug tuned H.F. Coils suit 144 Mls ... 4/6

AT5 POWER SUPPLIES

24V OPERATION

2 Genemotors, 550V 350MA & 250V
100MA, Chokes, Condensers, etc.,

£2/10/-

DURAL OXYGEN

BOTTLES

300lb test. Suitable for Aqualungs etc.,

£1/7/6

WANTED

Communication Receivers,
Test equipment, P. A. gear.
Large or small surplus stock.
Best prices. Call, write or
phone any time.

OIL FILLED CONDENSERS

.5UF 2.5KV .. 6/6 4UF 600V .. 6/6

.1 .1UF 7KV .. 15/- 5UF 400V .. 6/6

4UF 1KV .. 12/6 8UF 400V .. 10/-

7.5UF 330VAC 10/-

New Bendix B.C. 1206

Receivers, 6 valve. Converts to Carset or
QSER, 6R7, 6SA7, 6SK7, 6SQ7, 22SL6.

£5/17/6

INCLUDING CIRCUIT

BUZZERS

HIGH PITCH, VARIABLE NOTE

Including built-in Transformer.

7/6

Postage: NSW, 2/-; Interstate, 3/6.

OSTER MOTORS

NEW & TESTED.

THE MODELLER'S DELIGHT.

£2/10/-

GENERATORS

12V 500 WATT

TESTED — GOOD ORDER

£3/10/-

RECORDING TAPE

USED, EX LEADING

BROADCAST STATION

1200ft spools **£1/7/6**

PRICES

We supply at the Lowest Price
consistent with cost.

We guarantee to Sell at as Low or
Lower Price Than our Competitors
at any Time.

WE REFUSE TO BE UNDERSOLD

AMR 300

Australia's finest communica-
tions receiver. Built by STC. 10
valves, crystal gate, noise lim-
iter, Bandsread coverage 1.5
to 24 megs continuous. 240
volts AC operation Air tested.
Sensitivity better than 2 micro-
volts.

Including Specially Matched
Speaker & Leatherette
Cabinet

£47/10/-

Specially Realigned Calibrated
and Crystal Phased.

£52/10/0

NEW

INDICATOR UNITS

For that C.R.O. 10 valve 7.EF50.
1.879 1.EB34 1.5BPI

£8/10/-

NEW

V.H.F. WAVEMETERS

3 Valves, 0-1 M. A. Meter
Slow-motion dial

INCLUDING

CIRCUIT **£5/17/6**

160-220 M.C.S. readily

convert to 144 M.C.S.

NIGHT LIGHT

TRANSFORMERS

Operates Panel Lamp for Nursery,
Sickroom, etc.,

6d. per month for power.

5/- ea.

GENEMOTORS

Input	Output	
24V 250V	100MA	£1 0 0
24V 550V	375MA	2 0 0
24V 300V	250MA	1 0 0
24V 250V	60MA	1 5 0
12V 270V	100MA	3 15 0
12V 500V	350MA	8 10 0
12V 1200V	200MA	6 10 0
6V 500V	150MA	6 10 0




★ ★ ★ ★ ★ ★ ★ ★ ★ ★
RADIO

PHONE
LA 3845

136 VICTORIA RD. MARRICKVILLE, SYDNEY, N-S-W

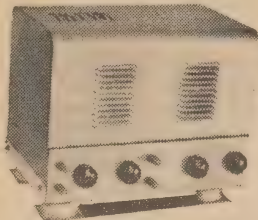
**EVENINGS and WEEKENDS: "KALUA", COLLAROY ST., COLLAROY—XW5956
 DULWICH HILL, UNDERCLIFFE, EARLWOOD TRAM AT DOOR. STOP No. 42**



AMPLIFIERS

FROM

£12/19/6

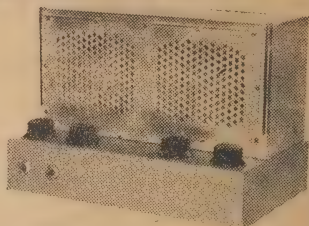

P.A. RANGE

240 V AC OPERATION

6 VALVE 10 WATT	£12/19/6
6 VALVE 25 WATT	£22/17/6
6 VALVE 40 WATT	£29/17/6

BATTERY OPERATION

5 VALVE 10 WATT 6V DC	£15/17/6
7 VALVE 12 WATT 12V DC	£17/17/6
7 VALVE 25 WATT 12V DC	£22/17/6
12V BATTERY & 240V AC OPERATION	
7 VALVE 12 WATT	£19/17/6
7 VALVE 25 WATT	£26/17/6

HIGH FIDELITY RANGE

Complete with the amazing New Jensen A.U.53 Twin Cone Speaker. Cross over network. Mounting ring and spider. Frequency response 50 to 12,000 cycle.


Separate Bass and Treble Boost

6 WATT PP TRIODE OUTPUT	£26/17/6
12 WATT PP BEAM POWER OUTPUT	£27/17/6
15 WATT PP TRIODE OUTPUT	£34/17/6
20 WATT PP BEAM POWER OUTPUT	£35/17/6

6 VALVE RADIOGRAM CHASSIS

Dual Wave. Bass and treble boost. Performance and quality. 12in Speaker, Rola, Jensen or Magnavox to your choice. PACKING, AIR FREIGHT FREE. RAIL 10/-

£21/17/6

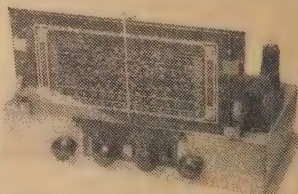


3-SPEED CHANGERS

Latest Turn-over Crystal Pick-up.

Stromberg, BSR, Monarch	£14/17/6
Collaro	£15/17/6

3 SPEED PLAYERS

Latest Model "Collaro" Turnover Crystal Pick-up	£10/17/6
---	----------

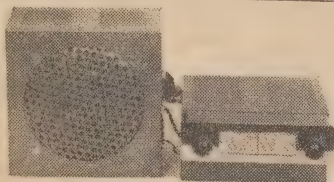

CAR RADIO

£27/17/6

Dials and Controls Tailored to suit your Car. State Make and Model.
A FULL RANGE OF CAR RADIOS TO SUIT ALL PURSES AND PURPOSES. Outstanding performance. Simple installation. Complete with aerial to suit you. Side, windscreen or cowl mounting. All installation, accessories guaranteed.

5 VALVE	£27/17/6
6 VALVE	£35/17/6
8 VALVE	£45/17/6

5 VALVE A.C. & 6-VOLT OR 12 VOLT UNIVERSAL	£32/12/6
6 VALVE UNIVERSAL	£36/17/6
and Car Radio. 5 valve	£27/17/6

Also the amazing new dry battery Portable

PALLIARD NEW 78 REV. CHANGERS. CRYSTAL PICK-UP. VARIABLE SPEED. £6/17/6

CONSTANT CURRENT SUPPLIES

Most workers are familiar with constant voltage power supplies, but many will be less familiar with power supplies deliberately designed to have exactly opposite characteristics. Of particular value in transistor circuits, the constant current supply is described in the following article reprinted from the *Aerovox Research Worker*.

IN most familiar vacuum-tube circuits, as well as straight electrical circuits, voltage is the independent variable. E-I tests of these circuits involve setting the voltage to predetermined levels and observing corresponding current values. Constant-voltage supplies, also known as "voltage-regulated supplies", are, therefore, desirable for operation of these circuits.

Modern electronics is becoming increasingly concerned with current-operated devices. Some of these are: semiconductor components, such as crystal diodes, rectifiers, transistors, thermistors, and non-linear resistors; saturable reactors; non-linear capacitors.


current variation, is now well known.

A constant-current supply on the other hand, is generally characterized by its appreciable internal resistance. Its terminal voltage is not constant, for the obvious reason that the voltage must adjust itself continuously, in order to maintain a stabilised current flow with variations of external loads.

From the foregoing descriptions and comparisons, it may be deduced that an elementary constant-current supply might consist simply of a voltage source connected in series with a limiting resistance—and this is true! However, both the voltage and the resistance must be large in most cases.

The following discussion will show why this is necessary:

Figure 1 shows an elementary constant-current system. Here, E is a

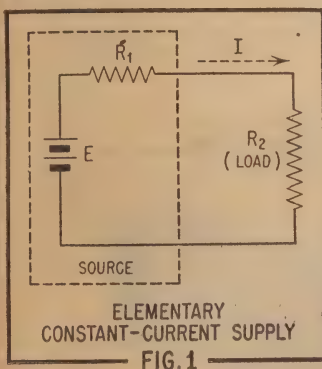


In many applications of these devices, satisfactory operation is obtained only by using constant-current power supplies. One case in particular (that of the point-contact transistor) is very important—the component can run itself to destruction when operated incorrectly from a constant-voltage supply!

Constant current in larger amounts is desirable in electroplating, solenoid operation, and instrument calibration.

Testing the E-I characteristics of current-operated components involves setting the current to predetermined levels and observing the resulting voltage drop across the component. This is the exact opposite of the technique used in checking voltage-actuated devices.

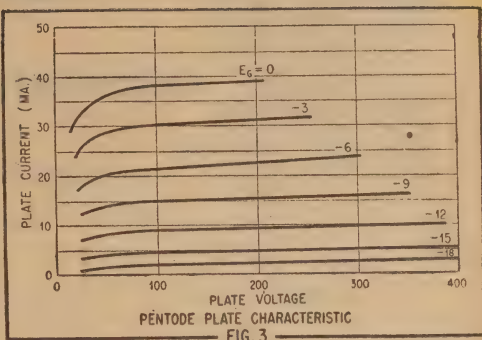A power supply must have an effective low internal resistance in order to maintain a constant voltage at its output terminals under varying load conditions. This type of supply, the operation of which is characterised by stabilised voltage over a wide range of output-



voltage source, R1 a series resistance associated with this source (internal or external), and R2 a load resistance.

The components E and R1 have been enclosed within the dashed-line box to segregate them as the constant-current source, generator, or supply, although it is understood that R1 can be connected simply to voltage generator E as an external component.

SAME CURRENT

The same magnitude of current, I, flows through both R1 and R2, since this is a simple series circuit. Now, to return to the requirement that the series resistor be high-valued, Ohm's Law shows that a large value of R1 (with respect to the load resistance, R2) will have more influence in determining the value of I than will the value of R2.


Hence, the load resistance can undergo considerable fluctuation without materially changing the value of I, when the ratio of R1/R2 is sufficiently high.

An example will clarify this point. When R1 is 10 times R2, for instance, a 10 pc change in R2 causes less than 1 pc change in the circuit current. And a 100 pc change in R2 causes only an 8 1/2 pc change in I. If R1 is 100 times R2 doubling the value of R2 produces only a 1 pc change in current.

Thus, the larger R1 is made, with respect to R2, the more constant the current will be maintained during large fluctuations of R2. However, increasing R1 to more favorable values means that voltage E must be increased proportionately, to produce the desired current value.

The required supply voltage, E equals $I \times (R1 + RL)$; where E is in volts, I in amperes, and R1 and RL in ohms. Here RL is the resistance of the current-actuated load device and is identical with R2 in Figure 1.

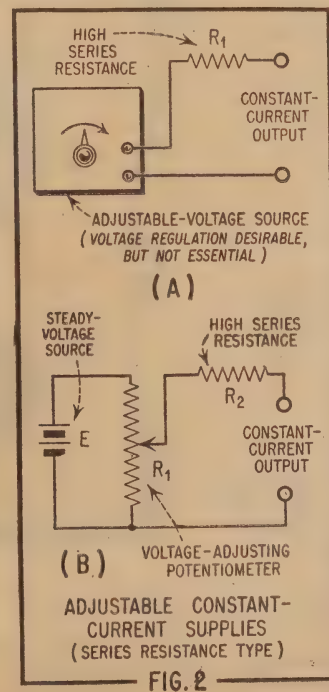A good rule of thumb often followed in laboratories is to make R1 at least 100 times R2 wherever practicable. It would, of course, be attractive to have R1 1000 times R2, but too high a limiting resistance





The **SWISS** have a word for it...

KATHODENGEGENKOPPLUNGSWICKLUNGEN

—a singularly factual one describing the design
of the output circuit of the **QUAD II** Amplifier

This circuit, nowadays sometimes called the “Ultra-Linear” arrangement is no untried novelty, having proved its worth in Acoustical Amplifiers for over ten years.

We do not propose to enter here into long technical descriptions: the compact size and high efficiency of the **QUAD II** Amplifier speak for themselves of the effectiveness of the arrangement.

And who, building a high fidelity radiogram, does not appreciate compactness and neatness of design in the components to be used? It is so easy to finish up with a “monster”!

*Have you also considered the many other
outstanding features of this model?*

RECORD EQUALISATION — The correct play-back curve at the touch of a button.

PICK-UP MATCHING — a versatile system adaptable to any pick-up.

**INDEPENDENT MICROPHONE, TAPE
AND RADIO INPUTS.**


SUPPLY SOCKETS for two radio units.

THE ACOUSTICAL FILTER SYSTEM
independent of bass and treble balance controls.


ACOUSTICAL **QUAD II** AMPLIFIER

For the closest approach to the original sound

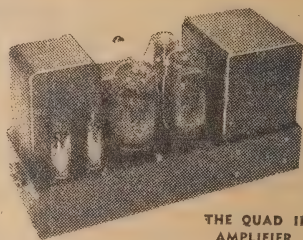Send for the **QUAD II** Folder giving full details of today's most advanced amplifier.
UNITED RADIO DISTRIBUTORS PTY. LTD., 175 Phillip St., Sydney. A British Merchandising Pty. Ltd. Agency.



THE **QUAD II**
AMPLIFIER

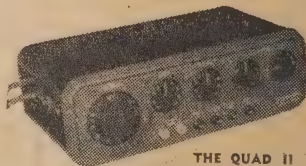

THE **QUAD II**
CONTROL UNIT



entails use of a voltage so high as to be unwieldy.

It is important to note that a certain percentage change in supply voltage E can cause the same current change that would be produced by the same total change in circuit resistance. A quite large voltage change must occur for a significant current change when R_1/R_2 is high.

Nevertheless, in applications demanding the utmost in stability, voltage E should be supplied by a voltage-regulated source.

While a DC voltage source is shown, for simplicity, in Figure 1, this circuit is not limited to direct-current applications. An AC voltage source also may be employed if an AC constant-current system is desired.

Figure 2 shows two arrangements for adjusting the constant-current output. Both are series-resistance-type units and secure their adjustable feature through control of the supply voltage.

Figure 2 (A) shows the simple addition of a high series resistance to an adjustable-output AC or DC supply. In Figure 2 (B) the power source itself is not adjustable, so a voltage-setting potentiometer, R_1 , has been added externally.

While a battery is shown for simplicity, E can also be an AC source, such as the secondary of a power transformer. It also can be a power-line-operated DC power supply.

To Determine Required Voltage

$$(1) \quad E = I(R + mR)$$

Where

E is the required voltage,

I , the desired current,

R , the resistance of the load device,

m , the desired ratio of series resistance to load resistance.

mR = Value of the series resistance.

To Determine Maximum Series Resistance for Use with a Given Voltage

$$(2) \quad R_s = (E/I) - R_L$$

Where

E is the available voltage,

I , the desired current,

R_L , the resistance of the load device,

R_s , the maximum permissible series resistance.

To Determine Current Regulation

$$(3) \quad \% \text{ Reg.} = 100 \Delta I / (I_1)$$

Where ΔI is the difference between the initial current value (I_1) and a final current value (I_2) resulting from a change in load resistance from an initial value (R_{L1}) to a final value (R_{L2})

$$I_1 = E / (R_s + R_{L1})$$

$$I_2 = E / (R_s + R_{L2})$$

Where R_s is the series limiting resistance, and R_L the load resistance.

These equations will be helpful in determining parameters required for constant-current supplies of the series-resistance type. In each case, E is in volts, I in amperes, and R in ohms.

The constant plate current characteristic of a pentode valve suggests utilisation of this characteristic to establish constant current in an external device. Adjustment of the DC control grid bias to various levels allows the selection of corresponding constant output-current values. In this way, the pentode valve can be used as a constant-current adaptor in conjunction with a DC voltage supply.

PENTODE CURVES

Figure 3 shows a typical family of Ep- I_p curves for a pentode. This family is plotted for seven values of control grid bias and are the characteristics of Type 6AK6 pentode operated at a screen potential of 180V. Note that each curve is nearly flat over a substantial portion of the plate voltage range and that the current level is reasonably constant.

A current-operated device connected into the pentode plate circuit would utilise this constant current. The resistance of the device might vary over rather wide limits, the lower limit of constant current being governed by the position of the lower bend in the curves.

Figure 4 is the basic circuit of a pentode-type current regulator. Plate and screen voltages are obtained from the DC source, E_2 . Control grid bias, adjusted by means

of potentiometer R , is obtained from DC source E_1 . Some advantage will be obtained by voltage-regulating each of these voltage supplies.

The current-actuated load device is connected to the CONSTANT-CURRENT OUTPUT terminals. Settings of potentiometer R allow selection of desired output-current values, monitored by DC milliammeter M .

Many modifications of this basic arrangement are possible. A variety



RONETTE

MICROPHONES & ACCESSORIES



TYPE B110

£3/19/7

Technical pamphlets will be mailed on request. Other types also available from

CHANDLERS PTY. LTD.

Albert & Charlotte Sts., Brisbane.
and leading wholesalers

Receivers - Transmitters - Amplifiers

**Specialised Service is now available for
YACHTSMEN, TRAWLER OWNERS, FIRE-
FIGHTERS, HAMS and OTHERS**

Disposal receivers and transmitters will be crystal controlled and modified to operate from the voltage required.

Communication receivers overhauled, aligned and modified.

Instruments repaired. Sig. Gens. calibrated.

The above service has, over the years, been instrumental in bringing into useful service much of the disposal equipment on the market.

Quotes on any work gladly given.

SPECIAL VALUE

Mullard 5-10 Amplifier, completely wired and tested including high quality output transformer **£25/10/-** plus freight.

Please quote voice coil impedance required. Superhet Broadcast Tuner for above **£6/10/-**.

OUR AMPLIFIER SECTION CAN CATER FOR YOUR REQUIREMENTS

We build amplifiers of all types using highest quality parts.


- Multiple point installations in factories, schools, hotels, offices etc., our speciality ●
- AC, vibrator or universal amplifiers up to 25 watts available from stock.
- Quotes given for any "R & H" or special project.

MIRROFONE ELECTRONICS

Phone LM1554

Phone LM1554

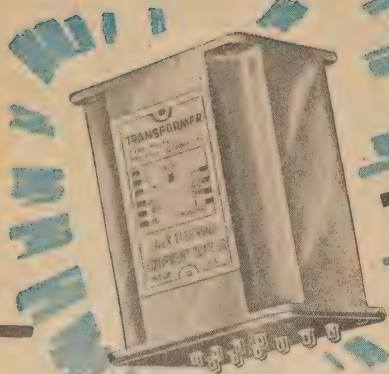403 New Canterbury Rd., Dulwich Hill, N.S.W.



A & R OUTPUT TRANSFORMERS

QUALITY

DEPENDABILITY

PERFORMANCE

APPEARANCE

MEDIUM FIDELITY

+ - 2 db 50-12,000 cps

TYPE 809 — 15 watts.
Prim.: 500 ohms.
Sec.: 15, 12.5, 8, 3.7 and 2 ohms.

TYPE 914 — 15 watts.
Prim.: 5000, 3000 ohms P.P.
Sec.: 500, 250, 166, 125, and 100 ohms.

TYPE 915 — 15 watts.
Prim.: 5000, 3000 ohms P.P.
Sec.: 15, 12.5, 8, 3.7 and 2 ohms.

TYPE 917 — 15 watts.
Prim.: 10,000, 8000 ohms P.P.
Sec.: 500, 250, 166, 125 and 100 ohms.

TYPE 918 — 15 watts.
Prim.: 10,000, 8000 ohms P.P.
Sec.: 15, 12.5, 8, 3.7 and 2 ohms.

TYPE 922 — 25 watts
Prim.: 8000 ohms P.P.
Sec.: 500, 250, 166, 125 and 100 ohms.

TYPE 891 — 35 watts.
Prim.: 6600 ohms P.P.
Sec.: 500, 250, 166, 125, 100 and 83 ohms.

TYPE 892 — 55 watts.

Prim.: 3200 ohms P.P.
Sec.: 500, 250, 166, 125, 83, 62 and 50 ohms.

SINGLE ENDED

plus — 2 db 50 — 12000 cps. **TYPE 928 — 5 watts.**
Prim.: 7000, 5000 ohms.
Sec.: 12.5, 8, 3.7 and 2 ohms.

TYPE 929 — 10 watts.

Prim.: 4000, 2500 ohms.
Sec.: 15, 12.5, 8, 3.7 and 2 ohms.

TYPE 930 — 10 watts.

Prim.: 4000, 2500 ohms.
Sec.: 500, 250 and 125 ohms.

HIGH FIDELITY

+ - 1 db 30-15,000 CPS

OUTPUT TYPE

TYPE 763 — 15 watts.
Prim.: 5000, 3000 ohms P.P.
Sec.: 15, 12.5, 8, 3.7 and 2 ohms.

TYPE 920 — 15 watts.

Prim.: 5000, 3000 ohms P.P.
Sec.: 500, 250, 166, 125 and 100 ohms.

TYPE 897 — 15 watts.

Prim.: 10,000, 8000 ohms P.P.
Sec.: 500, 250, 166, 125 and 100 ohms.

TYPE 896 — 15 watts.

Prim.: 10,000 8000 ohms P.P.
Sec.: 15, 12.5, 8, 3.7 and 2 ohms.

SPECIAL HI-FIDELITY

+ - 1 db 20-40,000 cps

OUTPUT TYPE

TYPE 870 — 6 watts.
Prim.: 10,000 ohms P.P.
Sec.: 2 or 8 ohms.
(for "Rola" 120X).

TYPE 871 — 12 watts.

Prim.: 10000 ohms P.P.
Sec.: 2 or 8 ohms.

TYPE 872 — 12 watts.

Prim.: 10,000 ohms P.P.
Sec.: 3.7 or 15 ohms.

FOR MULLARD

"5-10"

AMPLIFIER

TYPE 2505 — 12 watts.
Prim.: 6000 ohms C.T.
Sec.: As below.

Resp.: 10-50,000 cps.
TYPE 2505-8 for 2 or 8 ohms Sec.

TYPE 2505-15 for 3.7 or 15 ohms Sec.

ULTRA LINEAR

OUTPUT

TYPE 931-15: 20 watts.

Prim.: 4500 ohms P.P.
Sec.: 3.7 or 15 ohms.

Resp.: 10-60,000 cps.
Valve: EL37, KT66,

6L6, etc.

19% Screen Taps.

TYPE 931-8 20 watts.

Prim.: as 931-15
Sec.: 2 or 8 ohms.

Resp.: As 931-15.

Valves: As 931-15
931-15

19% Screen Taps

TYPE 921-15: 20 watts.

Prim.: 6600 ohms P.P.
Sec.: 3.7 or 15 ohms.

Resp.: 10-60,000 cps.

Valves: 807, KT66, etc.

19% Screen Taps.

TYPE 921-8: 20 watts.

Prim.: As for 921-15.
Sec.: 2 or 8 ohms.

Resp.: As 921-15.

Valves: As for 921-15.

19% Screen Taps.

TYPE 916-15: 12 watts.

Prim.: 8500 ohms P.P.
Sec.: 3.7 or 15 ohms.

Resp.: 10-50,000 cps.

Valves: 6BW6, 6V6, KT61, etc.

19% Screen Taps.

TYPE 916-8: 12 watts.

Prim.: As 916-15. Sec.: 2 or 8 ohms.

Resp.: As 916-15.

Valves: As 916-15.

19% Screen Taps.

TYPE 949: 12 watts.

Prim.: 8000 ohms P.P. Sec.: 2, 8, 12.5 and 15 ohms.

Resp.: 10-50,000 cps. Valves: 6V6, 6BW6, KT61, EL84, etc.

19% Screen Taps.

**FULL DETAILS OF
OUR COMPLETE RANGE
AVAILABLE FROM OUR
DISTRIBUTORS**

MELB. & VIC.

Homecrafts Pty., Ltd.,
J. H. Magrath & Co.
Pty. Ltd.
Radio Parts P/L
Warburton Frankl
Motor Spares Ltd.

STH. AUST.

Gerard & Goodman
Ltd.
196 Rundle St.
Adelaide

QUEENSLAND

A. E. Harrold,
123 Charlotte St.,
Brisbane.

WEST. AUST.

A. J. Wyle Pty.
Ltd.
1064 Hay St., Perth

TASMANIA

Homecrafts Pty.
Ltd.,
220 Elizabeth St.,
Hobart

N.S.W.

United Radio Dis-
tributors Pty. Ltd.
175 Phillip St., Sydney
Homecrafts Pty. Ltd.,
100 Clarence St., Syd.

A & R ELECTRONIC EQUIPMENT Pty. Ltd. MELBOURNE VIC.

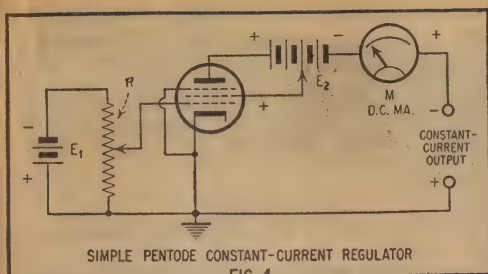


FIG. 4

of pentode-type valves is available, and several may be connected in parallel for higher current output. Ingenious practical arrangements are possible to supply grid, screen and plate voltages from a common DC supply through a voltage divider system.

While batteries are shown for simplicity in Figure 4, power-line-operated voltage supplies are entirely feasible in this application.

SIMILAR SHAPE

Since the collector E-1 curves of a junction transistor closely resemble the plate curves of a pentode valve, the transistor may be used as a regulator at low current levels in a manner similar to application of the valve. Typical maximum operating levels are: Currents up to 10 mA and power dissipations up to 150 milliwatts, depending upon the type and manufacture of transistor.

Figure 5 shows the circuit of a simple miniature constant-current DC supply employing a Type CK722 PNP junction transistor and suitable for output currents up to 4.5 mA. The polarities shown are correct for the PNP type of junction transistor. If an NPN type is used, both battery polarities and the meter polarity must be reversed.

EMITTER BIAS

The emitter bias is derived from the 1½-volt cell, E1, and is set by means of potentiometer R. The collector is biased by the 10½-volt battery, E2. The constant collector current (the level of which is determined by the setting of R) flows through milliammeter M and the external, current-actuated load device.

This small-sized unit allows any selected output current level between 0.5 and 4.5 milliamperes to be maintained with excellent regulation in output loads between 15 and 150 ohms.

Unlike the valve-type supply, the transistorised regulator can suffer from the pronounced temperature sensitivity of the transistor. However, in applications in which it is

feasible and practicable to stabilise the ambient temperature, this scheme offers many attractions for stabilising low current levels.

When the external load is removed from any of the current regulator circuits shown in this article, the full supply voltage (or very nearly this value) appears at the output terminals.

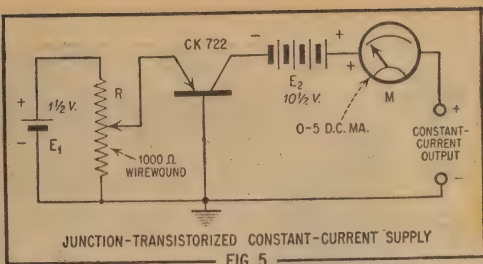


FIG. 5

The operator must keep this fact in mind, since the high terminal voltage is a probable source of damage to any high-resistance voltage-actuated device which might be connected to the constant-current terminals. It is also a source of electric shock, an important thing to remember when high supply voltages are employed.

RADIO ACCESSORIES

We specialise in Radio Parts and stock all reliable brands. We can supply: Coils, I.F.'s, Transformers, Resistors, Tubular Condensers, Valves, Wires, Flex, Meters, Testing Equipment, Radio Manuals, Irons, Toasters, Pressure Cookers, Jiff Toasting Irons, Trimmers, Padders, Gang Condensers, Motors and Pickups, Record Changers, Cabinets, Solder Irons, Solder and Electrical Accessories, 4 and 5 Valve Mantel Sets—Portable Sets, Console Radio and Radiogram, etc., Mantel, Console and Radiogram Cabinets, TECNICO Electric Lawn Mowers, Floor Polishers and Vacuum Cleaners, 2 and 3 Speed Motors and Turntables, G.P.20 Pickups and Microgroove Heads.

DAVIS RADIO CO.

Wholesale Radio Distributors

1st Floor, Wembley House, 841 George St., Sydney.

NEXT GLACIARIUM

Phone BA3917

Open Saturday Mornings

THE **BJ** ★ ARM for Perfect Tracking

Therefore

PRESERVES RECORD AND STYLUS LIFE
EXTENDS FREQUENCY RESPONSE.
MAINTAINS INNER GROOVE FIDELITY.
REDUCES TRACING DISTORTION.
ALLOWS LOWER TRACKING WEIGHT

ASK FOR FREE
COPY OF
'THE GRAMOPHONE'
TECHNICAL REPORT

Precision made, fully adjustable, £5/19/6, with template. Suitable for use with Decca, Garrard, Chancery and Acos heads. (Acos HGP39-BJ Adaptor unit, 21/-)

MARCO RECORDING STUDIO

Phone UY1812
Regd. 192 Tooronga Rd.,
Glen Iris, S.E.6, Vic.

DIS. BY ELECTRONICS AUST. PTY. LTD., 1034 HAY ST., PERTH.


Sled hits 1280 mph

A ROCKET sled had reached a record of 1280 miles an hour, according to a US Navy scientist.

The scientist, Mr. W. Drinkwater, said the sled had achieved the speed at a Mojave Desert ordnance station.

Mr. Drinkwater said the Navy hoped to achieve even higher sled speeds soon.

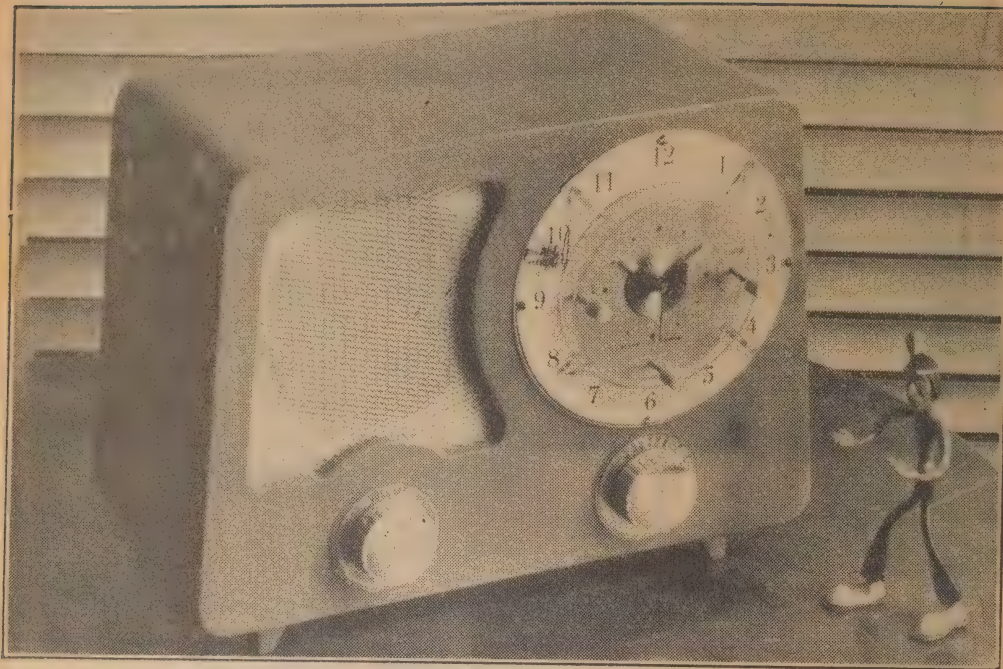The previous record for an unmanned sled was 1100 miles an hour at Edward Air Force base last year.



The finished Kloxette in a typical setting. This picture hardly does justice to the original, which was finished in bright red glossy lacquer. Other finishes will doubtless suggest themselves.

A 5-VALVE CLOCK RADIO SET

Our Kloxette, described in July this year, has already been acclaimed by suburban readers as one of our most attractive designs to date. Now we present it in a form which will appeal to readers in more remote areas and where it should prove just as popular.

THE Kloxette was originally intended as a conventional four-valve mantel set with the added feature of one of the now-popular in-built clock mechanisms, specially designed for such applications.

The idea behind these mechanisms, apart from telling the time, is a system of contacts which may be preset in various combinations and which are used to control the radio. As with an ordinary alarm system (which is also provided) the clock may be set to switch on the radio at any time during the following 12 hours. It may also be set to switch it off at any time within the following 60 minutes.

VERSATILE SET

Thus, as a bedside radio, it can be set to switch itself off after lulling you to sleep with soft music and also to wake you in the morning to something a little less raucous than a

jangling alarm. However, if you don't respond to such gentle treatment, the alarm will take over in about ten minutes' time.

In the kitchen it will save the housewife the bother of watching the clock for the time of her favorite mid-morning serial, interior decoration session, or whatever happens to be popular at the moment.

Truly a set for the lazy listener! When we had built the set, housed it in a cabinet of modern design,

and added some decorative touches we realised that we had produced a likely winner. So in fact it proved to be. While there was nothing special about the set proper, its combination with the clock mechanism and an attractive cabinet gave it a very high appeal.


SIMPLE CABINET

At the same time the cabinet, while unusual in shape, was not beyond the scope of the home constructor. We have heard of many that have been made from our original specifications and a couple, at least, are worthy of special mention.

One reader finished his effort in glossy black lacquer, offsetting this with a gold anodised aluminium speaker grill to match the gold finish of the clock and dial scales. The result was something of which

by Philip
Watson

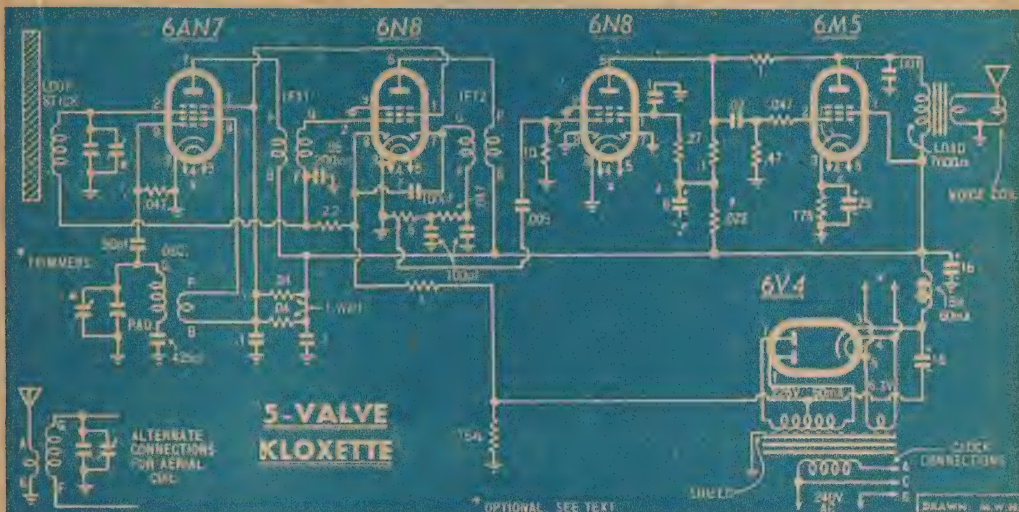CIRCUIT DIAGRAM OF 5-VALVE CLOCK RADIO SET



Apart from the valve only a handful of minor components are needed to add the extra stage to the original set. Note the HT decoupling circuit which should ensure freedom from hum under close listening conditions.

any commercial manufacturer would have been justly proud.

Another covered his cabinet with a veneer of blonde silky oak, made a first class job of it, and also finished up with a set which no one would suspect was home-made.

Doubtless many others have introduced similar original notes, though we still have a soft spot for the original, finished in bright glossy red with the speaker grill in its original color. It makes an attractive patch of color in any room.

So much, then, for the story of the set to date. But attractive and all though it may be, it is still only a four valve set and four valve sets have their limitations. They certainly do an excellent job in the city and nearby suburban areas and it is difficult to make a strong case for anything larger.

TOO SMALL

But a little farther out the lack of an audio stage begins to make itself felt and a four valve set is no longer a good proposition. To judge from our mail there are plenty of readers in these localities who would still like to build the Kloxette, but as a five valve version instead of the original. Again, a few have already built it and, while accepting its limitations, feel they would like to add an audio stage.

The latter group are in the happiest position, since they have done most of the hard work already and a handful of components and a couple of hours at the bench are all that is needed to make the conversion.

The first group would be well advised to study the original article in conjunction with this one, since it is impossible to repeat all the

text presented on that occasion. (There are a few back copies still available if your files are incomplete.)

However, for their benefit, here are a few points about the original set. It is built on a chassis measuring 11in x 6in x 2 3/8in. You may purchase a blueprint through our query service and make your own from aluminium, or purchase it ready made in steel from your usual supplier. The latter course is usually the more satisfactory unless you have a particular reason for wanting to make your own.

To obtain a logical placement for the tuning and volume controls, the tuning gang is mounted underneath the chassis, supported on two small brackets. It is driven from the tuning knob through a planetary reduction drive to give the conventional vernier control.

The type of drive we selected is fitted on the front with a bush tapped to take three small cheese head screws to hold a pointer. We made a pointer from a scrap of perspex and used it in conjunction with a fairly large white tuning knob.

PARTS LIST

- 1 cabinet
- 1 chassis 11 x 6 x 2 3/8in.
- 1 power transformer 225 V 50 Ma.
- 1 60 Ma. choke.
- 1 electric clock movement.
- 1 5in loudspeaker with 7000 ohm transformer.
- 1 tuning capacitor, 2-gang, Min. MSP, or AWA or similar.
- 1 min. oscillator coil.
- 2 min. IF transformers.
- 1 rod aerial with brackets.
- 1 min. planetary drive.
- 5 9-pin min. valve sockets.
- 1 6AN7, 2 6N8, 1 6M5, 1 6V4 valves.

RESISTORS

- 1 10 meg. 1 2.2 meg. 2 1 meg. 1 .47 meg. 1 .27 meg. 1 .1 meg. 3 .047 meg. 1 75 ohm. all 1/2 watt.

- 2 .04 meg. 1 .022 meg. 1 175 ohm.
- All 1 watt. 1 .5 meg. pot.

CAPACITORS

- 2 16 mfd 350VW electros. 1 8 mfd 350VW electro. 1 25 mfd 40VW electro.
- 3 .1 mfd 350VW paper. 1.02 mfd 350VW 1 .05 mfd 200VW. 1 .005 mfd 350VW. 1 .001 mfd 350VW.
- 1 425 pf mica (padder) 3 100 pf mica. 1 50 pf mica. 2 50 pf trimmers.


Sundries:

- Solder, nuts, bolts, hookup wire, 12in shielded hookup wire, 2 5 terminal tag strips, 6 3 terminal tag strips, 6 x 6 in extruded aluminium grille, printed clock dial volume and tuning dial, 2 knobs, mains flex and plug, 3 rubber grommets.



AC-DC MULTIMETER

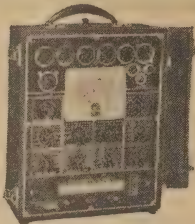Model MVA/2: This popular Multimeter is built to careful standards of accuracy and utilises 1 pc resistors throughout to ensure maximum efficiency. It covers AC-DC and output voltage ranges up to 1000 as well as D.C. current ranges up to 250 milliamperes. In addition there is a special 10 ampere D.C. range as well as four ranges of resistance up to 1 megohm.



VALVE AND CIRCUIT TESTER

Model T.S.T.: This versatile happy instrument operates from either 240 volts A.C. or a 6 volt battery. This makes it ideal for bench or portable use and it combines the functions of an up-to-date valve tester with a wide range circuit tester covering D.C. and A.C. volts as well as output volts, condenser checks, current and resistance. Write for special bulletin.



SERVICE OSCILLATOR

Model YOA: An "on the beam" Oscillator for efficient, profit making, radio service work. Covers from 30 m.c. to 150 k.c. Can be used modulated or unmodulated. Features "Spot tuning" for fast work. Supplied with leads, dummy aerial and instruction book. Write for leaflet.




DC PORTABLE MULTIMETER

Model D.C.M.: This self-contained Multimeter is small and readily portable and is suitable for quick checking of circuits. It covers D.C. voltages up to 500 as well as D.C. current up to 250 milliamperes. Two ohms ranges are provided and it comes complete with test leads and instruction booklet.



4-INCH SQUARE METER

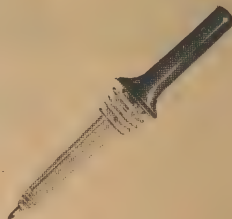Model W-4: This all polystyrene meter pioneered by University Instruments provides the ultimate in appearance and accuracy. Available as an 0-1 millimeter or any other type of standard range, it will enhance your equipment and yet will stand up to hard knocks as well as giving new beauty. This is one of the many meters in the University range.



30 KV TEST PROBE

Model B13: Although this high voltage probe is primarily designed for 30,000 volts test circuits, it offers a wide number of uses where polystyrene probes are required. It can be used for signal tracing work, high voltage work or a variety of other applications. Available with red or black handle as required.

MAIL THIS COUPON OR SEE YOUR DISTRIBUTOR

To: University Graham Instruments
Pty. Ltd., 5 North York Street,
SYDNEY.

Please send me details of _____

Name _____

Address _____



TEST PRODS


Type B1: These popular test prods come in pairs of one red and one black. Made of high quality moulded bakelite they have screw-in tips and are available at 3/5 per pair including Sales Tax.



TEST LEADS

Type B2: These popular test leads are of moulded high quality bakelite and come in a red and black pair. Standard tip jack plugs terminate one end and red and black braided wire of extra flexibility is provided. Push-on alligator clips allow the leads to be attached permanently to circuits. 10/6 per pair, plus 12% pc Sales Tax.

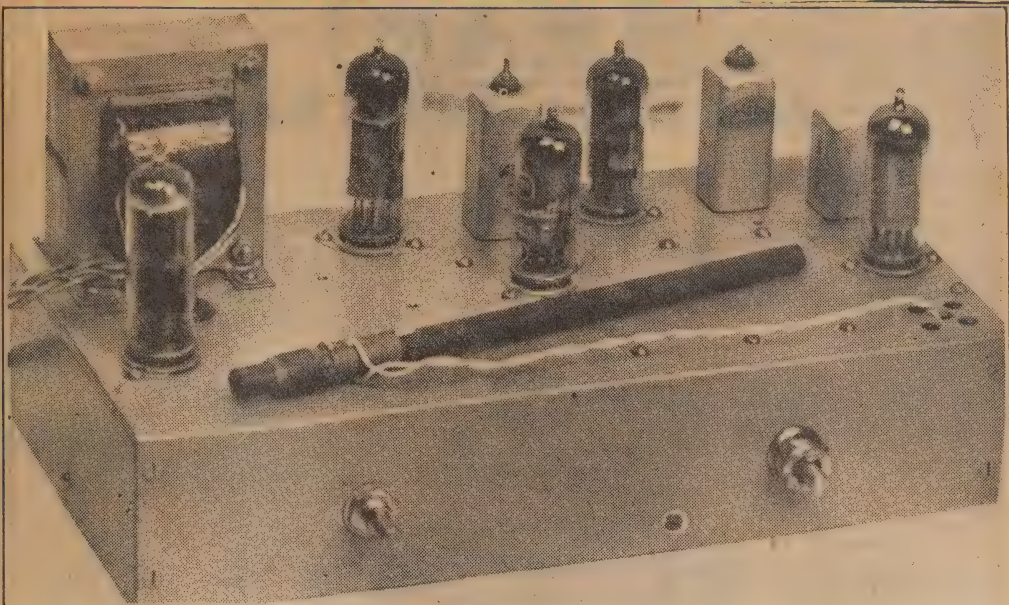TWO CHASSIS VIEWS OF THE 5-VALVE CLOCK RADIO




A front view of the completed chassis. The new valve is in the centre of the chassis, just in front of the second IF transformer. The extra socket hole was provided in the original chassis and only a few small extra holes are needed.

The dial proper is a simple type, readily available from at least one manufacturer, in the form of a transfer which is mounted on a disc of celluloid. Letters are in black

on a gold background, and scales may be obtained to suit the various states. A matching volume control scale is also available.

The conventional aerial coil is re-

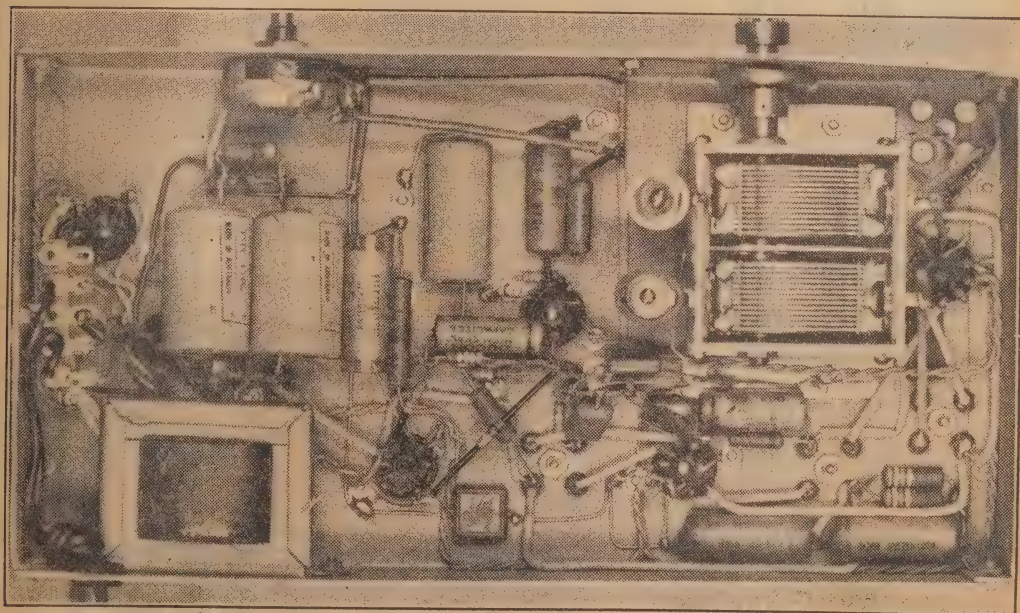placed with a ferrite rod aerial, which is very convenient where the signal level is adequate, since it avoids the usual trailing wire, which frequently does duty as an aerial.



The new socket is almost exactly central with the decoupling electrolytic to the left and above. The screen bypass is directly above with the .005 grid coupling capacitor alongside it. Note the new tag strip below and to the left.

the NEW



Pickup with Interchangeable Heads!

SPECIFICATIONS:

FREQUENCY RESPONSE: Total variation plus or minus 1 db 20,000 c/s to 40 c/s incl. transformer.

LOW FREQUENCY RESONANCE: 20 c/s plus or minus 5 c/s with the very lightweight arm.
HIGH FREQUENCY RESONANCE: on Vynil: 21,000 c/s plus or minus 2,000 c/s. 0.0025" radius on shellac, above 27,000 c/s. No grease or rubber is used, and frequency response is independent of temperature.

GENERATING SYSTEM: Dynamic (moving-coil). Coil impedance app. 6 ohms, 1,000 c/s.

PLAYING WEIGHTS: Between 2 and 3 grammes for LP. Between 5 and 6 grammes for 78. Automatically adjusted by the weight of the head.

STYLUS MATERIAL: Diamond only. Stylus size: 0.001in radius plus nothing minus 0.001in. 0.0025in radius plus or minus 0.0001in.

RECORD AND SYLUS WEAR: These are lower than on any pickup of which we have cognisance.

OUTPUT: The shielded step-up transformer delivers an output of 11mV for each cm/sec. rms recorded velocity. This means that an amplifier with a sensitivity of 40mV at 1,000 c/s will be easily loaded by the pick-up from commercial records. Recommended Load Resistance: 100,000 Ohms.

THE ARM: This is of advanced design having very low inertia. Friction is kept to a minimum by using a single pivot bearing. The arm is counterweighted and has provision for plug-in interchangeable heads. An arm rest is provided.

DIMENSIONS: From the centre of the fixing stem to the front of the pickup head, 9 1/2 in. From the centre of the fixing stem to the rear of the arm, 2 in. The height of the pick-up is adjustable and it can be used with any turntable. Distance from centre of turntable spindle to centre of mounting hole: 8 17/32 in.



The motor-board has been cut away to show the simplicity of mounting.

Supplies from
progressive
Radio Retailers
throughout the
Commonwealth.

PRICES

The arm: £5/19/8 (retail). LP head with diamond stylus: £12/10/3 (retail). 78 head with diamond stylus: £12/10/3 (retail). Mumetal-cased transformer: £3/18/8 (retail).



MADE TO YOUR ORDER!

●
TELL US WHAT
YOU REQUIRE
WE WILL DO
THE REST!
●

- ★ POWER TRANSFORMERS
- ★ ALL AUDIO AND OUTPUT TYPES
- ★ MICROPHONE TRANSFORMERS
- ★ FLASH GUN TRANSFORMERS
- ★ MODULATION TRANSFORMERS
- ★ TRIGGER TRANSFORMERS
- ★ REWINDS

SPECIAL TRANSFORMERS

19 KEMPBRIDGE AVE., BALGOWLAH—PHONE XJ4994

As a temporary measure, weak signals may be boosted by simply winding a few turns of insulated lead-in around the ferrite rod, assuming a reasonably efficient outside aerial.

The ferrite rod is supported from the inside top of the cabinet by means of two small brackets. These are normally supplied with the rod, but if you have to make your own be sure that they do not constitute a shorted turn around the rod, and which will seriously affect its efficiency. Also be careful handling the rod. They are very brittle and should be treated like glass.

Connections to the clock are shown in a separate diagram, and this should be read in conjunction with the coding letters of the power cable tag strip shown in the wiring diagram. A three-wire cable (three lengths of hook-up wire plaited) connects the clock to the tag strip and a similar cable serves for the loudspeaker. In this case the third wire is to earth the frame and voice coil. Both leads pass through grommets holes in the chassis.

The cabinet is made from* 3-8-in thick bonded plywood, and all the essential dimensions are given in the accompanying drawing. However, it should be finished by rounding the corners as shown in the photograph at the beginning of this article.

A rasp, a plane or some coarse glass or garnite paper may be used for this purpose. The exact amount of round produced will depend to some extent on taste, but, in general, we suggest the maximum that can be tolerated without weakening the corners. About $\frac{1}{16}$ in radius will be about right. Watch for nails if you are using a plane.

Dress the whole cabinet to a smooth finish with fine glass or garnite paper, make sure that all the dust is removed, and then finish with a glossy lacquer. The color may be chosen to suit your own taste or to match the color scheme of a particular room.

The clock we used was supplied without a printed scale so we made one for our own use and printed a quantity for our readers also. They are available through the query service.

This covers most of the vital points raised in the original constructional article and should bring the new reader pretty well up to date. From here on we will discuss the fitting of the additional valve.

The extra valve socket is accommodated in a spare hole which we thoughtfully provided in the original chassis for just this purpose. It is located alongside the second IF transformer in a spot which provides a clear space under the chassis for the extra bits and pieces.

We chose another 6N8 for this stage, simply ignoring the diode plates by connecting them to chassis. For bias we had the choice of a cathode resistor-capacitor combin-

[illegible]

This wiring diagram should help you locate all the parts as they were on the original. It should also help the beginner who may be puzzled by the circuit.

INTRODUCING

The New


P. R. - AMPLIFIER

MODEL "S-8"

ENTIRELY NEW IN BOTH APPEARANCE
AND PERFORMANCE — WILL GIVE YOU MORE PER £
THAN ANY OTHER AMPLIFIER

CHECK THESE FEATURES:—

Designed and constructed to give you the best possible quality in reproduction at a moderate price. It is not mass produced, but hand built like expensive test equipment — max power output 8 watts; Frequency response within 1 db 30 to 17,500 cycles. Hum and noise —70 db referred to max output; Sensitivity sufficient for all modern crystal pick-ups. Bass control at 30 cp/s plus 10 db to minus 8 db. Treble control at 10 kc/s plus 8 db to minus 8 db. Provision is made to connect a tuner, power supply having ample reserve. Controls — Volume; Bass; Treble; Radio/Gram Switch. Valves — 12AX7 Bass and Treble amplifier; 12AU7 Phase splitter and voltage amplifier. 2 type 6BV7 power pentodes in push pull. 5Y3GT rectifier. A special Bramco output transformer is used, which ensures the best fidelity.

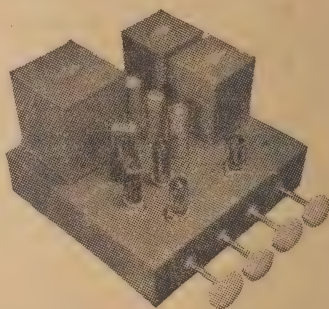

£35/-/-

AND THIS PRICE INCLUDES TWIN JENSEN SPEAKERS

FOR THE HOME CONSTRUCTOR—

M.S.P. JENSEN

TWIN SPEAKERS

Type 20928, 12in unit.
12.5 ohms voice coil.
Peak power 20 watts.
Type 20766 6in tweeter.
25 ohms voice coil.
Used in parallel with
1 mf in series with
tweeter. Bass resonance
55 cp/s Flat to
8.5 kc/s with useful
output at 12 kc/s.

**£7/10/6
PAIR**

RONETTE



The Ronette is without a doubt the best crystal pickup. Attractively finished in white plastic and chrome. A special pressure compensator and ball bearing ensures that your records receive the best attention. Output is free from serious peaks with a range from 50 to 12,000 cp/s. **£7/9/1**

COLLARO

Model 3/544, 3 Speed Record Player incorporating the Ronette Studio "O" cartridge. **£12/10/6**
Model RC/54, 3 Speed Record Changer Mixer with Studio "O" cartridge. **£22/7/6**

PHILIPS

Model AG2002 3 Speed Record Player with high quality turn-over crystal (Recommended by Mullard for use with their amplifier). **£12/-/-**

MULLARD 5-10 KIT

The Mullard 5-10 Amplifier is one of the best for the home constructor. Refer to Mullard advert in R & H Sept. for details. Complete kit including Bramco transformers. **£22**

MAGNAVOX H.F. 5

A special 5in tweeter with top frequency of 12 kc/s. Voice coil 3.7 ohms. Can be used with most 12in speakers. **52/1**


WE HAVE STOCKS OF ROLA 12-0: 12-0 Deluxe and 12-0X order now and save disappointment.

PRICE'S RADIO
5-6 ANGEL PLACE, SYDNEY

MAKE YOUR OWN CABINET FROM THESE DRAWINGS

CABINET MATERIAL
3/8" BONDED PLY


SCALE: 1/4" = 1"

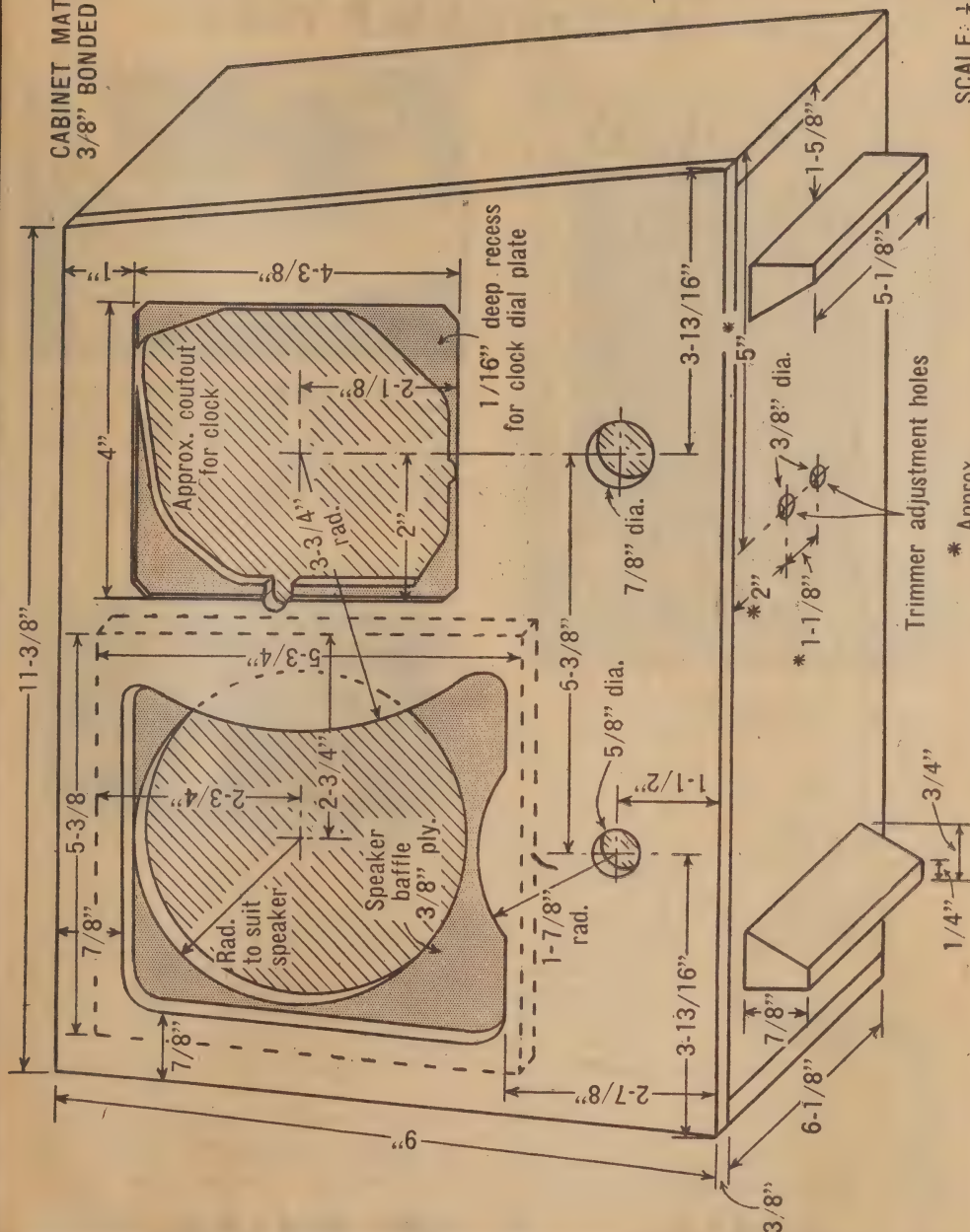

This drawing contains all the dimensions to enable you to reproduce our original cabinet. Note, however, that the corners are to be rounded after assembly. Check the clock cutout to suit your particular model.

Steane's HI-FIDELIGRAM

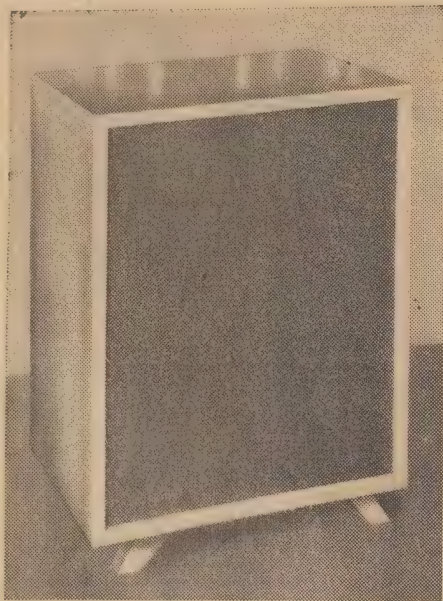for HIGH-FIDELITY RECORD REPRODUCTION
AT A REASONABLE PRICE



Speaker System

Speakers: 12in low note speaker and 6in high note speaker.

Filter: Constant resistance half section.

Crossover Frequency: 1000 c/s.

Type of cabinet: Vented Enclosure.

Impedance: 15 ohms.

Power Handling Capability: 15 watts.

Price £63/15/-


The HI-FIDELIGRAM System
consisting of the above three units

Price 150 gns.



Also Available

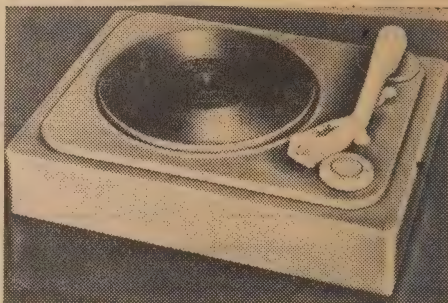Period style
Speaker System
finished in Rose-
wood (as illus-
trated) or Walnut
and record players
in matching finish.



Record Player, specially selected three-speed turntable and PU on base.


Response: Connected directly to amplifier with tone controls set for flat response — within 3db of R.I.A.A. characteristic from 30 to 10,000 c/s.

Needle tip Weight: 5/16oz.

Tone Control: 3 position high note filter on motor board.

Motor: Magnetically shielded asynchronous.

£25/10/-

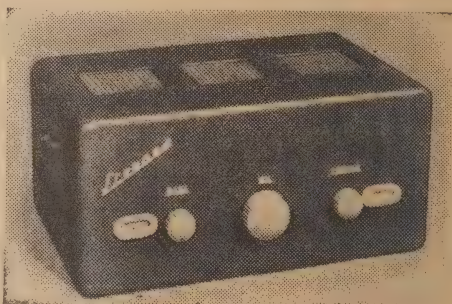

Amplifier

Response: Flat within 1db from 20 to 20,000 c/s.

Power Output: 10 watts in push pull.

Harmonic Distortion: Less than .1 pc at 8 watts.

Intermodulation Distortion: Less than 2 pc at 10 watts

using 4 to 1 ratio of 40 and 5000 c/s.

Input: 500,000 ohms at 250 mV.

Signal to Noise Ratio: 70db.

Tone Controls: Continuously variable bass and treble giving

plus or minus 12 db at 30 c/s and 15,000 c/s.

Output Impedances: 2, 8 and 15 ohms.

SPECIAL FEATURE: Visi-aid indicators enabling compensation to

suit recording characteristics.

Price 65 gns.

*From all leading Music Houses, or for
the name of your nearest supplier and
illustrated brochure, contact*

STEANES SOUND SYSTEMS PTY. LTD.,
60 Miller Street, West Melbourne, Vic.

ation or the use of a high value (10 meg.) grid resistor. We settled for the latter as being simpler and cheaper without any serious disadvantages.

We also added a simple feedback circuit, consisting of a one meg. resistor from the plate of the 6M5 to the plate of the 6N8. This helps to level out the response and take care of varying speaker load impedance, &c.

RF FILTER

Due to the higher gain in the audio section we found it necessary to provide a rather more elaborate RF filter in the diode load circuit, otherwise there was a chance that RF would find its way through the audio system and cause instability when the gain was fully advanced. As an additional precaution against this, it is advisable to make quite sure that the speaker voice coil and frame are both earthed to the main chassis.

In place of the simple 250 pf by-pass at the hot end of the diode load, which was adequate when no audio stage was used, we now have a .047 meg. decoupling resistor with a 100 pf capacitor at each end.

As a natural precaution against hum and low frequency instability, we decoupled the HT supply for both plate and screen, using a .022 meg. resistor and an 8 mfd. electrolytic.

This may be looked upon as something of a refinement, but, we think, a very desirable one. Admittedly, it is seldom employed in similar commercial sets, even where the mains filter system is by no means as generous as ours. Since the public seems content to tolerate the resultant hum level there may be some doubt as to the value of this additional precaution.

HUM PROBLEMS

It is true that the hum level encountered in such sets is usually not objectionable when the set is used in the usual way, that is in the kitchen or lounge room with the volume at a level to fill the room. The reason is simply that the hum level is then so much lower than the signal level that it is virtually inaudible.

But take one of these sets into the bedroom, put it on a bedside table, and operate it about a foot from your ear. Then you have a vastly different story. Because of the proximity of the speaker, plus a possible desire not to disturb other people, the volume will be turned well down. But the hum, being injected into the audio channel between the volume control and the speaker, remains at the same level as before. The result is a hum level which is quite high relative to the program and which can be most objectionable.


For this reason we feel that any set which is likely to be used as a bedside set (and the Kloxette most certainly is) should have the lowest possible hum level, certainly lower than is possible with many commercial sets.

Those who may feel that we are being unnecessarily fussy and are keen to save a few shillings, may omit the decoupling components. The result will still be better than many commercial sets, but not quite as good as our original.

Coming to the more practical side we have to consider the physical changes necessary to accommodate the extra components. In the original layout a four terminal tag strip was used to mount the 6M5 grid stopper, the bias resistor and capacitor, and the .02 coupling capacitor.

This is replaced with a five terminal strip mounted at right angles to the old one, and running alongside the 6M5 socket and the 2nd IF transformer. Its position can be seen in both the under chassis photograph and wiring diagram. On this is mounted the 6N8 screen and plate resistors, the 6M5 grid resistor, and the .02 coupling capacitor.

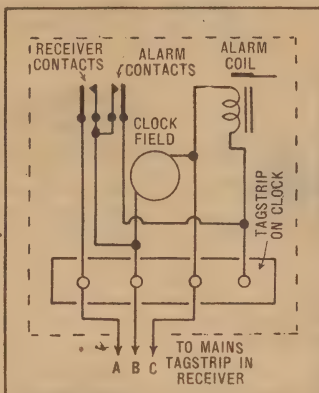It also provides terminals for the 6M5 grid stopper, the feedback resistor, and the HT decoupling resistor and capacitor. The 6M5 bias components occupy approximately the



This clock diagram should be studied in conjunction with the receiver wiring diagram, on which the corresponding connections are marked.

same position as before, but are earthed at a solder lug which also serves the negative end of the decoupling electrolytic. A new hole must be drilled in the chassis for this purpose.

A two terminal tag strip which previously supported one end of the one meg. AVC resistor and the back bias lead must be changed to a three-terminal type. The new strip serves the same purpose and in addition supports one end of the .047 meg. RF decoupling resistor, one end each of the 100 pf by-passes, and one end of the shielded cable to the volume control.


A three-terminal tag strip is also fitted near the front of the chassis approximately in line with the new socket. It serves to terminate the .005 mfd coupling capacitor and the shielded lead from the moving arm of the volume control. A solder lug under the same mounting bolt serves to earth the .1 mfd screen by-pass capacitor.

The new socket is mounted so that the gap in the pins is toward the volume control. An extra filament line is run from any convenient socket and we chose the 6AN7 as being the easiest. Pins 3, 7, 8, and 9, being the cathode, diodes, and suppressor in that order, are all earthed, along with the centre spigot.

Taking into account these points

(Continued on Page 127)

"WILLIS" Chassis Punches

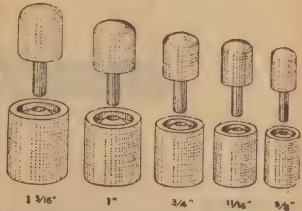

Manufactured especially for the Radio & Electrical Engineer and Constructor. Gives that clean cut professional appearance.

3-8in ..	21/-	1 1-8in ..	33/6
1 1/2in ..	22/6	1 3-16in ..	35/-
5-8in ..	22/6	1 1/2in ..	42/6
11-16in ..	23/6	1 1/4in ..	47/6
1in ..	24/6	2in ..	62/6
1 1/4in ..	31/6		

Special Sizes Made to Order
MADE OF FINEST QUALITY
TOOL STEEL
GUARANTEED 10,000 HOLES

BRITISH "Q-MAX" SCREW TYPE CHASSIS CUTTERS

5-8in ..	24/2	1 1/2in ..	38/4
3in ..	24/2	2 3-32in ..	62/6
7-8in ..	26/8	2 1/2in ..	74/2
1in ..	31/8	1in Square	47/11
1 1-8in ..	31/8		
1 1/4in ..	31/8	Spare Keys	
1 3-8in ..	35/-	All Sizes ..	1/6
1 1/2in ..	35/-		

The Ideal Chassis Hole Cutter
Where Equipment is Already Mounted

The Famous "WILLIAMSON" Amplifier Output Transformers

British "Woden" Manufacture
To Exact Specifications
as advertised on front pages of "Williamson" Amplifier Handbook

"WODEN"

A High Quality Name in British
Transformer Design
Available from Stock now

Price retail £19/18/6
(Inc. S/Tax)

TRADE ENQUIRIES INVITED

WILLIAM WILLIS

& Co. Pty. Ltd.
428 Bourke St., Melbourne, C1
Phone MU2426

NOW IS THE TIME

TO BUILD THAT CAR RADIO OR PORTABLE FOR THE XMAS HOLIDAYS

FOR THE PORTABLE



Q+ LOOP STICK TYPE LA1

Out-performs all normal loop aerials. Litz wound. Mounts easily with clips supplied. Can be mounted close to chassis, batteries with little loss of performance. Only 8 in long and 3/8in diam. Retail Price 23/9.



Q+ MIDGET R.F. COIL TYPE RCI.


Only 3in. square and 1 3/8in. high. High impedance primary high Q Litz wound secondary. Iron potted and cored. Single hole mount.

RETAIL PRICE 14/2.




Q+ MIDGET OSCILLATOR COIL TYPE O1

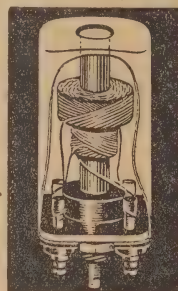Wound on grid resistor to suit 1R5 converter. Pigtail leads for direct connections. Suitable for personal portable. **RETAIL PRICE 7/7.**



Q+ MIDGET OSCILLATOR COIL TYPE O2

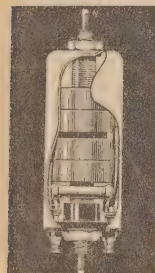To suit 1R5 converter. Only 3in square and 1 3/8in high. Litz wound primary and secondary iron cored. **RETAIL PRICE 12/8.**



Q+ MIDGET I.F. TRANSFORMERS. TYPE IF1 AND IF2.

Only 3in square and 1 7/8in high. Litz wound. Iron potted and cored. High stability ceramic condensers. Single hole mount. **RETAIL PRICE 19/10.**



Q+ CRYSTAL SET TYPE XS1. BUY ONE FOR JUNIOR FOR XMAS!

Features all cream plastic cabinet. High Q Litz wound coil with permeability tuning. Fixed germanium crystal detector. Fully enclosed. **RETAIL PRICE 49/6.**

FOR THE CAR RADIO



Q+ STANDARD CAR RADIO AERIAL COIL TYPE AC7

1 3/8in diam. and 2 1/2in high. Litz wound. Primary and secondary iron potted and cored with inbuilt top coupling condenser.

RETAIL PRICE 18/11




Q+ MIDGET CAR RADIO AERIAL COIL TYPE AC2.

Only 3in square and 1 3/8in high. High Q. Litz wound secondary iron potted and cored. Secondary tap brought out to base pin. Single hole mount. **RETAIL PRICE 14/2.**



Q+ MIDGET CAR RADIO R.F. COIL TYPE RC2.

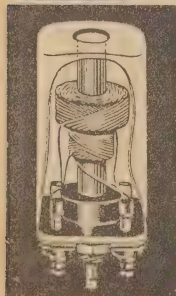Only 3in square and 1 3/8in high. High Q. Litz wound secondary iron potted and cored. Secondary tap brought out to base pin. Single hole mount. **RETAIL PRICE 14/2.**



Q+ MIDGET OSCILLATOR COIL TYPE O5

To suit 6BE6 converter, only 3in square and 1 3/8in high. Litz wound and iron cored. Single hole mount. **RETAIL PRICE 12/8.**



Q+ R.F. CHOKE TYPE RFC3.

Suitable for H.T. choke 2.5 mH at 100 Ma. only 3in and 1in. Iron cored. Single hole mount. **RETAIL PRICE 3/9.**



Q+ IGNITION HASH FILTER TYPE IC1.

Only 3in and 1in. Iron cored. Single hole mount. **RETAIL PRICE 1/11.**

ALL CAR RADIO COILS, TRANSFORMERS ETC., CAN BE SUPPLIED IN KITS WITH FULL INSTRUCTIONS

TYPE: CRK1.
Consisting of: IF1, IF2, RC2, AC2, O5, IC1

TYPE: CRK2.
IF1, IF2, AC2, O5, IC1.

TYPE CRK2 a
IF1, IF2, AC7, O5, IC1.

TYPE: CRK3.
IF1, IF2, RC2, AC7, O5, IC1.

MANUFACTURED BY

R. W. STEANE & CO. PTY. LTD., AUBURN, VIC.

PARTS FOR AUDIO GENERATOR

In response to requests from a number of our readers, who are building our new Audio Signal Generator, we give here further details about the availability of some of the special components used.

FIRSTLY there are the resistors for the oscillator frequency determining circuits. These should be preferably of the high stability cracked carbon type.

This type of resistor is very stable in its resistance and can be manufactured to close tolerances.

The resistors are being made in small quantities by at least two local manufacturers, namely Ducon Condenser, 887-895 Bourke Street, Waterloo, NSW, and I.R.C. (Wm. J. McLellan and Co. Pty. Ltd.), 126 Sussex Street, Sydney.

At the present moment the supply is not good, particularly in the higher values, but this position will no doubt improve as the demand increases.

If this type of resistor cannot be obtained, the normal carbon types could be used. As was mentioned previously it is not so much their absolute value which is important but the fact that they should be matched as nearly as possible in pairs.

A change in the absolute value will only effect the range covered by that particular pair of resistors, whereas a difference of value between two of a pair will change the feedback conditions in the oscillator. The main tuning control of the generator is a miniature two gang receiver condenser. The one we used was manufactured by Philips Electrical Industries, and should be the variety not fitted with trimmer condenser plates. This gang is small in size and uses ceramic insulation.

WHERE OBTAINABLE

Supplies of these gangs are available from the manufacturers at their head office at 69 Clarence St., Sydney, or from branch offices in other States.

Other types of gang could be used but, to our knowledge, this is the only type available locally which has ceramic insulation and is as small physically.

Some excellent overseas gangs have been available from time to time, but we felt that we should if possible use a gang which is readily available on the local market.

Some of the imported gangs are available with insulated rotors, which is of considerable assistance in screening the oscillator stage, as the gang frame can be earthed. This then acts as the screening for the active circuits.

Gangs are also available on occasions from disposals suppliers but, in general, they are somewhat larger and the chassis would need to be adapted to suit.

This is particularly the case if an ex-disposals type four or five-gang condenser is used, as has been suggested by some of our readers. The intention in this case would be to parallel each of two sections to in-

crease the total amount of capacitance.

While this does reduce the value of resistance required for a given range this is not the full story. Because of the larger dimensions of the gang the inherent strays may be higher. Also, unless the screening box is made a prohibitive size, the frame to ground capacitance will be greatly increased.

The overall result may well be inferior to that obtained with the simpler arrangement used in the original instrument.

For the range switch a ceramic type is to be preferred. These are manufactured by Manufacturers Special Products, 47 York St., Sydney, and supplies can be obtained through normal trade channels on special order.

At the risk of some change of calibration in damp weather on the lowest frequency ranges, the normal bakelite type wafer switches could be used. Care must be taken to see that these are scrupulously clean and free of any flux.

CERAMIC INSULATORS

The ceramic stand-off insulators are manufactured by the United Capacitor Co. Pty. Ltd., 433 Punchbowl Rd., Enfield, NSW. The type number is SI-2 and these are obtainable from the manufacturers.

As a possible substitute for these some small diameter polystyrene rods could be used in much the same way as was done for the gang mounting pillars. The main limitation here is probably the space into which these have to be fitted.

The Thermistor is a Standard Telephones type A5412/100 and can be obtained from them at 252-274 Botany Rd., Alexandria, NSW. At the time of writing the supply position is not good but further supplies are expected from overseas in the very near future.

The use of a Thermistor is much to be preferred to the lamp for control purposes as it is free from "hunting" effects and the output level is held to much closer limits. Also the large range of Thermistors which are obtainable enable the best operating conditions to be chosen.

The Thermistor also scores on the basis of size, as it can very readily be fitted into the shielded compartment of the oscillator.

The attenuator resistors in the original instrument were also of the high stability carbon type for the two highest values and wire wound types for the two lower values. A point of importance here is that the 1000 ohm resistor be made of the two-watt type, as there is a considerable amount of power dissipated in it.

The meter used in our instrument was a University Graham type S3/181. This is a 3in meter and is fitted with a special scale for the Audio Generator, marked in db and

millivolts. This meter is available from the manufacturers at 5 North York St., Sydney.

The cursor used for the main dial was made in our workshop from some 1/16in perspex and is affixed to a standard instrument knob.

OTHER COMPONENTS

All other components in the oscillator are standard radio components and no difficulty should be experienced in obtaining these from your usual supply house.

Several queries have also been raised as to the rise time of the Audio Generator.

In any system in which the square wave is obtained from the simple limiting and squaring of a sine wave, some initial slope of the wave front is inevitable because of the slope of the sine wave itself. However, in the circuit which we used, this effect is minimised.

A further limitation is that imposed by the frequency response of the other circuits. This becomes evident as we approach 50 Kc/s.

We checked the rise time at 50 Kc/s and found it to be of the order of 2 microseconds. To relate this to more usual terms, this is the same as the time taken for a complete cycle of a 500 Kc/s wave to take place.

AMPLASOUND CO.

HI-FIDELITY CENTRE

NEW GRAMPIAN-MULLARD 5-10 AMPLIFIER

With control unit. Compensation switch for 78 and L.P. records. Treble and Bass Controls. For Crystal Pick-ups, ... £48/6/-
LEAK TL10 AMPLIFIER & PRE-AMPLIFIER, ex-stock ... £70/7/-
GOODMANS AXIOM 150 ... £22/16/10
BARKER DUODE, 12in, ... £29/11/7
WHARFEDALE 12/CS/AL ... £41/4/8
GOODMANS 2-SPEAKER SYSTEM—
AXIETTE 101 ... £12/17/3
AUDIOM 60 ... £17/18/9
CROSSOVER—2 Chokes & Cont. £3/10/-
GARRARD STYLUS PRESSURE GAUGE
Post free anywhere in Australia ... £1/6/-
RONETTE PHONO-FIDEL PICK-UP.
With TO-284-P Cartridge ... £7/9/11

GOLDRING No. 500 PICK-UP.
V.R. Cartridge Response
20—16,000 c.p.s. ... £7/10/-
M.B.H. TYPE C. PICK-UP, 12in.
Level 20—20,000 c.p.s. one head £13/19/-
M.B.H. SAPPHIRE STYLUS, five for £15/-
COLLARO 3-SPEED RECORD PLAYER.
With Ronette Cartridge ... £11/10/-
THORENS CB33NS RECORD PLAYER £38/15/-
CONSOLE HI FIDELITY CABINETS

Attractively styled to house your record player, amplifier, tuner, etc., with storage space for over 100 records. Timbers modern honey-toned maple or walnut. Matched vented enclosures also stocked. Inspection invited. Goods freighted anywhere in Australia. Any surplus money refunded. If not in stock we will do our best to obtain it for you and advise you when it arrives.

126 Buckingham St., Sth. Sydney

Phone MX3124 After hours XJ4193

WALTHAM TRADING CO.

★ SYDNEY

96 Oxford Street, Sydney

Mail Order: P.O. Box 22, Oxford Street, Sydney.

★ MELBOURNE

319-323 Swanston St., Melbourne

Mail Order: Box 5234, G.P.O. Melbourne.

HAM SPECIALS

● TANK COILS

Wound with Silver-plated wire on Ceramic former. Contains built-in temp. compensator.

PRICE 10/-

● VERNIER DIALS

Slow motion, micro action, 6 inch 29/6
Micro Vernier 17/6
Planetary Vernier 25/-

● HEADPHONE ADAPTERS

Low to high impedance Headphone Adapters.

PRICE 2/6 each

● RECTIFIERS

Selenium Rectifiers, 300V 60 M/A 17/6 each
Copper Oxide Rectifiers, 150 x 150V 40 M/A 12/6 each
6-12 Volt Rectifiers, Approx. 30 watt 50/-

● X'MITTING CONDENSERS

Approximately 50-75 & 100 P.F. 12/6 each
Approximately 400 P.F. 15/6 each

● HOOK-UP WIRE

Fibre Glass insulated hook up wire. Each coil contains approximately 5 yards. Ideal for special jobs, 5/- coil

● AMPLIFIERS

V.H.F. Amplifiers R.F. Two stages CV.66 grounded grid amplifiers. Approximately 200 mcs. Price 39/6 ea.

● DETECTORS

Germanium Diodes 3/6
Westectors 2/6

● CATHODE RAY TUBES

1B-P.1. New in cartons. 5 inch screen. Made in Sylvania, U.S.A.
PRICE £17/6
Sockets to suit, 7/6 each.

● SOCKETS

832 Ceramic Sockets 12/6
Locktal Sockets 1/-

● PLUGS AND SOCKETS

Jones 12 Pin Plug and Sockets 8/6 each
Jones 8 Pin Plug and Sockets 5/6 each
Jones 6 Pin Miniature Plug and Sockets 7/6 each
26 Pin Cannon Plug and Socket 10/6 each
Astrograph 2 Pin Plug and Sockets 2/6 each

BC.800A HF RECEIVER

Contains 15 Valves. With modification will operate on 144 mcs Amateur band. R.F. Strip removable in two units for use as V.H.F. converter. Tunes approximately 176 Mcs. as is. Can easily be double converted to make good communication Receiver for 144 Mcs.

PRICE £7/10/-.

B.C.800B TRANSCEIVER

Brand new! Complete. Operates approximately 176 Mcs.

PRICE £17/10/-.

PHILIPS SIGNAL GENERATOR

Six bands. Frequency coverage 92.6. Kcs. to 23.85 Mcs. In good condition, complete with calibration charts.

Price £35/-/-.

TRANSCEIVER RT34/APS13

"Tail-end Charlie". Frequency Modulated. Approximately 450 Mcs. Valve line up: 9-6AG5; 2-2021; 5-6J6; 1-V3105. I.F. 30 M/C. Also contains Dynamotor; Input 27 Volt, 1.5 Amps. Output 285 Volt 60 MA

PRICE £10

TRANSCEIVER TYPE 1196

The ideal set for bushfire brigades, boat-owners etc.



A compact and very reliable Transceiver, designed to give efficient service under rugged conditions.

Dimensions: Length 18 ins., Width 11 ins., Depth 8 ins., Weight approximately 40 lbs.

Price £37/10/-

VALVES

6AC7	3/11
7193	2/11
AV11	5/-
EF50	3/6
6J7	12/6
6N6	3/11
6A6	12/6
2050 Thyratron	15/-
2051	15/-
6K6	12/8
6L7	15/-
12A6	7/11
807	17/6
6K7	17/6
1K5	2/6
CV6	2/11
1632	12/6
6V6 (Metal)	15/-
6SJ7	12/6
5Z3	12/6
6x5	12/6
6K8	12/6
6SH7	2/6
2x2	15/-
VR65	7/6
6U7	7/11
5V4	12/6
566	17/6
955	7/6
954	7/6
8004	7/6

CHECK THESE FEATURES

- Completely self-contained and ready for immediate use.
- 12 or 24 volt inbuilt power supply.
- Four fixed frequency crystal channels. Less crystals.
- Frequency coverage 4.3 to 6.7 mcs.
- 9 Valves.
- Headphones and Microphone provided.
- Brand new.

ORDER EARLY

Don't miss these Sets. As the supply is by no means unlimited and each set has to be individually air tested and adapted in our workshops, we strongly urge you to place your order early to avoid disappointment.

T.U. TUNING UNITS

Type TU.10B 10,000 to 12,500 Kcs	50/-
Type TU. 9B 7,700 to 10,000 Kcs.	50/-
Type TU.26B 200 to 500 Kcs.	50/-

WALTHAM TRADING CO.

★ MELBOURNE

393 Flinders Street

(Cnr. Queen's Bridge)

SHOOTERS . . .

**JUST LANDED—SHIPMENT OF
TELESCOPIC SIGHTS!**


The Sights offer the finest quality for the lowest cost obtainable anywhere. Being ex-Service equipment only the finest quality lenses are used.

Magnification of 4 power

Provision for altering focus.

Easily adaptable to all kinds of mountings.

Cross hairs fitted.

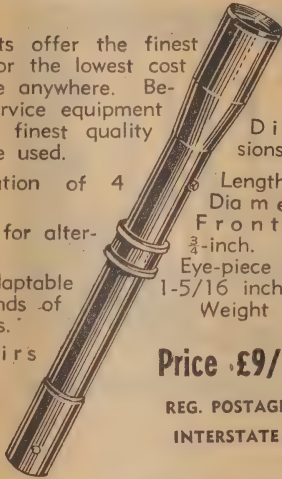

Dimensions:

Length 11 in.

Diameter

Front lens

3-inch.

Eye-piece lens

1-5/16 inch

Weight 16ozs


Price £9/17/6

REG. POSTAGE 3/6

INTERSTATE 5/-

English Angle Scopes

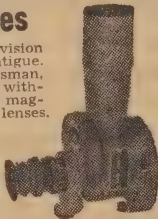Makes right angle or vertical vision easy. Cuts down eye strain and fatigue. The perfect Telescope for the marksman, giving clear sighting of the target without changing position. Six power magnification. Fitted with first-quality lenses. Ideal also as spotting telescope, astronomical sighting scope, &c. Easily mounted by means of three bolt holes in mounting plate. Brand new condition.



PRICE £5/-/-

Postage and Packing 5/-, Interstate 6/6.

ALDIS SIGNAL LAMPS

12 or 24 volt, 36 watt. The perfect light for night shooting, mooring light for boats or any purpose where a powerful concentrated beam is needed. Pistol grip, fitted with trigger switch and reflector. Angle adjuster. In carrying box, complete with sighting tube and leads.

PRICE £3/10/-

Packing and delivery to Melbourne railhead, 5/- extra.

LUCAS HEADLAMPS

Brand new in original packing boxes. 5-inch headlamp with plated reflector. Adjustable ball joint base fitting. Glossy black finish, 6, 12 or 24 volt, as required.

PRICE £2/17/6

Postage and Packing 3/-. Interstate 5/6.

★ ADELAIDE

New Branch at: 234 Rundle Street, Adelaide, S.A.

Mail Order: Box 1829 G.P.O., Adelaide, S.A.

BATTERIES

Wet Cell, 2 volt 20 amp. hours. New, in original storage state, never been charged. In bakelite case (as illustrated). Dimensions: 7ins. x 3ins. x 2ins. Weight 33lbs. Suitable for a variety of purposes—model aeroplanes, flounder spearing, spotlight shooting, etc.

PRICE 10/- each

24 volt 11 amp. hours model. Strongly built in metal case. Dimensions: 8ins. x 8ins. x 8ins. Weight 33lbs. Suitable for use in caravans, yachts, etc.

A Bargain at 39/6



TANK WHIP AERIALS

Made from strong, flexible, super-tempered, tubular steel, these Aerials are ideal for use with cars, trucks, boats, etc. In 4 ft. section they are available in either screw-in or plug-in fittings. Any number of sections can be fitted together to give the desired length.

Available in the following types:—

American screw-in type, 3 section (12 ft.), seamless 35/- per set
English slotted type, 3-section (12 ft.) 22/6 per set
English slotted type, 2-section (8 ft.) 15/- per set
Aerial Bases to fit above 7/6 each

Packing and Freight (All States)—5/- extra.


BLOWER MOTORS

24-volt A.C./D.C., as illustrated. Will operate efficiently on 12-volt supply. This unit is ideal for use as ventilating system for cars, trucks, &c. May also be used effectively as dryer for photographic work, cooling system for radio valves, &c. **PRICE 39/6.**
Postage & packing 4/6; Inater, 6/-.



BULL MOTORS

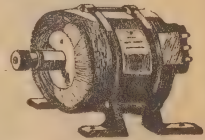A very useful 50-volt, 50-cycle Motor, which can be rewound to approximately 1-10 h.p., 230-volt A.C. It has a 3/4 inch shaft, self-aligning ball races. Ideal for handymen and hobbyists. 25/-.
Postage and Packing 3/-; Interstate 6/-.



SPECIAL!

SUMMER-WEIGHT FLYING SUITS

THE IDEAL ALL-PURPOSE OVERALL

Because of the quantities involved we are able to offer these Flying Suits at keen impossible-to-better prices.

Because of their lightness and remarkably tough wearing qualities, they are admirably suited for use as overalls for either outdoor or indoor use.

PRICE 29/6

Available in a wide range of sizes from Size 0 to Size 6.

● SPECIAL PRICES FOR QUANTITIES

Country Store Dealers, Aero Clubs, Motor Cycle Outfitters, etc. Please note, we have special prices for quantities. Write us your requirements.

IT MUST BE GOOD!

NOW EXPORTED TO ENGLAND & U.S.A.


SCOPE SOLDERING IRON Hot in 6 seconds!

Scope is the ideal Soldering Iron for all mechanical radio and electrical service, instrument and light sheet metal work. To fully appreciate its speed, its efficiency and its wide range of application you should test Scope yourself at any electrical supplier. If you do this you will understand why this new type of Soldering Iron is now being used in England and the United States.

- (1) Heats up in 6 seconds and ready for continuous use.
- (2) Compact design (10in long, weighs 3½oz), makes soldering easy in tight and awkward places.
- (3) Unique design assures that heat is applied only where and when it is required.
- (4) Solders delicate instruments as well as heavy duty work usually requiring 150 watt irons.
- (5) Light thumb pressure operates heat.
- (6) No necessity for frequent cleaning and tinning.
- (7) Replacement parts are cheap, always available and easily fitted.
- (8) Operates from A.C. Mains through National Transformer (optionally supplied), or from a car battery.
- (9) Scope easily solders jobs usually requiring intricate methods for ensuring sufficient heat transfer to work before damaging other components.
- (10) Scope is fully guaranteed.

Price 30/- (National Transformer, 47/11)

VIBROSCOPE ETCHING TOOL

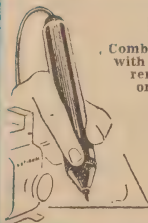

Combines mechanical vibration with electrical action to give remarkable etching results on ALL metals. Operates from Scope's Iron transformer, or AC/DC sources between 3 & 4 volts.

Price 35/-

Replacement Plunger Tip, 4/10.

SCOPE INDUSTRIAL ELECTROPLATING TOOL



... guarantees fast, efficient and reliable plating, and offers many indisputable advantages to hundreds of industrial and hobby applications. Portable, weighs 14lb, 12in x 8in x 8in. Used by TAA.

Price £23/18/-

Plus 12s 6d Sales Tax. Write for details.



Australia & Overseas Agents:

WM. J. McLELLAN & CO. PTY. LTD.

125 Sussex St (Opp. North of King St), Sydney, N.S.W. 1131

MANUFACTURED BY SCOPE LABORATORIES, MELBOURNE, VICTORIA

HYDRAULIC POWER IN INDUSTRY

(Continued from Page 19)

tion cap which, when it comes into contact with the roof, holds against it securely, while an automatic arrangement in the cap sets a limit to the pressure which can be applied in order to avoid too much stress.

When a tunnel is worked out, the prop is easily recovered by attaching a cable to the relief valve and, from a safe distance, releasing the fluid, whereupon the jack is lowered and pulled to safety.

This is a great safety device, as there is great danger in removing the conventional wooden struts holding up the roof of a mine.

One of the greatest of agricultural implements is the Ferguson tractor.

The conventional method of using a tractor is as a prime mover for drawing say a plough or harrow or other agricultural implement at the rear. These had to be very heavy in order to achieve traction.

THE FERGUSON SYSTEM

With the Ferguson system the tractor is comparatively light, and the implements are carried underneath the tractor. These add the necessary weight and are raised and lowered by precision hydraulic means. The whole scheme is a great advance on conventional methods.

An outstanding development in shipbuilding are the stabilisers which are now being fitted to modern ocean-going liners, such as the Arcadia.

These consist of streamlined fins set below the waterline of the sides of the ship. They are shaped somewhat like the ailerons of an aeroplane and act in a similar fashion.

They are really balanced streamlined rudders lying in the natural streamline on the side of the ship. They are arranged to rotate on a shaft, are balanced, and can be turned easily to suit the local conditions. The turning is done by hydraulic means and when not in use the fins are hydraulically retracted into recesses in the side of the ship.

BIG CORRECTION

It is claimed that a 14-degree roll can be reduced to one or two degrees by means of the stabilisers.

This might easily lead to higher fares because passengers may begin attending the dining room during the voyage! However, that's not my worry.


It is interesting to note that the steering of these large ships is also done by hydraulic machinery.

In aircraft the variable pitch of the propellers is accomplished by means of hydraulic machinery while the propeller is revolving. This varying of the pitch is necessary to allow for various flying conditions.

Then there are rivetting machines, shears, elevators, die-casting machines. In fact, the modern applications of hydraulics are legion. Sufficient has been said to show the importance of this great power for the aid of industry.

OFFICERS WHO FLY THE NAVY'S PLANES

ENJOY A LIFE OF TRAVEL... ADVENTURE!

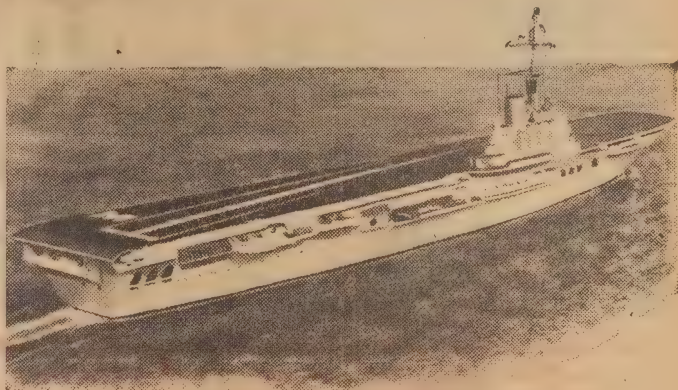

You can share this life and do a vital, well-paid job.

In the air you will command one of the Navy's new anti-submarine aircraft or all-weather fighters, operating from the new Carrier, "MELBOURNE." You will share in the teamwork as an Executive Officer aboard ship.

TO QUALIFY: You should be outstandingly fit; aged between 17 and 24 years on the 22nd October, 1955, a British subject of substantially European descent and hold an Intermediate Certificate or its equivalent with passes in at least four subjects including English and Mathematics.

Closing date for applications:—
3rd January, 1955


for entry in January, 1956.

METHOD OF ENTRY: On a Short-Service Commission, you serve for 7 years, and at any time during this period you have a good chance of qualifying for a permanent Commission with opportunities of rising to the highest ranks. Or you can leave at the end of the Short-Service Commission with a very useful gratuity.

TRAINING: Pilots and Observers (Navigators) receive their basic training in New South Wales and Victoria. On completion of training they receive their Commissions and carry out advanced operational training in jet aircraft before going to squadrons. Extra pay is received for flying duties. During service, opportunities are offered for specialist training overseas.

FLY IN THE FLEET AIR ARM

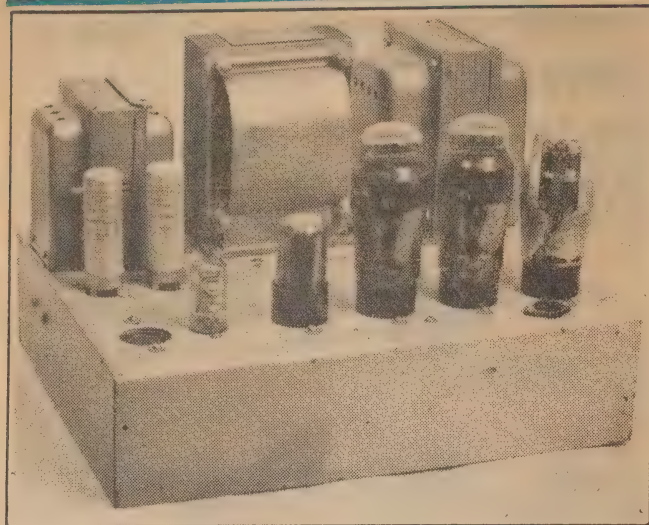NAVAL RECRUITING OFFICER, DEFENCE FORCES INFORMATION BUREAU, 77 York Street, Sydney. BX6077. COMBINED SERVICES RECRUITING CENTRE, Beach Road, Rushcutters Bay, Edgecliff. FB1261. Hours: Monday to Friday, 9 a.m. to 5.30 p.m. Saturday, 9 a.m. to 12.30 p.m. If unable to call, write to Deputy Director of Recruiting, Box XYZ, G.P.O., Sydney.



This is the 17-watt Playmaster amplifier the performance of which is discussed in this article. It more than compares with any commercial equivalent.

HOW GOOD ARE OUR AMPLIFIERS?

How good need an amplifier be to be good enough? A difficult question, for it is not yet established what is the maximum order of performance needed to cater for the most exacting type of signal input. This article outlines some of these difficulties, and attempts to provide an answer and to assess the performance of Playmaster amplifiers and some commercial types on this basis.

EVERY so often a reader writes to ask us which is the best amplifier he can buy or build. He has saved up his hard-earned cash and wants to make the best use of it.

Even more frequently we are asked whether the "Playmaster" amplifiers are as good as commercial types.

The implication is that, having been designed and built by amplifier specialists, factory-made jobs must be superior.

We don't like making comparisons between commercial amplifiers for many reasons. To be fair, we would need full test figures on them all, which is impracticable, and a full knowledge of the conditions under which the preferred amplifier would be operated, which is impossible.

FAIR CLAIMS

Most amplifiers bearing reputable names substantially live up to the claims made for them and we don't know of any which should be avoided because of outstanding faults. Their price varies according to the facilities offered, many of which have no direct bearing on the standard of performance.

It isn't so easy to avoid answering the question about the Playmasters, however, nor is there any reason

why it shouldn't be answered at least in broad terms.

We think our readers are entitled to know how they stack up against commercial amplifiers, and if they are as good or better. Most references are to the higher quality amplifiers, which at least clears the air!

It isn't necessary to go through a full and lengthy test procedure to supply such an answer. The presence or absence of serious faults can be detected by a comparatively few standard checks, and by intelligent interpretation of the results.

We can show the performance figures and curves of the 17-watt Playmaster, for instance, together with those of a high-grade commercial type, and let them speak for themselves.

But in attempting to make such a comparison it would be quite unfair not to point out the danger of over-

emphasising the significance of at least some of the performance figures.

These mean very little unless they are related to what might be considered optimum design.

PRACTICAL STANDARDS

An amplifier should not be judged by how much better it is than it needs to be, but how completely it meets the specifications known to be adequate to do its job with complete efficiency.

There must be a certain standard of amplifier performance beyond which there is no benefit to be gained. Every amplifier which at least meets this standard must be considered of equal quality as far as listening is concerned.

The trouble is to find out just what this standard is. It involves so many judgments that so far no one seems to know the answer. And yet it is essential to have some idea about it before deciding, not which amplifier is the best, but whether any of them are good enough.

A commercially made amplifier must be designed to some such specification, for the cost of manufacture must be kept within a reasonable limit. Neither the maker

nor the customer is served by adopting a standard higher than is necessary to set a reasonable selling-price.

A custom-built amplifier, on the other hand, can often show results better than those of even high-grade commercial units, but which may not, in the long run, be realised by ordinary listening.

Cost for cost, there is every reason why equipment should be made as good as it can be made, but even with an extra margin of performance, there must be some limits set by somebody in calling a halt.

In other words, it is becoming more and more important to find out just how good an amplifier should be to give us top performance.

But engineers and musicians are still far from unanimity about the answer.

AMPLIFIER FUNCTIONS

As a background to a discussion of amplifier standards, let us consider why we use amplifiers, and what we expect them to do. The reference, of course, is to amplifiers used for reproduction of speech and music primarily in the home.

We often hear it said that an amplifier should reproduce as near as possible a live performance.

by John
Moyle

But the sound of a live performance is not something which can be packaged, removed from a concert hall, and released under other conditions without substantial change.

It is not even a finite thing, for it is made up of the sound from the instruments or voices themselves together with an infinite number of reflections inseparable from the hall.

It will vary to a vast degree from one position in the hall to another.

It is affected appreciably by the size of the audiences and by many other variable factors.

For practical purposes, we must use one or more microphones with characteristics different from those of the ear, convert their output into sound via a single channel, and one or more loudspeakers, projecting the result into a room with acoustic properties largely uncontrollable. We must adjust the volume level for the listener's comfort, and sometimes for the comfort of the neighbors.

In most cases, the reproduced music sounds wonderful, but it has no direct relationship to what a listener heard in the hall.

Nor is there any reason why it should, when we can convert a necessity into a virtue.

MIKE PLACEMENT

The microphones can be placed to detect much more of the orchestra and in better over-all balance, with enough reverberation so that, when added to that provided by our lounge room, it gives a clear but lively sound to the music.

We have not duplicated reality as represented by a seat in the hall. We have presented the music in a new way so that, by preserving and even enhancing the impression of the original, it could only be approximated by the best possible listening position in space.

This is an essential difference and our thinking must start from this point.

Only once have I heard reproduced music so like the original as to give me the uneasy sensation that the performer was present in the room. I was using a vocal demonstration record. The piano accompaniment wouldn't have fooled anyone, but the voices were uncanny.

One or perhaps two instruments might have duplicated this performance. But an orchestra or a choir—never. Psychologically, apart from any other considerations, they would have been rejected.

QUALITY STANDARDS


What are the requirements for the finest reproduction?

Primarily we must receive a vivid impression that the instruments or voices we are hearing are those which made the original sound. To achieve this we look for an absence of any unpleasant distortion, and clear recognition of separate sounds either individually or in combination, and sufficient volume to create and maintain a sense of acoustic proportion.

These requirements make it possible for us to almost duplicate a live performance in some cases, but they do not depend upon it.

Our ears and our listening habits are so accommodating that we will accept an extremely wide variety

PLAYMASTER PERFORMANCE CURVE

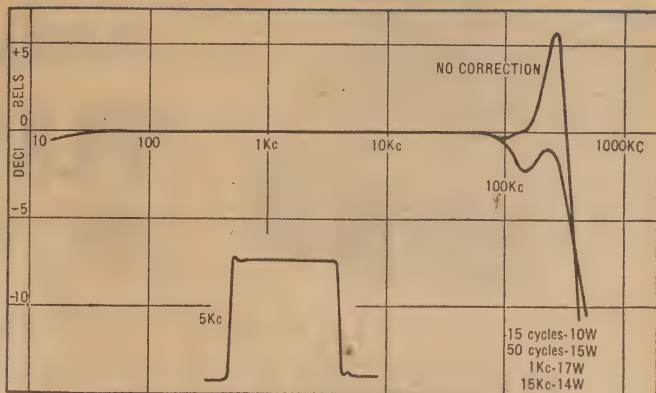

The response curve of the Playmaster is almost flat from 15 cycles to 300 Kc and its power rating is very good. Square wave response is better than any other amplifier we have tested. Even at 20 Kc it is substantially square, and there is virtually no ringing.

of reproduced standards with pleasure. But if we demand a system which does all these things with the best possible effect, I feel we have approached nearest to what we call high fidelity.

The first step in evaluating an amplifier is to establish how good it needs to be in achieving all these things, and to relate this to the performance it is practicable and economical to achieve. No amplifying system is or can be perfect—like all other engineering projects it demands compromise. It is our job to see that the amount of compromise is kept to a minimum.

Maybe we can now be more specific about technical matters.

The frequency response of the amplifier is very important, and can often point to faults or absence of faults.

It is essential to know that the amplifier has an even response over


the full range required for the reproduction of voice and music.

But its behavior beyond this point and up to several hundreds of kilocycles might show irregularities which will allow oscillation, overshoot and ringing, all of which will degrade amplifier performance in varying degrees.

Thus we will separate these two ranges for the purposes of examining their application to our problem.

The fundamental frequencies involved in speech and music run from about 35 cycles per second to 4.5 Kc or thereabouts. But as there are few pure tones in practice, the amplifier pass band should be extended to cover all the harmonic frequencies as well.

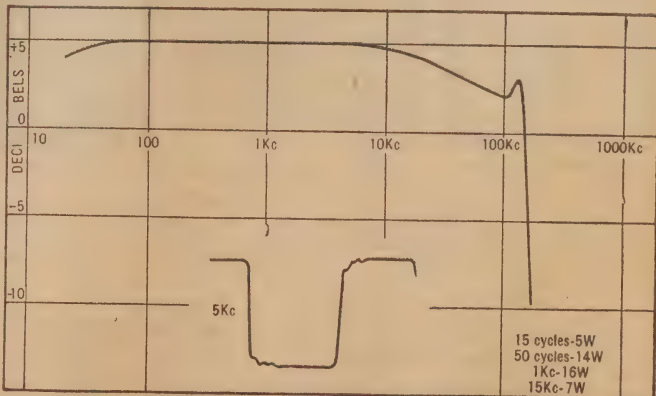Because the limit of hearing—the highest frequency at which normal-strength sounds can be detected—is generally set as being about 18 Kc., it is generally considered un-



These results were obtained from a high quality commercial amplifier of world reputation—two samples of which behaved similarly. They do not compare with the Playmaster results, although distortion is quite low. But this amplifier still sounds good. Test procedure was identical.



A FINE RANGE OF HI-FIDELITY AMPLIFIERS

"PLAYMASTER"

Designed by "Radio Television and Hobbies" these Playmasters bring you real hi-fidelity at low cost.

BUILD YOUR OWN OR OBTAIN IT COMPLETELY BUILT AND TESTED

There's a Playmaster design to suit YOUR requirements. You can build it yourself from an E.P. complete kit of parts, or we will build it for you.

- ★ 20 Watt Ultra Linear Amplifier.
- ★ 17 Watt Ultra Linear Amplifier.
- ★ 7 Watt Ultra Linear Amplifier.
- ★ 17 Watt Amplifier for Xtal P/ups.
- ★ 10 Watt Ultra Linear Amplifier.
- ★ 13 Watt Ultra Linear Amplifier for Xtal P/ups.

- ★ 8 Watt Amplifier with bass and treble Controls.
- ★ 6 tuners, including F.M.
- ★ Control Units Nos. 1 to 6.


Engraved panels now available for Control units 4 and 6.

Price £1/4/- post free


SEND FOR FREE ILLUSTRATED CATALOGUE

HOLIDAYS AHOY!

Build your own portable

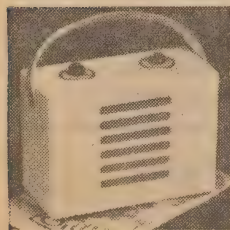

LIGHTWEIGHT PORTABLE

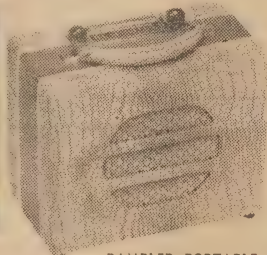

RAMBLER PORTABLE



CARRY-SET

Summer is coming—make YOUR outdoor pleasure doubly enjoyable with a portable radio. There's a model for every purpose and every pocket in the E.P. range of portable kits. All kits are to original "R.T. & Hobbies" designs. These portables, plus a full range of mantel sets, car radios, radiograms etc are fully described in the free kit set catalogue. Send for your copy today.

- LIGHTWEIGHT PORTABLE
- JUBILEE PORTABLE
- RAMBLER PORTABLE
- CARRY SET
- SENIOR PORTABLE
- etc., etc.

ELECTRONIC PARTS PTY. LTD.
THE KIT—SET SPECIALISTS

YES!

—we can supply the Mullard 5-10 amplifier kit, also recommended player unit, speaker etc.,

MULLARD HORN-TYPE ENCLOSURE

Now available in complete build it yourself timber kit or ready built. This is a craftsman made job and can be finished to suit your own furnishings.

ELECTRONIC PARTS PTY. LTD.

E.S. & A. Bank Building cnr. Broadway and City Rd., Sydney. (opp. Grace Bros.)
Phone: BA4891.

Dear Sirs,
Please mail me your free catalogue describing
X HI-FI equipment and kits.
X Portable and Radio Kits.

NAME

ADDRESS

necessary to worry about frequency response above that figure. Even 10-15 Kc is often considered high enough, on the assumption that realistic reproduction requires no more.

A frequency of 15 Kc represents the third harmonic of 5 Kc and is short of the fourth harmonic at 4 Kc. To accept a limit of 15 Kc here, although probably adequate for many sounds, may be based on the idea that we cannot hear appreciably higher than this rather upon the fact that these extreme frequencies are unimportant or non-existent.

But is it safe to work on such assumptions? Sounds as produced by cymbals, for instance, contain harmonics well into the super-sonic region, and the presence of such harmonics may well be detected by the nervous system even when the frequency is beyond the primary range of the ear.

Tests with an oscillator and a suitable radiator will soon prove this point, particularly if the effect is aggravated by using a more than normal power output.

Hearing is actually a process whereby the brain is stimulated by nervous reaction, and anything which contributes to this reaction must be considered part of a sound as we hear it.

Not all sounds involve the use of these very high frequencies, but we must consider them when setting limits for a high-fidelity system. Not all records, pick-ups and loud speakers — in fact only the very best — are likely to reach these limits. But it is now no problem to record and reproduce from records frequencies up to 20 Kc and even higher.

We will certainly improve on this as time goes on.

TOTAL RANGE

I would say, therefore, that we should aim at a perfectly flat response as high as 30 Kc to be on the safe side for a really good amplifier.

Furthermore, if other requirements of a good amplifier are to be met, the inclusion of such a range will be almost automatic.


What a pity it is that our hearing deteriorates as we get older, and can probably make best use of it while in our callow youth it is at its keenest!

On the low frequency side, there seems little reason to bother about frequencies below about 30 cycles. Even here we reach the realm of feeling, and really need to install our amplifiers in special auditoriums to make full use of such a range. We do hear of records including frequencies down to 16 cycles, but the task of reproducing these notes is very great.

You can trace out a standing wave at 20 cycles if you are able to walk in a straight line away from the loudspeaker, but you may have to move into the next room to avoid dead spots, and anti-nodes, all of which makes it rather difficult. We are assuming that you wish to hear our records sitting round the fire in a good-sized living room!

In a well-designed amplifier, the ultimate frequency response is almost entirely due to the characteristics of the output transformer, which is its most important single component.

SOME TRANSFORMER COMPARISONS

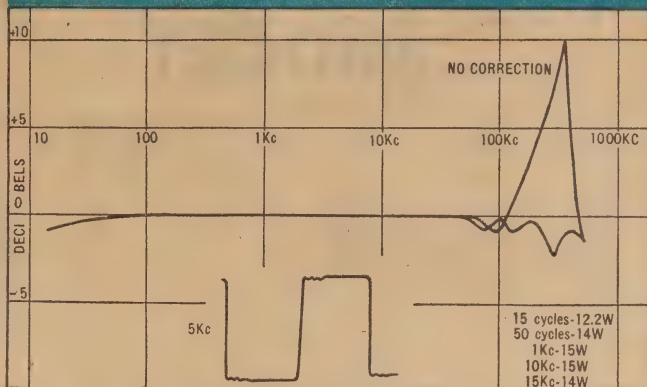

This is the curve of a different transformer fitted to the Playmaster. Its phenomenally wide range—1 db down at 500 Kc, is obtained at the expense of extra ringing from internal resonant circuits. These show up when the main peak is phased out. Note the extreme height of the peak without compensation. Its power curve is excellent but it was unstable with large amounts of feedback in our circuit. It can be classed as "too good".

This is one reason why negative feedback today is invariably taken from the secondary circuit of the output transformer, so that it is included in the feedback loop.

In essentials, negative feedback consists in feeding back energy from the output circuit 180 degrees out of phase with that appearing in the input circuit.

Any tendency for the response to vary over the frequency range is resisted by the feedback circuit.

In an ideal transformer, having an absolutely even response, feedback would be constant at all frequencies, and there would be no limit to the amount we could use.


But because there is a limit on the inductance which can be built into a transformer, the response will fall at the bass end, dropping to zero at zero frequency. It will also fall at the high frequency end, usually from about 20 Kc or so according to design, mainly due to capacitive losses between the windings and lack of coupling between them.

It is obvious, therefore, that although feedback may be reasonably constant in the centre portion of the response, where the gain is similarly constant, it will be reduced in some degree in the upper and lower regions where the amplification falls away.

If there is some sudden discontinuity in the ideal, smooth attenuation curve, it is almost certain that the feedback voltage will not preserve its initial negative relationship with the input voltage, and if the change is sufficiently acute, it may even rotate far enough to become positive.

In such a case oscillation will take place, once the circuit damping is overcome, and it will occur at a frequency related to that at which the discontinuity is found. It can thus occur at very low or very high frequencies, or both.

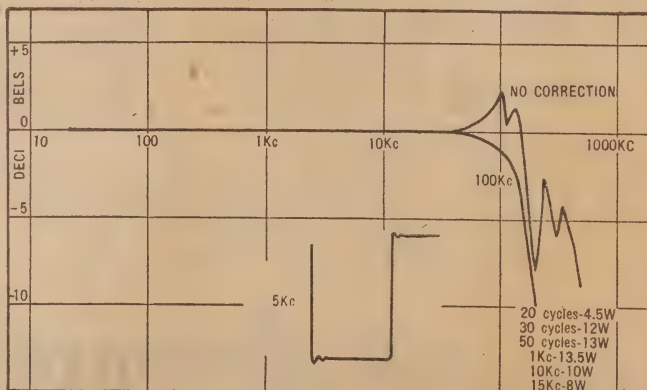In every output transformer the winding inductances and capacitances form a series of tuned circuits. The more sections in the




This curve, taken with the EL84 Playmaster, again illustrates multiple ringing which persists even after correction. No pronounced overshoot occurred. The U-L tap was only 5 per cent with this transformer. Feedback 20 db.

RELAYS MIDGET

Cat. No. Surface Mounting Type	No. of Poles	Normal Contact Position
28300U 28302U 28304U	1	open closed open and closed
28306U 28307U 28308U	2	open closed open and closed
28311U 28312U 28313U 28314U	3	3 open 2 open — 1 closed 1 open — 2 closed 3 closed
28315U 28316U 28317U 28318U 28319U	4	4 open 3 open — 1 closed 2 open — 2 closed 1 open — 3 closed 4 closed
28325U	3	3 pole Change-over

OPERATING COILS

A.C. Voltage 50/60 cycles	D.C. Voltage
6	6
12	12
18	18
24	24
32	32
110	36
220	50
440	115
550	230

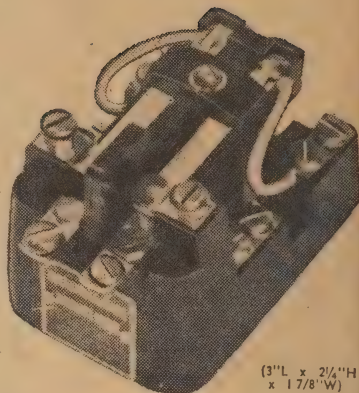

(3" L x 2 1/4" H
x 1 7/8" W)

Sheet metal case available

STOCKISTS

N.S.W. — Industrial Controls Pty. Ltd., **MA3448**
243 Castlereagh Street, Sydney.

Victoria — Ronald J. T. Payne & Co., **MU1416**
434 Collins Street, Melbourne.

WHOLESALE INQUIRIES INVITED



Volts	Each Pole amps.	2 Poles in Series amps.	H.P.
110 A.C.	10	10	1/4
220 A.C.	10	10	1/2
440 A.C.	5	5	3/4
115 D.C.	0.5	2.5	—
230 D.C.	0.3	0.5	—

Hi Fi NEWS from THE SOUND CENTRE

AMPLIFIERS:	Quad II	£108 3 0
	Armstrong A10	74 10 0
	Leak TL10	70 7 0
	Leak TL12	115 10 0
	Gramplan 5/10	48 6 0
PICKUPS:	Goldring 500	7 10 0
	B.J. Arm	5 19 0
	Acos	9 15 0
	M.B.H. All Types	
LOUDSPEAKERS:	Rola 12UX	21 0 3
	Goodmans Axiom	
	150 Mark II	22 16 10
	Barker	29 11 7
TEST RECORDS:	D.G.G. LP. Test	
	Records, each	2 4 6

LOUDSPEAKER ENCLOSURES:

Loudspeaker enclosures are available to suit Rola, Goodmans, Baker, Wharfedale, Barker and Leak loudspeakers, including the famous Wharfedale 3-speaker sand-filled corner enclosure. These cabinets are solidly constructed of 3/4" timber fully lined with suitable hair-felt and highly polished to match existing furniture. Vented enclosures are also available for Wharfedale and Goodmans 8" loudspeakers.

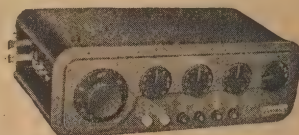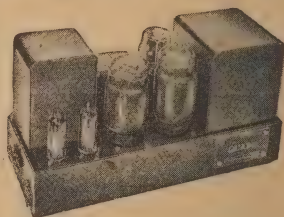

The distinguished Acoustical QUAD II
Amplifier and Control Unit £108/3/0.

THE AUDIOTORIUM

HIGH FIDELITY SOUND CENTRE

422-424 KENT STREET, SYDNEY, Phone BX6731.

transformer, the more tuned circuits will have. The main resonances formed by the total inductance of the windings and the capacitances between them and earth are too low in frequency to cause any trouble. But those formed by the capacitances of the windings and the leakage inductance between the primary and the secondary—an inductance representing the phase lag in mutual coupling—become very important in the performance of amplifiers with over-coupling. It is possible that the secondary winding inductance may also be responsible for introducing a resonant circuit.

LARGE PEAK

In a simple type transformer, in which the capacitance is comparatively large, a high-Q circuit will be found very close to the top of the audio range, and even medium-wave transformers might exhibit a strong resonance peak as low as 5 Kc.

In such an amplifier even a modest amount of feedback might be enough to cause oscillation, which can only be cured by reducing the over-all frequency response by some method that the attenuation at the peak frequency is great enough to prevent oscillation.

For instance, a phase-correction capacitor could be included to advance the phase of the feedback voltage, thus providing more feedback and reduced gain at or below the critical frequency.

Such a course will inevitably cause a high-frequency roll-off appreciably below the peak frequency and probably below our upper limit. There is grave danger, too, that large amounts of correction will send the feedback positive elsewhere in the range, unless the amount of feedback is reduced.

To make a good transformer, therefore, it is necessary to have adequate primary inductance, low inter-winding capacitance, and low leakage inductance.

These are not completely compatible. High inductance calls for many turns. Low capacitance calls for extra spacing between them, which makes it difficult to preserve an efficient coupling between primary and secondary necessary for low leakage inductance.

Standard practice is to break up the primary and secondary windings into sections, inter-connected in such a way as to reduce capacitances without prejudice to the more intimate coupling between windings.

This method generally pushes winding resonance well up into the supersonic region, and the more sections in the transformer, the more resonance peaks are likely to appear.

POSSIBLE OSCILLATION

Some are sure to combine to give one or more peaks of a high amplitude, and there is still the danger of oscillation with high degrees of feedback, even though the actual amount may have dropped to a fraction of its original value.

It is now possible, however, to "phase out" a resonance peak without causing frequency attenuation within the useful band. For instance, a transformer with a pronounced peak at 160 Kc may be so treated without detriment to frequencies below 100 Kc or even higher.

The point is, however, that without a full knowledge of the frequency response at several hundred kilocycles it may not be possible to design a stable amplifier to accept an adequate amount of feedback.

This is the key to our interest in the supersonic frequency range of the equipment.

Even with the amplifier quite stable under sine-wave tests, it may still be excited into oscillation when fed with a steep wave-front as produced by a signal rich in high order harmonics.

Even if the oscillations are sufficiently damped to limit their duration to only a portion of the operating cycle, this may be enough to spoil the transient response of the amplifier—its response to very sharp sounds.

EFFECTS OF RINGING

This is what we mean by "ringing", and there is considerable difference of opinion as to the latitude which can be allowed in respect to it.

Apart from spoiling the transient response of the amplifier, ringing absorbs power which should be spent in performing useful work, and in extreme cases it can cause the amplifier to overload at high frequencies with drastic results on quality. It is, in fact, short-term oscillation at some supersonic frequency.

The standard method of testing for ringing is to feed a square wave-form into the amplifier having a "rise-time" at least equal to that of any likely frequency met with

in practice. The "rise time" is the time taken for the steep wavefront to rise from the bottom of its trace to the top.

This time determines the maximum frequency represented by the "square" wave.

Because such a waveform will include all frequencies up to this figure, it will excite any circuit resonant at a frequency up to this limit, and each such circuit will tend to ring.

A multiple-wound transformer, which might have several resonant circuits, cannot include phase compensation for them all, but the circuit is generally treated to remove the effects of the most prominent peak, which is usually lowest in frequency. Such a transformer can be made to show an excellent frequency response up to .5 Mc or better, but is almost certain to exhibit waves on the flat top of the curve representing its various resonances.

SEVERAL PEAKS

It is extremely likely, too, that such a transformer will be running close to the stability danger line at extremely high frequencies, which, in any case, are far too high to be significant in audio work.

As some of the curves given here will show, it is possible to design transformers at reasonable cost, which cause a variation only a few db up to 200 or 300 Kc, and which are still able to show a very good waveform on a square wave test.

The square waveforms used in our tests are at 5 Kc, which is generally accepted as being the most

INVERTERS FOR EVERY PURPOSE

Glenradio Fluorescent Inverter

(for fluorescent lighting from car batteries)

NOTE THESE FEATURES:

- Low battery drain—improved lighting.
- Small size only 8" x 5" x 5".
- Completely filtered to prevent radio interference.
- Two ten watt fluorescents 12" long may also be used.
- Cold Cathode—instant start units also available.
- Correction condensers and ballast are internal.

Send for free leaflet—state your problem and obtain our advice.

STANDARD UNIT TO OPERATE ONE 20 WATT TUBE—Price 6, 12, 23 Volt input, £12/15/-.

Plus starter, fluorescent tube, sockets, channel light, already wired £1/10/-.

NOTE: Other units available for 40 watt—twin 20 watt—twin 10 watt—single 15 watt, etc.

GLENRADIO COMPANY

4 RENWICK ST., LEICHHARDT, SYDNEY. LM4545.

**430 Bourke St.,
Melbourne
Phone MU5032**

Ibbott

TOMORROW'S AUDIO TODAY

MICROPHONES. at left is illustrated actual size the new Mini-Mike by

Ibbott. Frequency range 40 cycles to 7kc, output -50db. Price £3/13/6

PICKUPS, knee action stylus gives low distortion, wide frequency response; centre groove distortion is eliminated. Output .3 volt. £12/16/6

TWEETER 2.5kc to 20kc; high efficiency and smooth response. £7/10/6

CROSSOVER NETWORK to suit above tweeter. Price £2/16/3.

Recording heads, microphone inserts.

Trade inquiries invited.

Ibbott is the only actual
manufacturer of crystal
devices in Australia.

B.S.R. TURNTABLE OWNERS

Speedy de-rumbling service is available
to owners of B.S.R. turntables. Send
in your turntable. Results guaranteed.

£2/10/- plus freight




FIDELITY with ECONOMY!

BAKER 12" DeLUXE SPEAKER



The Exponential Cone ensures

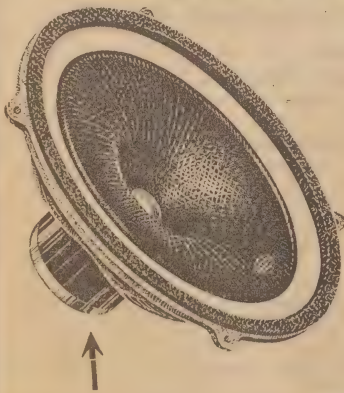**NON-DIRECTIONAL, EVEN
DISTRIBUTION OF SOUND**



ALSO NOW AVAILABLE:

The New BAKER 9" Junior De Luxe Treble Speaker

Suspension: Cloth; Cone Resonance (Exponential Cone):
55 c.p.s.; Frequency Range: 40/18,000 c.p.s.; Flux Density:
18,000 lines per sq. cm.; Max. Peak A.C. Input (Open
Baffle): 6 Watts; Voice Coil Diameter: 1".

The New BAKER 15"/CS* BASS Speaker

Suspension: Cloth; Cone Resonance (Exponential Cone):
30 c.p.s.; Frequency Range: 20/13,000 c.p.s.; Flux Density:
15,000 lines per sq. cm.; Max. Peak A.C. Input (Open
Baffle): 15 Watts; Voice Coil Diameter: 2".

Both these speakers have cloth suspension. With a Cross-
over Network they make an ideal Twin-Speaker System.

SPECIFICATIONS:

Suspension . . . Cloth
Cone Resonance (Exponential Cone)
app. 35 c.p.s.
Frequency Range . . . 20/17000 c.p.s.
Flux Density . . . 15,000 lines per
sq. cm.
Max. Peak A.C. Input (Open Baffle)
15 Watts.
Voice Coil Diameter . . . 1½".



**FOR ALL
FURTHER INFORMATION**
we suggest you contact
your Radio Retailer

N.B.: Owing to the ever-increasing
demand for these High Class
Speakers, Immediate Delivery may
not be possible at all times. A few
weeks waiting time will be well
rewarded when you enjoy the
absolutely realistic reproduction of
your BAKER speaker, but we would
advise you to place your order NOW!

useful frequency, and with an estimated rise time of about 2-3 microseconds. But do we in fact ever experience waveforms with a wavefront as steep as this?

It is extremely difficult to answer such a question. One estimate we have heard puts the maximum at no more than 7 microseconds, but even that may be too small a figure.

Obviously, the slower the rise time, the lower will be the frequencies at which ringing can be initiated, although the ringing which does take place at frequencies lower than represented by this rise time will still show up.

RISE TIME

If we assume 30 Kc to be the highest frequency in which we are interested, it will be accommodated by a square wave with a rise time of about 33 microseconds.

It would not be logical to claim this as a limit, however, for resonant circuits may still be excited by frequencies some distance from the fundamental, depending on the Q of the circuits concerned. If we allowed a 2-1 margin on this figure, a 16 microsecond rise time might be thought reasonable as a test frequency, at least for the purposes of gaining information on circuit behavior.

This type of calculation is not entirely valid, as multiple waveforms do not add in such a simple fashion, but it will do to indicate a line of thought.

Maybe we could resolve the problem by attempting to cut a square wave with a short rise time and playing it back with a low distortion pickup. This would at least relate the steepest wavefront we are likely to experience in practice with our testing methods.

So far I have not been able to persuade our local recording engineers to undertake the preparation of such a record. It would, of course, include any ringing effects inherent in the cutting head, and these might be quite appreciable. But even this information would be extremely valuable in supplying some of the answers we are seeking.

Incidentally the best pickups today give extremely low distortion figures. I have one for which .2 per cent. is claimed, and it sounds good enough to substantiate such a claim. It would almost certainly be good enough to reveal deficiencies in processing the record.

TOO STRINGENT?

It might be, therefore, that our square wave tests are too stringent to form a basis of amplifier comparison. The fact that a commercial design shows pronounced ringing and restricted frequency band as compared with a good Playmaster might mean that on instruments it is inferior, but in practice, where the waveforms encountered impose less stringent conditions, it might show up equally as well.

Nevertheless, it is inescapable that the better amplifier will be the one which will most successfully pass the stringent test, provided that its cost is equal or lower.

It would seem desirable to use a transformer with as few resonances as possible, preferably of such a nature that the main peak can be dealt with leaving a good frequency curve up about 200 Kc. This should mean that no ordinary transient is

likely to set up ringing. A smooth roll-off after the peak has been passed, with as few discontinuities as possible, will ensure that the feedback does not run positive and cause oscillation. Even the movement of a decibel in this region may be enough to cause trouble.

But it would be better to reduce this type of response, even drastically, rather than to operate the amplifier with severe ringing, or with the possibility of oscillation on sharp transient peaks.

In addition to the fairly straightforward phenomenon of ringing, which is merely the damped oscillation from a resonant circuit, there is a condition generally known as "overshoot."

Overshoot shows up as a sharp peak at the commencement of a square wave which is damped so quickly that it has scarcely any development at all as compared with the ringing phenomena.

It is most probably due to failure of the feedback voltage to take immediate effect at the commencement of a steep wave-front, due to the time lag in the amplifier — including the feedback loop.

It is hard to imagine overshoot

appearing in an amplifier without some resonant condition which permits the voltage peak to occur, and frequently when we are successful in removing appreciable ringing from an amplifier, evidence of the overshoot will remain at the commencement of the flat top.

UNBALANCED WINDINGS

Frequently it will be seen at the commencement of a vertical trace in one direction, but not in the other. In fact we have sometimes seen overshoot actually subtracted from the trace in one direction while appearing in pronounced form on the other. This presumably indicates a resonant condition being picked up in only one half of the primary due to an unbalance in electrical characteristics.

A phasing capacitor might remove the conditions from both sides of the trace, while having no effect on any additional evidence of ringing on both sides, indicating the operation of two distinct phenomena at different frequencies.

It is fairly common to observe ringing with no appreciable overshoot, but not to observe overshoot

ELECTRONIC ORGANS

(See also our advertisement on Page 111.)

We regret that we are still unable to issue a price list of components. We were completely cleaned out of stock for the home constructor, following on our July advertising, and, due to the recently applied import restrictions on "luxury" goods, we cannot obtain any more supplies from England or America. However, we are pressing-on with Australian manufactures, and will issue our catalogue as soon as we possibly can. This announcement also applies to the brochure we were going to issue in conjunction with the sale of "Simple electronic musical instruments for the constructor", by Alan Douglas.

If you are interested in this subject, please let us have your name—without any sort of obligation—for inclusion on our mailing-list.

NOTE: Anyone who has previously corresponded with us has had his name recorded already.

THE ELECTRONIC ORGAN COMPANY (AUSTRALIA)

9-11 CADOW STREET, PYMBLE, N.S.W.

(This address is that of our Registered Office, only: no business is carried on at these premises.)

CRYSTAL "ACOS" PICKUPS


The GP10, utilising the GP9 cartridge, incorporates a unique flexible assembly which renders the crystal virtually unbreakable. A novel beryllium copper spring enables needle pressure adjustment to suit user's preference. Combines purity of production with extreme reliability. Resonance-free response from 50/8000 c.p.s Output 1.5V at 1000 c.p.s.




£3/12/6

Available from leading radio houses everywhere


essential features

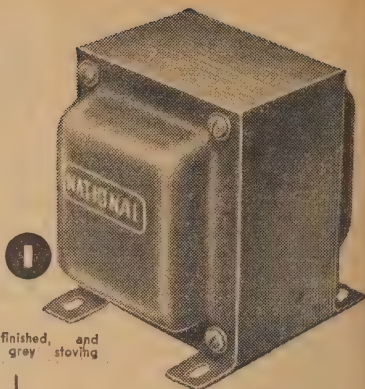

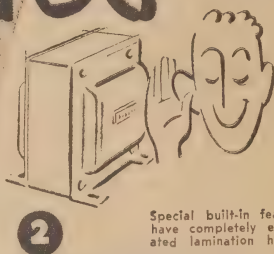
Attractively finished, and coated with grey stoving enamel.



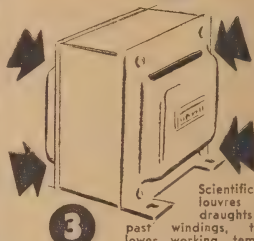
Special built-in features have completely eliminated lamination hum.



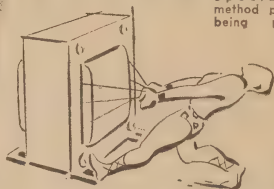
Scientifically placed louvres permit up draughts of cool air past windings, thus ensuring lower working temperature and added safety.



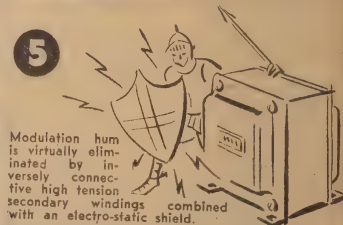Special anchoring method prevents leads being pulled out.



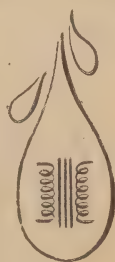Modulation hum is virtually eliminated by inversely connective high tension secondary windings combined with an electro-static shield.



Coil is impregnated with special varnish and baked to resist humidity.



Available in an unexcelled range of upright and flat types between 40 and 175m. for both radio and step down applications.

Australian and Overseas Agents,
Wm. J. McLELLAN & Co.
Pty. Ltd.

126 SUSSEX ST., SYDNEY, BX1131.
(50 yards north of King Street.)

National

POWER TRANSFORMERS

with a complete absence of ringing. The allowable amount of distortion has always been the matter of keen debate. Until recent times, the amount of distortion in a good amplifier was so much less than either the signal source or the loudspeakers that considerable latitude was in order.

Today the position is changing, but still appears possible to reach figures which might well be so low as to be lost in the overall picture.

DISTORTION

It is hard to discuss one type of distortion without mentioning others, or in many ways they are closely inter-related.

Inasmuch as it is possible to separate them, intermodulation distortion is the most objectionable. It is caused by the non-linear characteristic of some part of the amplifier, and creates a chain of sum and difference frequencies which were not present in the original input signal.

Its presence on complex waveforms is particularly severe, and with wide range equipment it is detectable in extremely small amounts.

Total Harmonic Distortion bears a relationship to intermodulation, although possibly not a constant one. At moderate proportions of full output it is often estimated as being about 25 pc of the latter.

Many listening tests have been carried out to determine the amount of distortion which can be detected. It is certainly more apparent on pure tones than on complex tones and must be considered a highly variable factor.

However, Olsen has shown that with a very wide range system about 15 pc can be detected on music and about 1 pc on speech, figures which were approximately doubled on a system with a 10 db attenuation at 4 Kc.

If these figures mean anything, very high-grade amplifier we have seen would pass muster, as most of them will show much less than 1 pc. Some will give full output with as low as .1 pc.

NOT A PROBLEM

It would seem, therefore, that provided care is taken in the selection of valve operating characteristics and grid input voltages in particular, distortion is not a major problem.

In fact, it is hard to justify very large amounts of feedback to obtain extremely low distortion unless this is possible without prejudice to good square wave response and overall stability.

It should be remembered, also, that not all the distortion represented by a total figure is objectionable.

A small admixture of second harmonic distortion, which is equivalent to adding the octave, is hardly likely to degrade the output or even to be noticed. It is the thirds and fifths which are probably most important, and these would represent only a portion of the total figure. In this respect, the drastic reduction of third harmonics by using an U-L circuit are worthy of special note.

It is probably reasonable to assume, therefore, that any amplifier which shows a total distortion figure of below 1 pc over its useful range would sound well.

It is always desirable to reduce

any kind of distortion to the lowest possible figure, but when we begin to observe it in small fractions of 1 pc, it is more profitable to ensure other requirements are met before reducing it still farther.

Power output can only be assessed in terms of proposed operating level. It is not possible to be dogmatic except to say that there should always be enough reserve to handle possible peak outputs as related to some average level. We should, however, consider a high-grade amplifier as being capable of being run at very loud volume without reaching its limit.

POWER OUTPUT

Probably the only way to relate average and peak output values would be by measurement, assuming we could agree on what was an average value.

To some extent the problem solves itself, for once we have agreed on a push-pull amplifier it is hardly worth while building anything below 10 or 12 watts, and often just as easy to go as high as 17-20 watts.

There is everything to be gained by doing so. An average output of .5 watts would represent very loud listening when fed to an efficient speaker system, and 15 watts would represent a margin of 30 times for peak accommodation. We believe this could be reached with modern recordings, and might even be exceeded. Indeed some figures put forward greatly exceed this estimate, although, on the other hand, some do not.

But it should be remembered that

if we accept an increase of 3 db as being the smallest appreciable increase in power, it requires twice a given output to achieve it.

Distortion invariably is lower the further from overload point the amplifier is operated. For this reason, a good amplifier should show as nearly the same output over the audible range. We have tested many otherwise good transformers which showed a pronounced drop in maximum output at 15 and even 10 Kc. This can only endanger the quality of peaks and transients which invariably involve the upper audible frequencies. A substantially flat power curve between 30 cycles and 15 Kc is something we should look for, but do not always receive.

LINEARITY

Linearity—input voltage plotted against output power—and speaker damping—the ratio between effective output impedance and voice coil impedance—are generally well looked after in modern amplifiers.

Invariably these use either triodes, or more recently ultra-linear circuits, and both will produce very good figures with about 20 db of feedback. Many claims are made by some designers for the use of positive feedback to obtain what is termed complete damping for loudspeakers, but not only are these claims open to some doubt, but they appear extremely risky to use if oscillation and speaker damage are to be avoided.

From this discussion it is possible to suggest some standard of


(Continued on Page 126)

Your "MULLARD 5/10" Amplifier will only be as good as its output transformer

The BRAMCO M5/10 has been approved by Mullard-Australia Pty. Ltd. with "top marks".

Primary 8000/6000; Secondary 15, 12.5 or as specified. Hermetically sealed in hammertone copper finished case with terminal connections.

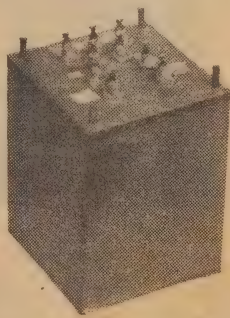If your usual supplier cannot deliver from stock, they can procure Bramco for you—they are worth waiting for!



Price—Output.. £5/15/-

A Product of Bramco Radio Components, Wallsend, N.S.W.

PRE-RECORDED TAPES ARE COMING!

Be ready to enjoy them—Make your own Tape Recorder

BUILD IT WITH ONE OF THESE PERFECT DECKS

THIS DECK KIT-SET CAN BE YOURS FOR

ALL PARTS
INCLUDED
WITH
DRAWINGS
AND
INSTRUCTIONS
TO THE
LAST
DETAIL



THE
K-TWO

£25-0-0

INC. TAX AND
POSTAGE

150 PARTS
ALL COMPLETE
AUSTRALIAN MADE

Two Motors — Two Heads — Two Speeds — TWO TRACKS

7-inch Spools. Fast Rewind. Records and Replays. Requires only hand tools to complete.

FOR FULL DETAILS SEND STAMPED AND ADDRESSED ENVELOPE.

DIRECT FROM THE MANUFACTURER

CASH OR LAY-BY

ELMEC

Phone LM4095

60 FERRIS ST.,
ANNANDALE, N.S.W.


"PAYNECO"

MIGHTY

MINIATURE

Synchronous

MOTORS

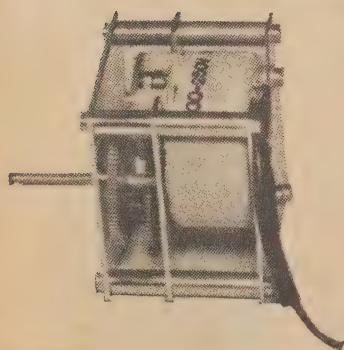

$2\frac{1}{4}$ "H x $1\frac{7}{8}$ "W x $1\frac{3}{4}$ " (App.)

Stock speeds 1, 6 and 10 RPM. Other speeds available from 60 RPM to 1 Rev. per 48 hrs.

TIMERS
BLOWERS
HOBBYIST
INDUSTRIAL
FLASHERS
WASHING
MACHINES

The most powerful instrument type synchronous motor available in Australia. 23 cm. gm. torque.

Q'LAND: S. L. Farr,
Perry House,
Elizabeth St., Brisbane. B4897.
VIC.: Ronald J. T. Payne &
Co.,
434 Collins St., Melbourne.
MU1416.
N.S.W.: Industrial Controls
Pty. Ltd.,
243 Castlereagh St., Sydney.
MA3448.
W.A.: Sales Pty. Ltd.,
1142 Hay St., Perth.
BA9781.

WHOLESALE INQUIRIES INVITED.

A COURSE IN TELEVISION

PART THREE—CATHODE—RAY PICTURE TUBES

Modern high-definition television has only become feasible because of the development of successful cathode-ray (or electron beam) camera and picture display tubes. In this article we explain the basic principles of the cathode-ray tube and how it has been developed for use in television receivers.

WE have already seen how the early mechanical television systems achieved the necessary scanning operation by passing light through an aperture in a revolving disc or a travelling film, or yet, again, by reflecting it from a series of inclined mirrors.

The original scene was scanned—analysed—by such means in the first instance, then the process reversed at the receiving end to constitute a corresponding image.

MORE LINES

We have also seen how the need for better picture definition made necessary to increase the number of lines and the picture repetition rate to a point where mechanical systems became largely impractical. Size, noise, and maintenance problems were out of all proportion to the results achieved. Engineers realised that, if progress was to continue, it was necessary

to dispense with mechanical devices altogether and resort to electronic methods, both to analyse the original scene and to reconstruct it at the receiving end.

The latter proposition presented no special difficulties, since the principles of the cathode-ray tube were known to early television workers. They were fully aware that a beam of electrons could be made to produce a spot of light by having it strike a suitable fluorescent coating at the end of a display tube.

They were also aware that the beam could be deflected by magnetic or electrostatic means and its intensity varied at the same time. These were the three basic requirements for displaying a television image, and the job of producing successful picture tubes was largely one of development from known principles.

How to analyse a picture by electronic means posed a more difficult

problem, which was nevertheless solved in fairly short order. We shall have something more to say about television camera tubes in a future issue.

Right now, the first job is to explain the theory of a simple cathode-ray tube and its development into the rather ambitious picture tubes currently used in television receivers.

Figure 17 illustrates the development of a cathode-ray tube from first principles.

Sketch (a) shows a simple diode, in which electrons from an emitting surface are attracted to a positively charged plate or anode.

ELECTRON STREAM

In sketch (b) a hole has been left in the centre of the anode, and it will be noted that some of the electrons, due to their initial velocity, pass right through the hole and cascade into the evacuated space beyond the anode.

Those having the highest velocity may actually strike the surface of the glass envelope, as indicated.

In diagram (c) an additional cylindrical electrode has been placed around the emitting surface. This tends to confine the electron flow into a beam. If this beam is then aligned with the hole in the anode, a larger proportion of the electrons emitted will flow through the aperture, ultimately striking the glass envelope beyond and dissipating their energy in heat.

However, if the inside of the glass envelope is coated with a suitable material, it will fluoresce under the impact of the electrons. In other words, the energy of the electrons striking the fluorescent coating will be changed into visible light.

COLOR, INTENSITY

The color of light so produced depends primarily on coating material, while the intensity of the light depends also on the material, and on the number and velocity of the electrons striking it. Fluorescent lights are an everyday example of the phenomenon.

That is the first part of the story. In practice, it is necessary to produce something much better than the poorly defined blob of light which would be produced by the simple electrode structure suggested in figure 17c.

A very small but intense spot of light is required, capable of substituting for the light spot, in a mechanical TV system, which passes



Figure 16: A giant television picture tube, manufactured in Britain and having a diagonal screen measurement of 27 inches. Contrast this with the 913, a midgey cathode-ray tube having a screen diameter of less than one inch and an overall size about the same as a metal 6L6.



"NOVATAPE"

RECORDERS and DECKS

STANDARD:

3 Speed — 3 Motors — 7in Reels

FULLY CAST ALUMINIUM FRAME, DIFFERENTIAL BRAKES (YOU CAN'T BREAK THE TAPE!)
COUNTER PLACE-FINDER

5-VALVE HI-FI AMPLIFIER with monitoring while recording. Most modern and attractive design.

With the unique one-knob control and differential brake system the operation of "Novatape" recorders is the most simple and foolproof.—BETTER THAN PUSH-BUTTONS AND NOTHING TO GO WRONG.

COMPARE THE QUALITY AND FEATURES AND

YOUR CHOICE MUST BE "NOVATAPE"

The "Midget" weighs only 19lb. Size 12in x 9in x 6 $\frac{1}{2}$ in complete with ZIP BAG for carrying
Foot switch attachment.

THE LOWEST-PRICED RECORDERS IN AUSTRALIA

To prove their reliability a NOVATAPE Tape Recorder was installed in the OFFICIAL PRESS CAR which covered the whole

"REDEX" Route

over 10,500 miles of rugged roads all around Australia

Read what they had to say about its performance:

Dear Sir,

We have just returned from the 10,500 miles 1955 Redex Round Australia Trial. Your tape recorder, which was installed in our De Soto, an Official Press Car, was used every day for a few hours to compile our Redex Round Australia Trial annual.

The recorder was naturally subjected to extreme conditions of dust, heat and severe vibration, but has returned in the same condition in which it started.

We used the speed of 1-7/8in. per second throughout and the tapes were air-mailed to our Sydney office for typing from a similar NOVATAPE RECORDER, etc., etc.

THUS "NOVATAPE" HAS AGAIN PROVED ITS SUPERIORITY IN DESIGN AND WORKMANSHIP

ULTRALINEAR

O/P TRANSFORMERS
for every type of valve

"NOVA" PIONEERED "ULTRALINEAR"
in Australia

UP to 12 WATT (2 impedances) £4/17/6
UP to 20 WATT (4 impedances) £5/17/6

Other types on application.

O/P Transformer for Playmasters 1 to 11 and for the

MULLARD 5-10 AMPLIFIER

TRANSFORMERS — KITSETS
COMPLETELY BUILT-UP,
SPEAKER COMBINATIONS

TRANSISTOR TRANSFORMERS
REWINDS AND ANY TYPE TRANSFORMER
OR COIL TO CUSTOMER'S SPECIFICATIONS

Call, ring or write for quotation of your needs.

BARGAINS:—

The New "AUROVOX" TAPE (Paper)
(Hi-Co) ONLY 38/6 per 1200ft.

1st Quality Plastic Tapes—EMI H60

Only 32/- per 1200ft.

MOTORS FOR CAPSTAN, take-up or rewind, £3/4/-
A FEW

"MAGNEGAPH" DECKS

AND RECORDERS LEFT

DECKS (new) only £24/10/-

RECORDERS (new) £90

HURRY WHILE THEY LAST!

Please add freight.

PHOTOFLASH

BUILD YOUR OWN 100 JOULE UNIT
SEE "RADIO & HOBBIES" APRIL & MAY, 1954

KITSETS AND COMPLETELY BUILT-UP UNITS
NEW REDUCED PRICES ON VIBRATOR TYPES.
GERMAN FLASH TUBES, 500 to 1000 volts, £3/5/-

MAGNETIC SOUND ON FILM

The long awaited ATTACHMENT TO CONVERT ANY
SILENT PROJECTOR into HOME SOUND MOVIES!
8, 9 $\frac{1}{2}$ and 16mm.

NOW AVAILABLE: The "FILMAG" attachment is
utilising the driving Mechanism of the projector and
no extra motor is required.

TERMS ON LOW DEPOSIT

For further details contact your dealer or

"NOVA"

311 SUSSEX ST., SYDNEY. BM 6138 — BM 2350.
Open Sat. Morning and Week Nights.

-----Cut out here-----

Please send without further obligation details of

11/55

NAME

ADDRESS

I enclose LARGE self-addressed envelope and 6d. in stamps.

rough a small aperture or is reflected from a critically adjusted mirror.

More effective means must be provided, in other words, to "focus" the electron stream into a fine beam, converging at the point where it strikes the fluorescent material. Provision must also be made to modulate (or vary — the intensity of) the beam at the required rate, then to deflect it in various directions and to provide a fluorescent surface (or screen) of suitable shape and dimensions.

On this screen the image will ultimately be displayed.

Some early types of cathode-ray tube relied for beam focusing on the presence in the envelope of a small quantity of inert gas.

Electrons streaming from the electrode structure would collide with atoms of gas and create slow-moving positive ions. These ions tended to concentrate near the centre of the beam, causing it to converge by reason of their attraction for the negative electrons.

NOT VERY USEFUL

While capable of operating on lower voltages than high vacuum tubes, gaseous display tubes are of practical interest in television receivers. Focusing is mediocre and prone to upset by intensity modulation of the beam. Furthermore, response to high-speed deflection is poor.

Figures 18 and 20 illustrate the essential details of practical high-vacuum cathode-ray tubes, using alternative means to focus and deflect the electron beam. Consider first figure 18, illustrating the principle of electrostatic focus and deflection.

A specially-designed cathode produces a copious supply of electrons. It is surrounded by a cylindrical element (G), which confines the movement of electrons to one direction, namely toward the fluorescent screen (S) at the large end of the tube.

This so-called "wehnelt" cylinder (E) is generally referred to as the grid, and it does resemble the grid of a normal valve in so far as it controls the flow of electrons from the cathode structure.

When the grid is at the same potential as the cathode, it allows relatively large number of electrons to flow forward but as the grid is made progressively more negative with respect to cathode, it reduces the electron supply and can actually interrupt it altogether.

By applying a fluctuating signal to the grid, the density of the electron stream can be varied (or modulated) at a rapid rate corresponding, for example, to the vision signal from a television camera system.

BRIGHTNESS

At the same time, the average density of the beam and the average light intensity of the spot it produces can be controlled by the initial bias on the intensity grid. In cathode-ray equipment this adjustment is commonly made by a so-called "Intensity" or "Brightness" control.

Electrons emerging from the cathode grid structure do so in a rather sluggish fashion.

Immediately they come under the influence of an accelerator electrode (H), which is roughly equivalent to

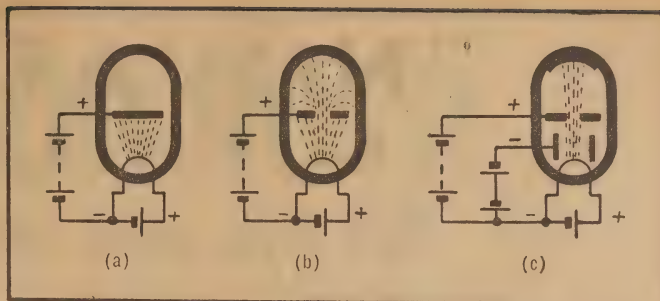


Figure 17: Illustrating the development of the cathode-ray tube from a conventional diode. Practical tubes are illustrated below.

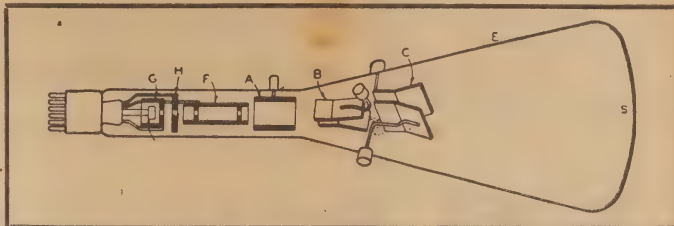


Figure 18: The arrangement of electrodes in a typical cathode-ray tube employing electrostatic focus and deflection.

the simple pierced anode of the previous illustration.

Identified generally as "anode 1", it operates at a mild positive potential. A few of the outer electrons may actually be collected by this first anode, but it is so arranged physically that most of the electrons pass through the aperture, being accelerated toward yet another electrode (F).

Known as "anode 2", this cylindrical electrode is generally operated at a higher voltage than (H), and increases further the speed of the moving electrons.

Beyond (F) there may be a third anode (A), which operates generally at a very high potential (several thousand volts). It is often connected within the tube to a graphite coating on the inner surface of the envelope and serving to supplement further the accelerating action of the whole structure.

The physical arrangement of the various anodes, and their operating potential, creates a number of electrostatic fields which operate on the electron beam in a manner reminiscent of glass lenses and light rays (see figure 19).

The "focal length" of the lenses depends on the exact potential and

position of the anodes, and it is usual to make the voltage on one anode readily variable as a "focus" control.

In figure 18, this would normally be the electrode F.

As the focus control is varied, the spot on the screen will be seen to enlarge or come to a brilliant pinpoint, which is normally the condition required.

SPOT OF LIGHT

By the time the electrons pass through A, they have been focused into a well defined beam and are moving with high velocity. When they ultimately strike screen (S) they create a bright spot of light, comparable in size to the head of a pin.

While we have drawn the analogy between an electron beam and light, there is the important difference that individual electrons tend to repel one another, since they are "like" negative charges.

Thus, despite the action of the electrostatic "lens", the electron beam tends to spread of its own accord.

This de-focusing effect becomes most marked when the density of the beam is increased in an en-


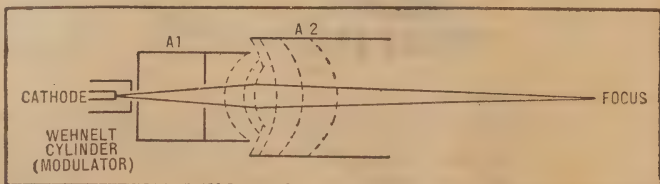


Figure 19: In an electrostatically focused C-R tube, electric fields between the adjacent edges of the circular anodes form a "lens" which acts on electrons in a manner rather similar to the action of a glass lens on light rays.

STOP NOISE IN YOUR SET

With R.C.S. aerial and line filters

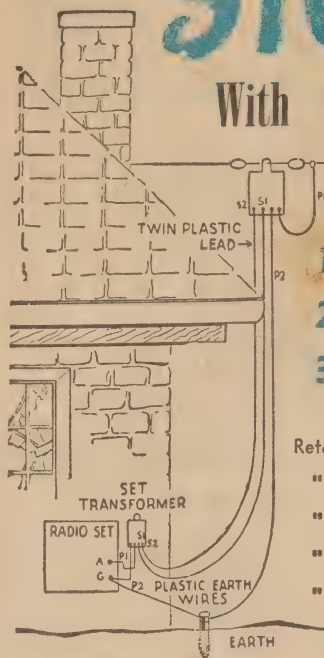


MAKE THIS SIMPLE TEST:—

1. Remove aerial from set. If the noise stops, you need an AF21C aerial filter, as the noise is coming through your aerial.
2. If the noise continues, you need an LF20 line filter as the noise is coming through your power main.
3. If any of the appliances shown below are causing the noise, then fit to it a line filter of the type shown.

Retail AF21C aerial filter	140/-
" LF20 line filter ..	37/-
" LF20C " " ..	42/-
" LF24 " "	50/-
" LF24C " "	55/-



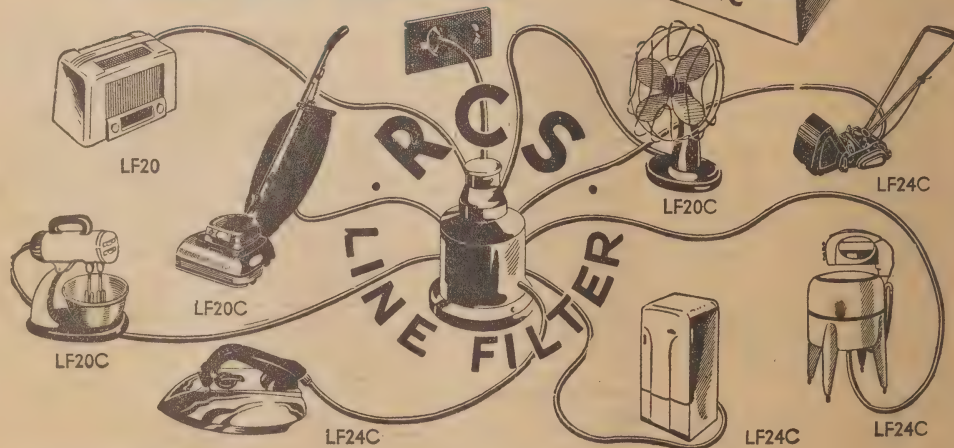CONFINE NOISE WHERE IT STARTS — WITH R.C.S. LINE FILTER



DISTRIBUTORS:—

N.S.W. Bloch & Gerber—Fox & MacGillycuddy—U.R.D.—
 John Martin — Lawrence & Hansom — Homecrafts —
 Martin de Launay — Radio Despatch — Cooke Bros. —
 W.A. Carlyle & Atkins

S.A.
 VIC.
 QLD.
 TAS.

Gerard & Goodman.
 R. E. Trickey—Homecrafts—Motor
 Spares—Radio Parts.
 B. Martin & Irvine—Chandlers.
 Homecrafts—W. G. Genders.

R. C. S. RADIO PTY. LTD.

651 FOREST ROAD,
 BEXLEY. PHONE LW 3491

avor to obtain a brighter fluorescent spot. It can be offset, however, by operating the tube with creased anode potential, thereby creasing the velocity of the flying electrons and making them less sensitive to mutual effects.

This point explains why it is necessary to use higher, and still higher operating voltages in a CR tube when a bright sharp image is required.

The term "electron gun" is commonly employed to describe the basic structure supplying the electron beam. It varies with tube type but comprises the heater, cathode, grid and at least one accelerating anode.

Although figure 18 shows three modes of specific shape, it does not allow that all such tubes are built to this exact pattern. The structure may be more simple or more complex, depending on the purpose and ideas of the designer, but the general principles remain the same.

ELECTRON GUN

The electron gun is an integral part of all cathode ray devices whether they are simple receiving tubes or more complex units intended for television cameras.

It is fortunate that the current drawn by the anodes in a CR tube is very small (in order of microamps) so that the power supply circuit does not have to handle heavy current, even though the voltages are high.

The exact figures, of course, vary with the type of tube, exactly as do the ratings for ordinary receiving valves.

The type of CR tube illustrated in figure 18 is said to employ electrostatic focus, since it depends on the voltage gradient between successive electrodes.

An alternative idea is to focus the beam by means of a magnetic field as illustrated in figure 20. In this case, the electron gun comprises simply a cathode, a "grid", a first anode and, possibly, a graphite coating on the inside of the tube walls acting as a high voltage accelerator electrode.

Electrons emerging from this structure pass through a magnetic field created by a coil wound around the neck of the tube. The electro-magnetic "lens" so formed tends to focus the electron beam, the focal point depending on the exact position of the focusing coil and the current flowing through it.

MAGNETIC FOCUS

CR tubes employing magnetic focus are commonly used in television equipment, the advantages claimed centering mainly on the comparative simplicity of the tube structure and the wide angles through which it is possible to deflect the beam.

To this point in our discussion we have seen how the electron beam is produced, how it can be modulated and focused by one means or another to a fine spot.

While this is all very interesting there is obviously not much point in having a stationary spot of light on a fluorescent screen. Indeed, the impact of the electrons would very quickly "burn" the fluorescent material.

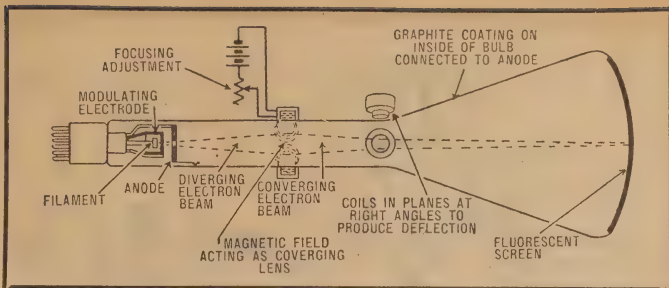


Figure 20: A typical cathode-ray tube employing magnetic focus and deflection.

What is required is some means to control the position of the spot on the screen so that it can be swept back and forth, up and down, in any desired fashion.

In other words, the electron beam must be induced to perform the function of scanning, exactly as in the mechanical systems we have already examined.

The desired result can be accomplished in two ways, namely, by electrostatic or by electro-magnetic "deflection".

The principle of electrostatic deflection is assumed in the illustration, figure 18. Two pairs of flat plates shown as B and C are mounted in front of the final anode (A). Their initial d-c potential is normally the same as (A).

The electron beam passes between each pair of plates, which can be connected to an external source of signal.

If, at a particular instant, one plate of a pair is more positive than the other, the electron beam tends to be deflected toward the positive deflector plate. At the next instant, the position may be reversed and the electron beam deflected the other

way.

Thus it becomes possible to swing the beam to and fro and, with it, the resulting spot of light on the screen.

By having one pair of deflectors vertical and the other horizontal, it is possible to swing the beam simultaneously to and fro and up and down as required.

In other words, the cathode-ray beam can be made to fulfil the requirements of a scanning system by providing suitable control voltages on the deflector plates.

BEAM DEFLECTION


As an alternative, the electron beam can be deflected as required by locating magnetic coils around the neck of the tube in front of the focusing coil. These are illustrated in figure 20. We need not worry overmuch at this stage about the exact shape that such coils take, the important thing being to grasp the principle involved.

Although the drawings show valves with a wholly electrostatic

(Continued on Page 118)



Figure 21: Assembling the "guns" of Mullard television picture tubes. Note that the gun structure is bent, the intention being to prevent heavy ionised atoms from striking the screen along with the electrons and causing ion "burns".

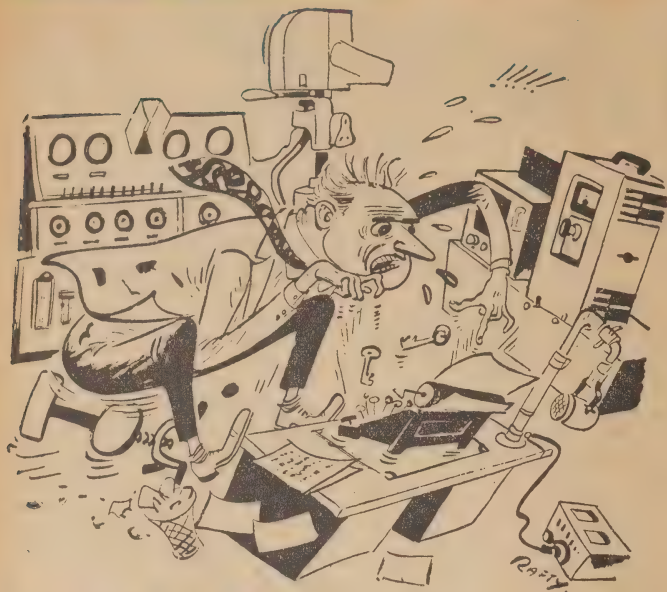

Let's Buy An Argument

This month, a letter from a New Australian reader raises a subject which, according to other members of the R, TV & H staff, is one very dear to my heart. There's a saying round the place that, if "WNW" has anything to do with a design, it's sure to include some fancy tone control system!

I **STOUTLY** deny it, of course.

We've featured in the past a whole series of multimeters and grid-dip oscillators and not one of them has ever had any provision for bass and treble boost!

But, setting aside the implied insult, I suggest that you read the letter in question, in the panel on the opposite page. Only the relevant portions have been quoted, retaining much of the original phraseology by way of "atmosphere". As you will note, our friend is a Dutchman, facing the difficulties of a technical subject in a new language.

DO THEY MATTER?

His key question is the third one, relating to the possible effect on listening of frequencies above and below the normal range of sound. Are they significant?

If they are, what account do we take of them in planning tone compensation networks?

Why do our curves show only the response of such circuits over the audible range?

In trying to answer these questions, I don't want to steal the editor's thunder, because he is pre-occupied at the very moment with the possible impact on the listener of subsonic and supersonic frequencies—particularly the latter. My remarks here must, therefore, be framed with this in mind.

It is quite true that the vast majority of compensation curves, published by this and other journals, are confined to the audible range, extending nominally from 20 to 15,000cps. We do this on the simple assumption that only the audible frequencies matter, as far as balance and compensation are concerned.

The lowest organ note ever produced or recorded is allegedly 16cps,

by *Neville Williams*

but, in actual fact, the bass response of most program material would extend a full octave above this. Therefore, to sustain response and compensation down to 20 cycles would appear, on the surface, to be generous.

At the other extreme, our normal "hearing" process fades out at about 15Kc, and it is commonly assumed that there is no justification for worrying about response over this approximate limit. We wouldn't hear the result anyway! We would remain blissfully ignorant, whether the response was sustained there after, or dropped away by reason of circuit losses.

In point of fact, it isn't hard to demonstrate that we do have some response to supersonic energy. A speaker projecting moderate power into a room at say 20Kc cannot be "heard" by most people, but it can rapidly produce a conscious degree of nervous tension and fatigue.

NOT DEFINITE

Whether the small, transient supersonic energy contained in everyday sounds is sufficient to produce an appreciable stimulus is problematical. Some are beginning to think that it might, but it's a pretty tentative kind of postulation.

To date, it hasn't been sufficiently strong to warrant specifying the performance of tone compensation cir-

cuits outside the limits of hearing. Until enough strong evidence comes to light, I guess that our tone compensation curves will continue to look much as they have done in the past.

That doesn't mean, of course, that we ignore the response of an amplifier system outside the limits of hearing. Once upon a time we might have done so, but not now. We've learned that the response at extremes of the range is important anyway, for other than musical reasons.

STABILITY

As the editor points out elsewhere in the issue, the extent and shape of the main amplifier response in the high frequency region governs the stability of the system and its reaction to transient pulses. Careful study of the main amplifier in this region is warranted, therefore, if only to guard against producing a design which will go into supersonic oscillation at the drop of the proverbial hat.

If it is shown that an extended,

smooth response into the supersonic region is also essential for musical realism, then some of the attention being currently paid to basic amplifiers will have to be transferred to earlier links in the chain.

Recording engineers will have to look to their laurels, pickups will have to undergo yet another revolution and control units will have to start borrowing from video techniques. All the well-known recording curves will have to sprout "extensions" along with their complementary playback curves.

But the game is hard enough already, and, until somebody proves the necessity for the more elaborate approach, I can't see too many designers adopting it.

Right now, the most obvious effect of extending the input circuit response would probably be to render the whole outfit inordinately sensitive to switching transients in the house wiring—and that isn't a good thing.

BAD FOR NERVES

It's just amazing how "electrifying" 15 watts of "plop" can be, emanating from a big speaker in the dead of the night!

Of course, this tendency could be minimised in turn by building in an effective line filter, but there we go again—complicating the equipment to counter some previous complication that may not have been necessary anyway!

At the other end of the range—below about 20cps—the shape of the response curve has a lot to do with the tendency of the system to "motorboat" and its sensitivity to motor rumble, cabinet vibration and so on. It must, therefore, be considered.

A classic example of this fact was provided by the basic Williamson amplifier which, by reason of a peak at about 2cps, was extremely prone to motorboating troubles, when extended to include a preamplifier and tuner, operating from the same power supply.

It led us into extensive decoupling systems, voltage regulation and the final abandonment of the circuit as "too hard" for the average home constructor.

THE "PLAYMASTERS"

On the assumption that a response to less than 2cps was unnecessary and, in fact, a bad thing, we introduced the "playmaster" series of amplifiers and tuners. Their acceptance is now history, for they provided all the bass response that could presumably be justified, with no serious stability problems.

There are some who contend, of course, that it isn't good design to operate a complete amplifier system from a common power supply; that each unit should have its own power supply irrespective, duly filtered and regulated!

This is a rather extreme view, I fear, having its strongest supporters among those who can afford it.

Profligate use of parts can actually amount to BAD design, if it is made necessary by some undesirable or redundant characteristic or if it fails to contribute anything useful to the prime function of the equipment.

But, maybe, that's asking for an argument on another subject.

ABOUT TONE CONTROL CIRCUITS

I have a few questions about tone controls, which you might like to answer in your "Let's Buy An Argument" pages.

You draw a nice diagram covering the audio range (30cps to 15Kc) and that is all. Is it ideal to stop at 15Kc or is it needed to go much higher?

Most circuits drop in the extreme bass and treble but some systems go higher than 20 or 30Kc.

Can you suggest what happens when you get boosting under or above the limits of hearing; does it affect the normal sound?

One well known tone control system is of the resonance type with peaks at 30 cps and 10Kc, giving a sharp peak of up to 20db with a roll-off beyond it.

And what about the cut-off in the treble? When you have a sharp filter, it does not sound nicely. The one I heard was in a voice coil filter. The ordinary roll-off control that is used sounds nicely.

Now my letter is possibly not clear at all. Will or can you please give me the needed information if it is possible? ("Will" in Dutch means asking someone something, not "must").

Yours Faithfully, N.F.G.

Whether or not there is any virtue in achieving a DC-like bass response, the undeniable fact remains that an extreme downward extension of the frequency range does multiply the chances of the speaker cone flopping around with rumble from the turntable, imperfections in the record and vibrations from the floor and cabinet.

Even if the cone movements aren't immediately audible as "sound", one can still be aware of them and, in any case, there is the chance that they will modulate the normal bass content of the programme.

To avoid such troubles—or rather minimise them—the usual course has been to let the response fade away below about 20cps, even making some effort to see that it is not sustained into the region where motorboating and rumble problems predominate.

PLAYBACK CURVES

For this very reason, the AES playback curve has given place to others which allow a flattening off below about 25cps and do not call for circuitry which almost "guarantees" that the channel response at 10cps will be higher than it is at 20cps.

But if, in turn, an extension into the subsonic range is shown to be necessary, then we'll have to solve a few more problems. Truly rumble-free motors will have to be made, pickups without obvious arm resonance, even better output transformers and, of course, bigger and better speaker systems.

In the face of all this, the elongation of a control unit response curves

wouldn't be an insuperable problem. But, of course, along with the recurring need for higher gain, it might push us beyond the limit that we're already approaching, where stable operation from a single power supply is impractical.

This statement brings us back almost where we started. But why worry? This is an argument, isn't it?

Then N.F.G. raises the question of using compensation circuits built around resonant chokes. Well, what about them? Are they good or bad?

My first encounter with resonant type compensation circuits occurred when I was a mere youth, which is a roundabout way of saying that it's a pretty old scheme.

As I remember at the time, the two resonant chokes, each shunted by a variable resistor, were connected in series in the plate circuit of an early pentode voltage amplifier. Included in the circuit was a resistor of a few thousand ohms to provide a permanent plate load for the valve.

BOOST EFFECT

With the pots, at minimum resistance and the chokes shunted out, the response was level. Removing the shunt from either or both chokes allowed them to develop their respective peaks, giving bass or treble boost as desired.

I remember being quite impressed at the time by the effectiveness of the system. I also remember that the words "Bass" and "Boomp" were practically synonymous in those days and no one was unduly perturbed about the resonant nature of the circuit. If it produced plenty of boomp, then it had a good bass response. That was the end of the matter!

Nowadays, high-fi fans do their level best to avoid such resonance, either in the amplifier itself or in the speaker system. They resort to negative feedback, special cone suspension and to anti-resonant baffles. The object is to retain maximum control over the speaker cone at all times and to prevent it from developing a damped wave train every time it is hit by a substantial low frequency signal.

I remember being impressed also by the performance of the resonant control at the top end of the range, but, of course, this was a long time ago, in terms of audio development.

Microgroove records didn't exist, pickups cut off well below 10Kc and wide-range speakers were rather futile curiosities. It was quite a novelty to turn a knob and hear the sibilants hiss at you.

But, of course, the novelty angle of treble, as such, has gone and the emphasis is now on true treble, clean and non-peaky. Over-prominent sibilants indicate failure, not success.

AVOIDING PEAKS

We still have a lot to learn about the subject but, among other things, modern practice is to try to minimise circuit "ringing" and to avoid peaks in the response, which noticeably "color" the reproduction and emphasise record noise.

With this end in view, designers of high quality pickups take great


MOTOR SPARES LTD



CATHODE RAY TUBES

VCR138, 3 1/2 inch diameter Cathode Ray Tubes, ideal for oscilloscopes, etc.
 Characteristics as follows:
 Filament Volts 4
 Filament Current 1 amp
 Anode 2 200 Volts
 Grid 1 -50 Volts
 Diameter 80mm
 X Plate Sensitivity .14
 Y Plate Sensitivity .33
 Anode 3 1200 Volts
 Electro-static deflection
 Colour Green
 Socket connections can be supplied to each purchaser.

Price 32/6

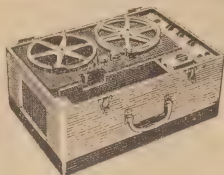

TAPE RECORDERS

These Recorders are standard size using 7 1/2 inch spools of tape. Tape speed is 7 1/2 inches per second, fast forward and fast rewind positions are provided. Will play for 1 hour on each tape. Excellent tone and sensitivity. Crystal microphone with each.

Well worth £120/0/0.

Our price £75/-/-

CHIEFTAIN MILLIMETER

New Model using 100 ohms internal resistance meter, sensitivity 1000 ohms per volt. Voltage readings 0-15, 0-150, 0-300, 0-600. Ohms 0-100,000. This is a pocket size meter, ideal for the Electrician, Radio Serviceman, amateur Motor.



Price Only £4/12/6

CARBON RESISTORS

1 Watt. All brand new and in good condition. Sizes listed in Ohms.
 250, 350, 400, 450, 500, 600, 650, 800, 850, 1000, 1500, 2000, 3000, 4000, 4700, 5000, 6000, 10,000, 12,000, 15,000, 25,000, 40,000, 60,000, 70,000, 75,000, 1 meg, 1.5 meg, 2 meg, 2.5 meg, 3 meg, 3.5 meg, 5 meg, 1.75 meg, 2.3 meg, 3 meg, 5 meg.
 Price only 4d each, 3/4 doz., 15/6 per 100.
 1/2 Watt. Sizes listed in Ohms.
 50, 300, 500, 600, 2000, 5000, 10,000, 25,000, 40,000, 50,000, 60,000, 100,000, 25 meg, 3 meg.
 Price only 3d each, 2/6 doz., 16/8 per 100.
 1/4 Watt. Sizes listed in Ohms.
 150, 250, 300, 320, 350, 450, 600, 750, 800, 900, 1200, 1800, 1900, 2200, 3000, 3200, 6500, 7500, 7900, 8000, 10,000, 13,000,

15,000, 25,000, 37,000, 80,000, 90,000, 15 meg, 16 meg, 25 meg, 35 meg, 4 meg.
 Price only 3d each, 2/3 doz., 15/6 100.
 2 Watt Carbon.
 100, 200, 800, 6000, 10,000, 15,000, 80,000
 Price 6d each.
 3 Watt Carbon, 3 meg.
 Price 6d each.

WIRE WOUND RESISTORS

All brand new and in perfect condition.
 5 Watt. Sizes in Ohms.
 100, 200, 300, 350, 400, 450, 500, 550, 600, 650, 700, 750, 800, 1000, 1200, 1250, 1500, 2000, 2500, 3000, 3500, 4000, 4500, 5000, 6000, 7000, 9000, 10,000.
 Price only 9d each.
 8 Watt. 150, 200, 250, 300, 350, 400, 450, 500, 550, 600, 700, 750.
 Price only 1/- each.
 10 Watt. 125, 150, 175, 1000, 1250, 1500, 1750, 2500.
 Price only 1/- each.
 12 Watt. 800, 4500, 14,200.
 Price only 1/3 each.
 20 Watt. 50, 75, 125, 150, 175, 200, 250, 300, 400, 500, 750, 1250, 1750, 2000, 3000, 4000, 5000, 15,000, 50,000.
 Price only 2/- each.
 25 Watt. 30, 75, 100, 125, 175, 200, 250, 300, 400, 750, 1250, 1500, 1750, 3000, 4000, 7500.
 Price only 2/6 each.
 30 Watt. 150, 1000, 2000.
 Price only 4/6 each.

The following are Resistors especially made for the British Navy or Australian Army, etc. All are brand new and guaranteed. They are exceptionally good value.

Resistance in Ohms.	Wattage	Tap	Price
10	75	Variable	5/-
18	100	CT	6/-
20	50	Variable	4/-
36	100	None	6/-
45	100	None	6/-
50	10	None	1/6
50	20	None	2/-
60	60	CT	5/-
100	40	None	4/-
100	50	Variable	4/-
120	80	None	5/-
150	20	—	2/-
200	100	Variable	6/-
250	50	None	4/-
300	85	None	5/-
350	25	Variable	2/6
400	50	Variable	4/-
430	200	None	2/6
450	27	—	2/-
500	100	—	6/-
700	20	—	2/-
850	20	—	2/-
1000	100	Variable	6/-
1000	150	CT	7/-
2000	75	Variable	7/-
2000	150	None	7/-
2500	10	—	1/6
2500	50	—	2/-
2500	50	—	2/-
3750	30	None	4/-
4000	20	—	2/-
5000	20	—	2/-
5000	40	—	4/-
3500	12	—	1/6
10,000	55	3000	4/-
10,000	50	None	4/-
15,000	50	Variable	4/-
25,000	30	None	3/-
25,000	40	—	4/-
25,000	75	—	5/-
50,000	80	—	5/-
50,000	150	—	7/-
75,000	150	—	7/-

SPECIALS

- 1.4 mfd 750 volts wkg. Block Condensers brand new and perfect. 5/8 each.
- 2.4 mfd 500 volts wkg. Block Condensers as above. 5/- each.

SPECIALS

- Germanium Diodes. Ideal for Crystal Sets, meter rectifiers and radio set detectors. Brand new. Only 4/11 each.
- 954 Valves. Pentode Detector amplifier, acorn type with 6.3 volt filament for high frequency work. Brand new. Only 5/6 each.
- VR 130-2 200 volt battery triode valves. octal base. 2/6 each.
- NR74 Output tetrode valves, same as 807 but with 4 volt filament and special English base. Each valve will be supplied with a socket and chart, showing connections.
- A bargain for 5/- each.
- AV11, high voltage rectifier valves. 8/9 each.
- FF50 Valves. Brand new and boxed. 7/6 each.
- Ferroxcube rod aeriels. Ideal for portables. Takes the place of a loop; equal to 60ft outdoor aerial. Price only 16/6 each.
- Record Changers. Reconditioned single speed, guaranteed in working order. Well-known makes. Garrard, Collaro, H.M.V., Stromberg-Carlson, Plessey. Price only £4/10/- each.
- Gramo Motors. Single speed, reconditioned and guaranteed in working order. Each motor has magnetic pick-up and automatic stop. Price only £2/17/6 each.
- 3 Speed Gramo Motors to operate off 230 V AC. Each has speed control knob with 33, 45 and 78 rpm positions. Suitable playing standard and microgroove recordings. Price only £5/10/- each.
- High Fidelity turnover head type crystal pick-ups to suit above motor. 2 built-in sapphire needles provided. Suitable for both standard and microgroove recordings. Price only £3/15/- each.
- 3 Speed Record Playing Units consist of Motor and Pick-up with automatic stop on unit plate suitable for playing both microgroove and standard recordings. Two sapphire needles supplied fitted to each pick-up. A bargain for £8/19/6.
- 3 Speed Record Player in leatherette covered case similar to above. Worth £18/18/- Our price £12/19/6.
- Spring Gramo Motors, wind up type, suitable for replacements in portable gramophones, etc. Complete with turntable and fittings. Price only £2/19/6 each.
- 0-5 ma Meters. Square face 2-inch scale, 7 ohms internal resistance. An excellent English meter. 19/6 each.
- Phone Jacks. Closed circuit P.M.G. type. Brand new. 2/6 each.
- Low Impedance Headphones. British manufacture, new and boxed. Price 18/6 each.
- High Impedance Phones, made in Germany, light weight, excellent quality, adjustable. Price 39/6 each. Brand new and boxed.
- 21.2 Valve Amplifiers, type A1134, less valves. Components in each amplifier, 1-8 pole PMG switch, 3 position Toggle. 1-2 Way Toggle Switch, 4 Transformers Audio, Input and Output. A number of resistors and condensers, all in metal box. 6 1/2 in x 4 1/2 in x 4 1/2 in. Price only 10/6 each.

SPECIAL NOTICE

All parcels sent Registered Post unless otherwise stated. Postage or Freight must be included with order.

547 ELIZABETH ST., MELBOURNE

BENALLA BENDIGO BROKEN HILL
 GEELONG MILDURA SHEPPARTON

ALSO AT - ALBURY ARARAT

COLAC DANDENONG ECHUCA
 ST. ARNAUD WAGGA

BAIRNSDALE

SALE WANGARATTA

BALLARAT

FRANKTON WARRAGUL

pains to push any peak as far up the range as possible and to damp it as much as possible, so that it will have a minimum effect on the end result.

Peaks in the speaker system are regarded with grave misgivings.

In the face of all this, to introduce a resonant circuit in the guise of tone compensation, appears clearly to be a retrograde step. It is much safer to use a simple R/C circuit, which takes up and rolls off gradually and does not normally produce a slope exceeding 6db per octave.

If it is of any comfort, it gives the same kind of compensation curve as is common throughout the audio industry.

Chokes can make sibilants hiss-at-you.

Trace CRO patterns charmingly Lissajou;

But transient pinging
Is turned into ringing
And ends up a horrible zizzi-goo!

Besides that NFG, chokes are costly and they pick up hum feet away from motors or transformers.

NOT MUCH USED

They've had their day, I fear, except for very special purposes, such as teasing the last ounce of treble from badly copied 16mm sound films.

But you wouldn't call that audio! Well hardly.

Perhaps this condemnation of resonant compensation circuits does not seem to tie in with our erstwhile sponsoring of voice coil filters—which are obviously of the resonant low-pass type. This is probably the situation that NFG anticipated when he raised the subject. Are we being inconsistent?

I just wonder about his statement that a sharp cut-off filter does not "sound nicely". Is he conveying the wrong sense or is he basing judgment on some amplifier-filter combination which is ringing badly for one reason or another. Such ringing can be very unpleasant, amounting almost to an echo effect.

NOT OBJECTIONABLE

I can assure NFG that the R, T and H filter does not (or should not) sound like that. To be sure it changes the character of the reproduction and record noise in a most obvious fashion and it takes a few moments for the ears to grow accustomed to the change in frequency content. But the end result is never positively objectionable. When the filter is justified, its use always makes the program more listenable. To appraise the filters properly, one must appreciate why they were suggested in the first place.

We've been through this before, but the story, briefly, is this: Many readers bought wide-range speakers when they were first introduced and attached them to their pet amplifier systems. On the new microgroove records, which were then just appearing, the speakers sounded excellent, while they were quite good also on radio.

This was all to the good, but the rub came when the enthusiast tried to play his ordinary 78 records through the system. Quite a bit from sounding dull and noisy, which could be expected, the reproduction

TRANSISTOR SET

Dear Sir:

I have been interested for quite some time in building a transistorised radio receiver, but have had trouble finding a suitable circuit. I had decided on a four transistor set suitable for a car radio, and the other day I discovered your article in *Radio Television & Hobbies* of August this year, so I decided to use that circuit.

There are a few points that I would like a little extra information on. Firstly, the driving transformer for the push-pull stage—are there any suitable transformers on the market? If not, how many turns of what gauge wire are required with what type of core? (Size is not particularly important.)

Next the speaker—I am thinking of using a 7in X 5in oval one with as near to 2 ohms impedance as I can get, so what type of transformer is used with that? Lastly, how is it possible to modify this circuit for either 6 volt or 12 volt operation?

suffered from a most objectionable distortion on high frequencies not unlike the buzzing effect of a loose turn on the voice coil or some such speaker fault.

The trouble was due in part to the record grooves, in part to stylus problems, with the general imperfections of the pickup, the amplifier and the speaker itself thrown in for good measure.

We had to face up to the problem, like everyone else.

Conventional tone control measures, giving a slow roll-off, didn't prove to be a good answer because, to be effective enough at the top end, the roll-off cut unnecessarily into the middle register. The contrast with good, wider-range reproduction was rather appalling.

In due course, we got around to the sharp-cut voice-coil filter idea and it provided the kind of answer we were looking for. The sharp roll-off proved very effective against the distortion we were worried about, while having a minimum effect on the usable portion of the range.

EMERGENCY MEASURE

But don't get us wrong, NFG. A sharp cut-off resonant filter is not a good thing in its own right—but then neither is the kind of noise and distortion against which it was designed to operate. It is a clear case of the end justifying the means.

Nowadays, the pickup and record position has improved to the point where at least the more affluent quality fans can pick and choose between records and pickups to guarantee a more nearly distortion-free input signal.

For such folk, a voice coil filter unit is unnecessary.

But where one cannot be so discriminating, or where one wants to draw on an existing library of 78 rpm records, or where static or line noise is a problem on occasions, a sharp cut-off voice-coil filter is a

handy thing to have at the end of a switch knob.

Maybe it does amount to curing one evil with another but, if the end result is more acceptable, what of it?

And what if the filter does ring on square-wave input and what if it does appear to have a 2db bump before the roll-off? Wouldn't you rather put up with these second order effects than the horrible scratchings and buzzings that emanate from a wide-range system reproducing distorted programme material.

I would, any day!

In conclusion, N.F.G. says that an ordinary roll-off control "sounds nicely". Once again I'm wondering whether it is a matter of phraseology or whether he has failed to appreciate the purpose of the circuitry in question.

WRONG IDEA

Perhaps he has fallen into the same trap as another reader who spoke to me recently. This reader was trying valiantly to use a top-cut filter in the voice coil circuit to compensate for microgroove pre-emphasis.

Actually he didn't quite realise what he was trying to do, but that's what it amounted to. His amplifier was an old style affair to which he had attached a modern crystal pickup.

The few microgroove records he had purchased naturally sounded "rather thin" on the outfit, both because they contained an unaccustomed amount of treble and also because this treble was pre-emphasised in accordance with normal microgroove practice.

The reader concerned could largely have corrected the situation by turning his tone control down a little but this he was unwilling to do on the grounds that he did not want to "throw away the treble response".

TOO EASY!

Furthermore, it didn't seem right that a terribly technical operation like providing de-emphasis could be accomplished by simply turning back a tone control knob.

Accordingly, he had gone ahead and built up a voice coil filter unit. This had allegedly improved matters but he felt that the balance "still wasn't right".

He took quite a bit of convincing that his approach was completely wrong; that he wasn't throwing treble away by using his tone control as suggested, because the records were cut with exaggerated treble which actually required to be attenuated during playback.

By not using his tone control as suggested, he was allowing the overall treble response to rise, in accordance with the pickup and recording curve, toward the region where the filter operated. This removed all frequencies above the roll-off region, so that the overall curve was quite peaky.

The result would inevitably be a rather strident kind of reproduction, lacking really high frequencies and exhibiting a rather prominent noise level.

He agreed that this was, in fact,
(Continued on Page 119)

MAGNETIC SOUND INDUSTRIES

Australia's one and only specialist service in

TAPE RECORDERS

from **£65**

NOTHING
BUT TAPE
RECORDERS

Nowhere in Australia but at Magnetic Sound will you find a whole organisation, a whole floor devoted to selling, servicing and hiring nothing but tape recorders. That's why only Magnetic Sound Industries can offer you:




See the full range of new machines at Magnetic Sound. New model "Elcom" (above) is a radio-recorder with 7 valve radio input, £140 or 22s dep. "Technicorda" (right) gives 2 hours recording and is ideal for home movies, £149/2/-.

- **EXCLUSIVE TO MAGNETIC SOUND**
- **Long-awaited ELECTRIC TIME CLOCK**

Here at last! The revolutionary time clock that, once set, will automatically switch on any tape recorder or radio, then when the programme or item is finished, automatically turns the power off! Now you can record any programme while you are out . . . even while you're asleep! Makes a handsome and accurate electric clock when not in use. £12/17/6.

TAPE BARGAINS:

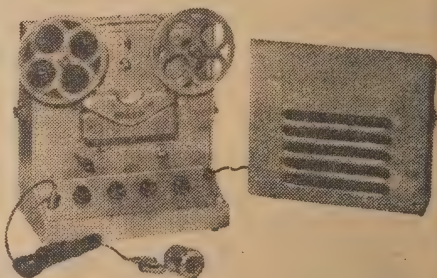Special: B.A.S.F. to clear, 7in reel, 1200ft usually £3/15/- now £2/5/-
 Scotch recording tape 1200ft £3/10/-, 600ft £2/5/-.
 A g f a: special price 1200ft. £2/14/6, 600ft 30/-.
 B.A.S.F. super quality, 1200ft £3/5/-, 600ft 39/6.
 E.M.I. new '88' 1200ft £3/5/-, 600ft £2/5/-.
 Empty spools from 5/-
 Microphones from £2/10/-
 Microphone stands 15/-, 21/-, £3/17/6




We will buy your tape recorder for cash

Magnetic Sound Industries will buy all makes and models for cash. Highest prices paid for your tape recorder.


MAGNETIC SOUND INDUSTRIES

387 GEORGE STREET, FIRST FLOOR ● **BX4440**
 (OPPOSITE STRAND ARCADE) ● **BX4587**

TRADE REVIEWS AND RELEASES

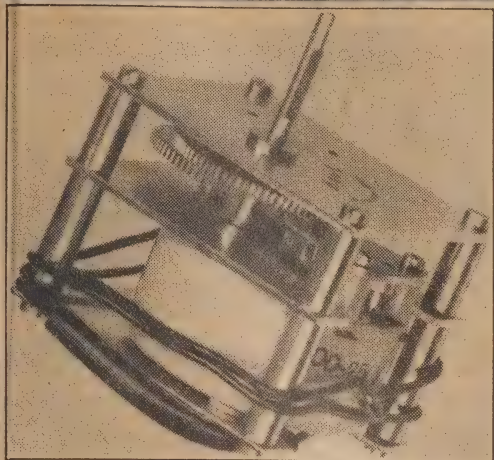

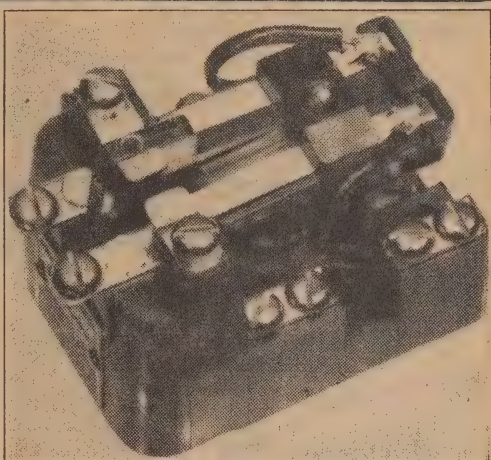Small synchronous motor with gear train reduction for driving window displays etc.



A two-pole changeover relay, AC operated Cat. No. 28308U. Other types can be supplied if required.

FLASHERS, RELAYS FROM PAYNES

From a large range of electronic equipment, R. J. Payne & Co., of 434 Collins St., Melbourne have submitted a number of items for review.

THESE include a well-made and powerful synchronous type motor, suitable for many purposes, including the operation of revolving advertising displays, etc.

This motor is claimed to have the highest torque of any similar type available, and can be supplied ex stock in 1, 6 or 10 rpm.

Another line handled by Payne's is represented by a change-over relay, AC operated, and with sturdy

contacts for heavy loads. The relay is built on a bakelite body with an adjustable spring loading. Made by Arrow of Sydney, it is obtainable in a variety of types. The base measures 2-11/16ths by 1-7/8in.

"Payneco" products include a large selection of flashing and timer units for various purposes. One of these is a bayonet adaptor into which is built a flasher which operates at

about 12 flashes per minute. It is suitable for lamps up to 100 watts, AC or DC.

A similar flasher unit is available as a separate item.

Another type of flasher is designed for 6 or 12 volt operation to handle 6 amps AC or DC, particularly suitable for display work and automotive turning indicator lights. Different types can produce either 40 or 80 flashes per minute.

Larger motor driven flashers can be supplied to accommodate multiple globes up to 2400 watts.

Paynes are also distributors for Solartron British-made test equipment including wide range oscilloscopes, oscillators, pulse generators and regulated power supplies. These are all high quality products, specifically designed for laboratory work where modern electronics is concerned.

T. J. Payne will be happy to send details on any of this and other equipment on application.


IBBOTT CRYSTAL TWEETER

An interesting, Australian-made crystal type speaker for audio work is the IBBOTT tweeter illustrated at left.


IT comes complete with matching transformer and cross-over network for connection into a 15 ohm output circuit. Suitable networks are available for operation from both 15 and 2 ohm sources.

The frequency range is given as 2500-20,000 cycles with a dispersion angle of 60 degrees.

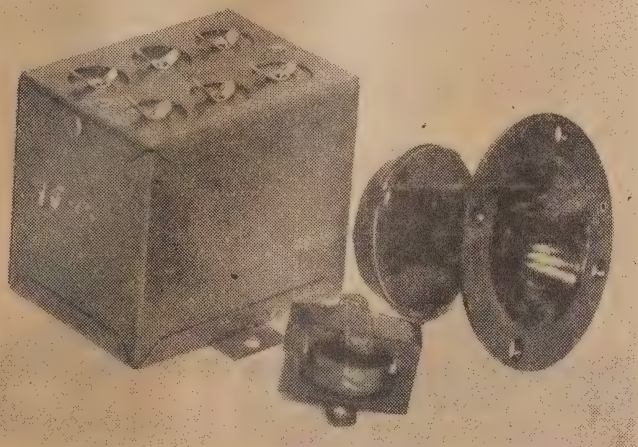Used with a bass-middle speaker in a vented enclosure, the tweeter sounded very good. It has a commendably smooth response which appeared to hold well to at least 14 Kc. Its small size could be a great advantage in many cases.



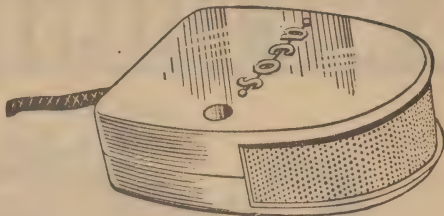The Ibbott tweeter cross-over network and coupling transformer.



A NEW SENSATIONAL CRYSTAL MICROPHONE!

ACOS MIC 35 (HAND AND/OR DESK TYPE)

**AT THE
AMAZING
PRICE OF
£2'15'0**

A general purpose microphone with high sensitivity and substantially flat characteristic. Housed in attractive Die Cast Case of very robust construction is particularly suitable for use in recording apparatus — Public Address Equipment — Dance Bands — and similar applications.

Provided with built-in shunt resistance of 2 megohm giving response substantially flat from 50/5,000 cps. Resistance of the input circuit will reduce the low frequency response. A grid leak of 4 megohm will reduce the output at 500 cps by 3 db and proportionately at lower frequencies.

Approximate capacitance of the microphone is 750pF and cable capacitance will reduce output proportionately.

Frequency response Substantially flat from 50/5,000 cps.

Output level \pm 55 db ref. 1 volt/dyne/cm².

Load resistance 2 megohms included.

Cable

Weight

Dimensions

This microphone is supplied with approximately 4ft. 1.2 metres of co-axial cable (type Unirad 32).

Microphone only — 6oz. (approx. 170 grammes) complete with packing 7oz. (approx. 198 grammes).


Microphone only 2 7/8in x 2 1/8in x 7/8in plus cable.

Complete with packing 3 3/8in x 2 1/4in x 2 1/4in

Sole Australian Agents:—

Victorian Distributors:—

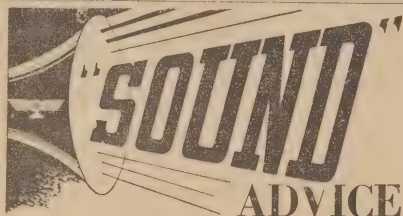AMPLION (A'sia) PTY. LTD. 88 Parramatta Rd., Camperdown,
Sydney, N.S.W.
DISTRIBUTORS CORPORATION 403 BOURKE ST., MELBOURNE.



Buy your Hi Fi Equipment
from

AUDIO ENGINEERS PTY. LTD.
"The Sound Wholesalers"

Manufacturers of:

HIGH FIDELITY AMPLIFIERS
SCHOOL RADIO SYSTEMS
PUBLIC ADDRESS SYSTEMS
HOSPITAL AND FACTORY PAGING SYSTEMS
PORTABLE SCHOOL RADIO AND RECORD
PLAYING EQUIPMENT
HIGH FIDELITY HOME MUSIC SYSTEMS
SAND-FILLED AND VENTED LOUDSPEAKER
ENCLOSURES
LOUDSPEAKER CROSS-OVER NETWORKS

N.S.W. Distributors of:


LEAK TL10 AND TL12 HIGH FIDELITY
AMPLIFIERS
GRAMPIAN-MULLARD 5/10 AMPLIFIERS
LEAK DYNAMIC PICKUPS
WHARFEDALE LOUDSPEAKERS
BAKER LOUDSPEAKERS
THORENS HIGH FIDELITY RECORD
PLAYING EQUIPMENT
ORTOFON PICKUPS
BELMONT SPEAKER MATERIAL
D.G.G. TEST RECORDS

WHOLESALE OF

Quad II high fidelity amplifiers, Leak TL12 and TL10 high fidelity amplifiers, Armstrong A10 and audio engineers ML20-5A high fidelity amplifiers, Gramplan-Mullard 5/10 amplifiers, Wharfedale, Baker, Goodmans', Barker, Rola and Leak loudspeakers Thorens and Dual high fidelity record players and changers, Ferrograph tape recorders, Van Ruyten 50 cps. vibrator power supplies, Ferrotape, Scotch, Magnetoband LGS and Agfa recording tapes, Ferranti, Leak, B.J., Acos, Goldring 500, Ortofon pickups, Connoisseur and Ronette pickups. All types of sand-filled and vented enclosures, and cross-over networks.



422-424 KENT ST.,
SYDNEY.

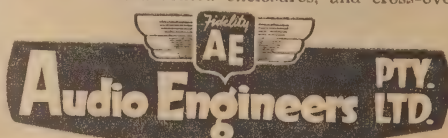

PHONE BX6731.

BATTERY FLUORESCENT LIGHT

Now being manufactured by the Glenradio Co. Sydney are a range of inverters that will allow the operation of a fluorescent light from a battery supply.



THE standard model supplies one 20-watt tube and can be ordered for 6, 12, or 32 volt operation.

The inverter section is contained in a grey hammerglow finished metal case 8in x 5in x 5in, weighing 9lb. This unit has an internal ballast and is fitted with a standard Oak vibrator.

Filtering is provided in the unit to obviate interference with radio equipment and the current drain is stated as 2½ amps for the 12-volt model and twice this for the 6-volt model.

The tube, its mountings and the starter comprise a second unit connected to the inverter by leads supplied with the equipment.

On test the unit was quick in starting and gave a satisfactory light output. Starting was still maintained at 10 volts input to the 12-volt model.

Some mechanical noise was evident from the vibrator, which may call for isolation of the power unit in quiet rooms.

This equipment would be ideal for caravans and similar applications where a high level of illumination is required for moderate battery drain.

The standard inverter unit retails for £12/15/- and the 20-watt lamp with the fittings and cables for £1/10/-. Other higher wattage units can be supplied to special order.


USEFUL DIAL KIT FROM JABEL

Watkin Wynne Pty. Ltd. have now released in the Jabel line of components a new dial assembly. The dial can be purchased in two separate sections to suit the needs of the experimenter.

ONE packet contains the 5 to 1 planetary reduction drive which is fitted with a cursor mounting flange and screws and a 3-8in to ¼in insulated reduction bush. This packet sells for 15/- retail.

The second packet contains a calibrated dial scale, straight edge cursor, Perspex panel and control knob. This packet sells at £1/1/- retail.

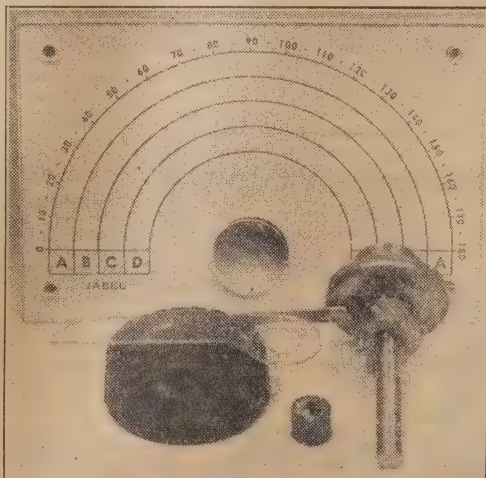
While the packets may be purchased separately, the two assemblies, combined, form an excellent dial arrangement for test equipment and other items requiring individually calibrated scales.



Also available is the normal 5 to 1 planetary drive without the cursor mounting flange; this retails at 11/-. Supplies of all these items are available through the normal trade suppliers.

FERRIS Electric TRAINS

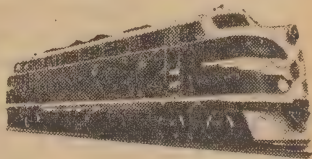Accurately Engineered
just like the real ones



NEW DIESEL ELECTRIC LOCO

Another true-to-the-real-thing achievement by Ferris. The F53 is modelled on the famous diesel electric locomotive that pulls the "Spirit of Progress" and "The Overland". It features the usual sweet running motor and sturdy construction.

Price £8/9/9



F51/5 LOCOMOTIVE

This engine looks and is a powerful unit. It will fit into any "0" gauge layout. Powered by the new Ferris electric motor with automatic stop, start and reverse and rubber tyres fitted to the main driving wheels. An engineered job at only £12/3/0

Carriages, trucks, luggage vans, rails, points etc. are available for use with the locomotives illustrated.

Cut and Mail this Coupon.

To FERRIS BROS. PTY. LTD.
252 Dowling Street, East Sydney.

Please send me an illustrated brochure and price list of all Ferris Train equipment available.

NAME

ADDRESS

R & H

OFF THE RECORD — NEWS & REVIEWS

The number of recorded operas being released at present is sufficient testimony to their popularity, undoubtedly due to the long playing record. Whether many of the old timers are as successful today as in their time is a matter of opinion, but doubtless there would not be purchasers if many people did not think so.

By JOHN MOYLE

ONE hopes that it is charm of the music and not the libretto which is the main attraction, for some of the stories demand extreme feats of imagination.

One of these is *I Puritani*, The Puritans, by Bellini.

Not only is it sung in Italian, and scored with lush music of a type which the Puritans could scarcely be expected to countenance, but it is filled with action and characters only to be found in such fairy tales.

BELLINI—*I Puritani*. Opera in three acts with Maria Meneghini Callas (Elvira) and Giuseppe di Stefano (tenor) and the Chorus and Orchestra of La Scala Opera House, Milan, conducted by Tullio Serafin. Columbia 33CX1058-1060.

This was Bellini's last opera, and with Norma probably the only one ever heard today.

The music is romantic in a Weberish-Verdi style with all the basses, tenors and soprano in the right places, singing tuneful arias and choruses over the six sides.

All the singers are good, with Maria Meneghini Callas probably the best. I don't think anyone will be disappointed on this score, but it is a pity the star numbers are not tied together with less stilted action.

As a recording I thought it very good, although only one familiar with a performance could really assess many aspects of it, and I doubt whether there are many such among my readers. The singers are heard well, the orchestra balances suitably, and plays throughout as though it knew its business.

The surface is virtually noiseless. I believe this is the only recording

of *I Puritani*, but it is quite good enough not to let that worry you.

The booklet containing the full text is well presented and invaluable.

GOUNOD — *Romeo and Juliette*. Opera in Five Acts with Janine Micheau (Juliette) and Raoul Jobin (Romeo) and the Chorus and Orchestra of the Theatre National de l'Opera, Paris, conducted by Alberto Erede. Decca LXT 2890-2892.

The recording runs away with the honors in this release—it is Decca's top grade standard, obvious from the first few bars.

It is hi-fi stuff as compared with *I Puritani*, and I found the greatest pleasure in listening to it for that reason alone. The chorus I thought equally good.

The general standard of the singers didn't please me as much. It's extremely doubtful whether Gounod's lovers are intended to be in the same age group as Shakespeare's, and I couldn't persuade myself that Juliet at least was quite as juvenile. Emotionally even the Bard didn't achieve such maturity.

Much of the action, too, although sung suitably agitato, somehow didn't convey full conviction. Surely the critical swordfight should have been accompanied with some "noises off", for instance.

It's hard to avoid staginess without some visual action, and it might be a good thing for recordists to remember this when undertaking a long haul of this kind.

Once again, those who buy the opera for Gounod's music will get exactly that, and are not likely to be disappointed.

MASCAGNI—*Cavalleria Rusticana* with Maria Meneghini Callas (Santuzza) and Giuseppe di Stefano (Turiddu) and the Chorus and Orchestra of La Scala Opera House, Milan, conducted by Tullio Serafin. Columbia 33CX1182-3. Fourth side vacant.

This opera stands up much more vigorously than either *I Puritani* or *Romeo and Juliet*. It is nearer to the earth—nothing of the drawing room romanticism here, but a violent story of passion and sudden death.

Compared with the Decca release recently reviewed, the only point in which it is inferior is the recording.

This is rounded and full, but hasn't the impact of the Decca release, and at times the tempo hangs a little more.

But in every other respect, it is vastly better.

Both the leading tenor and soprano to my way of thinking are in a higher class. They are first rate, particularly Callas, who once again takes the honors, even more definitely.

It is a role which I thought suited her admirably.

There are other superior points as well. Most noticeable is the better voice of Alfio. He sings his opening aria to a most convincing accompaniment of whip-cracks which give the "noises off" atmosphere I mentioned earlier as being so important.

Having so recently reviewed this opera, I'll say no more than this—I you want a Rusticana, this is definitely the one to buy. Being by the same company, its general recording atmosphere is similar to that of *Romeo and Juliet*.

SCHUBERT—*Symphony No. 8 in B minor (Unfinished)*. *Symphony No. 5 in B flat major.* Played by the Vienna Philharmonic Orchestra, conducted by Karl Bohm. Decca LXT2998.


If you like these symphonies played at a slow tempo, every phrase beautifully and sympathetically turned, then you'll like this recording.

Personally I feel that the Unfinished in particular drags far too much when played at this pace. I don't even see the music that way—it can come to life with more urgency than this. It's just a bit too much like bedtime music, particularly when the recording lacks enough weight to sustain this particular approach. The second movement fares somewhat better, but still tends to drag. There are few symphonies in which just the right pace is so rewarding.

ROYCE

PHONE FB2592.
RECORDING EQUIPMENT

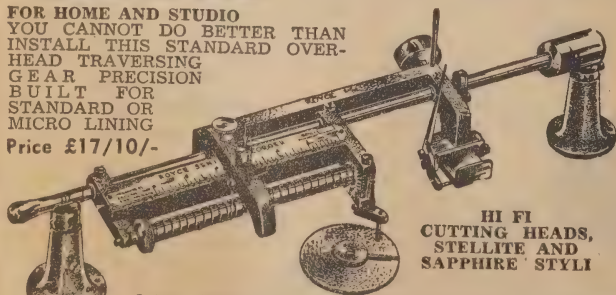FOR HOME AND STUDIO
YOU CANNOT DO BETTER THAN
INSTALL THIS STANDARD OVER-
HEAD TRAVERSING
GEAR PRECISION
BUILT FOR
STANDARD OR
MICRO LINING
Price £17/10/-



HI FI
CUTTING HEADS,
STELLITE AND
SAPPHIRE STYL

Labels, Stroboscopes, Turntables, Blanks and All Accessories
for the Recordist. Write for Catalogue of Prices.
PLAYBACK RECORDING SUPPLIES — BOX 5041Y, G.P.O., MELB.,
SALES AND SERVICE, 291 EXHIBITION ST., MELB.
South Aust. Rep., Scott Sales, Richards Bldgs, 99 Currie St., Adelaide.

I have the same general criticism of the 5th, although here the conductor is more successful in making his point.

Apart from this matter of tempo, the playing is distinguished and the recording clean and clear. There are a couple of obvious tape joins, one near the middle of the first movement.

In brief, OK if you are not in a hurry. Two symphonies on one disc makes good value.

The Decca curve is best with a little bass boost. The surface is good.

DEBUSSY—La Mer. RAVEL—Daphnis and Chloe Suite No. 2... Played by the NBC Symphony Orchestra conducted by Arturo Toscanini. HMV OALP1070.

The competition for La Mer is from the recently reviewed recording for Columbia by von Karajan, and in my opinion he takes the honors. Toscanini misses that touch of mystery, that nebulous quality that Karajan achieves better than anyone else to date.

The orchestra is more forward and the parts more clearly defined, but lacks the right amount of reverberation, which is essential to tie the sound together. I don't think the greater impact of the new record is called for in this case, although it is by no means the dead atmosphere we learned to detest with many early Toscanini efforts.

In all other respects I liked this side. There is plenty of good stuff in it.

Daphnis and Chloe does much better, and, although missing some of the delicacy of the Andre Cluytens record for Columbia, gains through its more immediate recording. It lacks the chorus and the added color it brings, but the orchestra has a better chance to whip up the excitement.

Unfortunately, there is some rather obtrusive, low-pitched tape hum, which wide range machines will pick up—I'm sure it isn't in the score!

Altogether a good disc, and one of Toscanini's best all round recordings. Use the EMI setting. The surface is not perfect, but compares well.

BRAHMS—Sonata No. 1 in G major, Opus 78, Sonata No. 3 in D minor Opus 108. Played by Isaac Stern, violin, and Alexander Zakin, piano. Philips AO1143L.

Violin and piano sonatas aren't the easiest things to make sound convincing, to say nothing of the difficulties which surround a recording. Here the violinist particularly is out on his own, and with a recording as forward as this one, his every touch and stroke must be perfection itself. There is absolutely no escape for him.

In my eyes, therefore, it is a tribute to these two, and to Stern, in particular, that I became so immersed in the music that to write about it became almost an irritating intrusion.

Both performances I thought superlatively good. These are two of the finest and loveliest sonatas in the book, and they are played with an authority and musicianship of the highest order.

The recording is quite forward, although only on odd occasions does the violin take on its full edge,

which many people don't like on records, and which can only be successfully handled with the best equipment.

Instrumental balance is good, and there is a fine understanding between players. It would be exceedingly difficult to find a jarring note on either side. The surface for the most part is inaudible.

To have two such performances on a single disc makes this record an automatic selection for anyone building a library of representative works.

WALTON—Facade, with Dame Edith Sitwell, and Peter Pears. The English Opera Group Ensemble conducted by Anthony Collins. Decca LXTA2977.

Facade was a product of the twenties—the very clever twenties of Noel Coward and the experimental in music and verse. Not that there isn't experiment today, but anyone who lived through that period will know what I mean, and will be able to date this extraordinary composition accordingly.

I am not competent to comment on its success or otherwise, because it isn't the kind of stuff which moves me to more than a passing interest. After one or two spasms, it all seems very elementary, despite the doggedly enthusiastic efforts of Dame Edith Sitwell, who must have been a little more lively and more interesting in 1922, when it was first performed.

The recording, however, can be highly praised. The whole thing is a studio production, and its realism is good enough for a demonstration piece if you can find a bit where Dame Edith isn't giving you the creeps.

It is, nevertheless, an authoritative performance of Facade, and if you like it I can't imagine a better Christmas present.

TCHAIKOWSKY—Violin concerto in D major, played by Mischa Elman and the London Philharmonic Orchestra, conducted by Sir Adrian Boult. Decca LXTA2870.

I cannot raise much enthusiasm for this record. Mischa Elman wasn't a young man when I heard him in my youth, and the kindest thing I can say is that he plays like an elder statesman.

This isn't much of a concerto at the best, despite its lush moments, and requires an extremely brilliant hand at the helm. Elman never was brilliant. His smooth, dark tone is still evident, particularly in the middle movement, but elsewhere he is ponderous and uncertain. At all times he gives the impression of making heavy weather of it, and more than once is caught scratching.

The recording is fairly good, but this isn't enough to make the record worth high marks.

CHOPIN—Sonata No. 2 in B flat minor, Opus 35, Ballade in G minor Opus 23, Nocturne in F sharp minor Opus 15 No. 2. **LISZT—Au Bord D'Une Source, Hungarian Rhapsody No. 6 in D flat major.** Played by Vladimir Horowitz. HMV OALP1087.

To me, Horowitz is a man who plays with his head and his hands —impeccably, dramatically and often

"IT'S" BACK AGAIN

A SUPERB CRYSTAL MICROPHONE INSERT

THE "ACOS" MIC 19-4

- Frequency response flat from 40 to 6000 c.p.s.
- High output level — 50db.



Price

£1/19/6

Available from leading radio houses everywhere.



RONETTE

MICROPHONES & ACCESSORIES



Type RFC5
£14/19/2

(High impedance)
Type RFC5/L

£19/-/-

(Low impedance,
200 ohms.)

Technical pamphlets will be mailed on request. Other types also available from

NEWTON McLAREN LTD.

17 LEIGH ST., ADELAIDE
and leading wholesalers

NOW AVAILABLE!

Connoisseur

SUPER
LIGHTWEIGHT
PICK-UP
with DIAMOND
STYLUS!



FACSIMILE
IN SOUND!

MAGRATHS offer you the "Connoisseur" 2-head PICK-UP with armature system fitted with diamond stylus. Complete with one head diamond stylus (either standard of microgroove, 33 1/3 and 45 r.p.m.) £14/14/- inc. S.T. Each extra head, £10/15/10 inc. S.T.

SPARE DIAMOND TIPPED STYLUS to fit Connoisseur Super Lightweight Pick-Ups, £7/17/6 inc. Sales Tax.

ORDER YOURS NOW!

SPEEDY MAIL ORDER SERVICE.

J. H. MAGRATH & CO.
PTY. LTD.
208 Lt. Lonsdale St., Melb. FB3731.

APPROVED HI-FI COMPONENTS

Engineered by the world's most outstanding High Fidelity technicians. Each unit has been subjected to the most rigid final test, assuring you of the ultimate in HI-FI performance.




The British ARMSTRONG SUPER 10

High Fidelity Amplifier and pre-amp control unit embodying

- ★ Six-way audio filter.
- ★ 15 db bass and treble boost controls.
- ★ Four way pick-up equalisation control.
- ★ Four separate inputs for high and low impedance pick-ups, radio and mike.

Control panel in handsome florentine bronze.
£74/10/-

VORTEXION PROFESSIONAL PORTABLE RECORDER

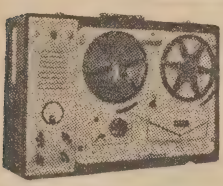

Uses the famous Wright & Weaire deck plus these new features:

- ★ Vortexion Low Noise amplifier.
- ★ Adjustable bias setting to compensate for various tape characteristics.
- ★ Synchronous capstan motor.

Two head models from £175

Magnecorder Three Speed Tape Recorder

The only three speed professional unit.

- ★ 10 watt broadcast amplifier.
- ★ Plug-in equalisers.
- ★ Amplifier flat to 20,000 cycles.
- ★ Suitable for rack mounting.
- ★ Studio type VU meter.
- ★ Heavy duty studio type synch motors.




The world's most widely used recorder! From ... £299

The ELAC MIRACORD three speed changer


with

- ★ PAUSAMATIC
- ★ MAGIC WAND SPINDLE
- ★ AUTO REPEAT

£36/10/-

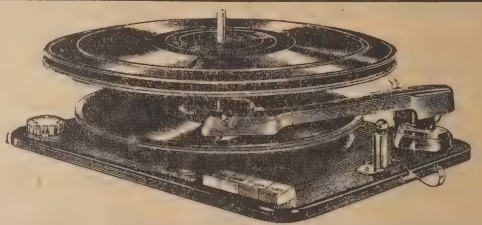

TRUVOX TAPE DECK

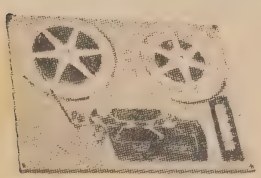

Build your own amplifier to the British Truvox circuit design, furnished free with each deck.

2 SPEEDS

£49/10/-

★ PEERLESS SPEAKERS

The Danish PEERLESS Twin Cone and Co-Axial Speakers. Flat 2db 40-15,000 cycles.

- ★ Twelve inch co-axial with in-built 5in. tweeter and cross-over unit ... £16/16/-
- ★ Twelve inch Twin Cone ... £7/19/6
- ★ Eight inch Twin Cone ... £6/10/-

★ BASF Megnetophon Recording Tape


- ★ 1800' on 7" spool ... £4/15/6
- ★ 1200' on 7" spool ... £3/7/6
- ★ 600' on 5" spool ... £2/19/6
- ★ 400' on 4" spool ... £1/19/6
- ★ 213' on 3" spool ... £1/1/-
- ★ 1150' on 5½" spool ... £3/5/-

★ PRE-RECORDED TAPE

FLORENCE MAY FESTIVAL series of pre-recorded classics on tape. Eighteen of the master classics recorded in Vienna and now available to music lovers on high fidelity tape.

Write for special concession catalogue offer.

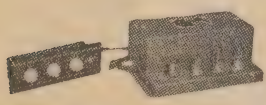- Single Track Recordings ... £4/17/6
- Double Track Recordings ... £6/15/-



TRIXONIC AMPLIFIER

All imported Trixonic 4 watt amplifier with remote control unit.

Economy priced at ... £39/10/-

NOTE: All prices shown are given as at date of publication and are subject to change without notice.

Magnecord Australasia Pty. Ltd.

Kyle House, 31 Macquarie Place - - - Sydney

beautifully, but I doubt whether there is a pianist who moves me less.

His pianistic command is incredible. There is just nothing he can't do, and its odds on before any selection is finished that he will do it.

Horowitz can no more avoid dramatics than he can stop breathing. I long to hear him play something, just once, simply and unadorned. To one with such an enormous control over dynamics, with such an easy and yet perfectly controlled change of pace, with such effortless technique, the flow of musical thought seems different from that of lesser men.

In Chopin, for instance, he shapes the melodic line as an essential framework to which ornament and elaboration are but secondary color—he collects them as he goes along, but he does not take us on a menial journey through them.

Maybe it all comes too easily to him, maybe his very perfection tends to discount what he is playing. Your reaction will be essentially a personal one—either you will think it magnificent or you will be disappointed.

The recording is distant, possibly for safety's sake; for Horowitz often plays with great power. The general tone is not bright, there is a light tape hum, and even a suspicion of capstan wow. But the surface is very good and otherwise it plays quite cleanly.

DVORAK—Cello Concerto in B minor Opus 104, played by Pierre Fournier and the Vienna Philharmonic Orchestra conducted by Rafael Kubelik. Decca LXT2999.

This is a warm, glowing performance of a concerto which deserves to be better known. That it is not so probably because cellists who can handle such stuff are few and far between, and we rarely hear them in this country.

Without competition, I feel Decca's flort would be received with hanks, for there is much good in

But it has to stand comparison with one of the finest cello records ever issued—that of Janigro and the Vienna State Orchestra under Dean Dixon. To my ears it is rather like listening to the master and the pupil.

Janigro hasn't the same romantic approach of Fournier, and some might consider him rather too cool and aloof by comparison. But it isn't really so. Janigro's almost flawless playing has something of the Heifetz touch about it (as applied to the cello, of course), while Fournier rather "lays it on" a little too much for me. His tone, too, while warm and sympathetic, isn't the equal of his rival, either in its consistency or in the way it is produced.

I noticed some slight groove echo, too, on Fournier's performance.

There is evidence of over-control of microphone balance with Janigro, but this is one of the few criticisms I would make. Westminster's recording is superb, Decca's quite good effort is dull by comparison.

This sounds rather like a review of the wrong record, particularly as it is far too good to be summarily dismissed. But, to my ears, for all its virtues, it must take

second place to Westminster's fine disc.

MOZART—Concerto No. 9 in E Flat Major—Concerto No. 15 in B Flat Major. Played by Wilhelm Kempf, piano, and the Stuttgart Chamber Orchestra with the wind of the Suisse Romande Orchestra conducted by Karl Münchinger. Decca LXTA2861.

There is an unhappy quality about this record, which prevents me from being over enthusiastic, although William Kempf gives a well-shaped and sensitive performance.

But the orchestra seems to have an uneasy ability to penetrate without achieving anything like a really good balance. It may be multiple mike job, but I had the impression that I had one ear close to the piano while the other was parked somewhere in the strings and woodwind.

Nor is the tone of the latter always as smooth, as it might have been. The piano, on the other hand, is quite good, although the whole performance is on the "small" side.

I'll leave you to judge this one. The surface is good.

TURINA—Canto a Sevilla, for soprano and orchestra. Played by the London Symphony Orchestra conducted by Anatole Fistoulari and sung by Victoria de los Angeles. HMV OALP1185.

Turina isn't very well known here. Noteworthy on records is the Sinfonia Sevillana recorded and

released on 78's by the Sydney Symphony Orchestra a few years ago.

The same characteristic charm of that music is heard in this suite of seven parts. This work has the same simple and direct idiom—there are more than snatches common to both. Even on first hearing, it wouldn't be at all hard to place the composer.

Some of the sections include a part sung beautifully by Victoria de los Angeles, whose rich voice and smooth consistency fits the music like a glove.

The work is descriptive of the city of Seville, where Turina was born, and about which so much of his music is centred. It pivots around Holy Week in the city, but its programme, if it can be so called, is little more than a thread which holds it together. The general air is romantic, delicate and beautiful.

The recording is admirable in every respect. The voice, particularly, is a joy to hear—it is one of those records where the mechanics of recording melt away before gracious sound.

WAGNER—Dawn, and Siegfried's Rhine Journey; Siegfried's Funeral Music; played by the Vienna Philharmonic Orchestra. Brunnhilde's Immolation and Closing Scene sung by Kirsten Flagstad with the Philharmonia Orchestra. Conductor Wilhelm Furtwangler. HMV OALP1014.

There is little need to plug this record. In it we have both Furtwangler, who is now dead, and Flag-

BY RETURN POST! LONG PLAYING TAPE BASF MAGNETOPHON

50% more tape on the same size reel!

and still 4 times stronger than ordinary tapes because of its PVC Luvitherm base. Post Free:—

Tin Reel. 1,750ft 95/6d. 5in Reel, 1,080ft. 65/-

MARCO RECORDING STUDIO Regd. UY1812
192 TOORONGA ROAD, GLEN IRIS, S.E.6. MELBOURNE.

THE "ACOS" MAGNETIC PICKUP




GP32
£2'12'6

Provides a good standard of reproduction with normal equipment at a reasonable price. Element incorporates new high-permeability sintered bi-metal magnet. Output voltage — $\frac{1}{2}$ volt at 1000 cps.

Available from leading radio houses everywhere



THE FULLY-AUTOMATIC SELECTOR CARRIAGE

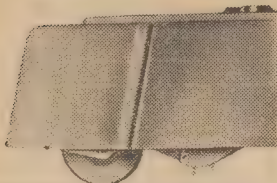

of
Dual 280

- determines intelligently
- the diameter of any
- record. By pressing key
- M or N the pick-up glides
- across the record, and,
- on reaching the disc's
- edge, the selector with-
- draws and places the
- RIGHT stylus upon the
- first groove.

This unit will play all

standard (N) and Microgroove

records singly and automatically

at all three speeds.

The large centre spindle supplied with each

280 will change TEN 7" records with the large

centre hole.

• PRICE £24/15/-

*Available from selected dealers anywhere.
Illustrated folder gladly posted upon request.*



FRED A. FALK & CO
PTY. LTD.

28 KING STREET, ROCKDALE, N.S.W.

TELEGRAMS: GRAMOFALK. PHONE: LX 4783
AGENTS IN ALL STATES

stad, who has retired, in the kind of music they did best, coupled with two of the leading recording orchestras and some high grade recordings.

It wouldn't matter much what other versions were or are obtainable, this one would not only be hard to beat, but has its own virtues which cannot be duplicated.

Furtwangler's intense dramatic imagination and his broad dynamic control are made to order for this music, possibly the highlights of the entire Ring cycle.

In it we will note Furtwangler's fine judgment of musical shape, and his ability to build a dramatic outline in which neither highlights nor shadows are ever saturated.

No matter how massive he builds the sound, there is still some in reserve even as the peaks are reached and recede. In my view this is Wagner of the highest order, no one can hear it without being moved.

Flagstad's contribution is on an equal plane, although there are spots where her voice shows signs of its decline.

The recording has emphasised the blending and weight of the orchestra, as is proper, but in the things that matter, the sonorous strings and eloquent brass, it is strong and effective. The slight surface rustle is quite lost behind it.

RACHMANINOFF — Concerto No. 2 in C Minor Opus 18. Preludes in G Major and G Minor. Played by Geza Anda, pianist, and the Philharmonia Orchestra, conducted by Alceo Galliera. Columbia 330CX1143.

In its own way this recording is no more or less successful than several others we have heard in the past 18 months.

It scores over the recent Farnardi record mainly on the score of pace. Farnardi (or Scherchen) dragged interminably — the more so on a second hearing. The new disc is more like that of Moura Lympany, but the recording is very much better. It would probably share with Cor de Groot the first place in a not very hot field.

The truth is none of the versions to date are good enough to reach the top line.

Most of them try to make too much of the music, without allowing it to set its own pace. Others use a too forward piano, which ruins the whole conception of the concerto. Anda does all of these things, the impression being that he has not yet evolved consistently in what he is trying to do. As a result I tended to lose interest between his frequent spells of very nice playing. And for the most part the orchestra didn't impress me as being very interested either.

Some day, a really outstanding record of this concerto will be made, and will I welcome it!

The two preludes are as good as anything on the record.

Surface noise is enough to be noticed on soft passages.

BRAHMS — Symphony No. 3 in F major Opus 90. Played by the Philharmonia Symphony Orchestra of New York conducted by Bruno Walter. Philips ABR4031.

Most people take a full 12-inch disc to accommodate this symphony,

but Bruno Walter does it on a 10-inch.

Some of the compression is probably due to careful micro-grading. But a good deal of it is the result of a pretty brisk pace which is held throughout, and which I'd say is on the verge of being too fast.

I'm not one for dragging things as a rule — I'd always like a little extra pace as against a dool, but this symphony I think gains by being unhurried.

There isn't any reason in the music or elsewhere to take it fast — this is music which stands to make its own pace, and which shows up a false tempo quite smartly.

Bruno Walter gave me the impression that he had an urgent date with the end of the record. Perhaps he had.

Something between this and Karlo Bohm on his Decca release would have done me very nicely. Bohm's is good, but Walter has the firmer outlines.

The recording hasn't got nearly the open sound of the Decca, but of its type it is very good. The tone is round and the colors have an authentic glow. The surface is noiseless.

If it's not too fast for you, I'd say this is perhaps the bargain of the month.

WAGNER — Tannhauser Overture and Venusberg Music: Prelude and Liebestod from Tristan and Isolde. Played by the Philharmonia Orchestra conducted by Paul Kletzki. Columbia 330CX1129.

These long excerpts from Wagner can be frankly dreary and shapeless things unless tied together by a conductor whose sense of form and judgment of dynamics is impeccable, and who, in addition, has steeped himself in the story and mood of the music.

Obviously Kletzki is one of the latter, for his performance, particularly of the Prelude and Liebestod, is to my mind near perfection.

There is a real emotional tug in his handling of the mounting tension, and authentic rapture in the impassioned climax. His sense of timing and his shaping of the musical line create a glowing surge of color which builds conviction into what is so often merely melodrama.

I thought this the most impressive side, although the excerpts from Tannhauser are of similar quality. The Philharmonia is in first rate form.

This is really good Wagner, beautifully recorded, if you are looking for it.

HANDEL — Water Music (complete) played by the Boyd Neel Orchestra conducted by Boyd Neel. Decca LXT2988.

The Boyd Neel in my mind has always been associated with authentic and impeccable playing, and we have certainly heard enough from it in the past to justify this impression.

I was therefore surprised, and not pleasantly, to note a far from impeccable performance of the Water Music on this disc.

The recording itself has the finely etched outlines that Decca can give us, which expose with a merciless eye any fall from grace.

We can't miss, I am afraid, some sloppy and badly synchronised playing which occurs in the very first

sections of the suite and which don't noticeably improve as we go on. The horns have a prominent and vital part in this music, but the players here often disgrace themselves in a manner which even the unpractised ear will reject.

Nor has the playing the flexibility and grace the music demands. It's a school-masterish hand which doesn't sit at all easily.

No greater contrast could be imagined with the famous Harty records of earlier days from which so much of our listening standards flow. I think we can do better than this.

OFFENBACH — Overtures, Orpheus in Hades; La Belle Helene. Played by the Los Angeles Philharmonic Orchestra conducted by Alfred Wallenstein. Festival-Decca CFR10-716.

A lively, clean, studio-type performance of two tuneful Offenbach overtures.

The studio is bright although without much echo. This tends to make the tone sound a bit shallow, particularly as the microphone placement isn't really close. The net effect, although by no means unpleasant, is what is often called "dry" as against the rounded sound of a bigger, more resonant chamber. The frequency range isn't extreme, although the cymbals and so forth ring out impressively enough.

An attractive disc which should sound well on any instrument. A good surface.

VERDI—La Traviata, Opera for Orchestra, played by Andre Kostelanetz and his Orchestra. Philips N02108.

Operatic arrangements for orchestra by no means a novelty but I don't remember having heard virtually a complete opera treated in this way before.

Assuming that you have no objections to the practice—and with an opera so filled with good tunes as Traviata I don't think you will—you'll enjoy this record.

It is played in quite a straight style—none of the tricks that go with many popular orchestrations of the day. Kostelanetz has made a serious attempt to keep the mood of each number strictly in sequence and in style.

The high pressure strings, particularly in representing the heart-broken Violetta in the last act, I found overpowering at times, but they certainly get the effect.

Some lovely cello playing, and recording, should be noted in Di Provenza, and in several other parts appropriately pitched.

The recording isn't wide range, but with such a silent surface I found the AES curve brightened it rather more than the EMI for which it was probably designed. The orchestra is forward and there is some very nice bass here and there.

Of its kind a good disc. An excellent Christmas present for someone who likes a good tune, and if it comes to that, don't we all?

GERSHWIN—Porgy and Bess. Tchaikowsky—Pique Dame, an Opera for Orchestra. Played by the Philharmonic Symphony Orchestra of New York conducted by Andre Kostelanetz. Philips N02111L.

My main impression of this record

is that it makes a great deal of rich sound out of a background which has no scratch, no clicks, no hum, no nothing.

It has in addition a remarkably wide dynamic range, and this gives great force to the sudden dramatic changes which occur on both sides.

On both, too, there is plenty of free and vigorous scoring, sudden plunges of brass, upsurgings of strings and a mighty lot of weight when everything gets going at once.

It is this sense of restrained power about it which will undoubtedly impress you.

I thought the reverberation of the studio a bit more than desirable. This gives nice, airy sound, but it tends to make some of the instruments sound a "bit near the back".

The Porgy and Bess is a free and tuneful arrangement by Robert Russell Bennett, and naturally features all the main hits from the opera.

Pique Dame is a companion "Opera for Orchestra" to the Traviata record also reviewed here, and, if anything, it is even more successful.

It exploits the spectacular music with disarming frankness, introducing each mood with a capital letter, and making a very good fist of it.

Of its type, this record, like its predecessor, is in the top bracket. Once again the AES curve sounds best.

HANDEL—Arias and Choruses from the Messiah, with George Maran (tenor), Jennifer Vyvyan (soprano), Norma Proctor (contralto), and Owen Brannigan (bass), with the London Philharmonic Choir and Orchestra conducted by Sir Adrian Boult. Decca LXT2989.

Not everyone is in the market for a complete recording of the Messiah, although for my part I must admit that, with the quality of recordings now available, I find it much easier to listen to and enjoy a full performance (time permitting) than ever before.

It is filled with magnificent music. As pointed out on the jacket of this disc, the Messiah lends itself to an abridged version much better than many other works. Consequently I find no difficulty at all in accepting the condensation represented by this release.

The excerpts are taken from Decca's full length recording, which was issued last year, and which is probably the finest of them all.

The soloists are all good. The chorus sounds rather restrained, and hasn't the full weight of a big choir of the type we generally hear in Australian performances.

But it certainly makes up in quality what it lacks in size. The truth probably is that today's heavyweights are less authentic than these more modest numbers, and Decca went to some trouble to reproduce the original intent on these records.

Best of all, there is no sign of distress or distortion such as so often overtakes recorded choirs, particularly when they sing all out.


At no time does this one reach full pressure.

In For Unto Us a Child is Born, we might miss the full emotional power of the cry, "Wonderful" as I have heard it done, but in quality, diction and every other requirement we gain by the restraint.

AWA

RONETTE

MICROPHONES & ACCESSORIES

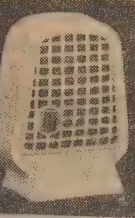

Type 44


Price

£3/19/-

Hand or desk mounting, counter balanced base, ivory plastic housing.

NICHOLSONS LTD.

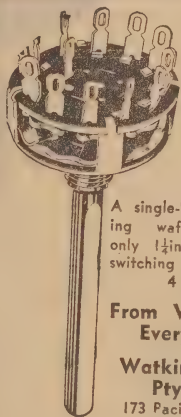BARRACK ST., PERTH and leading wholesalers



JABEL

Rotary wafer

SWITCH

A single-bank, space-saving wafer-type switch, only 1 1/4 in dia. Provides switching for 1, 2, 3, or 4 circuits.

From Wholesalers Everywhere!

Watkin Wynne Pty. Ltd. 173 Pacific Highway, North Sydney.

SAVE £££'S On Car Welding

with your own Electric Welding Kit. Just connect it to a 6 or 12 volt car battery and weld that job in a jiffy. 101 uses. Welds cracks and holes in car bodies, mudguards, radiators, silencers, water tanks, roofing, radio chassis, sheet metal work, etc., etc. Solder and brazes, too. No previous welding experience necessary. You'll find it welds as easy as A.B.C. Do your own welding jobs, and get terrific savings. Send now for this complete welding kit, comprising a high-grade welding tool, earth cable, welding goggles, assortment of welding rods, brazing rods, fluxes, solder, electrodes and instruction book. Quickly pays for itself in time and money saved. This complete welding kit is yours for the amazingly low price of £8/8/-, post free. Money refund guarantee. Send your order at once. Hurry! Stocks are limited. Sorry, no C.O.D.'s.

Pacific Auto Supplies, Dept. 8-23, 47 McLeod Road, Carrum, Victoria.

Printed and published by Associated Newspapers Ltd., at the registered office of the company, 60-70 Elizabeth Street, Sydney, NSW.

And now...



HIGH STABILITY PRECISTORS

IRC High Stability Precistors are supplementary to the well-known range of IRC Metallised Resistors, and are ideally suited for applications where resistance stability over long periods is important. Under normal load conditions it can be expected that the resistance change in value will be less than 1% over life. **A range is now available from local production.**

APPLICATIONS: IRC High Stability Precistors are particularly recommended for:

1. Circuits in which the characteristics of carbon composition resistors are unsuitable, and wire-wound precision resistors too expensive.
2. Metering and voltage divider circuit requiring high stability and close tolerance of the resistance values.

Type	Commercial Rating at 40° Ambient	Resistance Values	Length	Diameter	Maximum Working Voltage
DCC	$\frac{1}{2}$ -watt	75 ohms to 2 megs.	9/16"	5/32"	350
DCF	1-watt	150 ohms to 3 megs.	29/32"	19/64"	500
DCH	2-watt	300 ohms to 5.1 megs.	2-1/16"	19/64"	750

TOLERANCE: Precistors are available in standard preferred values in 5%, and special tolerance of 2% and 1%.

VOLTAGE COEFFICIENT: Type DCC is less than 20 parts per million per volt. Types DCF, and DCH approximately 10 parts per million per volt.

TEMPERATURE COEFFICIENT: Between -0.02% and -0.08% per deg. C.

Write or phone your supplier for full details.

IDEALLY SUITED FOR
APPLICATIONS WHERE
RESISTANCE STABILITY
OVER LONG PERIODS
IS IMPORTANT

SOLE AGENTS FOR AUSTRALIA

Wm. J. McLELLAN & Co.
Pty. Ltd.

126 SUSSEX STREET, SYDNEY, N.S.W.
(50 yards north of King Street)

There is too much good work in his record to particularise—far better to judge for yourself. Note particularly the fine work of the harpichord.

The surface is beautifully clean.

WALDTEUFEL — Waltzes Estudiantina, Espana, Golden Rain and The Skaters. Played by the Philadelphia Orchestra, conducted by Eugene Ormandy. Philips SO6612R.

There's little doubt about the appeal of these Waltzes. Waldteufel was a contemporary of Strauss, and, like the famous master, he wrote large numbers of similar compositions.

In their own way, they are as successful and as well known as many of Johann's, and are often accepted as being among those written by him.

The recording is spacious, and, with a remote touch which gives rather an effective ballroom atmosphere.

On the EMI curve it sounds a little dull, so I switched to AES with good effect. This gave an extra touch to the top.

Once again, no surface noise.

A particularly smooth, bright disc—a real Philadelphia production.

CUSTOM RADIO SERVICE

MANUFACTURERS OF ELECTRONIC EQUIPMENT

Custom three speed record player, with built in three valve amplifier and speaker.

- "Collaro" three speed motor unit with turn over crystal pickup.
- Three valve amplifier, with built in speaker.
- Full tone and volume control.
- Expanded aluminium speaker grille.
- Attractive "Vynex" covered case in two tone brown and cream.
- Fully portable.
- 240 volt operated.



PRICE £25/5/-

RECORD CHANGERS ALL THREE SPEED

"VELVET ACTION" model N/C/	£15/10/-
"GARRARD" 110	£17/10/-
"COLLARO" RC/54	£18/10/-

All these changers have three speed turntable and turnover crystal pickup.

Use our mail order service for fast delivery.

No freight or packing charges if delivered in the eastern states. For fast return of your order please forward full address for parcel despatch

5 POWELL STREET, COOGEE. PHONE FX7829.

OUR NEXT ISSUE

OUR next big issue is due on sale, Friday, December 2.

Watch out for these features, which are now in the course of preparation:

- A detailed description of the audio mixing panel pictured elsewhere in this issue. The circuit can be followed in detail or readily adapted to meet a variety of requirements.
- More information on multiple loudspeaker systems, with emphasis on speakers of more modest design.
- A preliminary article by Reg Rawlings on the design of Vacuum-Tube Voltmeters. This will clear the way for the description of a companion instrument to our widely acclaimed audio generator.
- An "Argument" about electric organs. PLUS a variety of other features which are still in the Editorial "melting pot"!

Nixa continues to pile up its list of popular and special records, and some good ones have been received lately.

Volume A of "Jazz at the Philharmonic" was, of course, made at an original performance, and features Illinois Jacquet, Hank Jones, Bill Harris, drummer Jo Jones and others, tied together in the atmosphere of Carnegie Hall. It's a Clef original. Another good Clef is supplied by sax player Lester Young, who performs the extraordinary feat, according to Norman Granz' jacket note, of exhibiting a "coolness" with heat behind it. You can check this up by asking for MGC-124.

On MGC-120 Clef is Count Basie with eight numbers, the first LP of his latest recordings. And a Cook original comes eight by Lizzy Miles, with Sam DeKemel with typically vivid sound.

BOOKS RADIO-TV ELECTRONICS AND ELECTRONIC MUSIC

We are now holding large stocks of the following books:

Practical TV Aerial Manual—by R. Laidlaw	Price 6/9
Television Test Equipment—by E. N. Bradley	Price 7/6
Simple Electronic Musical Instruments for the Constructor—by Alan Douglas	Price 7/6

Elementary maths, for wireless operators . . . sold as a pair, only Price 6/6

Definitions and formulae for radio and TV students . . . Price 18/9

"A FIRST COURSE IN WIRELESS"—by "Deibel" (Published by Sir Isaac Pitman & Sons Ltd, London) . . . Price 18/9
This is probably the best known book on the principles of radio for the beginner. It is simply written—without complicated mathematics—and, going right from the start, takes the reader through to the stage of explaining such things as AVC, negative feedback and push-pull circuits. This is the 1955 reprinting, and we can wholeheartedly recommend it to anyone wanting a good grounding in radio and TV.

PLEASE NOTE: We NEVER charge postage—either directly or indirectly—and all our books are offered at the fixed Australian prices.

BOOKS ON ELECTRONIC MUSICAL INSTRUMENTS

Send for our catalogue which gives details of what is the largest range in the Empire. Any book will be more fully described, by letter, on request.
"The Electronic Musical Instrument Manual"—by Alan Douglas . . . Price 45/-
"Electronic Organs"—by Robert L. Eby . . . Price 68/-
Coming publications—

"Electronic musical instruments", "Build your own Hammond-style organ" and "Build yourself an organ". This latter book describes the engineering and construction of our electronic organ kit-set, which will be available at a later date. . . If you are interested in this project, let us have your name and address, in order that you may receive full details when ready.

SEE ALSO OUR ADVERTISEMENT ON PAGE 87

Please make cheques, money orders and postal notes payable to the Company. Address all correspondence to—

Publications Division.
THE ELECTRONIC ORGAN COMPANY (AUSTRALIA)
9-11 CADOW STREET, PYMBLE, N.S.W.

SEND FOR OUR CATALOGUE (POST FREE) AND HAVE YOUR NAME PLACED ON OUR MAILING LIST.

There are 48 PAGES of real life stories in **PEOPLE**!

SHORT-WAVE TESTS BY AIR CUSHEN

RAPID EXPANSION OF RADIO PAKISTAN

Though it has only been in operation seven short years, Radio Pakistan has made rapid strides and now broadcasts 96 program hours daily.

ESTABLISHED with the head offices at Broadcasting House 71 Garden Rd., Karachi, Radio Pakistan first commenced broadcasting on August 14, 1947, and now has over 10-million home and many thousands of overseas listeners. Broadcasting House in Karachi was opened on July 16, 1951. The building contains 14 studios which are air conditioned, and eight booths embodying the latest sound equipment and studio devices.

SEVEN TRANSMITTERS

Radio Pakistan, a State monopoly, has now emerged as a compact and full-fledged national broadcasting organisation. Directors of External Services, Monitoring, Music, Research, Installation, and Maintenance, are located at Karachi, while news directors are at Lahore, Rawalpindi, Peshawar, and Dacca. A network of seven stations are located at Karachi, Lahore, Rawalpindi, Peshawar, Dacca, Rajshahi and Chittagong, on the broadcast band, and Karachi, Lahore and Dacca on short wave. The high powered Karachi station provides a national link with all zonal stations for broadcasts of national programs and centralised news in English, Urdu, Bengali, Pushto, Baluchi and Kashmiri languages.

SHORT WAVE SERVICE

The high powered stations at Karachi also carry the voices of Pakistan to foreign countries, through seven external services, one each in Arabic, Afghan-Persian, Iranian, Burmese, and Gukrati. Two services in English are also presented, and the total duration of these broadcasts come to 4 hours 50 minutes each day. To this must be added the musical transmissions, which take a further 5 hours and broadcast to the United Kingdom, Turkey, Indonesia, South Asia and South East Asia. The linking of East and West Pakistan is made possible by a short wave link and a teleprinter service between Peshawar, Rawalpindi, Lahore and Karachi. Six language publications are printed fortnightly in Urdu, English, and other local languages. Radio Pakistan now broadcasts some 96 hours each day as against 26 when first inaugurated. Pakistan operates two time zones, Eastern Pakistan (Dacca) is 4 hours behind Eastern Australian, and West Pakistan (Karachi) 5 hours behind.

The short wave transmitters have a combined power of 175 Kw with the main transmitters at Karachi. Karachi—2 is 50 Kw, Karachi—3 50 Kw, Karachi—4 10 Kw, Lahore—2 1 Kw, Dacca—7 5 Kw.

TIME STATION CHU

REPORTED recently as being received by readers in Australia and New Zealand, our verification from CHU Dominion Observatory, Ottawa, Canada, indicates that the station first commenced broadcasting on January 1, 1955, and as well as being heard in this area has also been heard in Europe and throughout North America.

CHU Ottawa broadcasts on the three observatory transmitters and are on the air continuously with broadcasts on 3330 Kc 300 W, 7335 Kc 300 W and 14870 Kc 300 W. The transmitters use a three wired folded dipole antenna, on each frequency. The observatory point out that the transmitter frequencies are not to be considered as frequency standards. The musical pitch of 1000 cycles per second, which is characteristic of these signals, is derived from the transmitting quartz clock.

TIME ANNOUNCEMENTS

THE announcements which are given in speech each minute are obtained from

either one of two machines constructed in France. The voice is produced from sound track cut from 35 mm film, mounted in grooves on a drum which is revolved at 30 rpm by a synchronous motor. The transmission consists of ticks, each one being 0.25 second duration and the beats are correct to better than 1000th of a second. The voice announcement is given between 50 and 59 seconds past each minute, and consists of the announcement of the time in Eastern Standard Time, a 24-hour clock being used, "Dominion Observatory, Canada, Eastern Standard Time, hours minutes" is the type of announcement used.

The signal is relayed by stations of the Canadian Broadcasting Corporation over a network of over 60 stations, while the service is also used by telegraph stations.

The verification from Malcolm M. Thomson, of CHU is two interesting pamphlets on the station, and he appreciates reports which are valuable to them to determine the range and usefulness of the CHU time signal. The return postage was returned by the station, and they hope that CHU will provide a service for listeners in this area in determining the correct time, which is so essential in the hobby.

WBOU REPLACES WNBC

AS we go to press we have heard a new call sign, WBOU, which appears to have replaced WNBC. Announcing on three frequencies, all of which were heard on different programs, the calls were given as "This is Voice of America station WBOU, Bound Brook, New Jersey, operated by the National Broadcasting Company, New York." Two transmitters have been heard from 4.30 a.m. to 8.45 a.m. on 15440 and 15150 Kc with broadcasts of the Armed Forces Radio and Television Service, New York, beamed to Europe. The other transmitter on 11870 Kc has the VOA broadcast in Russian from 7.15 to 7.45 a.m. and the same identification is given. Formerly W3XL and more recently WNBC, the signals have shown a marked power increase. WNBC and other short wave transmitters use a call sign which was formerly held by NBC key station in New York, which operates on 660 Kc. Some months ago this became WRCA and the shortwave station took the call of WNBC. As it is common practice for the four American networks to use the network letters in the call sign, such as WCBS, WABC, there is every possibility that shortwave station WNBC has also a new call sign.

FLASHES FROM EVERYWHERE

NAURU ISLAND The Australian Territory on the Equator is expected to commence operating a low powered broadcasting station in mid 1956. Like many others of the Pacific Islands a low frequency is expected to be used, and one in the vicinity of 2000 Kc will probably be the first to be given an experimental trial.

ROME'S 13 metre outlet, provides good signals on the band with a broadcast of English news at 8.40 pm, while previous sessions include Indonesian to 7.50 pm followed by French. The 16 metre transmitter on 17770 Kc also carries these broadcasts.

RADIO AUSTRALIA now broadcasts the DX session at 2.00 pm on 15200 Kc to North America, 5.30 pm on 18000 Kc to Africa, 6.44 pm on 17790 Kc to United Kingdom, and Europe South and South East Asia, on Sundays. The session at 2.15 am on Sundays on 1220 Kc, 11900 Kc to South and South East Asia and Europe.

KENYA'S Forces Broadcasting Service which has played such an important part for troop entertainment during the recent emergency, has commenced using two new frequencies, reports World Broadcasting Service No. 2, and with the mailing address of Post Office 10, Nairobi, the station is at present operating as follows: 1.00-3.00 pm and 7.00 pm-6.00 am on 5934 Kc with 250 watts, while the same power is radiated on 9112 Kc, this transmitter being on the air from 2.00 pm-6.00 am.

PEIPING has introduced a second home program, and this is currently heard on the following: 7.00-8.00 am on 6790, 6810, 6890, 6937, 6970, 7485, 7770, 8.15-11.00 am on 9170, 9330, 9390, 9460, 11.00, 11515, 11600, 12.50-4.00 pm on 11100, 11515, 11600, 15465, 15590, 15710, 15880, and 6.50-10.00 pm on the frequencies listed at 8.15 am, 10.10 midnight on 7370, 7485, 7770, 9170, 9330, 9390, 9460 Kc. The interval signal is played at the beginning of each period.

These notes are compiled by Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are Eastern Australian.

EGYPT'S overseas transmissions now embrace all continents, and the latest schedule shows the introduction of a service from Cairo to North America. The Egyptian Forces Radio is operating as follows, Arabic to Middle East, 5.00 pm on 7050 12030 Kc, 2.30-3.29 am on 11670, 5.00-7.00 pm on 9795 (new frequency), 9.00-9.55 pm on 7050, 12030, 10.00-11.00 pm on 9795, 10.00 pm-2.28 am, 7050, 12030, 12.45-3.52 am on 9790, 3.00-6.59 am on 7050 and 12030 Kc, 4.00-8.00 am on 9790, 11670 Kc. Broadcasts in Hebrew, 2.45-3.00 am on 7050, 12030, Swahili, 2.45-3.00 am on 17765, South East Asia transmission is broadcast 9.30 pm-12.30 am on 17765 (this consists of Indonesian 9.30 pm, Arabic 10.30 pm, English 11.00 pm, Urdu 11.30 pm, To Western Asia, Persian 1.00-2.00 am on 9475, 4.00-8.00 am on 9475 (Italian 4.00 am, English 5.00 am, French 6.00 am), to South America 9.30-11.30 am on 11670 (Portuguese 9.30 am, Arabic 10.00 am, Spanish 11.00 am). To North America in Arabic only on 9790 Kc 10.00-11.00 am.

ITALIAN SOMALILAND which is seldom reported in this area these days is now using a more powerful transmitter, and broadcasts from Mogadiscio. The station uses 7072 Kc 300 W and 4978 Kc 4000 W daily as follows, Somali 7.30-8.00 pm, Italian 8.00-8.45 pm on 7072, 11.30 pm-1.00 am, 2.00-3.00 am in Somali 300-4.00 am in Italian on 4978 and 7072 Kc.

A standard procedure has been inaugurated for the use of NSW radio amateurs operating in Emergency Nets. It should allow the most effective working of these nets and ensure the maximum benefit to the community in times of flood and bushfire.

UHF IN THE WEST

THE Council of the NSW Division of the WIA have set up a series of rules for the guidance of radio amateurs during emergencies.

The rules lay down the standard procedure for operation in official WIA nets with VK2WI.

The first action of any amateur is to advise VK2WI (MU1092, MU1879) that an emergency is developing, and that he is about to, or has, offered his services as a member of the WIA Emergency Net to the district control officer of the State Emergency Services.

If no such officer has been appointed in the area, his services should be offered to the senior police officer.

Amateurs should advise the officer that the WIA net has been alerted and he is in a position to handle traffic to VK2WI in Sydney, or if in the Hunter Valley to K2AWX official station of the Hunter branch of the WIA.

Other stations in the affected area should report in to VK2WI for instructions in the event of being required to handle traffic in other nets such as to VK2AA official PMG station.

All messages from an emergency area must be authorised by the officer appointed by the State Emergency Controller or by the police officer in charge of the area. Service traffic handled will be authorised by the senior army, air force, or naval officer.

Amateur stations adjacent to the emergency area are requested to report to VK2WI in case their services are required.

Official VK2WI frequencies will be 560 and 3575 kc/s and VK2AWX as arranged. These frequencies have been selected after careful checking with amateurs in all areas likely to be affected by floods to ensure no harmonics from V and other stations will cause serious interference.

Until definite procedure for message handling is laid down by the combined services, Police Dept., and WIA &c, the Council recommends the adoption of the MG's Department's Telegraph procedure.

VHF links are recommended for contacts between stations in any area. The vision would also appreciate early requests for equipment and personnel if they are likely to be required.

It is anticipated that all amateurs will fully support the official WIA nets and so ensure that the movement will receive a maximum recognition for their work in these emergencies.

the array would stay in one piece. The message reached them but could not be passed further north. Their only contact was with Peter Adams, VK2JX, at Wentworth Falls in the Blue Mountains, over a distance of 265 miles. Roy Berry VK2NY at Grafton some 75 miles away was heard at 89.

VK2ZAR journeyed to Sojala on the highlands over a terrific road but returned when the weather deteriorated. VK2AWZ was located at Mt. Tomah but also unable to man the highest point and transmissions were restricted.

The weather appeared to affect conditions and VK2WH of Forbes who operated all day only, he, VK2ANF of Sydney for a short period.

Also in the field were VK2AZO and VK2ATO at Hassen Walls, VK2LG at the Libby, VK2HL at Razor Back and VK2ANU at Murrumbidgee. Other stations were active from their own QTH's. The total number of contacts made were small and paths normally covered were not open, the weather certainly affected the overall success of the day. VK2WI was manned by Bob Winch VK2OA for the field day.

WOY WOY TO COME

An extensive program has been arranged for the NSW Division's Annual Woy Woy Field Day and those attending are assured of an interesting day.

Attendances since the event's inauguration have always exceeded 200 and this year's event should be well supported.

Assembly will be held at the Masonic Hall Woy Woy, the date November 27 and registration will commence at 10.30 am.

The morning session comprising competitions will commence at 11 am and an all-band scramble will be conducted from 11.45 to 12.30. The lunch break will be from 1 to 2 pm. At 2 pm searchers will leave on the 144 Mc/s hidden transmitter search. The transmitter will operate until 3.15 pm. Special events will be conducted from 2 pm for the ladies and the juniors.

The general reunion and prize presentation will be held from 4 to 5 pm. Make Woy Woy the location for your Sunday outing, the field day is an excellent opportunity to show your wife the social side of amateur radio, there will be dozens of prizes for all attending.

NEXT WORLD CONFERENCE

It appears that the next full scale International Telecommunications Conference will probably take place at Geneva in 1957, when frequency allocations throughout the radio spectrum will again be reviewed.

Prior to this meeting in August 1956, the Technical Convention will be held at Warsaw. Amateur Radio Societies in Region 1 (Europe and Africa) have decided to hold an International Amateur Radio Union Region 1 Conference in Italy early in 1956.

It is hoped at this meeting to discuss all aspects of amateur radio organisation and to obtain ideas of effective action to be taken at the forthcoming international conferences. The question of direct amateur radio representation at both these international conferences will be discussed as it is considered by the RSGB that such action is desirable as proved when RSGB delegates represented amateurs at the 1947 Atlantic City ITU conference.

The activities of the Region 1 Bureau of the IARU are financed from contributions from all national societies in the region and excellent liaison will be maintained all the varied amateur movements.

The Italian Society (ARI) have offered to act as hosts, the selected venue Como, and it is anticipated that many European and African societies will be represented to plan for the future of amateur radio.

The last meeting of the VHF group was held at the residence of Don VK6ZAV. The usual large gathering was present. The growth of the group has been remarkable in the six months of its existence. Very soon we will have to hire a hall to accommodate the numbers.

Frank VK6CC gave an interesting lecture about the effect of moisture on receiving equipment illustrating his talk with his experiences in the tropics and in eastern States.

The remarkable improvement in the sensitivity of AR8 receivers from 10 microvolts to less than 1 microvolt by merely heating the receiver in an oven was a graphic illustration of how much loss can result from a humid atmosphere.

The November meeting of the group is to take the form of our first fox hunt. Those without mobile gear should make a determined attempt to assemble some sort of receiver and antenna for the event.

The following are believed to be the VHF records in the West:

50 Mc/s: VK6HK/VR2CG, date 3/1/55, distance 3928 miles.
144 Mc/s: VK6BO/VK5GL, 3/1/51, 144 Mc/s: VK6BO/VK5GL, 9/2/52, and VK6BO/VK5QR 9/2/52, all over a distance of 1328 miles. The world record is 1400 miles, 288 Mc/s: VK6BQ/P to VK6DW/P, 1949, 25 miles.

Any claims for recognition for greater distances should be made to Stan Stewart, VK6ZAS, 95 Railway Pde., Mt. Lawley, W.A.

The above notes were contributed by Wally Howse, VK6ZAA.

ROSS HULL CONTEST

It is intended to extend the frequency range of operation in this year's Ross A. Hull Memorial Trophy Contest in accordance with the previous decision at a previous Federal Convention of the WIA. To date the contest covered the 50 Mc band only. It is anticipated the contest will now include the 50, 56, 144 and 288 Mc/s bands. VHF amateurs here are divided on the extension of the range of the contest in view of experience gained since the convention decision.

Seventy-eight members and visitors attended the September general meeting of the NSW division of the WIA when Mr. E. Stern, of the Civil Aviation Department, lectured on the Instrument Landing System in use at Mascot. The lecture was enjoyed by those attending as evidenced during a 30 minute question time.

Considerable discussion was also centred around the future plans for the setting up of a permanent HQ for the division and the possibility of establishing of VK2WI at a point distant from the city.

This would allow effective transmissions to be carried out with higher power on the lower HF bands.

SOUTH-WEST CONVENTION

The South-Western Zone's Convention held at Albany was extremely successful and some 70 amateur XYL's and YL's were in attendance. Visitors from Sydney, Melbourne, Bendigo, Cobram and Wollongong were in evidence.

The convention was officially opened by the Mayor of Albany Ald. C. E. Buntton OBE, who welcomed the visitors to Albany. He was introduced by the chairman zone officer Jim Edge VK2AJQ, Jim Corbin MBE, VK2YC, president of the NSW division responded on behalf of the members of the WIA.

A full program was arranged varying from a visit to the Hume Weir, an official dinner, field events, musical quiz, pick-a-box, &c.

HF ON LABOR DAY

The Labor Day holiday week, the first October, is always a busy period for amateurs in NSW. Three major events are held over the week-end. The South-eastern Zone's Convention, the VHF Section's Spring 144 Mc Field Day and the Hunter Branch's Picnic held at Ackalls. These events are always well supported.

The weather was not very pleasant during the week-end and had serious repercussions on the VHF Section's 144 Mc Field Day.

High winds on Sunday October 2 reaching 60 mph hindered parties from reaching elevated spots and prevented some parties from venturing out.

The object of the event was to relay a message from VK2WI to Brisbane on 144 Mc/s.

A vital link in the north at Mt. Ebor from Armidale was again manned by Roy Hart, VK2HO, and Perc Healy, VK2AF who journeyed from Sydney.

They found it impossible to operate from the higher point due to the gale. Sheltered by trees they were able to work from the car at a position down from the peak. How then it was dubious how long

ZEPHYR "90" SERIES DYNAMIC MICROPHONES





Australian manufacture throughout.

Designed especially for both wire and tape recorders, schools and P.A. work. Precision built Moving Coil generator provides high quality reproduction, will withstand rough usage.

Modern appearance, extreme sensitivity at low cost. Not adversely affected by temperature or humidity changes.

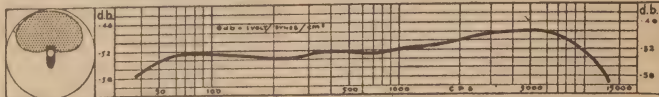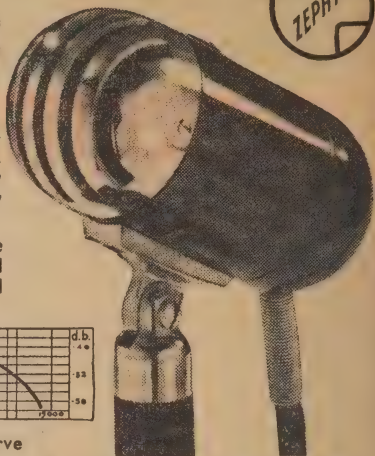Lightweight, durable chrome and baked enamel metal case and swivel with full tilting head.



Pick-up Pattern

Approximate Frequency Response Curve

Model 90MA GRID-90MB 500 ohms-90MC 200 ohms £11/6/3, 90MD 50ohms £9/8/0 Retail

STOCKED BY LEADING WHOLESALE IN EACH STATE

IF UNABLE TO OBTAIN FROM YOUR DEALER WRITE DIRECT TO—

ZEPHYR PRODUCTS PTY. LTD.

Phone
BL1300

58 HIGH STREET, GLEN IRIS, S.E.6. VICTORIA

TRADE INQUIRIES INVITED FROM MANUFACTURERS AND WHOLESALE

SOLE DISTRIBUTORS OF ZEPHYR MANUFACTURES IN AUSTRALIA

ARE YOU CONSCIOUS of your INNER-CONSCIOUSNESS?

There exists a wealth of infinite knowledge just beyond the border of our daily thoughts which can be aroused and commanded at will. Telepathy, projection of thought, the materialising of ideas into helpful realities are no longer thought by intelligent persons to be impossible practices but, instead, *demonstrable sciences* by which a greater life of happiness may be had.

The Rosicrucian teachings enable intelligent men and women to benefit from their inner-consciousness.

You can learn how to direct your thought-energy towards a specific objective to produce positive results. Learn how to marshal your mental powers to improve your business and social career.

Dedicated to an inspiring object, the attainment of the universal Brotherhood of Mankind, the Rosicrucians are a Non-Political, Non-Profit Making Fraternity.

To absorb the Rosicrucian teachings, to harness your inner-most powers to direct benefit, you must approach this matter with a mind unfettered by prejudice or inhibitions. If you are confident that you have such an open-minded attitude you are invited to write for our free 32-page book "The Mastery of Life," From the inspired pages you will be given an insight into the advanced teachings of the Rosicrucians.

Scribe P.Z.B. The Rosicrucians (AMORC),
Box 3988, G.P.O., Sydney.

Please send me, without cost, the book "THE MASTERY OF LIFE".

NAME

ADDRESS

STATE

THE VK-ZL CONTEST

Radio amateurs enjoyed this year's VK/ZL DX contest run jointly by the WIA and NZART. Support for the contest was greatest for some time. Opening to the world on 21, 14 and 7 Mc/s reflected the great improvement in propagation conditions and some excellent scores will undoubtedly be recorded.

Morning conditions were interrupted on 7 Mc by extensive Russian amateur station activity. As noted last year, it appears that the Russians run a contest on the same week-end as the VK/ZL test. DX contests should again become popular as it is possible even with restricted operation to contact a host of stations.

The contest was conducted by the Federal Contest Committee currently located in South Australia and logs for the contest should be forwarded to reach the committee Box 1234K, GPO, Adelaide not later than October 31.

Commercial QRM on the exclusive amateur sector 7000 to 71000 Kc/s is undoubtedly on the increase but the effort of BAB/BAB2/BAB3/ Chinese Press station on 14 Mc/s is worth recording. In a long list of frequencies on which they operate they include 14140 Kc/s and they surely cause serious interference.

DX CONTEST

The WAE DX contest conducted in late September was well supported and afforded stations located in Europe an opportunity to work with stations in the other continents. It ran for two 48 hour periods, one for CW one for telephony. The regular openings now appearing to Europe gave VK stations many contacts on both 7 and 14 Mc/s over long periods.

The control of this contest is varied annually and rotated between the various national amateur radio societies in Europe.

This year's contest was organised by the German National Society the DARC. The RSGB Bulletin carries further news of proposed amateur radio activity on the Gough Island Scientific Expedition. D9AD should be in operation in mid-October. The equipment to be used by 33HPM includes a Panda 120V Transmitter, an Eddystone 680X receiver, six 150T sectional masts, 3000ft of various types of feeders and sufficient wire for a variety of antennas.

Operation will be on all bands covered by the transmitter including 1.7 Mc/s.

Likely emphasis will be on the 21 Mc/s and using both CW and telephony. It is hoped that the ARRL will recognise Gough Island as a separate country.

ZD9AD will not reply to calls within 0 Kc/s of his own frequency and stations who call when he is in contact with another station will be black-listed. QSL cards have already been printed and will be forwarded via the RSGB.

QSL Bureau incoming cards should be sent the same way.

It is anticipated the expedition will remain on the island for a period of six months.

Amateurs in the US have officially been co-opted to attend atomic tests at Yucca Flat. The NEC of the ARRL, emergency co-ordinator George Hart, VINJM, was requested to attend. Although no amateur frequencies were used during the tests, a considerable number of amateurs were included in the government emergency exercise group which was responsible for the communications of the test.

A.O.C.P. CLASS

The Victorian Division A.O.C.P. Class will commence on Thursday, November 17, 1955.

Morse and Regulations are held on Monday and Theory on Thursday evenings from 8 to 10 p.m. Persons desirous of being enrolled should communicate with the Secretary, W.I.A., Victorian Division, 191 Queen St., Melbourne.

Phone FJ6997 (from 10 a.m. to 4 p.m.), or the Class Manager on either of the above evenings.

VHF NEWS FROM N.S.W. DIVISION

The attendance of the October meeting of the NSW Division's VHF section reached an all time high when Mr. R. Mondel of the NSW Technical Education Department recently returned from America lectured on TV and T.V.I. In a comprehensive review Mr. Mondel covered all aspects of TVI including many little known sources and told of his actual experiences in these matters. It was a lecture of considerable importance to members and gave a further insight into possible problems ahead.

Visitors to the meeting included well known country VHF amateurs Keith Dodd, VK2ZAA, of Tumut and Stewart Savage, VK2PL, of Griffith.

The section will conduct their initial 144 Mc communication tests on October 16 with the Spelaological Society at Jenolan Caves and will check the value of radio as opposed to telephone contact in the society's work.

At the conclusion of the NSW Division's VHF section's Sunday evening broadcast over VK2VI a surprise 144 Mc scramble was announced. Commencing immediately at the conclusion of the broadcast it ran until 10 pm, approximately 21 hours. The winner of the event was Peter Adams, VK2XC, with 24 contacts, second place was filled by VK2ZAR, VK2LG, and VK2APQ all with 22 contacts and third VK2HE with 21 contacts.

BEAR HANDY TAPE

BRAND



MAKES 'HOME WORK' EASY

TAKE HOME A ROLL TO-DAY

LABELLING JARS AND BOTTLES

CAKE

SEALING CAKE TINS

MENDING BOOKS

COOK BOOK

LABELLING FOODSTUFFS FOR DEEP FREEZE



MASKING DOOR FRAMES

MASKING WINDOW PANES

TRIMMING SKIRTING

MASKING HANDLES AND POWER POINTS

MENDING BLINDS

SPICING HANDLES

BEAR HANDY TAPE HAS LIMITLESS USES




From attic to basement, from front porch to back door, you'll find countless uses for "BEAR" brand HANDY TAPE. Any professional painter or carpenter will tell you what a blessing it is to any handy man or woman.

Made by BEHR-MANNING (AUST.) PTY. LTD., LIDCOMBE, N.S.W.
Also Manufacturers of Bear Transparent Tape, High Quality Sandpapers and "Plookote".

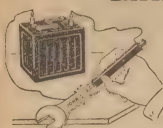Q18C

AT LAST THE ELECTRIC
ENGRAVER THAT WORKS OFF
ANY 6 OR 12 VOLT CAR
BATTERY



29/6

Complete
with
Instructions

Engrave your own tools, name
plates, dog collars, cutlery, watch
cases, cigarette cases, etc. Engraved
articles are never stolen.

Agents wanted for Interstate and
all Country Towns. Write for details

ENGLISH SMITH 8-DAY CLOCKS



As used
by the
R.A.F.

Luminous
Dial

£5/15/-

Makes
ideal
car clock.

Fitted with Sweep Second Hand.
Ideal for any car or truck.


24-VOLT MOTOR COMPLETE With Fuel Pump

Ideal for
Caravans.
Takes the
place of
Hand
Pumps.

£5
Each.



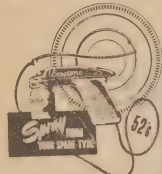Many uses
on the Farm.
Will Transfer
Petrol or
Any Liquid
from Drums,
etc.
Will work
from 24
or 32 volts
AC or DC.



**Spray YOUR CAR
TOYS, HOBBIES
FURNITURE**

52/6

Spray from your
Spare Tyre.
An Ideal Tool for
touching up
damaged
paintwork.
Will spray Lacquer,
Paint, Enamel.

ARMY SPOTTING TELESCOPES
Many uses on the farm. Ideal for
Sheep Spotting.



Useful on the rifle range, 3 draw
17in long, 6in closed, 1in object
lens, 18 magnification. **£7/19/6**
Made in England


AIR MIN MULTI TESTER

COMPLETE
WITH
TEST
PRODS
£5/17/6
TESTS
OHMS AND
VOLTS



Reads
0-10 Volts,
0-50 Volts,
0-250 Volts
Also
0-10,000
Ohms.

BALL AND SOCKET INSPECTION MIRRORS

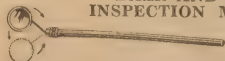

8/9


Ideal for mechanics, radio repairs.

LUCKY PURCHASE
GENUINE R.A.F.
RUBBER DINGHIES
BE EARLY. A FEW
ONLY.

£8/15/-

**BRAND NEW SURVEYOR OR
BUILDERS' DUMPY LEVELS**
Fitted with high class Telescopic
adjustable lever.

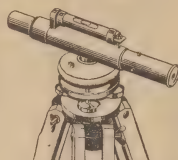All spare parts available.
Complete with wooden carrying
case and adjustable wooden tripod.



Never
before
at this
price

£36/10/-
complete.

STUDENTS' BRAND NEW MICROSCOPES

THE IDEAL XMAS GIFT

Not a toy.
A real
Microscope.
Hours of
enjoyment
for any boy
or girl
Student.



3 Turrets
3 Mag-
nifica-
tions.

£4/19/6

100, 200 and 300 times magnification

BINOCULARS, BRAND NEW. VERY POWERFUL.

Complete
in solid
pig-skin
leather
case.



£7/15/-

Fitted with High Class Ground Lenses.

BRAND NEW LEVER TYPE GREASE GUNS WORTH £4/19/6




47/6

Ideal for all types of Trucks,
Tractors or Cars, 7500lb pressure.

STEEL ARMY TANK AERIAL RODS WILL MAKE IDEAL RADIO AERIALS FOR CARS OR TRUCKS.

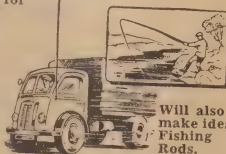Too long for
postage.
Advise
nearest
railway
station.
Bases
to suit
Aerials,
12/6
each.



Will also
make ideal
Fishing
Rods.

12ft long, 3 sections. Each section
4ft, 22/6. 8ft long, 2 sections, 15/-.

SURPLUS


512 Elizabeth St., Melbourne, C.I.

Phone: FJ5904. Just 4 doors

Mail Orders Carefully Packed
Please add Freight or Postage


Aircraft 24 volts Motor complete
with 400 gal. per hour Pump.

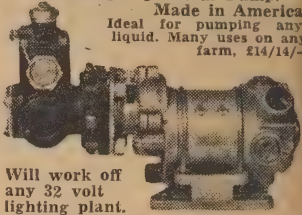Made in America.
Ideal for pumping any
liquid. Many uses on any
farm, £14/14/-



Will work off
any 32 volt
lighting plant.

Pump only, 55/-.

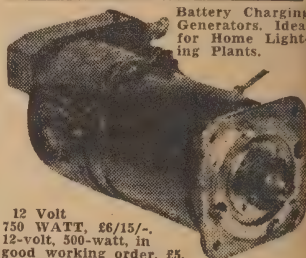

Battery Charging
Generators. Ideal
for Home Light-
ing Plants.


12 Volt
750 WATT, £8/15/-.
12-volt, 500-watt, in
good working order, £5.
24-volt, 1000-watt,
£9/10/-.
200 amp Generator, Ideal for
welding. Made in America.
Brand new £40

Replace those broken side curtains
with cellulose acetate which takes
the place of celluloid and lasts four
times longer. Will not discolor.
32/6
SHEET




Non-inflammable acetate sheet is
recommended for all types of side
curtains. Sheets are 20 thousandths
of 1 inch thick. Size of sheet, 24in
x 52in. Can be sewn or cemented
into frames.

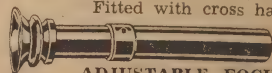ARMY FOCUSING TELESCOPE
Easily converted for use on dumpy
levels. Can be used as a rifle sight.
Excellent magnification . . £4/19/6
Fitted with cross hair.



ADJUSTABLE FOCUS.

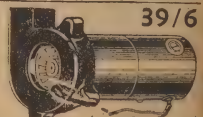English
Motor and
Blower,
24 volts.
Will work
off any
Lighting
Plant.



39/6

Large size also available that will
work off 12 or 24 volts, £3/15/-.

STORES

512 Elizabeth St., Melbourne, C.I.
from Victoria Street. Phone FJ5904.

and Efficiently Despatched
Include State in Address.

SPECIAL DISPOSALS METER OFFER

- 0-3 amp meters, AC-DC, 2 1/2 in dial 45/-
- 0/1 milliamp, 2 1/2 in dial 37/6
- Weston 0-50 volt 0-100 amps, combined M/coil, £3/10/-
- English 50-0-50 Ammeters, M/coil 37/6
- English 50-0 Ammeters, AC-DC 42/-
- English 0-40 Voltmeter, M/coil 25/-
- English 0-300 AC-DC Voltmeters 55/-
- English 0-5 Milliammeters, 2 1/2 in 37/6
- English 0-25 Ammeters, 2 1/2 in M/c 30/-
- English 0-10 Ammeters, 2 1/2 in dial, Moving Coil 45/-
- English 0-50 Voltmeters, 2 1/2 in dial, AC-DC 42/-
- English 0-40 Ammeters, 2 1/2 in dial, AC-DC 42/-
- English 0-30 Ammeters, 2 1/2 in dial, AC-DC 45/-
- English 0-14 amps AC-DC 4 1/2 in dial, 59/6
- ng. 0-20 amps, 2 1/2 in dial, M/C 25/-
- ng. 0-13 Milliamps, 2 1/2 in dial, M/c 19/6
- ng. 0-200 Ammeter, M/coil £4/10/-
- ng. 20-0-20 Ammeter, M/coil 37/6
- ng. 0-30 Amps AC-DC 2 1/2 in dial 42/-
- ng. 0-50 Amps AC-DC 3 1/2 in dial 75/-
- ng. 0-80 Amps AC-DC 3 1/2 in dial 75/-
- ng. 0-1 Amps DC 2 1/2 in dial 35/-
- ng. 200 Amps AC-DC 3 1/2 in £4/19/6
- ng. 0-5 Amps AC-DC 2 1/2 in 45/-

Now you can make your own music box with these Swiss music units. They can be fitted to any type of box, oil, jug, teddy bears, etc. Hours of enjoyment for all the family.



30/-

EACH

Tunes available, Lili Marlene, Jingle bells, Blue Danube, Harry Lime theme, Wedding March, The Merry Widow, Happy Birthday, Annie Laurie, How Dry We Are, Roll Out The Barrel, Silent Night, Teddy Bears' Picnic. Also available, a few only double units which play 2 tunes, 50/- each. Miniature Music Units fit cigarette case, Lady's Compact, etc. 39/6, also 230 volt music unit, works continuously, 59/6.

Not secondhand. BRAND NEW ENGLISH G.E.C. RECTIFIERS. Make yourself a Battery Charger 2v 2 amp... 32/6 5v 3 amp... 50/- 2v 3 amp... 45/- 5v 2 amp... 24/6 5v 4 amp... 45/- 2v 5 amp... 39/6 transformers to suit above Rectifiers. amps, 39/6; 6 volt, 5 amps, 45/-; 12 volt, amps, 55/-.

Brand New American Wobble Pump, semi-rotary



continuous flow. PHOSPHOR BRONZE VANES. Ideal for caravans, emptying or filling toilet tanks, water tanks, etc.

MECHANICS' STETHOSCOPES
Ideal for Testing Engines, etc.
Very sensitive

35/-

R.A.F. LEATHER FLYING HELMETS, 50/- each.

Intercommunication Tubes 50/-.

MK7 Goggles 37/6 Pair.
MK8 Goggles 48/6.

Wool Lined Flying Boots. £5/19/6 pr.

HUGE PURCHASE
Waterproof Flying Suits.
Special Price £4/7/6.

Dalton Computers in good working order, 50/-.

JUST ARRIVED

TELESCOPES

Latest Model, complete with Tripod

Achromatic Coated Lens. £9/15/-
Ideal for Rifle Shooters.
25 Magnifications.

At last the spotlight you have been waiting for.

Fitted with genuine American sealed beam globes. No motorist or boat owner should be without one. 6 Volt, 90/-; 12 Volt, 95/-.
Complete with Switch and Flex.

COMPLETE BATTERY CHARGER

Fitted with Brand New English Selenium Rectifier.

Works off 230V. Household Supply.

Charges any battery. 6 volts at 4 amps, £6/15/-, complete. Also available 6 or 12 volt Charger combined. Charges 4 amps, £7/15/-, Brand new 6 volt, 3 amp Chargers, complete, £5/15/-.

AMERICAN VACUUM or AIR PUMP

Builds up air pressure to 20lb at 1000 R.P.M. develops up to 120lb of hydraulic pressure; will pump 7 1/2 gallons S.A.E. oil or other liquids per minute. Useful for spraying, milking, presses, oil burners, hydraulic systems, £3/10/-.

ENGLISH ARMY SPOTLIGHTS

IDEAL FOR SHOOTING FIT ONE TO YOUR CAR.

6-volt, 37/6
12-volt, 25/-
Fitted with Mirror Reflector.

WATCHMAKERS and INSTRUMENT MAKERS

English Tweezers... 6/6 and 5/6
Eyeglasses... 6/6 and 8/6
Extra strong double lens Eyeglasses 15/-
Screwdrivers, set of five... 13/9

SPECIAL OFFERS FROM OUR MOTOR ACCESSORY DEPARTMENT

American Shrader tyre pumps, work from your spark plugs, 39/6. Car tyre fire extinguisher. Every car should carry one, Cost £7/10/-, £4/10/-.

Mechanics' steel tool boxes, 19/6. Brand new 7/8 in spark plugs, suit most old type cars, 2/6, or ideal for tractors. S.A.E. or Whit. Spanner Sets, open one end, ringed the other. 6 spanners to set, 23/6. Army steel tow ropes, looped ends, 17/6. S.A.E. open end spanners, 6 to set, 24/6. Whitworth, 4 to set, 18/6. Whit socket sets, 13/6 set. Mudguard type rear view mirror, 16/6. Inside car rear view mirrors, 4/11. S.A.E. socket sets, 15/-.

Engineer's pliers, 4/6. Car jacks, 37/6. Tyre levers, 3/10 each. Hydraulic 2-ton jacks, £4/15/-.

6-volt wind-screen wipers, £4/12/6. 12-volt £4/19/6. Car pumps, 14/-.

Shifting Spanners 4in 6/9; 6in 8/-; 8in 10/-; 10in, 11/-; 12in, 18/6. Metric Socket Set, complete with bar, 59/6. Feeler Gauges, 4/6. Tail Lights, 5/9; 12in Steel Rulers, 3/6. 6in, 2/6. Set of 3 Screwdrivers, 2/6. Hydrometers, 11/6. Piston Ring Compressors, 15/-.

Pressure Oil Cans 9/6. Combination Pliers, 5/6. Car Amp Meters, 15/6. 4 1/2 in saw blades complete with arbor, ideal for making saw bench with electric drill, 25/-.

Bell-ringing generators, ideal for telephones, 25/-.

German Army marching compasses, work similar to prismatic, 32/6. 110 volt 1000 watt projector globes, 32/6. 2in Black and Decker 230 volt electric drills, £11/15/-.

4in, £24/8/3. Magnifying Glasses, 8 mags., 8/6. 10 magnifications, 12/6. 24 volt motor and hydraulic pump, capacity 3 1/2 gals. per minute, £3/15/-.

New headphones suitable for crystal sets, 17/6 pair. Army Mosquito Nets, ideal camping, 27/6.

Tap-ped Transformers, 6, 12, 18 and 24 volts, 3 amps, 39/6. 230 volts in put 5 amps at above voltages also available 45/- each.

Brand new American Cutting and Welding Torches £4/4/- complete.

Army Slouch Hats in good order, 19/6. Generator Test Meters, 35-0-35 amp meters, 4 1/2 in dial, 45/-.

0-10 volt meters, 4 1/2 in dial, 45/-.

Loading Resistors can be supplied to make meters read 10.20 at 12/6. Medical Scalpels, many uses, photographers, etc., 6/6.

A COURSE IN TELEVISION

(Continued from Page 95)

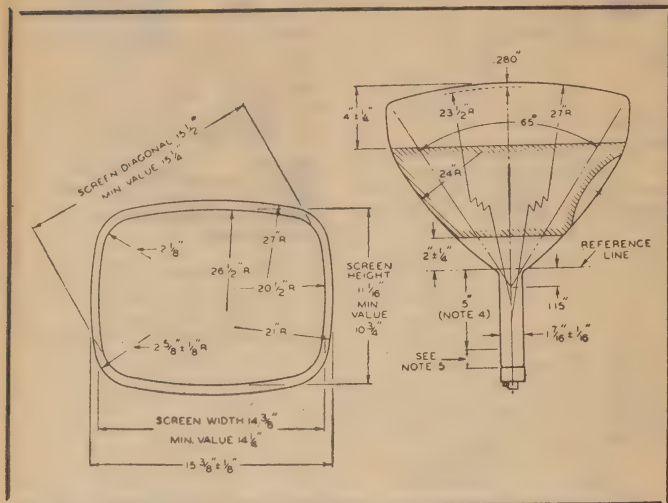


Figure 22: This diagram gives the essential dimensions of the 17BP4-A picture tube (or "kinescope"). It is one of the types scheduled for local production. Prototypes have already been assembled and demonstrated.

or a wholly electromagnetic controlled beam, it would be possible to combine the principles so that a particular tube may have electrostatic focus and electromagnetic deflection—or even the reverse! This is purely a matter of tube design.

To date, practically all television picture tubes have used magnetic deflection. The main reason for this is that the magnetic system is capable of deflecting the beam through much greater angles without loss of focus. As a result, picture tubes can be made with large screens without, at the same time, being prohibitively long.

Magnetic focusing has commonly been used, more or less to be consistent with magnetic deflection. A great deal of development has gone into focus and deflection coils and modern types using ferrous cores are far more efficient than the earlier open style windings.

We shall have more to say about these items in a later article.

OVERSEAS TREND

In the meantime, there is an evident trend overseas toward tubes employing electrostatic focus and electromagnetic deflection. Special proportioning of the electrodes makes the focus so non-critical that the need for a focus control has been eliminated altogether. The various anodes are simply connected to a predetermined divider network across the EHT supply.

It seems doubtful at the moment whether such tubes will go into immediate use in this country, the present intention of manufacturers being to standardise on conventional magnetic-focus and deflection tubes with a 17in rectangular screen.

This measurement, by the way, is an overall diagonal one, corresponding to the diameter of a round-face tube necessary to produce the same-sized image. Dimensions of a typical "17in" picture tube, the 17BP4-A, are shown in figure 22. As a matter of interest, the weight of this tube is about 25lb.

Such conventional 17in tubes are available overseas in a variety of brands and are scheduled for production in local valve factories under the appropriate type numbers.

HIGH VOLTAGES

In service, these tubes typically require an EHT (Extra High Tension) supply of between 14,000 and 18,000 volts.

As might be imagined, the generation, distribution and control of such voltages call for considerable care in receiver design, not to mention the safety factor in relation to those who have to build, service and operate the equipment.

Even apart from the problem of high voltages, large screen tubes have to be very carefully constructed to withstand air pressure on the envelope.

The total pressure on the screen of a large picture tube can be reckoned in tons and an undetected flaw in the glass could easily cause it to collapse. The resulting "implosion" could hurl fragments of metal and glass over considerable distances and cause severe injury to anyone in the vicinity.

In any case, large picture tubes must always be handled carefully, to avoid jarring or scratching.

Various applications of cathode ray tubes have led to the development of screen materials having a

variety of color and persistence characteristics.

By way of example, American CR tubes carry a phosphor number associated with their type designation.

To quote the most popular ones, "P-1" indicates a green, medium-persistence screen, especially suited for use in a cathode ray oscillograph. "P-5" is a blue screen with very short persistence; while "P-11" is of similar color, but simply designated "short persistence". "P-7" is a cascade phosphor showing an initial blue color, which fades to a greenish-yellow, long-persistence trace.

Most cathode-ray tubes intended for television receivers use the "P-4" screen, which gives a nominally white trace and exhibits a medium persistence characteristic.

COLOR OF IMAGE

In many cases, the trace is actually bluish-white in color. It is claimed that a bluish-white image is less tiring on the eyes, particularly if noise and interference is present along with the vision signal.

Some picture tubes, and in particular the larger types, have an "aluminised" screen, the normal fluorescent coating being backed up by a layer of very finely divided aluminium particles. These particles provide a partial mirror which reflects forward light which would otherwise be wasted inside the tube.

A notable increase in picture brightness is claimed, particularly in larger tubes where the electron beam has to "illuminate" a much larger screen area.

Tinting of the glass is also employed in some tubes, or tinting of the safety glass in front of the tube face. Purpose of this is to minimise the reflection from the tube face of ambient room lighting. The picture brightness is also reduced, but the ratio of picture to reflected light is improved, because the reflected light has to pass twice through the tinting, the picture only once.

One other interesting point should be mentioned by way of conclusion. In most modern picture tubes, the electron gun assembly does not point directly at the centre of the screen, as indicated in figures 18 and 20. Instead, the gun assembly is bent so that the cathode-grid structure points obliquely toward the neck of the tube.

Purpose of this modification is to protect the screen from damage by heavy ionised atoms which may be accelerated toward it along with the electron stream.

NEGATIVE IONS

These negative ions are formed when low speed electrons attach themselves to atoms of residual gas. They are not readily influenced by the magnetic deflection fields and, if not diverted in some way, would simply strike and "burn" the centre of the fluorescent screen.

By offsetting the gun at a slight angle, the ions are directed toward the side of the tube and never reach the screen. A small magnet is sufficient to deflect the electrons, however, back into their correct path.

Examination of the gun structures in figure 21 will show their bent construction quite clearly.

(To Be Continued)

LET'S BUY AN ARGUMENT

(Continued from Page 99)

fairly accurate description of the results he was getting.

We duly explained that the correct procedure was to switch his meter to the "wide open" position and simply use his tone control to achieve the most pleasing overall balance. If certain records, particularly the older 78's, sounded distorted and harsh, then he was to set his filter for as low a cut-off frequency as necessary, only retarding his tone control if further restriction of the treble seemed desirable.

It was simply a matter of appreciating how the controls were to be used—one to achieve a suitable balance on pre-emphasised records and the other as a purely emergency measure to combat distortion and noise.

In discussing this point, I may be doing N.F.G. an injustice. He may now as much about it as I do. But then again he may not. In any case, what I have said may serve to put somebody else on the right track. By way of conclusion, a few remarks may be appropriate about transistor sets, in particular those we described earlier this year.

Right from the start, we were most careful to point out that the designs were purely exploratory and intended to familiarise our readers with transistor principles. We pointed out that they had very little F gain as such, that regeneration could not be relied upon and that they were only suitable for use in areas of high signal level—good suburban locations, &c.

CLASS-B SET

Then came the description of the class-B output job for which we claimed an output of about 370 milliwatts. This was no exaggeration and, whenever we have switched the set on since, feeding into a large speaker, we've had to reassure ourselves that all that noise was really coming from a 9-volt (as battery via a couple of transistors).

It sounds really loud. BUT we also mentioned that the gain was lower than the earlier class-A job, that a modest outdoor aerial was necessary and an earth wire was essential. In other words you couldn't get a lot of sound out without feeding a lot of signal in.

Despite such statements, several readers have been enthused by the idea of building a transistorised car radio, using the class-B circuit.

The letter reproduced earlier under the heading "Transistor Set" is quite pical.

When will people learn the difference between power output and gain?

To be sure, the class-B transistor set can make a lot of noise but only when it is fed with a large enough signal. Only when it is connected, as we said, to a reasonable outdoor aerial and an earth and used in a good location.

If the length of aerial is reduced a few feet, as in a car, and if its height is reduced to an average of about 3ft from the "earthy" car body, instead of at least 15ft above

ground, the signal it can pick up becomes very small indeed.

So, if the set doesn't have a lot of gain—and no simple transistor set has—then it lacks the ability to amplify the weak signals to the required degree. Far from the output being just a "bit weak", it would actually be nil.

Contrariwise, a set having a lot of gain can amplify weak signals to a useable level even though, in the ultimate, it may not be able to drive the loudspeaker quite as hard.


Transistor sets will not become a good all-round proposition for home-builders until it is feasible to achieve both high gain and adequate power output—economically, of course.

When this day arrives, they will really be an attractive proposition for car sets for they will operate straight from the car's electrical system, without need for a vibrator supply and all its attendant worries. They will draw so little current that drain on the battery will not be significant.

But that day hasn't arrived—yet!

**For
Appliances!
Television!
Radio!**

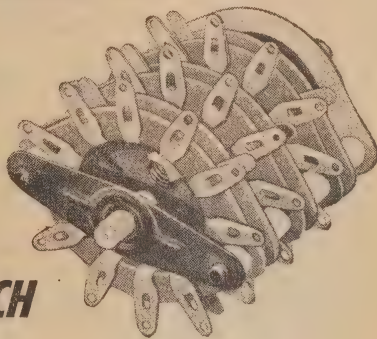PALEC ROTARY
10 AMP. SWITCH
(World Patents pending)



FEATURES:—

HEAVY CURRENT RATING:
(Temp. rise on contacts with 10 Amp. Conductors)

at 10 Amp. 100° C. rise
at 20 Amp. 300° C. rise
at 30 Amp. 500° C. rise

SMALL DIMENSIONS: Interchangeable with or can be used in conjunction with Standard "Oak" Decks.

LONG LIFE: The rotor contact travels "through air" between contacts, thus avoiding unnecessary wear and losses. Has been tested over one million operations.

LOW CONTACT RESISTANCE: Silver plated. Resistance 800 micro-ohms.

LOW CAPACITIVE LOSSES: Less than 1 micro-microfarad between contacts and to earth (suit U.H.F.).

DECKS: Single or Multi.

POLES AND POSITIONS PER DECK:
1 Pole max. 12 positions
2 Pole max. 6 positions
3 Pole max. 4 positions
4 Pole max. 3 positions

OVERALL DIAM.: 2½ in.

OTHER FEATURES:

Standard Water in 1st Grade Bakelite. Can supply in Ceramic on request: Positive Clicker: Single hole mounting.

PRICES AND ORDERING CHARTS
on application to—

Paton Electrical Pty. Ltd.

90-94 VICTORIA STREET, ASHFIELD, SYDNEY • UA 5266 (5 lines)

AWA

RONETTE

MICROPHONES & ACCESSORIES



Type C53

£4/19/1

Hand or stand mounting, omnidirectional, black plastic housing and hand grip. Ideal for tape recorders and similar applications.

Noyes Bros.

59 GEORGE ST., LAUNCESTON.
and leading wholesalers

**REAL LIFE stories in
PEOPLE** EVERY
FORTNIGHT

Two Months Clearance Sale


OF LARGE QUANTITY OF DISPOSAL RADIO AND ELECTRICAL EQUIPMENT

FOUR PAGES OF BARGAINS AVAILABLE DURING
OCTOBER AND NOVEMBER ONLY

**IF WHAT YOU REQUIRE IS NOT ADVERTISED WRITE
ENCLOSING SELF ADDRESSED ENVELOPE FOR
SPECIAL SALE QUOTE**

NEW RADIOGRAM - CHASSIS KIT - SETS

**5 VALVE
DUAL-WAVE**

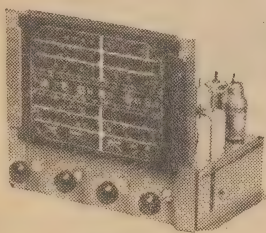

Complete kit of parts including 12in Magnavox or Jensen Speaker, five valves (1 6SA7, 1 6K7, 1 6SQ7, 1 6V6 and 1 6X5) and all other parts to the last nut and bolt to complete the five valve dual wave chassis illustrated.

These chassis when completed give excellent overseas, local and interstate reception as the coils supplied and intermediate transformers are high gain Permatune iron cored. Pick-up switch and volume control with A.C. switch supplied. Suitable for use with any crystal or high impedance magnetic pick-up.

LIST PRICE OF PARTS £25 ..SPECIAL PRICE £12/17/6

WIRED-AND-TESTED £2 EXTRA

**All goods advertised available at either
LEICHHARDT or ST. PETERS**

PERCENTAGE OF STOCKS RESERVED FOR MAIL ORDERS

Please address all correspondence to 479 Parramatta Rd., Leichhardt, N.S.W.

METROPOLITAN RADIO SUPPLIES

**640 KING STREET, ST. PETERS
N.S.W.
PHONE LA6087**

**479 PARRAMATTA ROAD,
LEICHHARDT, N.S.W.
PHONE LM3610**

NEW SPEAKERS BY LEADING MANUFACTURER

(5C) 5" STANDARD-PER-MAG.—20/-
(5F) 5" HEAVY DUTY PER-MAG.—24/-

Available with 10T
or 7T Transformer.

POSTAGE & PACKING
EXTRA: N.S.W. 4/6 —
INTERSTATE 5/6.

ALL GOODS ADVERTISED ON THIS PAGE ARE NEW

NEW VIBRATOR POWER-SUPPLY

Input 6V. output 230V. at 50 MA: These units made by A.W.A. are free from hum or hash. Supplied complete with standard synchronous vibrator. **£3/5/- F.O.R.**

Electrolytic Condensers

12mfd 525 V	3/9
500mfd 12 V	2/-
4mfd 600 V	1/9
8mfd 350 V	2/-
10mfd 40 V	1/6

(Plus Postage)

12-inch P.M. SPEAKERS

Heavy duty 12in per-mag speaker by well-known manufacturer. 10T. CT. or 5000 Transformer. **NOW 45/-**
Postage: NSW, 5/6; Interstate, 7/6.

Muirhead Vernier Dials

These New Vernier Dials are ideal for test equipment, receivers, etc.
(as used on AR8 sets)
27/6 ea.

DYNAMIC SPEAKERS

7in Dynamic speakers by leading manufacturer,
1,500 ohm Field coil,
7,000 ohm Transformer
or

Ovaltone Dynamic Speaker
9in x 6in. 1,000 ohm
Field, 5,000 or 7,000 ohm
Transformer

NOW 17/6 EACH

(POSTAGE—NSW 3/9, Interstate 5/9.)

VALVE SOCKETS

Teletron Standard Octal
Sockets (moulded bakelite)
3/- doz.

Eight pin local sockets moulded
3/- doz.

Six pin wafer sockets, 2/6 doz.
(All plus postage.)

CARBON RESISTORS

Color-Code
Card-Supplied

Well-known make of carbon resistors in values of 100 ohms to 5 megohm. In 1-watt, ½-watt and 1/3-watt. All resistors are standard color coded and in original cartons. In lots of 100 mixed values comprising 50 1-watt, 25 ½-watt 25 1/3-watt.

Price: Box of 100 **7/6**
Post 1/6.

Power Transformers

New midget power trans. Upright mounting with cover plates. 240v. Pri. Sec. 225 x 225 at 50 Mill. 17/6
and 6.3V at 3AMP.
Plus postage 2/6 NSW, 3/9 interstate.

60 mill. upright mounting 240v. Primary, sec. 265 x 265 at 60 mill. 6.3 and 6.3 volt filament windings. **22/-**
Postage: N.S.W. 3/6; Interstate, 5/6.

I.F. TRANSFORMERS

Standard I.F. transformers, square can. (1½) 455K.C., permatuned. **3/9 each.**
Plus Postage

CONDENSER SPECIAL

Boxes of 100 new mica and paper condensers in values ranging from 50pf. mica to .5 400v paper. Values include .0001, .00025, .00075, .01, .02, .05, .1 etc.

25/- PER 100

Plus postage.

TELEPHONE GENERATORS

New small telephone generators, ideal for bell ringing etc.
8/6

Postage extra.

I.R.C. RESISTORS

100 I.R.C. carbon resistors, ½, 1 & 2 watt. in values 50 ohm to 5 meg. including many popular sizes, 3T, 15T, 20T, 25T, 50T, 100T, 250T, 500T, etc.
(Standard resistor color code supplied.)

Box of 100 **16/6**
(Plus 1/6 postage.)

NEW VIBRATORS

6 volt A.W.A. gas-filled vibrators. Heavy duty synchronous **NOW 7/6 or 70/- per doz.**
2V. Synchronous vibrators **12/6**
A.W.A. standard six pin synchronous vibrators, in original cartons, 12 volts. Half price.

12/6

Plus postage.

NEW IT4 BATTERY VALVE

10/- ea.

PICK-UP CARTRIDGES

Rothermel high fidelity pick-up cartridge. Replacement for most pick-ups. **6/6 ea.**
ACOS Cartridges 7/6

SAPPHIRE NEEDLES

Rothermel sapphire needles play 2000 recordings. Made in England. Each 2/9 or 25/- dozen.

POTENTIOMETERS

Standard ½ or 1 meg. switch pots long spindle d/p switch.
5/6

½ meg. or 25T. ohms short spindle switch pots **2/6**

½ meg. or 100T. standard pots. long spindle. **3/-**

½ meg. or 100T. short spindle. **1/6**

All plus postage.

Please address all correspondence to 479 Parramatta Rd., Leichhardt, N.S.W.

METROPOLITAN RADIO SUPPLIES

640 KING STREET, ST. PETERS, N.S.W.
PHONE LA6087

479 PARRAMATTA ROAD,
LEICHHARDT, N.S.W. PHONE LM3610



£7/15/- F.O.R.

NEW AMERICAN INDICATOR-UNIT

These indicator-units contain the following valves:

Six 6SN7GT, one 6G6, one 6H6, one 6X5GT, one 2X2, and 3BP1 C.R.O. tube which is fitted in a separate shield on a 4ft shielded lead and supplied with control box and plug; case and shield are finished in black brocade. In original cartons.

TRANSFORMER TO CONVERT THIS UNIT FOR 240 VOLT OPERATION AVAILABLE AT £3/-/- EXTRA, plus postage.

MIDGET GENEMOTOR

Input 28 to 32v at 1.1 amp. Output 250v. at 60mA. New in carton.

£2/-/-

Used but in good order.

£1/10/-

Postage extra.



Input filter supplied with genemotors

28-volt GENEMOTOR

Input 28 to 32v. Output 250v at 65mA. Used but AS NEW

£1/-/-

POSTAGE EXTRA

NSW 5/-, Interstate 11/-

American Radar

Transmitter

Type ASB

CONTAINS

Two U.H.F. Triodes Type 15 E

Four Sets of Lecher Bars.

Transformers, ceramic mountings, Motor Blower, etc. Also High Voltage Vacuum Change-Over Relay. Nominal Frequency 515 m/cs. Ideal for conversion to U.H.F. Channels, Variable Coaxial Cable and Link Matching Lines. Contained in Aluminium Case.

Dimensions 18in x 7in x 8in.



£2/-/- F.O.R.

A.C. AMP METERS

A.C. Amp Meters (ex-Country Council). A necessity in any electrical workshop.

RANGE. 0.5 amps. (can be extended by shunts).

MOVEMENT. 300 degrees.

SCALE LENGTH. Nearly 15 inches.

DIAMETER. 7½ inches.

25/-



Postage extra — N.S.W., 6/6 — Interstate, 11/6.

H.F. OSCILLATOR

Frequency approx. 200 m/c Adaptable to the 144 m/c Band. Complete with 2-7193 Valves, and two pair Pye Co-ax Connectors.

Type "B" 12/6

POST FREE



NEW AMERICAN WALKIE-TALKIE CHASSIS

Type SCR-536 less valves, case, crystal. £3/17/6

Valves used 2.354, 1.1T4, 1.1S5, 1.1R5, postage extra.


FULLAPHONES

Containing pair of headphones, morese key, buzzer key switches etc.

Post N.S.W. 6/6 interstate 8/6.

15/-

6SH7 VALVES—TESTED 3/

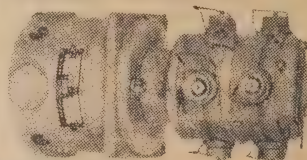

22/6

PLUS POSTAGE

AMERICAN ANTENNA SWITCHING MOTORS

Complete with 8 Pye-Type Co-ax Bases, R.P.M. 1750, Ball Bearing, 24 Volt.

PLUGS AND SOCKETS

New 26-pin shielded plugs and sockets with silver-plated contacts.

5/- pair, plus postage

5-pin shielded plugs and sockets 2/9

TRICKLE-CHARGER KITS

Kits for trickle-charger as described in R. & H., June issue Comprising transformer with 18V winding tapped at 12V-3 100mA rectifiers and 50 ohms control.

Postage: NSW, 5/- Interstate, 7/6

32/6

NEW METERS

English 3in turner, flush mounting. 10MA movement

English 0-600v, with shunt, 3in flush

20/-

20/-

Please address all correspondence to 479 Parramatta Rd, Leichhardt, N.S.W.

METROPOLITAN RADIO SUPPLIES

640 KING STREET, ST. PETERS, NSW.
PHONE LA6087

479 PARRAMATTA ROAD,
LEICHHARDT, NSW. PHONE LM3610

NEW AMERICAN TELEPHONE WIRE CLEARANCE

Rubber-insulated with stainless steel and copper conductors supplied on metal reels each containing half a mile of wire.

$\frac{1}{2}$ -mile reels NOW 15/-

Post
Extra

In case lots—6 reels (3 miles)
NOW £4/0/0

RADIO ALTMETERS, TRANSMITTER RECEIVER TYPE RT-3A/ARNI.

Complete with the following valves:—5-12H7, 2-12H6, 2-12SJ7, 2-995, 2-9004 and one VR150. Midget 28V. Genemotor. £4/17/6 f.o.r.

AIRCRAFT BOMB SIGHTS

These sights contain 4in spirit filled compass with corrector. Two spirit levels, rack and pinion and many useful gears. The unit is mounted in wooden case with locks and handle.

£1/17/6 F.O.R.

TELEPHONE RELAY PANELS

These panels contain 50 volt 100MA Rectifier, sensitive relay bezel with lamp and holder, phone jacks, etc.

8/6

Plus 5/- postage

NEW VALVES

807 --- 12/6
7C7 --- 3/6
7C5 --- 5/6
6K7G --- 7/6
6V6G --- 12/6

All
Plus
Postage

12SR7 . . 2/6
12SQ7 --- 2/6
1T4 --- 10/-
KT61/6U7 7/6
1K5 --- 2/-

OIL-FILLED CONDENSERS

20mfd. tapped 600V. 15/-
15mfd. 600V. 10/-
4mfd. 600V. 5/6
3mfd. 2000V. 15/-
1mfd. 400V. 2/9

All
Plus
Postage

RELAY-TYPE COUNTERS



("Mercury" American Made)
These relay counters register from 0 to 99,999. Can be supplied with 250ohm, or 5,000ohm coils.

22/6

plus postage

P.M.G. TYPE RELAY-COUNTER

0-9,999.

1,300 ohm coil 15/-

TELESCOPIC AERIAL

These new all-brass 108 aeriels measure 13 inches and extend to 5ft 3 inches in five sections . . . 12/6
Bakelite mounting base for above 3/6

Plus Postage 3/6.



BUTTERFLY CONDENSERS

Capacitance range 3-35 microfarad. Size $1\frac{1}{2} \times 2\frac{1}{2} \times 2\frac{1}{2}$ inches. Brass plates: Ultra high frequency installation; $\frac{1}{4}$ inch shaft 8/6
Price each
Packing and postage, NSW, 1/-; Q., T. and V., 1/6; WA, NT, 2/-.

24-VOLT MIDGET MOTORS SHUNT WOUND



Fully Laminated Fields. Wound Armature. Sixteen Segment Commutator, ball-bearing Armature. Ideal for Model Trains, Hobbyists, etc. Condition New.

Price, each 32/6
Packing and postage: NSW 1/6; Interstate 2/6.

Transformer and metal rectifier to operate either of above. From 240V AC 30/- Plus postage.

NEW FLEXIBLE DRIVES

Flexible drives to suit command transmitters or receivers 5ft 6in long. 12/6 Plus postage.
To suit compass receivers 2ft long. 10/6 Plus postage.

HEAVY DUTY GENERATOR

Suitable for conversion to A.C. motor (approx one-sixth H.P.) Fully laminated. Can be used as 6 or 12 volt generator at 20 or 13 amps. £2/10/- f.o.r.



Please address all correspondence to 479 Parramatta Rd., Leichhardt, N.S.W.

METROPOLITAN RADIO SUPPLIES

640 KING STREET, ST. PETERS,
N.S.W.

PHONE LA6087

479 PARRAMATTA ROAD,
LEICHHARDT, N.S.W.

PHONE LM3610

SAPPHIRE! Australia's lowest-priced two-speed Tape Recorder

**Now available for
low deposit**


When you twist the neat playback dial on the Sapphire Hi-Fi Tape Recorder, you'll be amazed to hear that business conference, kiddies' party, choir or orchestra, come back to you with startling reality. Designed for superb playing and recording wherever there's a power-point, the Sapphire Hi-Fi tape Recorder is ideal for all recording purposes. The many precision-built features include: Two speeds (3½ in and 7½ in per sec.). Three motors. Independent base and treble controls for playback. Electro-dynamic take-up and braking. Amplifier output is (1) 3 watts undistorted; (2) 5 watts with 10% total harmonic distortion.



Weighing only 31 lbs., the
Sapphire Hi-Fi Tape Re-
corder is

£112 or £12 deposit

Pathe movie equipment

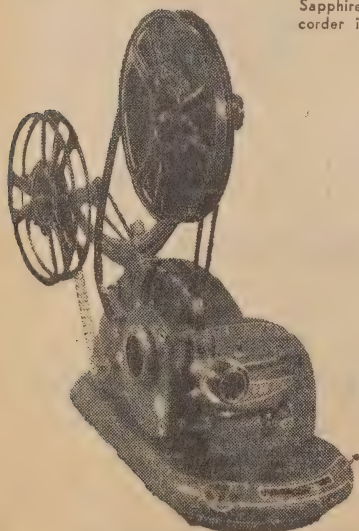

**The "Patheoscope" GEM
9.5 mm. Projector**

This ideal projector provides: variable speed control, use of 900ft reels; independent light switch; 1½ in lens in combination with optical system gives a 6ft screen at 20ft; built-in transformer; sturdy lamp for 50 hours' screening. All revolving parts self-lubricating. Price £54/10/-, £13/10/ deposit.



The Pathe 'National'

Designed for the advanced worker the "National" features an F1.9 coated Som Berthiot focusing lens (half meter to infinity), built in optical view-finder with masking for four lenses and parallax correction down to one meter; can take single pictures. Is capable of speeds from 8 to 32 frames per second, fully swing-open gate and has 30ft daylight charger loading.

£58/19/6, £14/19/6 deposit.



The Pathe Model 'H' Camera

This camera is ideally suited to the needs of the amateur who desires first class results. Finished in black crackle enamel, the Model "H" is supplied with an F2.5 20 mm fixed focus superior quality lens in an interchangeable mount. It can take single pictures or continuous running has footage counter and tripod bush.

£33/5/- or £8/5/- deposit.
A second four speed model "H" camera (10, 16, 24 and 32 frame per second) is also available for £56/10/- or £9/10/- deposit.

BOYLANS

14a OXFORD STREET, SYDNEY
FA8787, 2 doors from Winns.

ANSWERS TO CORRESPONDENTS

D.H. (Ormond, Vic.) asks us if it would be possible to add a 6M5 output valve to the Super Three circuit described in the June, 1952, issue of the magazine.

A: The main point of the Super Three was to be able to build a receiver which gave good results with only three valves. This was accomplished by the use of one double valve to act as audio amplifier and output stage. If you wish to build a receiver having more than three valves it would be better to use one of the more standard receiver circuits.

Typical circuit is the Little General for 151 described in the July, 1951, issue of the magazine which uses the valve types 6X4, 6N8, 6M5 and 6X4.

J.V.Z. (Nudley, Qld.) asks if it is possible to solder aluminium to aluminium or to other metals.

A: From time to time various solders become available through hardware stores which are claimed to be able to do this. We have not had the opportunity to use these to determine how good they are, although we have private doubts. One of the reasons there are ultrasonic soldering irons which use high frequencies to break down the oxide which readily forms and makes the soldering of aluminium so difficult. For further information on these we would refer you to Mullard Australia Pty. Ltd., 35-43 Forelance St., Sydney, NSW.

H.B. (Windale, NSW) asks us to inform him of the manufacturers of the Regency 1 transistor receiver described in a recent Technical Review.

A: We regret H.B. that the only information that we have available is that it is in current production in the USA. As far as we know, there are no local agents or distributors.

P.R. (North Balwyn, Vic.) writes to tell us that he used a .5 and a .25 resistor in series for the feedback resistor in the record player described in the Feb. 1949 issue instead of the .75 resistor specified. When he shorted the junction of the two resistors to earth the volume of the amplifier increases.

A: This is because in shorting out this resistor you short out the negative feedback from the output valve to the first valve. Whilst the gain increases so can the distortion be expected to increase because of the removal of this feedback. However, if you prefer to use the amplifier in this condition, there is no special reason why you should not do so.

E.B. (Walourie, NZ) writes and asks us if we can advise him on the capacitance of the gang used in the shortwave converter in the July 1955 issue of the magazine as he is unable to obtain the AWA type given in the parts list.

A: The gang used was a standard miniature broadcast gang and any similar type gang which is obtainable on your local market would be satisfactory. However, we suggest that you get in touch with the AWA representative in New Zealand and see if supplies are available.

C.R.C. (Cohden, NZ) says that he has tapped our crystal set (Aug. 1954) as a receiver for his amplifier. He says that the general performance is very good.

A: There is certainly something to be said for the idea in a good locality. The high gain of a modern amplifier often allows the crystal set to operate with a minimum of aerial and detector coupling, thereby making the best of selectivity. We are glad to note that you like the "Argument" series.

C.E.S. (Barcardine, Qld.) writes to the serviceman in support of F.J.C. who suggested that the serviceman should publish regular assessments of commercial radio receivers, whether such remarks are complimentary or not.

A: Many thanks for your letter and comment, C.E.S., and we will pass these on to the serviceman for his possible comment. It must be realised, of course, that there is far more to it than a mere publication of one's opinion. Derogatory remarks may be hard to "prove" if they are ever challenged in a court of law.

B.B. (Ravenshoe, Q.) writes to request details of all the seven and nine-pin valve types together with their electrical characteristics, substitutes, and equivalents in the octal range. He also asks for information on the use of ultra-violet lamps in the search for minerals and the type of power supply required. A further request is for information on the making of an electric fence.

A: Well, B.B., we suggest that for valve information you could not do better than consult the various valve companies who will be better able to assist you in this matter. It would not be possible for us to print all the available information in the magazine, as it would just about fill a complete edition. From the same source you should be able to obtain information on the ultra-violet lamps. With regard to the electric fence information, this is obtainable through the normal two-shilling query service and will be sent on request.

T.B. (no address) comments on an audio amplifier design.

A: Many thanks for your letter of the 18th ultimo and for your comments about audio amplifier design. They are logical material for use in the "Argument" columns and, space permitting, we will discuss them at length in a forthcoming issue.

E.W. (Dubbo, NSW) renews his subscription to R. T. and H. and says he is getting excellent results from his "1952 Advance" receiver.

A: Thanks for your letter and the enclosed subscription. We are pleased to note that your set is performing well and that you find "Off The Record" so helpful. It is to be hoped that your "Playmaster" gear will materialise soon. We agree that the motor is a problem and a high-priced unit appears inevitable if the best results are to be assured. The set-up you are planning should be capable of excellent results.

G.W.L. (Christchurch, New Zealand) asks for further information on the Induction Stethophone mentioned in the News and Views in the July issue of the magazine.

A: We had several requests for further information on this unit and accordingly published a more complete article in the October issue which should be of interest to you.

A.P.T. (Montmorency, Vic.) has observed that the first figure of American valve type numbers bears a relation to the filament voltage but is confused over the use of "1" as a prefix of such 2-volt valves as the 1M5, &c.

A: Yes, A.P.T., it does appear a little confusing at first and, in fact, there are many who believe that the ideal valve numbering system is yet to be evolved. In the case you mention confusion arises over the need to differentiate between 2-volt and 2.5-volt types. The system provides that all voltages up to and including two shall be designated by the figure "1" and values above this but below three by the figure 2.

R.M.M. (St. Kilda, Vic.) has read our transistor articles with a good deal of interest. He wants to know how their power output compares with a portable battery set.

A: We are glad to note that you liked the articles, particularly the one on class-B. The gain of the class-B set is not very high but on a strong station it can make a good deal more noise than the average battery portable. We have never liked transistors in push-pull parallel but they could probably be made to work in a class-B circuit. Drive might be a problem, however. Class-A operation might be more critical, since the bias requirements of the individual transistors may not be close enough to give optimum conditions for all units simultaneously. Higher powered transistors are already on the way.

A.H.G. (Bexley, NSW) has built the Basic crystal set of March, 1951, and has obtained good results from it until the recent increase in power, which is causing severe interference. He wants to know what can be done to improve matters.

A: Reducing the length of the aerial or tapping it farther toward the earth end of the coil should help, though only at the expense of signal strength. At the same time you may still be better off than before the increase if an optimum setting can be found. Alternatively, we suggest the Twin Tune Crystal Set of April, 1951, since this permits the coupling between two tuned circuits to be adjusted for optimum selectivity and sensitivity. Copies of this circuit are available through the normal query service.

The Radio, Television and Hobbies Query Service

All queries concerning our designs, to which a POSTAL REPLY is required must be accompanied by a postal note or stamps to the value of TWO SHILLINGS.

For the same fee, we will give advice by mail on radio matters, provided the information can be drawn from general knowledge. UNDER NO CIRCUMSTANCES, however, can we undertake to answer problems involving special research, modification to commercial equipment or the preparation of special circuits.

Whatever the subject matter, we must work on the principle that a letter is too involved if the reply takes more than 10 minutes of our time.

Queries not accompanied by the necessary fee will be answered FREE in the columns of the magazine and presented in such a way as to be of interest to other readers.

To those requiring only circuit reprints, &c., we will supply for TWO SHILLINGS diagrams and parts lists from our files covering up to three constructional projects. Scale blueprints showing the position of all holes and cut-outs in standard chassis can be supplied for 5/-. These are available for nearly all our designs but please note they do NOT show wiring details.

Address your letters to The Technical Editor, RADIO, TELEVISION and HOBBIES, Box 2728C, GPO, Sydney.

Note that we do not deal in radio components. Price quotations and details of merchandise must be obtained direct from our advertisers.

How Good are our Amplifiers?

(Continued from Page 89)

performance, which should be achieved by a high-quality amplifier.

OUTPUT: Not less than 10 watts for any kind of listening, 15 watts for loud listening, and 30 watts for very loud listening.

FREQUENCY RESPONSE: Level between 35 cycles and 30 Kc, and, if possible, to over 100 Kc. In any case flat to plus or minus 1 db up to the final roll-off, which should occur at a regular rate not greater than 6 db per octave.

DISTORTION: Not more than 1 pc THD at full output nor more than .25 pc at say half-power point. Not more than 1.5 pc IM at full output or more than .5 pc at half-power.

TRANSIENT RESPONSE: No more than 10 pc of overshoot on 5Kc square wave with 2-3 micro-second rise time. Ringing should be much lower in amplitude and damped completely within 50 pc of the flat top or less. More work is needed to clarify the importance of this test.

POWER CURVE: Flat between 50 cycles and 10 Kc. Not more

than 10 pc down at 25 cycles and 15 Kc.

STABILITY: No sign of oscillation at full output on sine waves, or square waves at 5 Kc with speaker load. (Full output tests on speaker load are rather impracticable.)

NEGATIVE FEEDBACK: The main loop should include the output transformer and be not less than 15 db, or more than 20 db unless all other requirements are met. With triode or U-L circuits this should ensure adequate speaker damping. With U-L circuits there is already a feedback loop around the output circuit approximately equal to 6 db.

LINEARITY: Should show no variations up to overload. Triodes or U-Ls connection should ensure this.

Any amplifier which can meet these requirements must be considered in the superlative class, and it should be virtually impossible to tell one from the other no matter how much these figures were improved upon. Even amplifiers, which fall short of some requirements, may still lay claim to extremely high quality.

We have built so many Playmasters using such a wide variety of output transformers that it is impossible to list them in any order of excellence. But any of the triode or U-L types using the very best transformers available should meet these requirements.

Some of the curves shown here illustrate this point in some degree. The 17-watt job we considered the best all-round amplifier we had.

On the other hand, commercial types tested from time to time would not meet some of the essential points. One of them is also represented by the curves with this article. It would be quite unfair to mention names, and we will not do so, but even this amplifier sounded good on a comparative listening test.

ACTUAL TESTS

Intermodulation tests with the Playmaster show that distortion is less than 1 pc up to maximum output, and below .5 pc for most of its power range. At 1 watt it was virtually immeasurable.

Quite recently, with the co-operation of a friendly broadcasting station in Sydney, we had a check made of the harmonic distortion of this amplifier, as it was after about eight months continuous use with the original valves and components. No adjustments of any kind were made to it prior to the test.

Distortion figures were so low that the overall distortion of the measuring equipment at times was greater than that of the amplifier. This made final estimated figures difficult to obtain and somewhat unreliable, as instrument distortion does not add and subtract arithmetically as we were forced to do.

However, for what they are worth the THD figures showed .075 pc at 1 Kc and 1 watt, .12 pc at 5 watts and .2 pc at 15 watts.

At 50 cycles and 10 watts, distortion was .15 pc, and at 7.5 Kc and 10 watts it was .15 pc.

A check on the amplifier before testing would almost certainly have reduced distortion still further, and would have provided a better comparison with commercial amplifiers. Obviously, however, it is so low as to be negligible right up to full output.

OTHER FIGURES

Incidentally, the amplifier gave 20 watts at 1 Kc with 6 pc distortion. Its hum and noise figure was particularly good at 76 db below 1 watt, or a VU figure of about -46.

The sum total of all this discussion seems to be that we do not yet know enough about the absolute requirements of a maximum fidelity amplifier, certainly not enough to lay down absolute specifications, all of which are founded on an accurate basis. There is a rich and fascinating field of investigation wide open for someone to explore.

We can, however, say without hesitation that, using the best components available today, the Playmaster series of amplifiers is at least as good as any commercial counterparts, and in our experience is generally better.

Whether differences are detectable by ear, when comparing amplifiers of this class, is another matter. We must use our own judgment until such time as we can relate the comparison to reliable standards.

MORE Skill in your Fingertips. **TRIX X-acto** HOBBY KNIVES and TOOLS

WHATEVER your hobby you'll want no better knives than X-acto. These knives with their range of 23 inter-changing blades, gouges and routers, put precision in all your cutting.

No. 1 complete 5/6
No. 2 complete 6/9
No. 5 complete 12/9

KNIFE SETS


No. 51. The No. 1 Knife with 6 various blades.
No. 52. The No. 2 Knife with 6 various blades.
No. 53. The Nos. 1 and 2 Knives with 12 various blades



X-acto BLADES, GOUGES, ROUTERS
23 kinds—a blade for every cutting purpose—made of finest surgical steel. Packets of five from 4/6

No. 82. TOOL CHEST

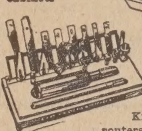A comprehensive kit. 3 knives and a range of X-acto blades in polished wooden cabinet.



57/6

No. 78

WOOD CARVING SET

The No. 1 and No. 5 Knives with gouges, routers and blades on a stout platform block.

72/-

No. 77. WOOD CARVING SET

The No. 5. Knife, blades and gouges on platform block for easy access

45/-



The BURLINGTON Hobby Chest

159/6

complete A first-rate kit in a magnificent moulded cabinet. The three knives, all the blades, and a fine range of tools make this a workshop in itself.

Obtainable from leading Hobby and Hardware Stores.

If you have any difficulty in obtaining supplies the agents will be pleased to direct you to your nearest dealer.

JACOBY, MITCHELL & CO. PTY. LTD.,

477 Kent Street, Sydney, Phone MA3411.

Trade Inquiries Welcome.

FROM THE SERVICEMAN WHO TELLS

(Continued from Page 43)

time the rubber holder was pushed in far enough to be securely held there was a grave risk of shorts to the metal channel.

With all these hazards, replacing the dial lamps in a manner which would ensure reasonable freedom from shorts was quite a ticklish job.

Truth to tell I am a little ahead of myself at this point. To be quite accurate I should have interrupted my description of the dial lamp problems soon after I started it, because it was then that the "strange noises" suddenly appeared.

The noises were indeed strange, even by servicing standards. It was a cross between a whispering and a ringing effect, with just enough of the latter to suggest microphony at some point.

This was confirmed by tapping, which aggravated the condition, and it was eventually traced to the vicinity of, and then directly to, the 6K32 converter. Replacing it with a good one cured the trouble and several changeovers confirmed that it really was the valve.

This done I reverted to the dial lamp installation as already described. Then a general once over, in alignment check, and the set was ready for its owner.

Summing up these two jobs one point is immediately obvious: several of the faults should never have happened. Firstly, while no one expects a dial cord to last forever, it is certain that it will last longer if the mechanism it is to drive is easy to move; either because it is mechanically well designed or because it is not gummed up with congealed grease.


Again, the instability (after the shield had been repaired) should never have occurred, being an obvious case of poor design.

The over-greased volume control cannot, of course, be blamed on the set manufacturer.

THE R. & H. CROSSWORD No. 19

ACROSS

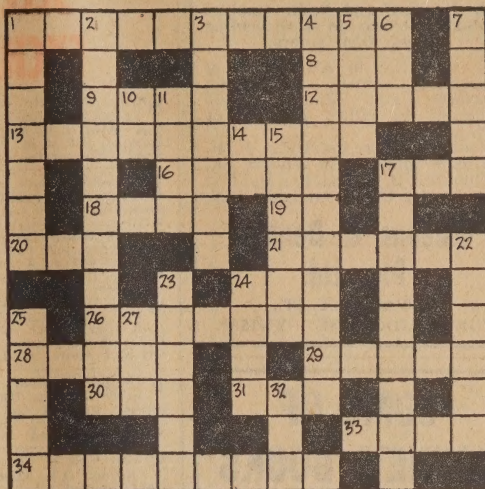1. Number of cycles per second (pl.).
2. Short sleep.
9. Send out.
12. Meeting by appointment.
13. With wave-lengths of less than 20cms.
16. Device for measuring an interval.
17. Atmosphere.
18. Used for book binding.
19. Credit (abbrev.).
20. In time past.
21. Adjusting a resonant frequency.
24. Higher range of audio frequencies.
26. Special milk preparation.
28. Metric unit of length.
29. Boy's name.
30. Electrical Engineer's Nomenclature (abbrev.).



31. Finish.
33. Girl's name.
34. Variable resistor (down).
1. A set form.
2. Electrolytic conductor.
3. To wreathe round.
4. — continuous waves.

5. Organs of hearing.
6. Conveys information secretly.
7. Part of an electric motor.
10. Mister (abbrev.).
11. A jot.
14. Amplitude Modulation (abbrev.).
15. Straight line.
- depicting magnitude and direction.
17. Adjustment of receivers.
22. Harness-ed.
23. Deputies.
24. Melody.
25. Color.
27. A mined substance.
32. Complementary to a bolt.

Solution and further crossword next month

Building a 5-valve Clock Radio

(Continued from Page 73)

In the layout, the additional wiring should not present any problems. In fact, apart from the filament line, all the connections can be made with the pigtail of the components. On the other hand, although we have described the changes in some detail, the layout is not particularly critical. We merely laid it out that way because it seems to be the easiest and most logical way to do it.

ALIGNMENT

The finished set will need to be aligned in the usual way, preferably using a modulated oscillator and output meter. However, if these are not available, a good job can be done using the broadcast stations as a source of signal. If you are not familiar with either of these alignment procedures, we can supply a pamphlet giving the process in detail. It is available through our postal query service, price 1/-.

In any case it is essential to realise that the proper performance of

the set cannot be expected until this has been done. If necessary, seek the assistance of your local serviceman or someone who has the necessary equipment and experience.


The only points peculiar to this set concern the trimmers, oscillator slug, and ferrite rod aerial. The trimmers and oscillator slug, by reason of their position and the need to adjust them in conjunction with the dial setting, must be adjusted after the set is mounted in the cabinet. Holes should be provided in the bottom of the cabinet to allow this to be done.

The ferrite rod aerial is adjusted at the low frequency end of the band exactly as in the case of a slug in the aerial coil. The adjustment is made quite simply by moving the winding along the rod until a position of maximum output is obtained. This will be quite sharp and, once it is found, the winding should be fastened in this position in a positive manner.

That done, you should have a re-

ceiver which will be hard to beat for sensitivity and all-round performance, plus the convenience of the clock mechanism and a truly handsome cabinet.

Last Month's Solution

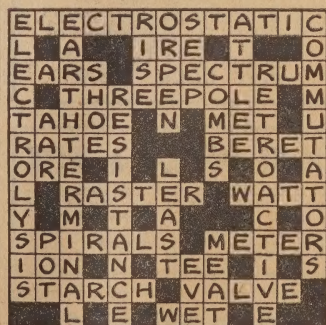

INSTRUMENT CASES

Wholesale and Trade only

All Standard and Radio Hobbies Cabinets obtainable at all leading Radio Distributors.

We specialise in All Classes of Covered Cabinets—Instrument, Portable and Mantel Radio Cabinets in either Leather or Leatherette.

Interstate Representatives J. H. Williams and Co., 50 William St., Melbourne; B. L. Andrews and Co., 144 Gawler Place, Adelaide, S.A.

Gibbons & Denham
Pty. Ltd.

15 FARIOLA ST.,
NORTH LIDCOMBE, YX1530.

SOME OF COYNE'S BOOKS

TRANSISTORS. Their Practical Application in Television, Radio and Electronics, 16/- plus 1/2 reg. postage. **INDUSTRIAL ELECTRONICS,** 39/6 plus 1/10 reg. postage.

PRACTICAL TELEVISION SERVICING AND TROUBLE SHOOTING MANUAL, 44/6 plus 2/- reg. postage. **LATEST TESTING INSTRUMENTS FOR SERVICING RADIO-TELEVISION,** 34/9 plus 1/9 reg. postage.

Published by the Coyne Electrical School, Chicago, U.S.A.

Exclusive Representatives in Australia and New Zealand:

ASSOCIATED TRADE JOURNALS CO. PTY. LTD.,

N.Z.L. House, 42 Bridge St., Sydney, N.S.W. BU4091.

Learn

TELEVISION

now

Comprehensive courses in
**TELEVISION SERVICING,
T.V. AERIAL INSTALLATIONS**
For enrolment particulars
write to Tee Vee School of
Electronics, P.O. Box 33
FIVE DOCK, N.S.W.

MAKE POUNDS A WEEK

in spare time or start full time business. Many making £20, £30 and £40 a week. Write for details of Guaranteed Money-Making Planes. J.O'Rourke, Director, Profitable Enterprises (reg.), Dept. RH, Box 5070, G.P.O., Sydney.

CAMERA NEWS
of the WORLD in **PIX**

WANTED TO BUY, SELL OR EXCHANGE

SELL: Complete set of Modern Test Equipment, new condition, guaranteed O.K. Also Hi-Fi Amp; Ham gear; Tubes. Send for list, B. M. Plovman, 78 Murdoch Road, Wangaratta, Vic.

FOR SALE: Back issues of R. and H., every copy available. Ex-stock, good stocks late issues 4/- per copy, incl. post. Write for information on circuits, etc., in back issues—designs for all types of radio gear—test equipment, etc., etc. T. Weir, 73 Gibson Avenue, Padstow, N.S.W. UY8056 Prompt Service.

SELL: Garrard 201B 3-speed transcription motor, unused, 1 price £15; Rola 120X speaker, RJ cabinet, £9/10/-; R. & H. wide-band tuner, new, £5. Colson, Oriental Hotel, Mudgee, N.S.W.

FOR SALE: Four 5BPI Cathode Ray tubes and one 1500 volt power transformer to suit C.R.O. All new and original packages, £10. W. Johnson, 152 North East Road, Walkerville, S.A.

SELL: A. & R. Ultralinear output transformer O.T. 921-8 20W 6,600-4-8.2, £7. New, unused. L. Jenkins, 557 Malvern Road, Toorak, Vic.

SELL: 5 new 826 Tubes, £1 each. B. Glassop, 343 Kissing Point Rd., Dundas

SELL: Thorens CBA 83 hardly used and perfect, £38. Type 3 MK 11 T.R.P.S. Two Xtals £20, two each £240, 866JR, 807, one 813 with SKT, £9 F. Leybourne, 6NA, Narragin, W.A.

SELL: MN—26C compass set, 150-1500 K/c, 28 volt, new with plan, TR196A, 3-9 K/c, 12 volt, unused. Kit to make 4in reflect, telescope. Offers wanted. 188 Gilles Street, Adelaide, S.A.

WANTED: Radio Service Manual Vol. 9 in good order. Write to A. Ginter, 16 Chrysler Rd., Croydon, S.A.

SELL: Technical Booksellers, 56 Hunter St., Sydney. For radio Television Books. Write for lists.

SELL: Printing, Special Offer—100 Business or Visit Cards, 30/-; 100 Letterheads, 30/-; 200 £2. Send anywhere by mail. Do it now! W. Hiley, 541 George St., Sydney.

FOR SALE: R. and H., Jan., 1950-Jan., '55, complete except for Aug., Sept., '52. New condition. Offer, Smith, 76 Bellbird Avenue, Norlane, Vic.

SELL: Printing Machine and Accessories, new condition, good supply type, ink. Worth £150, sell £85, rail anywhere free, can make good money with this. Hallett, Jeweller, Roma, Queensland.

SELL: Complete new radio servicing outfit, including University's Supertester Supertracer, Oscillator, together with over 100 new modern valves, large quantity new components, total cost £280 wholesale a few months ago. Sell the lot for £150. Bidgood, 139 Avoca Rd., Avoca Beach, via Gosford, Phone 3.

FOR SALE: UHF Portable Aerial System, F3219, 3 Marville Av., Kingsford, Sydney.

Pen Friends—Everywhere!

Interested in swapping ideas with pen friends in Australia and many other lands? Write for full free information on this fascinating hobby. Send name, age and address to:

UNIVERSAL PEN CLUB,
Dept. 2, Box 5189, G.P.O., Sydney.

ANSWERS TO CORRESPONDENTS

J.E.P. (Toorak, Vic.) would like to know if we have published circuits and articles dealing with photographic timers. He also sends in a circuit for one, and mentions one approach, in which the heating up time of a valve is utilised for timing.

A. Several circuits for photographic timers have been published in this magazine. J.E.P., and you will find them in our June, 1949, and January, 1952, issues. Copies of these circuits are also available through our query service. The circuit you have sent in should also work, as far as we can see at a glance. However, the idea of using the heating time of a valve would be quite unsuitable for such applications. As you say in your letter, it would be far too inaccurate to have any practical value.

W.T. (Ravenshoe, Q.) asks us if a licensee is required to operate a Walkie-Talkie, and if we can supply any circuits of such equipment.

A: It is not possible to operate any transmitting equipment without a licence, and a Walkie-Talkie is no exception. As regards circuits we described in 144 Handy Talkie in the Oct. 1950 issue of the magazine and copies of this are obtainable through our two shilling query service.

R. G. (Bexley, NSW) writes to ask us to explain the theory of the vacuum voltmeter.

A: As this question would call for too long an answer for these columns and as the question is one of general interest, we suggest that you watch the "Answer Tom" section of the magazine. We may be able to give the answer that you require.

AWA ROSETTE

MICROPHONES & ACCESSORIES



Type 088/F
£8/12/-

Technical pamphlets will be mailed on request. Other types also available from

Noyes Bros.

252 ARGYLE ST., HOBART
and leading wholesalers

ALWAYS RELY ON R.D.S.

R D S Suppliers of Tecnico Tape Deck and 10/12 Mullard Amplifier Parts.

We can supply all Radio and Electrical Components and are agents for the famous Hotpoint Radio Sets, Distributors of Test Equipment, Valve and Circuit Testers, Multimeters, etc.

A Complete Mail Order Service for the Countryman. Call, write or phone to—

**The Independent Wholesaler,
RADIO DESPATCH SERVICE**
Radio and Electrical Distributors,
GROUND FLOOR, WEMBLEY HOUSE,
841 GEORGE ST., SYDNEY.
Phone MA1876. Open Saturday Mornings.